

⇒ Ohm's Law:-  $V = IR$

$V$  = Potential difference across the resistor

$I$  = Current in resistor

$R$  = Resistance of Resistor.

Vector form of ohm's Law

$\vec{J} = \sigma \vec{E}$        $\vec{E} = \rho \vec{J}$

$\vec{J}$  = Current density

$\sigma$  = Conductivity of material

$\vec{E}$  = Electric field inside the material

$\rho$  = specific resistance or resistivity.

NCERT Exempler Q6) which of the following characteristics of electrons determines the current in a conductor

- (a) drift velocity      (b) thermal velocity
- (c) both  $v_d$  &  $v_{T}$       (d) Neither drift nor thermal velocity

$i = neAv_d$

$\langle \vec{v}_T \rangle = 0$

⇒ For conductor

We know  $T \uparrow R \uparrow$

Let at  $0^\circ\text{C} \rightarrow R_i$

at  $t^\circ\text{C} \rightarrow R_f$

$$R_f = R_i(1 + \alpha \Delta T)$$

$\alpha =$  Thermal Co-efficient of Resistance

1) Fraction change in resistance

$$R_f = R_i + R_i \alpha \Delta T$$

$$R_f - R_i = R_i \alpha \Delta T$$

$$\frac{\Delta R}{R_i} = \alpha \Delta T$$

⇒

$\alpha = +ve \Rightarrow$  Conductor  
 $T \uparrow R \uparrow, T \downarrow R \downarrow$

$\alpha = -ve \rightarrow$  Semiconductor  
 $T \uparrow R \downarrow, T \downarrow R \uparrow$

$\alpha = -ve \rightarrow$  Insulator

$$\% \frac{\Delta R}{R} \times 100 = \alpha \Delta T \times 100$$

\* Q) Resistance of a wire at  $0^\circ\text{C}$  temperature is  $1\Omega$ . Its temperature co-efficient is  $10^{-3}$  per  $^\circ\text{C}$ . Find temperature at which resistance becomes  $1.5\Omega$ .

$$R_i = 1\Omega$$

$$\Delta T = (T - 0)$$

$$\alpha = 10^{-3}/^\circ\text{C}$$

$$R_f = 1.5$$

$$R_f = R_i (1 + \alpha \Delta T)$$

$$0.5 = 10^{-3} T$$

$$1.5 = 1 (1 + 10^{-3} \Delta T)$$

$$T = \frac{0.5}{10^{-3}}$$

$$1.5 = 1 + 10^{-3} T$$

$$1.5 - 1 = 10^{-3} T$$

$$0.5 = 10^{-3} T$$

$$T = 0.5 \times 10^3 = 5 \times 10^2$$

$$T = 500^\circ\text{C}$$

In Conductor



$$R_f = R_i (1 + \alpha \Delta T)$$

$$S_f = S_i (1 + \alpha \Delta T)$$

$$R_i \Rightarrow \text{at } 0^\circ\text{C}$$

$$R_f \Rightarrow \text{at } t^\circ\text{C}$$

**AIEEE** \* \* \* \*

$R_1 = 6\Omega$  at  $200^\circ\text{C}$

$R_2 = 5\Omega$  at  $50^\circ\text{C}$

Resistance of wire at  $0^\circ\text{C}$ .  
 So) Resistance at  $0^\circ\text{C} = R_0$

at  $0^\circ\text{C}$   
 $R_f = R_i (1 + \alpha \Delta T)$

$6 = R_0 (1 + \alpha (200 - 0))$  — (i)

$5 = R_0 (1 + \alpha (50 - 0))$  — (ii)

$$\frac{6}{5} = \frac{1 + 200\alpha}{1 + 50\alpha}$$

$$6 + 300\alpha = 5 + 500\alpha$$

$$1 = 200\alpha$$

$$\alpha = \frac{1}{2 \times 100} = 0.5 \times 10^{-2} = 5 \times 10^{-3}/^\circ\text{C}$$

$$6 = R_0 (1 + 5 \times 10^{-3} \times 200)$$

$$6 = R_0 (1 + 1)$$

$$R_0 = \frac{6}{1.5} = 4\Omega$$


$R_0$  given

$R_f = R_0 (1 + \alpha \Delta T)$

⇒ Combination of resistance:-

① Series Combination:-

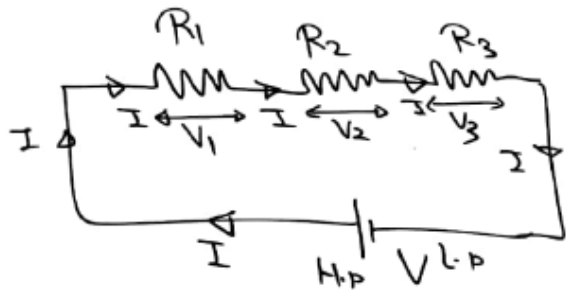⊕ [Current must be same through all resistor]




$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} > 1$$

$$R_{eq} > 3$$

$$R_{eq} > 2$$

$$I = \frac{V}{R_{eq}}$$

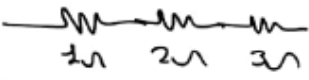

$$R_{eq} = 1 + 2 + 3$$

$$R_{eq} = 6\Omega$$

① In series combination current is same in all resistor.


② ∴ Equivalent Resistance is greater than largest Resistance

$$V = V_1 + V_2 + V_3$$

$$I R_{eq} = I R_1 + I R_2 + I R_3$$

$$I R_{eq} = I (R_1 + R_2 + R_3)$$

⇒ Combination of resistance:-

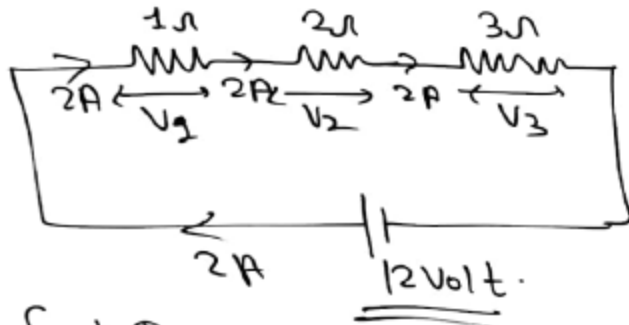

(a)  $R_{eq} = R_1 + R_2 + R_3$

$R_{eq} = 1 + 2 + 3$   
 $R_{eq} = 6\Omega$

(b)  $I = \frac{V}{R_{eq}} = \frac{12}{6} = 2\text{ Amp}$

$I = \frac{12\text{ Volt}}{6\Omega} = 2\text{ Volt}/\Omega = 2\text{ Amp}$

(a) Find  $R_{eq} = ?$

(b)  $I$  in circuit.

(c) Potential drop across each resistor.

(c)  $V_1 = I R_1$   
 $V_1 = 2 \times 1$   
 $V_1 = 2\text{ Volt}$

$V_2 = 2 \times 2$   
 $= 4\text{ Volt}$

$V_3 = I R_3$   
 $= 2 \times 3$   
 $= 6\text{ Volt}$


Check

$V = V_1 + V_2 + V_3$   
 $V = 2 + 4 + 6 = 12\text{ Volt}$

⇒ Combination of resistance:-


Parallel Connection of resistor:-

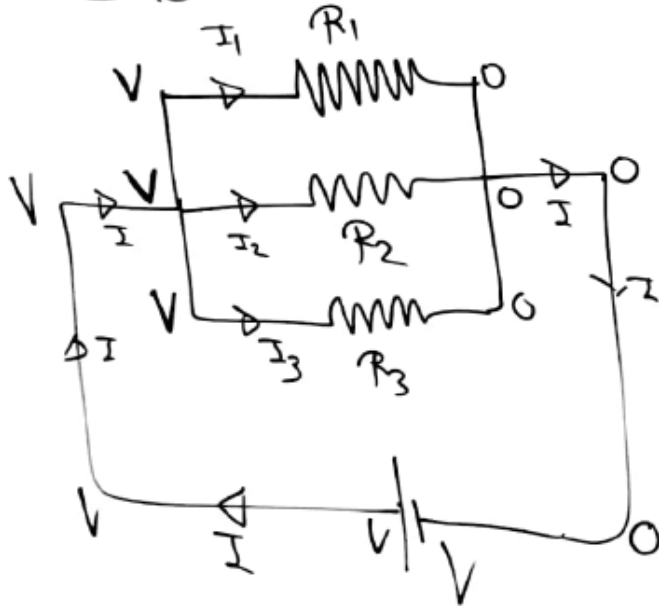⇒ Potential difference ~~across~~ across each resistance "must" be same.



$$I = I_1 + I_2 + I_3$$
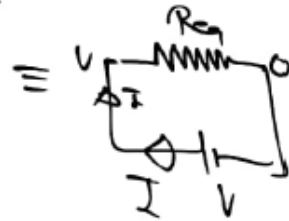
$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$



$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$V = IR \quad I = \frac{V}{R_{eq}}$$


Ⓝ (i) Potential across each resistance is same

Ⓝ (ii) Req is smaller than small Resistance

$$\boxed{\begin{aligned} R_{eq} &< R_1 \\ R_{eq} &< R_2 \\ R_{eq} &< R_3 \end{aligned}}$$

Combination of resistance:-

Q.2)

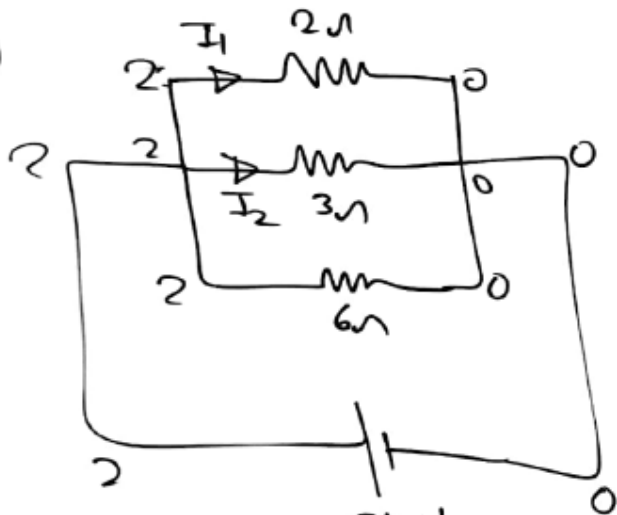

$$I_1 = \frac{2}{2} = 1A$$

$$I_2 = \frac{2}{3} = 0.67 \text{ Amp}$$


$$I_3 = \frac{2}{6} = \frac{1}{3} = 0.33 \text{ Amp}$$

$$I = I_1 + I_2 + I_3$$

$$R_{eq} < R_1$$

$$R_{eq} < R_2$$

$$R_{eq} < R_3$$

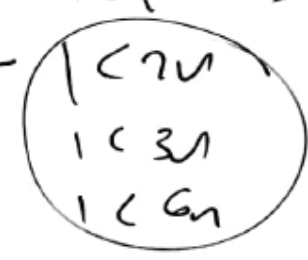

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{3+2+1}{6} = \frac{6}{6}$$

$$\frac{1}{R_{eq}} = \frac{1}{1} \Rightarrow R_{eq} = 1\Omega$$

(i) find  $R_{eq}$ .

(ii)  $I_1, I_2, I_3, I$

