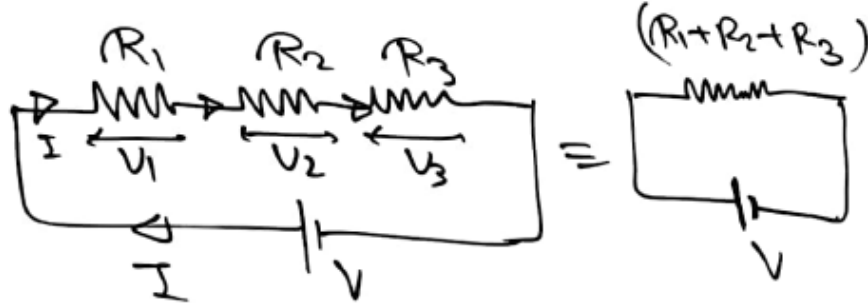


⇒ Circuit problem

⇒ **P** Series Connection




$$V = V_1 + V_2 + V_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

⊕ Current must be same in all resistor.

f Parallel Connection

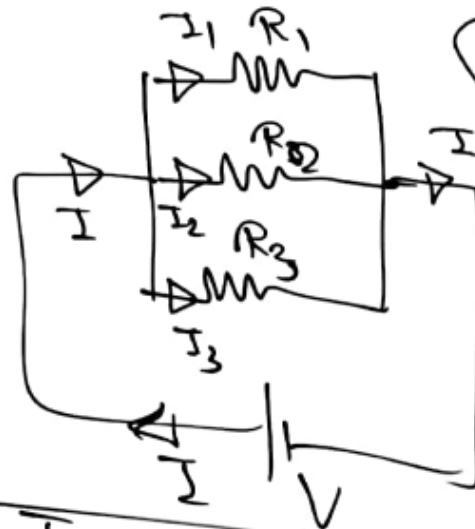


⊕ Potential Across All the Resistance is Same

$$I = I_1 + I_2 + I_3$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

⇒ Circuit problem

H.C.V

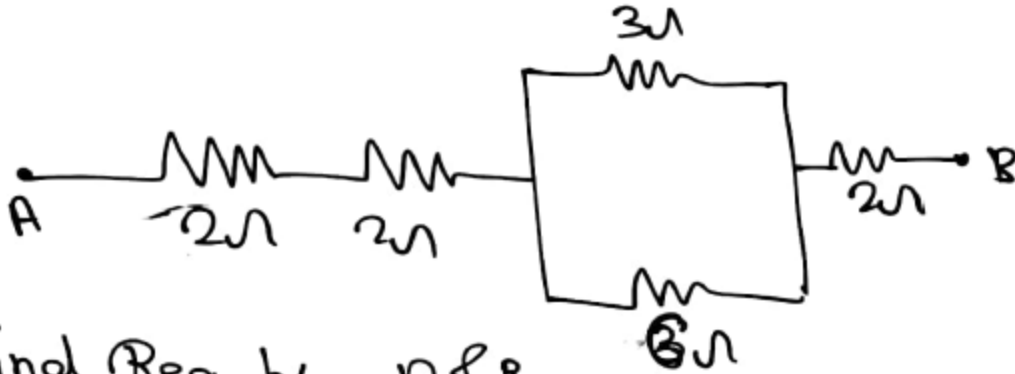

Find R_{eq} b/w A & B

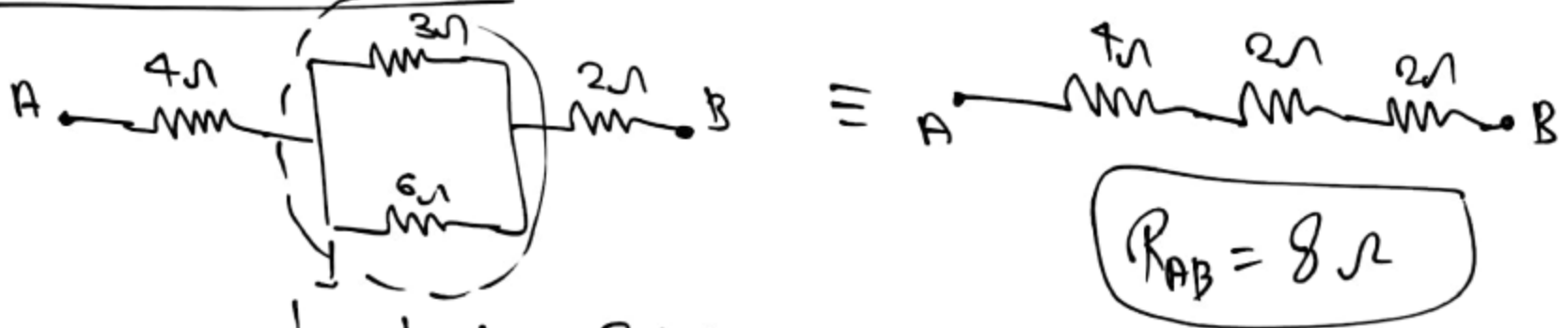

$$R_{AB} = 8\Omega$$




$$\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{6} = \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\underline{R_{eq} = 2\Omega}$$

⇒ Circuit problem

⇒

Find Req b/w A & B

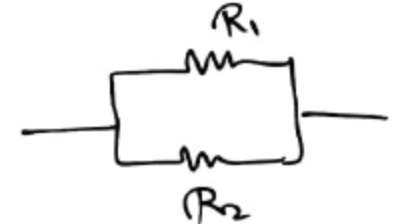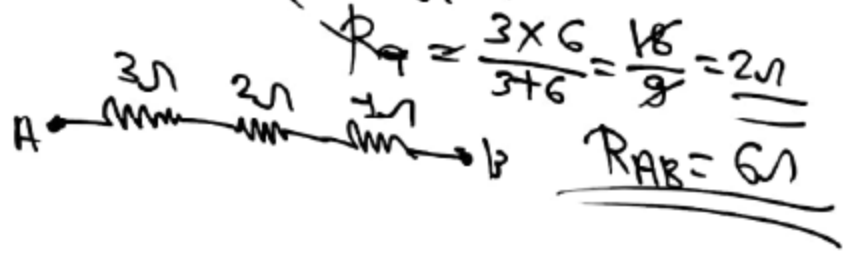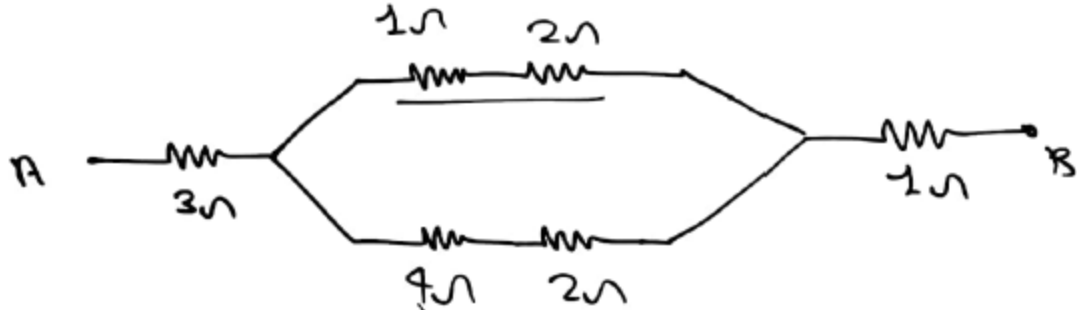

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{R_2 + R_1}{R_1 R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

⇒ Circuit problem n

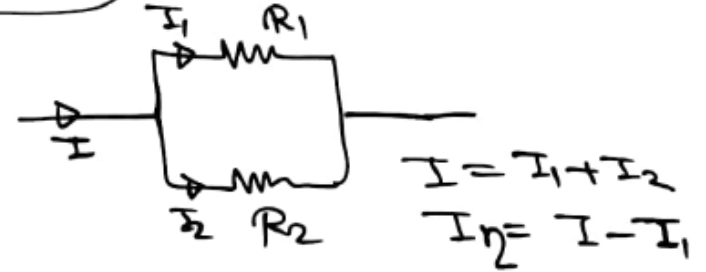
Q3:

Find Current in 3Ω & 6Ω resistor. In General



⇒ Smart way:

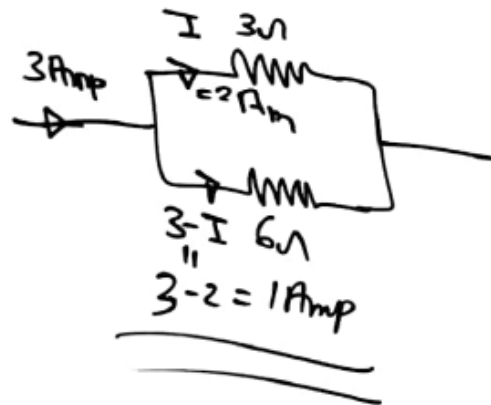Sol Point ① - Potential drop across 3Ω & 6Ω are same.



$$I \times 3 = (3 - I) \times 6$$

$$I = 3 - 2I$$

$$3I = 3$$

$$I = 1 \text{ Amp}$$

$$I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$\frac{I}{I - I_1} = \frac{R_2}{R_1} \Rightarrow I_1 R_1 = I R_2 - I_1 R_2$$

$$I_1 R_1 + I_1 R_2 = I R_2$$

$$I_1 (R_1 + R_2) = I R_2$$

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$


⇒ Circuit problem n

Q3:

Find Current in 3Ω & 6Ω resistor. For General

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$
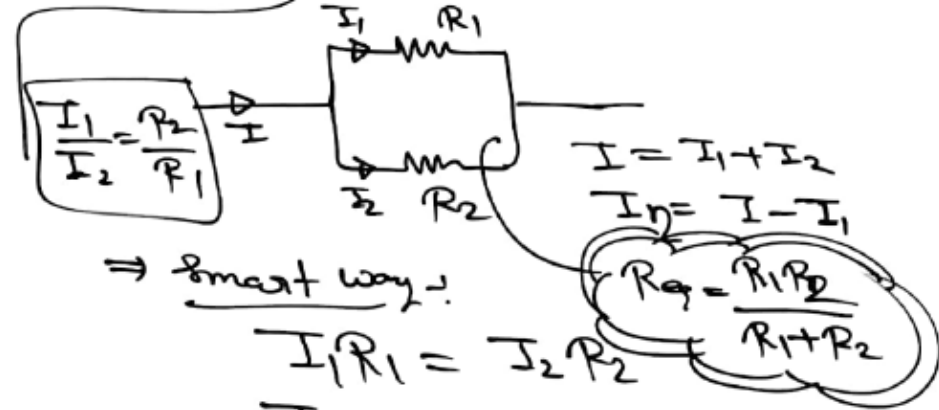
$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I$$



⇒ Smart way:

$$I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$


$$\frac{I}{I - I_1} = \frac{R_2}{R_1} \Rightarrow I R_1 = I R_2 - I_1 R_2$$

$$I_1 R_1 + I_1 R_2 = I R_2$$

$$I_1 (R_1 + R_2) = I R_2$$

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$

9)

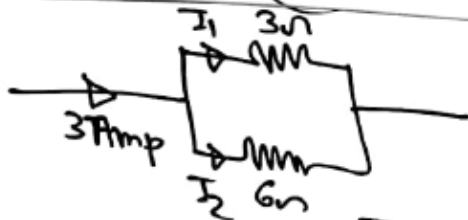

$$I_1 = \left(\frac{6}{3+6} \right) \times 3$$

$$I_1 = \frac{6}{9} \times 3 = 2 \text{ Amp}$$


$$I_2 = \left(\frac{3}{3+6} \right) \times 3 = 1 \text{ Amp}$$

Equivalent resistance of CKT

8) Find R_{eq} b/w A & B

both are same

Find R_{eq} b/w A & B


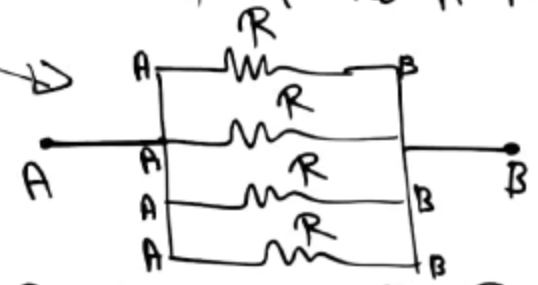


- (a) $\frac{3R}{4}$ (b) $\frac{R}{4}$ (c) $4R$ (d) N.O.T


$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$

$$\frac{1}{R_{eq}} = \frac{1+1+1+1}{R} = \frac{4}{R}$$


$R_{eq} = \frac{R}{4}$

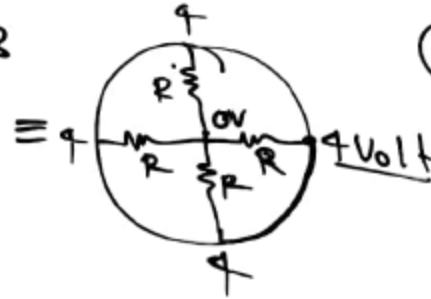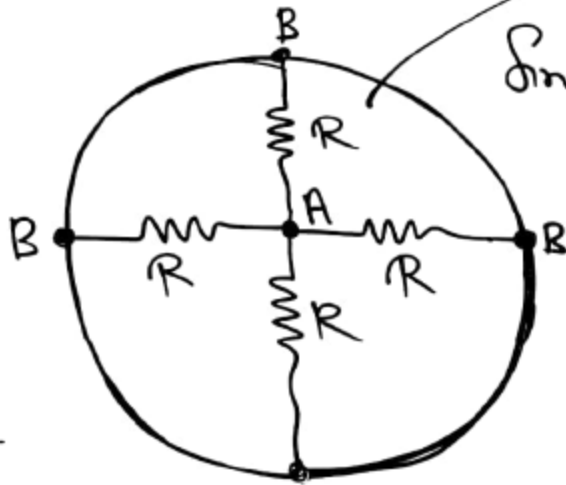

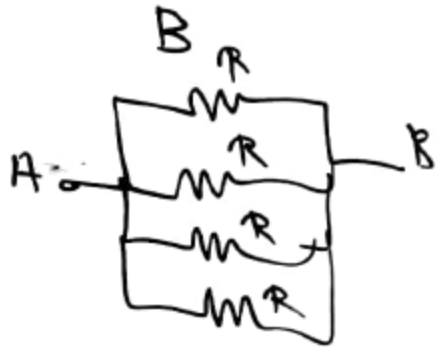- (a) $\frac{3R}{4}$
 (b) $\frac{R}{4}$
 (c) $4R$
 (d) N.O.T.




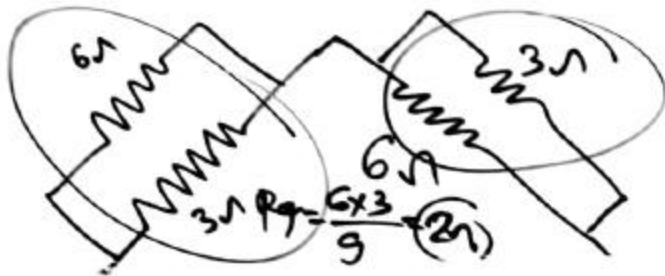(Equivalent resistance of CKT) # Short Circuit



- (i) Req b/w A & B when switch is open
- (ii) Req b/w A & B when switch is closed.

Sol) (i) Open

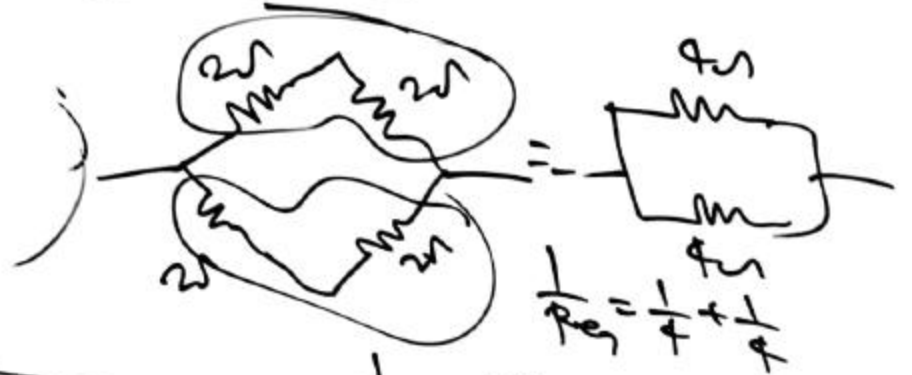

$$\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R_{eq}} = \frac{2}{4} = \frac{1}{2} \quad R_{eq} = 2\Omega$$

(ii) $R_{eq} = 0$ when S is closed