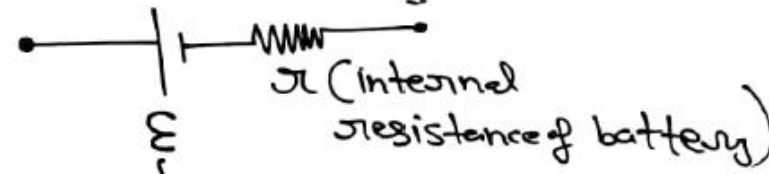


Current - Electricity

Emf:



→ terminal potential / terminal voltage.



(Emf) → (Electromotive force → Unit volt)



##

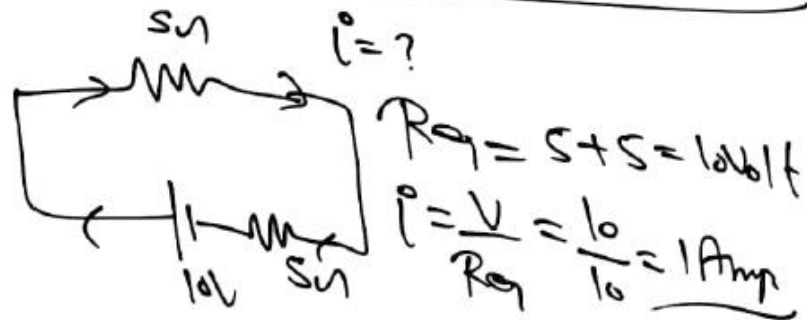
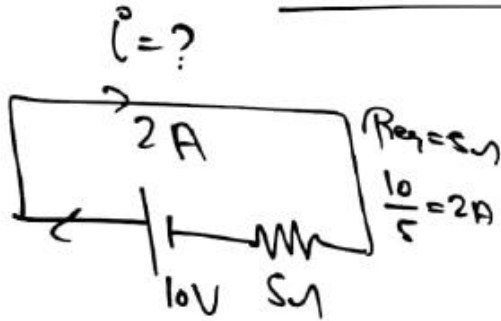


Current - Electricity


Kirchhoff's Law -:

first law -: [based on Conservation of charge]

Prove

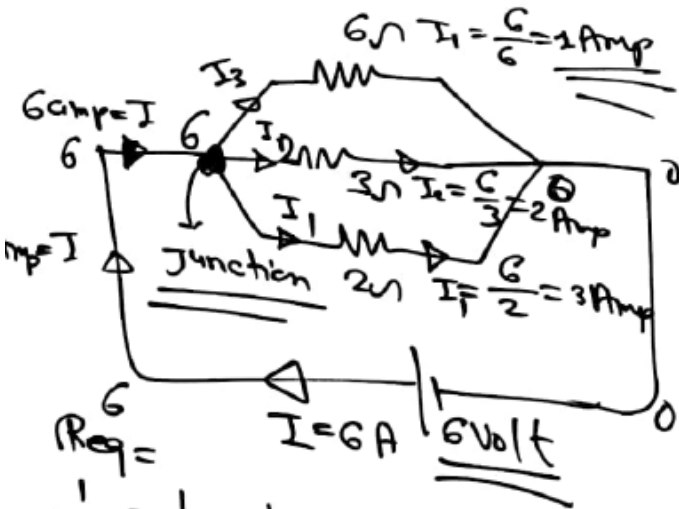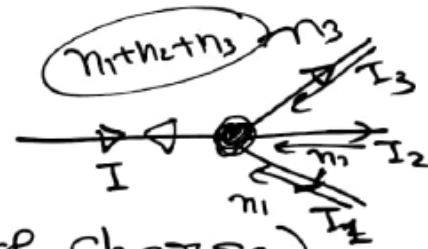


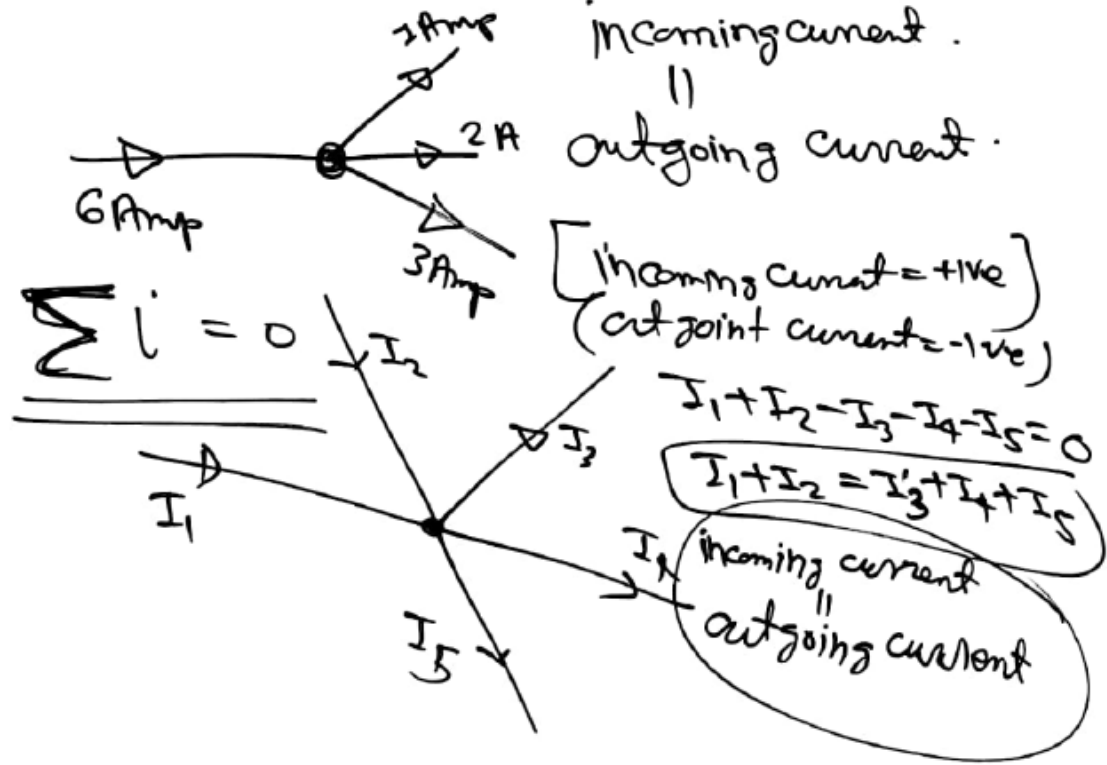$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}}$
 $= \frac{1}{\frac{3+2+1}{6}} = 1\Omega$
 $R_{eq} = 1\Omega$



ent - Electricity


Q1)

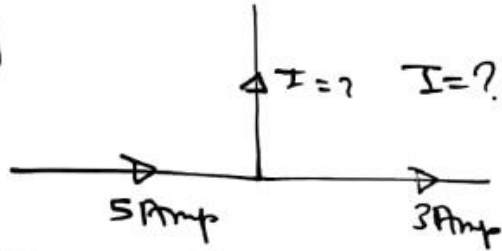

$$5 - 3 - I = 0$$

$$\underline{\underline{I = 2 \text{ Amp}}}$$


Q2)

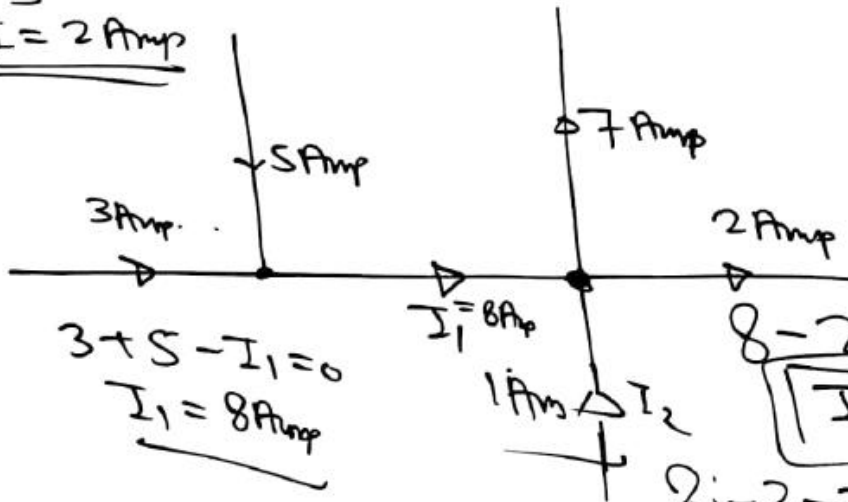

$$3 + 5 - I_1 = 0$$

$$\underline{\underline{I_1 = 8 \text{ Amp}}}$$

$$I_1 = 8 \text{ Amp}$$

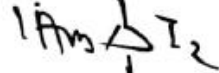


$$8 - 2 - 7 + I_2 = 0$$

$$\boxed{I_2 = 1 \text{ Amp}}$$

$$8 - 2 - 7 + I_2 = 0$$

$$-1 + I_2 = 0$$
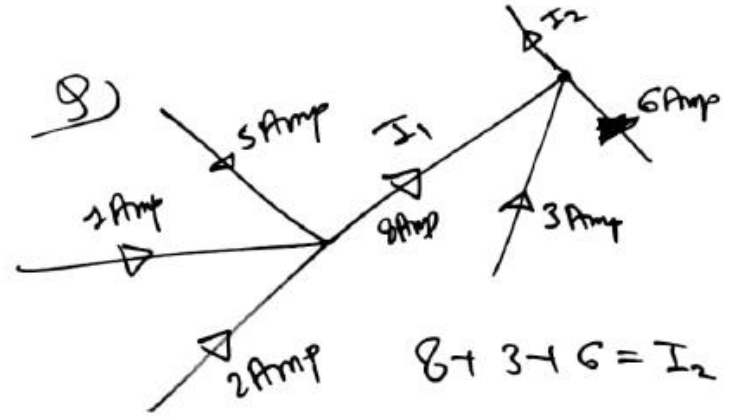
$$\underline{\underline{I_2 = 1 \text{ Amp}}}$$



$$8 + 3 - 6 = I_2$$


$$\underline{\underline{I_2 = 17 \text{ Amp}}}$$

Kirchhoff's second law: [based on Conservation of Energy]

⇒ (KVL)

[Kirchhoff's Voltage Law];

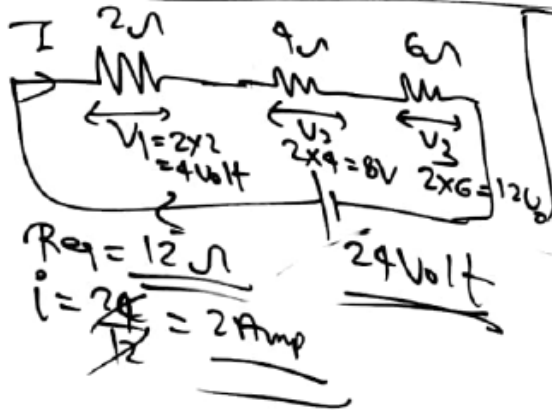
$$\Rightarrow \boxed{\sum IR + \sum \mathcal{E} = 0}$$



$$\begin{aligned} V_1 + V_2 + V_3 &= V \\ V_1 + V_2 + V_3 - V &= 0 \\ V - V_1 - V_2 - V_3 &= 0 \\ \hline \mathcal{E} - I \times 2 - I \times 4 - I \times 6 &= 0 \end{aligned}$$

Kirchhoff's Second Law:-

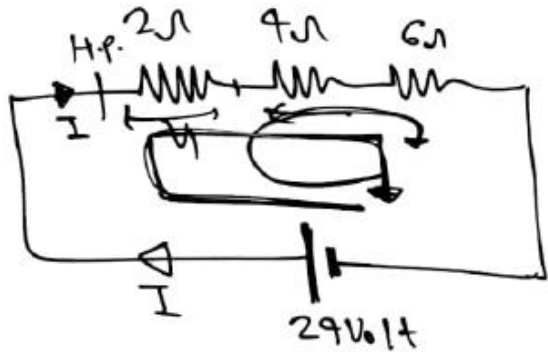[based on Conservation of Energy]
In a circuit



$$\sum \mathcal{E} + \sum iR = 0$$

$$29 + (-I \times 2) + (-I \times 4) + (I \times 6) = 0$$

$$29 - 2I - 4I - 6I = 0$$

$$29 = 12I$$




$$I = 2 \text{ Amp}$$

$$\Rightarrow \sum IR + \sum \mathcal{E} = 0$$

$$\# \text{ Req} = R_1 + R_2 + R_3 = 12 \Omega$$

$$V = 29 \text{ Volt} \quad I = \frac{29}{12} = \underline{\underline{2 \text{ Amps}}}$$

Kirchhoff's Second Law:-

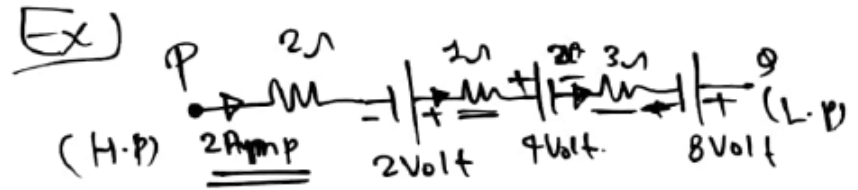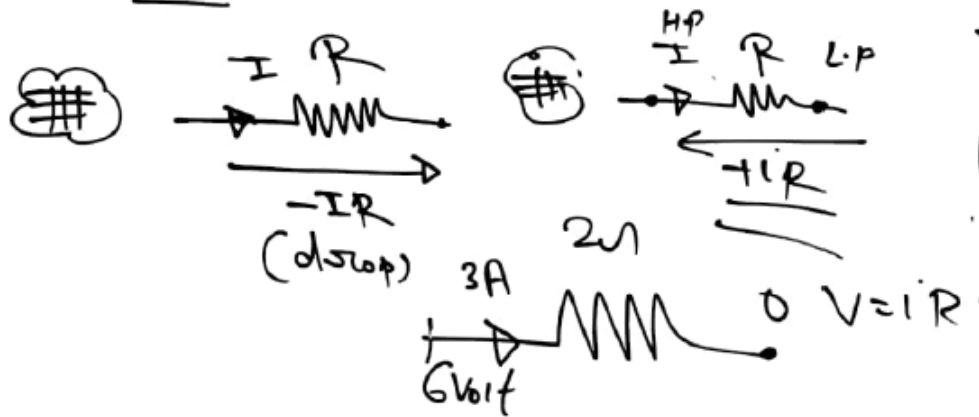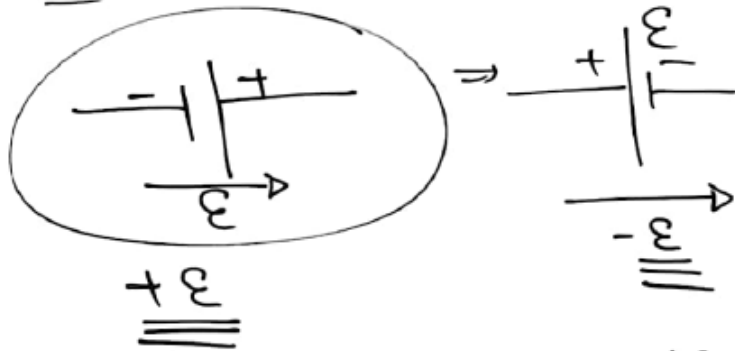


$$V_p - 2 \times 2 + 2 - 2 \times 1 - 4 - 6 + 8 = V_q$$

$$V_p - 4 + 2 - 2 - 4 - 6 + 8 = V_q$$

$$V_p - 8 - 6 + 8 = V_q$$

$$V_p - V_q = 6 \text{ volt}$$

Kirchhoff's second law:-

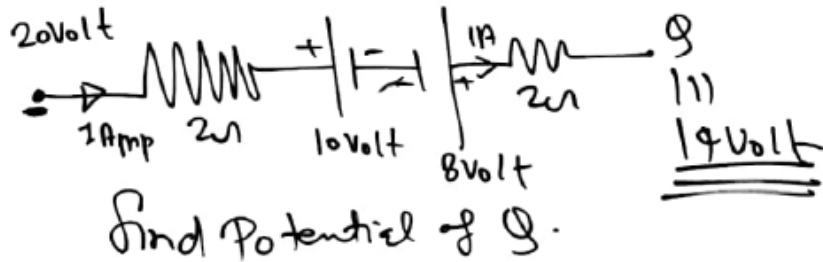



KVL

$$20 - 1 \times 2 - 10 + 8 - 1 \times 2 = V_Q$$

$$20 - 2 - 2 - 2 = V_Q$$


$$20 - 6 = V_Q$$

$$V_Q = 14 \text{ Volt}$$

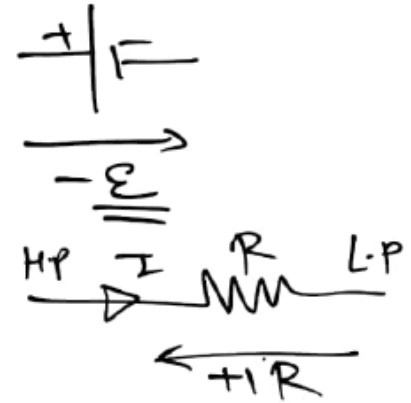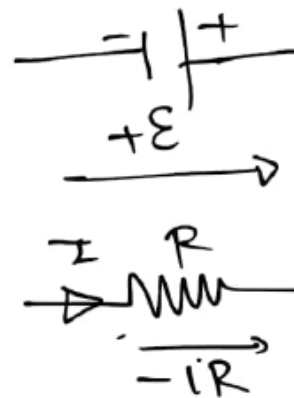

Potential of Q.

Q3)

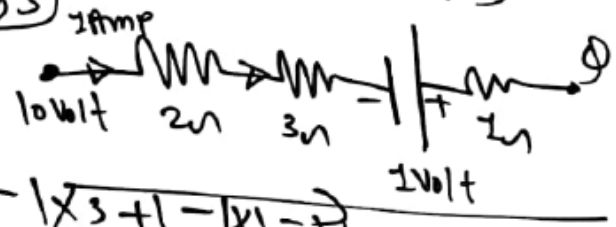

$$10 - 1 \times 2 = 1 \times 3 + 1 - 1 \times 1 = V_Q$$

$$10 - 2 - 3 + 1 - 1 = V_Q$$

$$S = V_Q \quad V_Q = 5 \text{ Volt}$$

Q) Find Potential of Q.

