
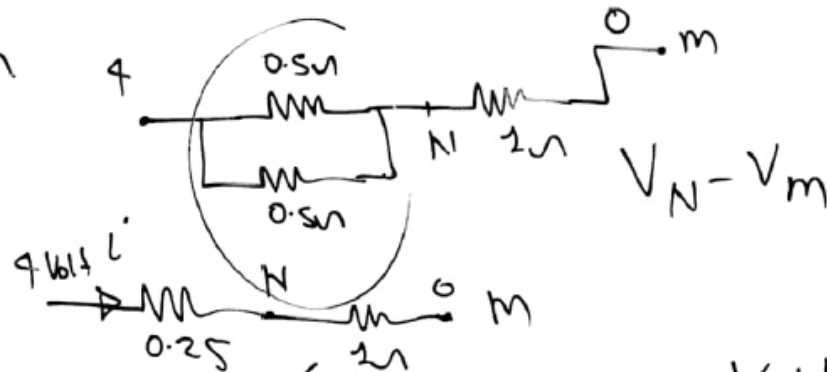


⇒

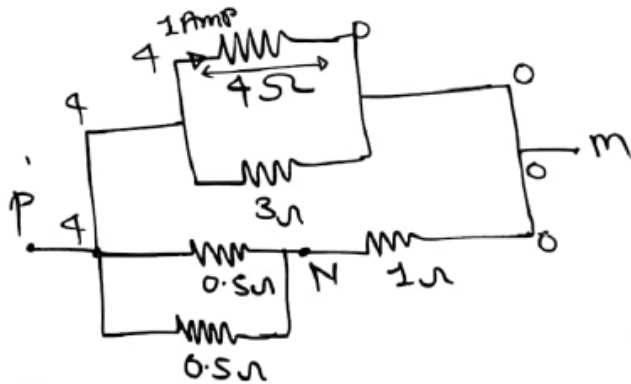Q 12 PMT

In the ckt shown, the current through the  $4\ \Omega$  resistance is  $1\ \text{Amp}$  when the points P & M are connected to a d.c. Voltage source. The potential difference b/w the point M & N is:

$$\frac{1}{R_{eq}} = \frac{1}{0.5} + \frac{1}{0.5} = \frac{2}{0.5} = \frac{1}{R_{eq}} = 4 \quad R_{eq} = \frac{1}{4} = \underline{\underline{0.25}}$$




$$R_{eq} = 1.25$$

$$i = \frac{4}{1.25} = \frac{400}{125} = \frac{16}{5} = \underline{\underline{3.2\ \text{Amp}}}$$


$$V_N - V_M = iR = 3.2 \times 1 = \underline{\underline{3.2\ \text{Volt}}}$$

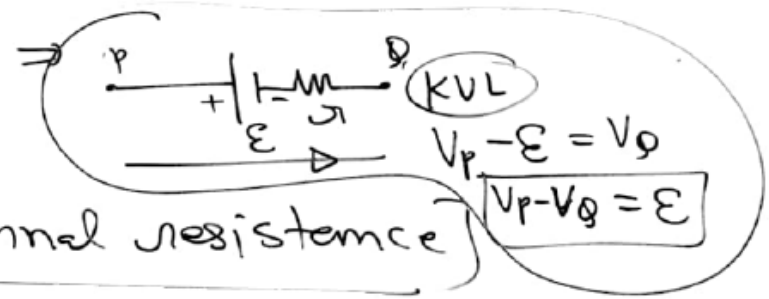- (a) 0.5 Volt.
- (b) 3.2 Volt. ✓
- (c) 1.5 Volt.
- (d) 1.0 Volt.


⇒ Emf :  $(\mathcal{E})$  (Electromotive force) :  
 (Volt)



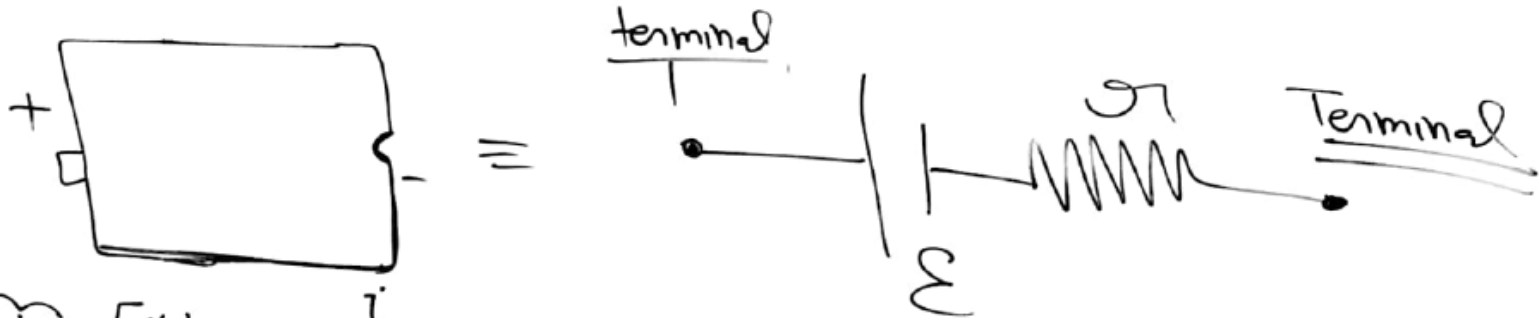⇒ battery : [ Emf + internal resistance ]



Ex:-

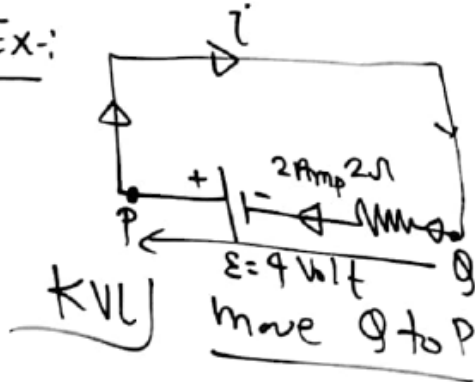

$$i = \frac{\mathcal{E}}{r}$$

$$i = \frac{9}{2} = 2Amp$$


$$V_Q - 2 \times 2 + 9 = V_P$$

$$V_P - V_Q = 0$$

terminal potential

Emf of battery:-

(1)

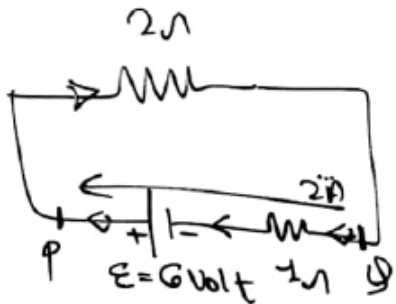

KVL

$$V_Q - 2 \times i + 6 = V_P$$

$$V_P - V_Q = 4 \text{ Volt}$$



⇒ Emf of battery = 6 Volt

⇒ Terminal potential = 4 Volt

⇒ Emf ∴ If  $i = 0$

$$\underline{\underline{T.P = E}}$$

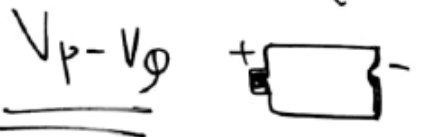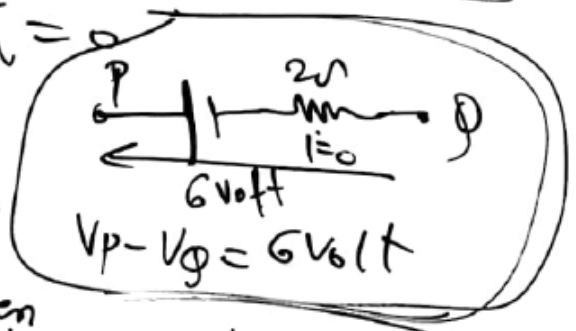
When battery is connected with open CKT then its terminal potential equal to its Emf.



$$R_{eq} = 2 + 1 = 3 \Omega$$

$$i = \frac{E}{R_{eq}} = \frac{6}{3} = 2 \text{ Amp}$$

(i) discharging of battery:-

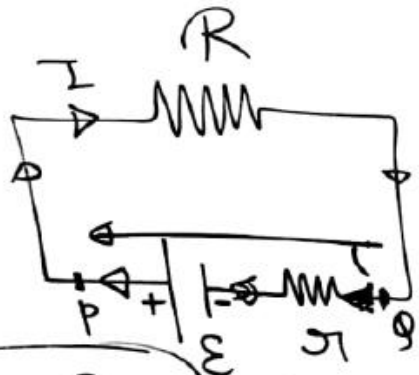

$r$  = internal resistance of battery

$R$  = External Resistance

**\*\***  $\epsilon$  = Emf of battery.

$$R_{eq} = r + R$$

$$T.P = V_p - V_q = \epsilon - \left(\frac{\epsilon}{r+R}\right)r$$

$$T.P = \epsilon - ir$$

$$I = \frac{\epsilon}{R+r}$$

Terminal Potential (T.P) =

$$V_q - ir + \epsilon = V_p$$


$$T.P = V_p - V_q = \epsilon - ir$$

**\*\***  
**\*\***  
**\*\***  
In case of discharging  
of battery


$$T.P < \epsilon$$

$$T.P < \epsilon_{mf}$$

(i) discharging of battery:-

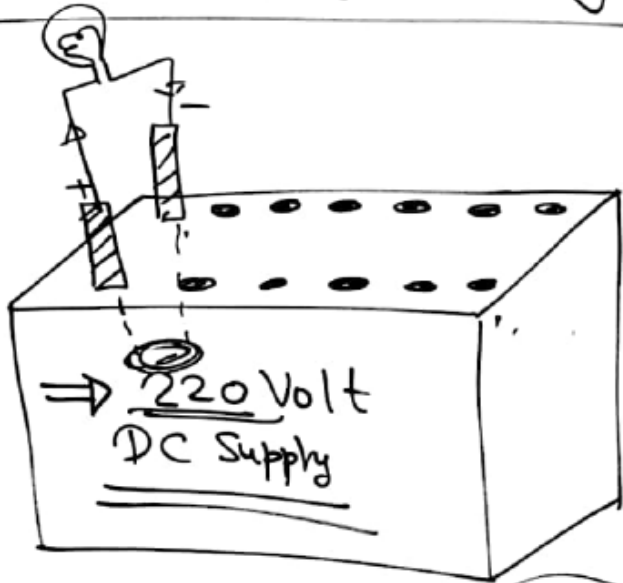


≡

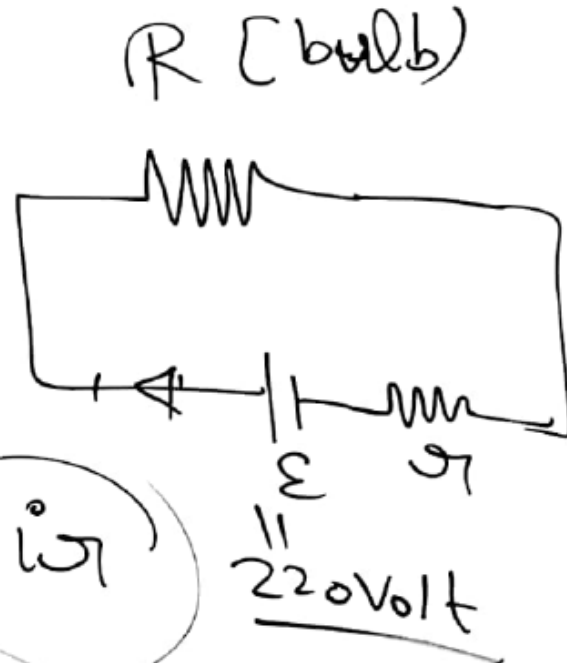

Tip =  $\mathcal{E} - i r$

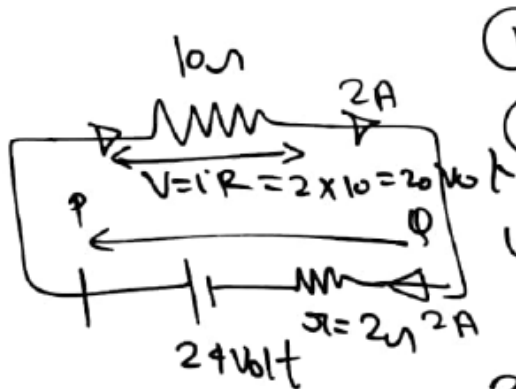(i) discharging of battery:-

⇒ Q.2) Find terminal potential of battery.



(i)  $i = 2$

(ii) T.P of battery = 20 Volt

(iii) Potential across resistor  $R$

$$\underline{V_p - V_q} = \underline{\epsilon - i r}$$


$$= 24 - 2 \times 2$$

$$\boxed{\text{T.P} = 20 \text{ Volt}}$$

(2)  $R_{eq} = \frac{10 + 2}{1} = 12 \Omega$       $i = \frac{24}{12} = 2 \text{ Am}$

$\epsilon_{mg} = 24 \text{ Volt}$

⇒ Charging of battery

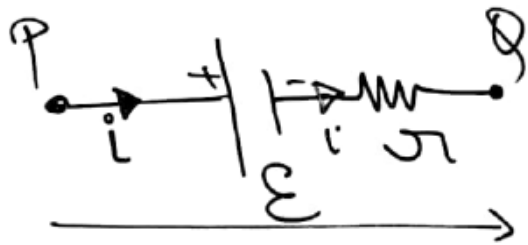


$V_P - V_Q = T.P$

$V_P - \varepsilon - i r = V_Q$

$V_P - V_Q = \varepsilon + i r$

$T.P = \varepsilon + i r$  [  $T.P = V_P - V_Q > \varepsilon$  ]

Discharging of battery

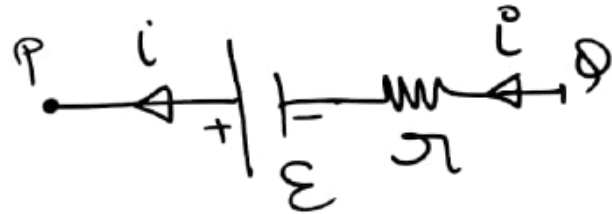

$T.P \Rightarrow V_P - V_Q = \varepsilon - i r$

$V_Q - i r + \varepsilon = V_P$

$V_P - V_Q = \varepsilon - i r$

$T.P = V_P - V_Q < \varepsilon$


#

Electrical Power (P) :-

$V = IR$  [from Ohm's Law]

$$P = Vi = V\left(\frac{V}{R}\right) = \frac{V^2}{R} \quad \left[i = \frac{V}{R}\right] = Vi = (iR)i = \underline{\underline{i^2 R}}$$

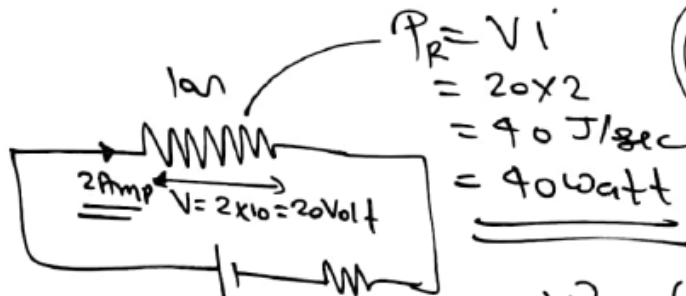Power = (Potential drop across resistance) (Electric current through resistor)



$$P_R = Vi = 20 \times 2 = 40 \text{ J/sec} = \underline{\underline{40 \text{ watt}}}$$

$$P = Vi = \frac{V^2}{R} = i^2 R$$


$$i = \frac{20}{10} = 2 \text{ Amp}$$

$$P_R = \frac{V^2}{R} = \frac{(20)^2}{10} = \frac{400}{10} = 40 \text{ J/sec} = \underline{\underline{40 \text{ watt}}}$$

$$P_R = (2)^2 \times 10 = 4 \times 10 = 40 \text{ watt}$$



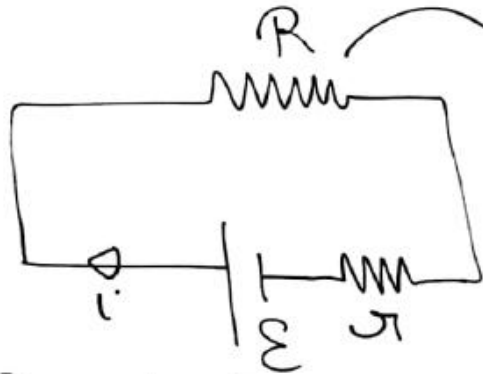⊕ Value of  $R$  [external resistance for maximum power dissipation]



$$\text{Power} = i^2 R$$

$$P = \left( \frac{\epsilon}{R+r} \right)^2 R = \frac{\epsilon^2 R}{(R+r)^2}$$

For maximum power  $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = 0$$

Condition  $r = R$

- (i)  $R$  = external resistance  
 $r$  = internal resistance  
 $\epsilon$  = Emf of battery.


$$i = \frac{\epsilon}{R+r}$$

\*\*\*\*  
 External resistance  
 ||  
 Internal resistance

For maximum Power  
 dissipation

# Value of R [external resistance for maximum power dissipation]


Q3)

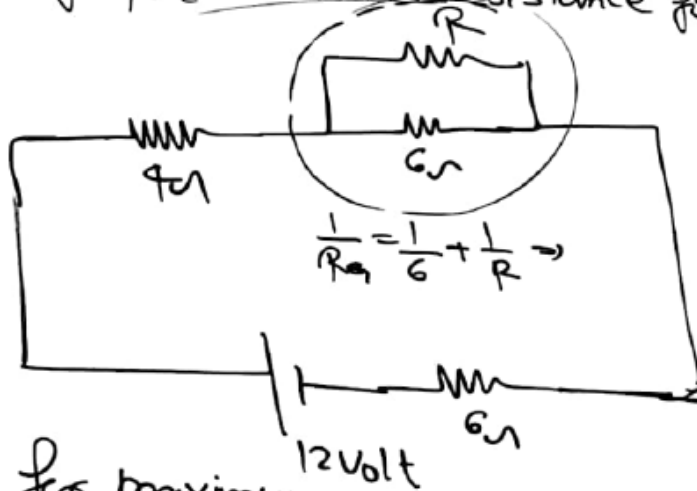

\* For maximum power consumption Value of R is equal to

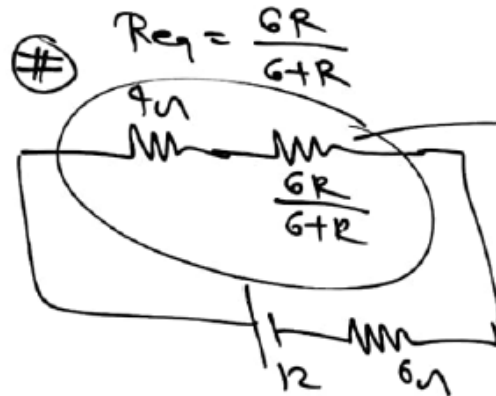- (a) 9Ω
- (b) 3Ω
- (c) 6Ω
- (d) A.I.O.T.

Hint] For maximum power dissipation  
 $R = R_{ext}$



$$R_{ext} = 9 + \frac{6R}{6+R} = 6$$

$$\frac{6R}{6+R} = 6 - 9$$

$$\frac{6R}{6+R} = -3$$

$$6R = -3(6+R)$$

$$6R = -18 - 3R$$

$$9R = -18$$

$$R = -2$$

$R = 3\Omega$