
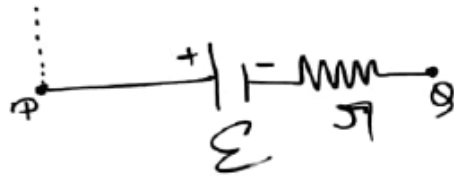


→ Cell:-

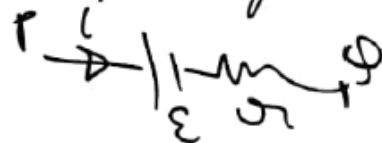

$$V_P - V_Q = \epsilon$$

⇒ (iii) charging of battery.




$$V_P - \epsilon - i r = V_Q$$

$$V_P - V_Q = \epsilon + i r$$

$$\boxed{T.P > \epsilon}$$

(ii) when battery is discharging.

⇒

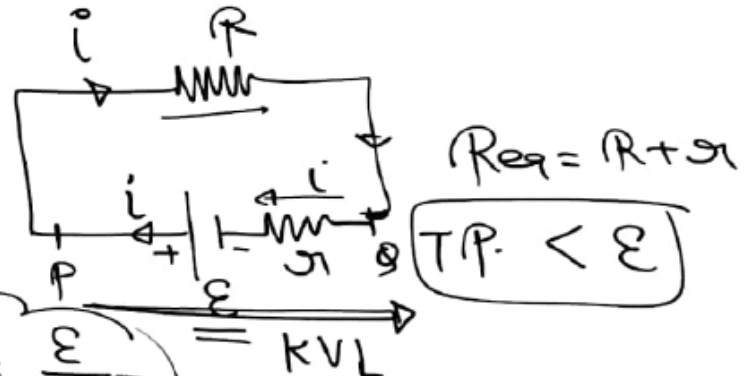


$$i = \frac{\epsilon}{R + r}$$

$$V_P - \epsilon + i r = V_Q$$

$$V_P - V_Q = \epsilon - i r$$

$$\boxed{T.P = \epsilon - i r}$$

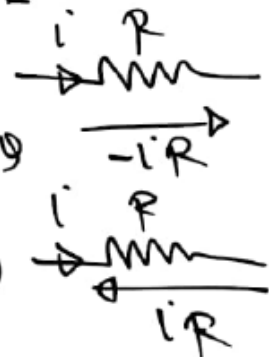

Electrical Cell

- ⇒ Internal resistance of cell
- ⇒ dependency of internal resistance.
- ⇒ How to increase or decrease internal resistance of cell


$\sigma \propto d$  (ii)

$\sigma \propto \frac{1}{T}$

$\sigma \propto C$

$\sigma \propto \frac{d}{T}$


$\sigma \propto \frac{1}{A}$

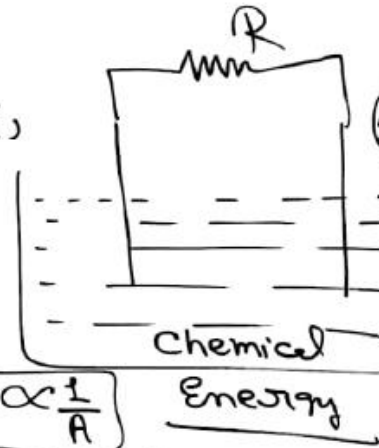

$\sigma = \frac{dC}{AT}$



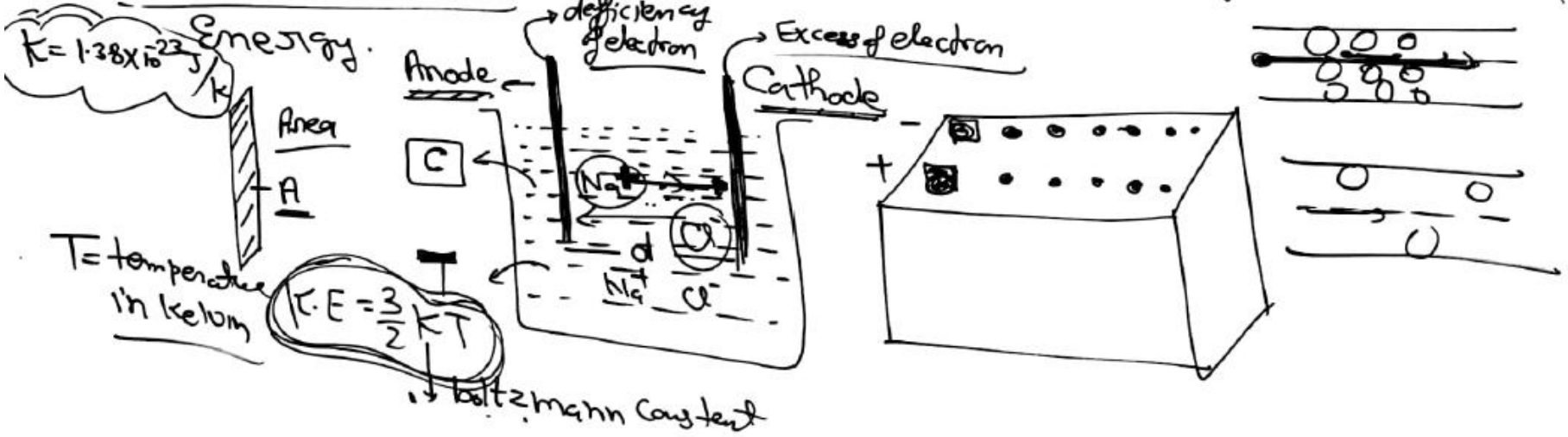⇒ Electrical cell: It Convert Chemical Energy into Electrical



$k = 1.38 \times 10^{-23} \text{ J/K}$

$K.E = \frac{3}{2} kT$

T = temperature in kelvin


↓ Boltzmann Constant

- series Connection -
- Parallel Connection -
- Mixed -

①  $R_{eq} = R + r_1 + r_2 + r_3$


$E_{net} = E_1 + E_2 + E_3$

$i = \frac{E_{net}}{R_{net}}$

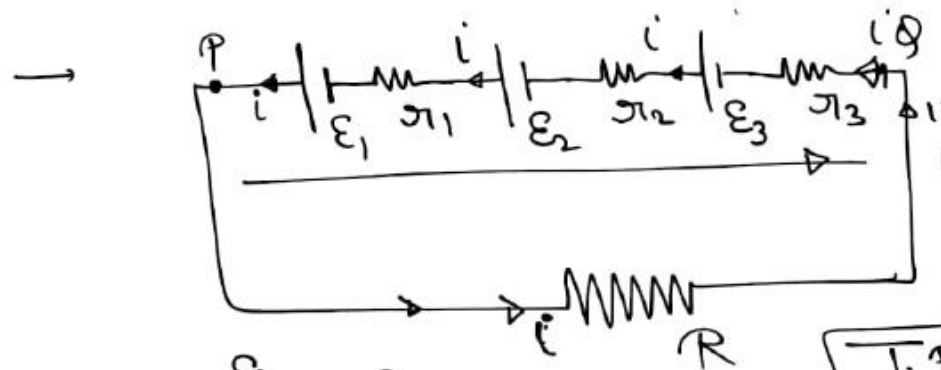



$i = \frac{E_1 + E_2 + E_3}{R + r_1 + r_2 + r_3}$

$T.P = V_P - V_Q = i R$

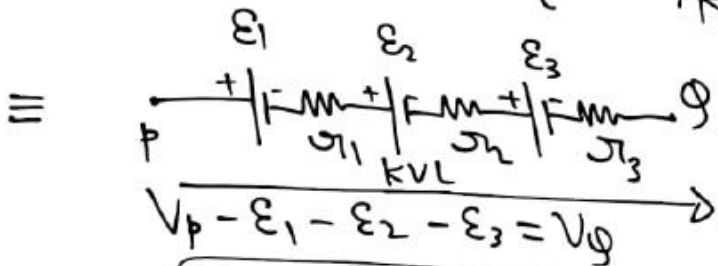

$V_P - V_Q = E_1 + E_2 + E_3$

$T.P = E_1 + E_2 + E_3$

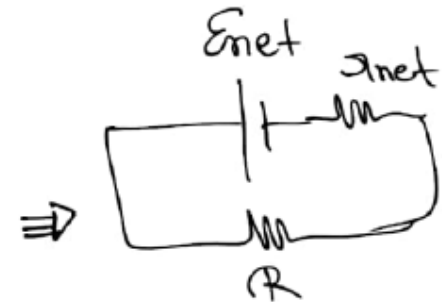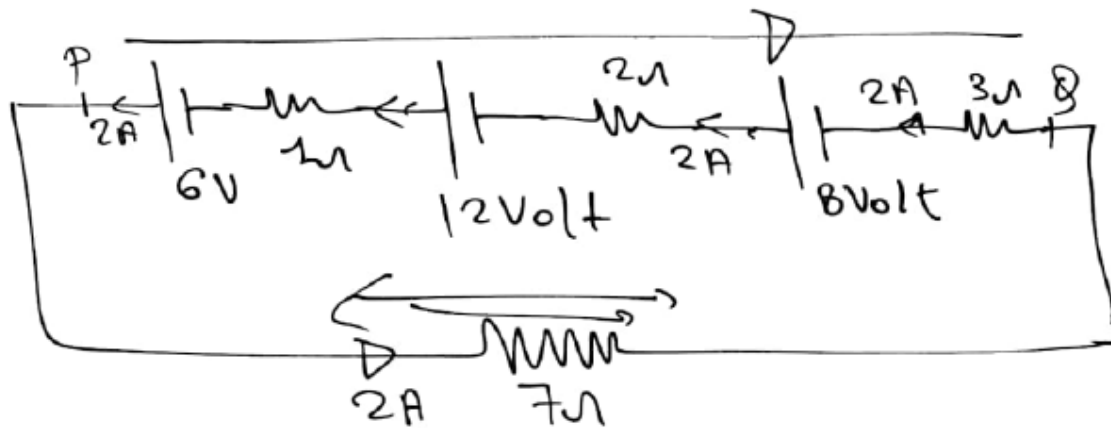



(i)  $E_{net} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 = 6 + 12 + 8 = 26 \text{ Volt.}$

(ii)  $R_{eq} \Rightarrow R_{eq} = R_{int} + R_{ext} = 6 + 7 = \underline{\underline{13\Omega}}$

(iii)  $I \text{ in ckt } I = \frac{E_{net}}{R_{net}} = \frac{26V}{13\Omega} = \underline{\underline{2 \text{ Amp}}}$

(iv) Tip across the battery  $V_p - V_\phi = 2 \times 7 = \underline{\underline{14 \text{ Volt}}}$

#

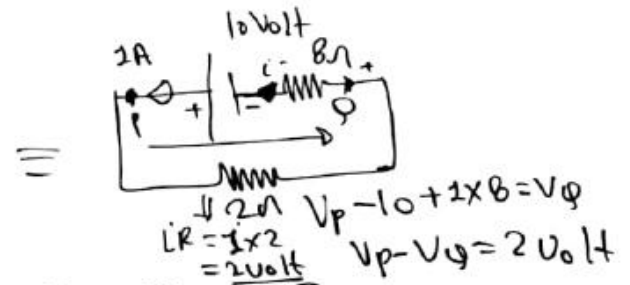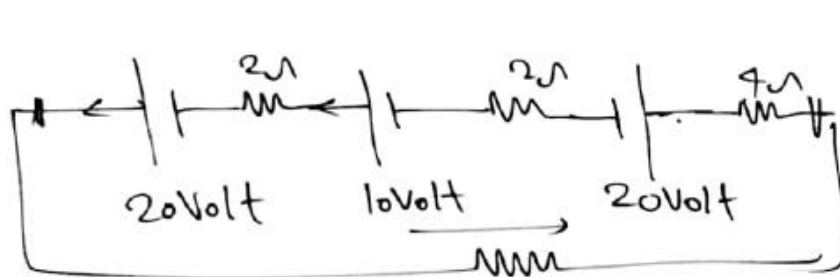

(i)  $i_{in} \text{ CKT} = \frac{E_{net}}{R_{net}} = \frac{10}{10} = \underline{\underline{1 \text{ Amp}}}$

(ii)  $E_{net} = 10 \text{ Volt}$

(iii)  $i_{net}$ , Req of the CKT


(iv) T.P across the combination of battery.

$E_{net} = E_1 + E_2 + E_3$   
 $= 20 + 10 - 20$

$E_{net} = 10 \text{ Volt}$

$i_{net} = 8 \Omega$

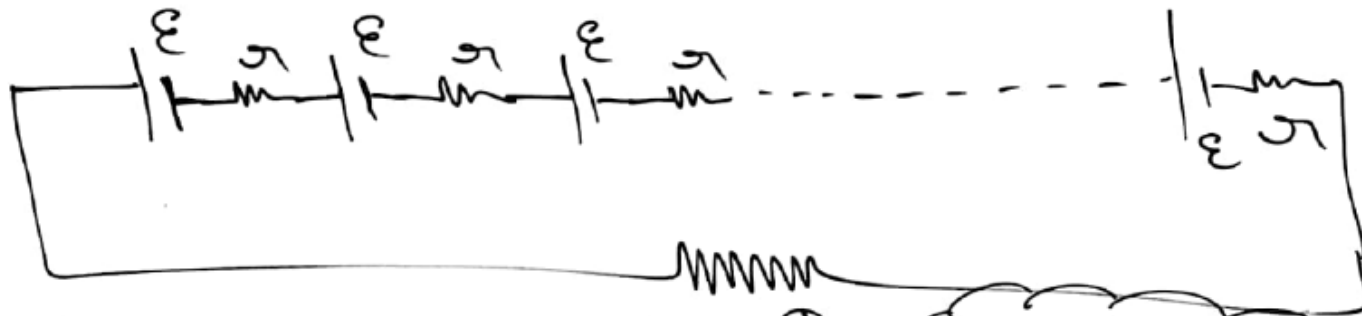⊕ ⊕  $n$ -cell of Emf  $\mathcal{E}$  & internal resistance  $r$ .  
 Connected in same polarity. Find  $\mathcal{E}_{net}$ ,  $r_{net}$  if it is  
 with  $R$  External resistance  $R$ .  $n$ -cell



$$\Rightarrow \mathcal{E}_{net} = \mathcal{E} + \mathcal{E} + \mathcal{E} + \dots - n \text{ times } R$$



$$= \underline{\underline{n\mathcal{E}}}$$

$$\Rightarrow r_{net} = r + r + \dots - n \text{ times}$$

$$= \underline{\underline{nr}}$$

$$\underline{\underline{R_{eq} = R + nr}}$$
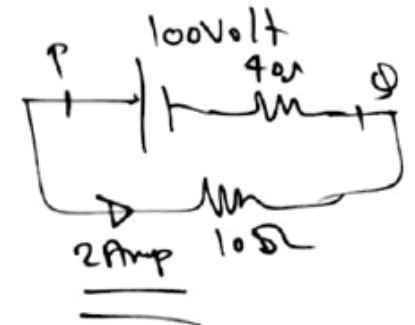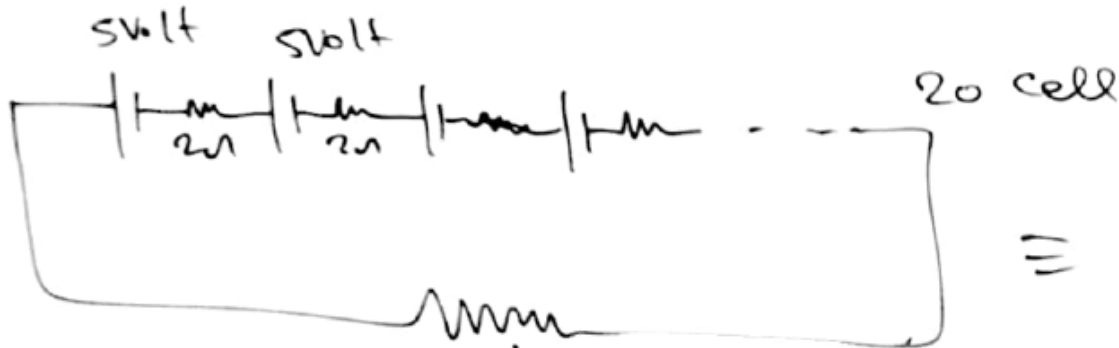
$$i = \frac{\mathcal{E}_{net}}{R_{net}} = \frac{n\mathcal{E}}{nr + R}$$



→  $E_{net} = nE = 20 \times 5 = 100 \text{ Volt}$   
 $E_{net} = 100 \text{ Volt}$

$r = \frac{100}{50}$

$i = 2 \text{ Amp}$


$V_p - V_q = 2 \times 10 = 20 \text{ Volt}$

$r_{net} = 20 \times 2 = 40 \Omega$

$r_{net} = 40 \Omega$

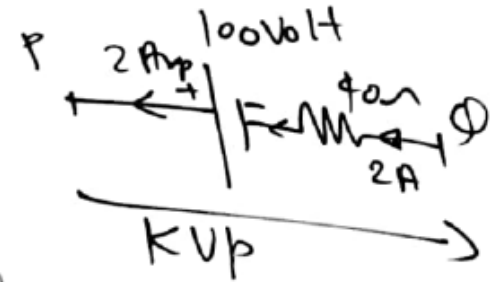
# T.P

$R_{net} = r_{net} + R$   
 $= 50 \Omega$



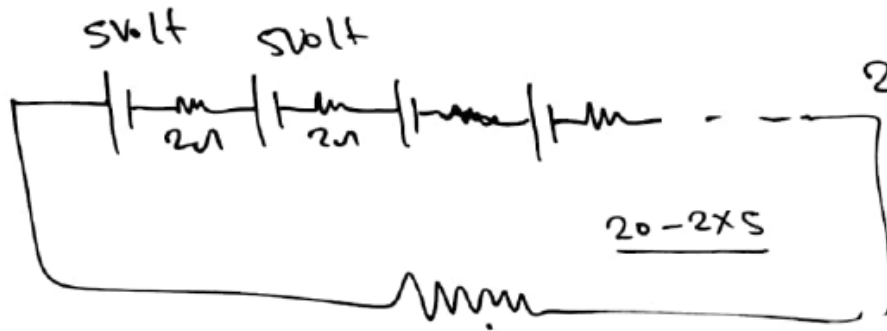$V_p - 100 + 2 \times 40 = V_q$   
 $V_p - V_q = 20 \text{ Volt}$





$n$  cell  
 $20$  cell  
 $(n - 2m)$   
 $20 - 2 \times 5 = 10 \text{ cell} = 50 \text{ Volt}$

$m$  cell reverse  
 $5$  cell

$\Rightarrow$  If 5 cell connected opposite polarity in out of 20 cell.

