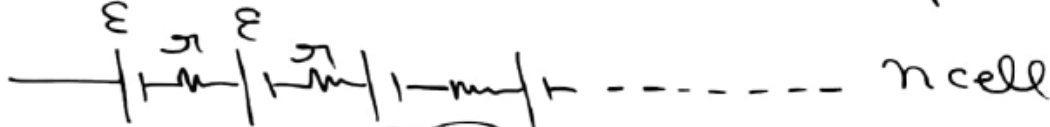


Series Connection of battery



n -cell are connected in series with polarity.



$E_{net} = n\epsilon$

$r_{net} = nr$


$E_{net} = 6\epsilon - 2\epsilon$

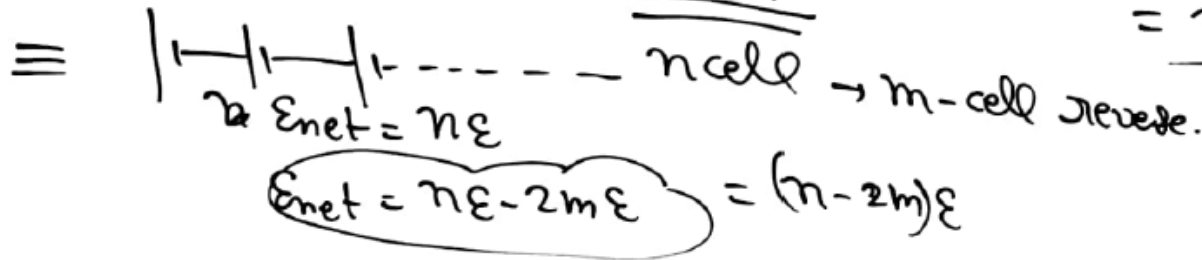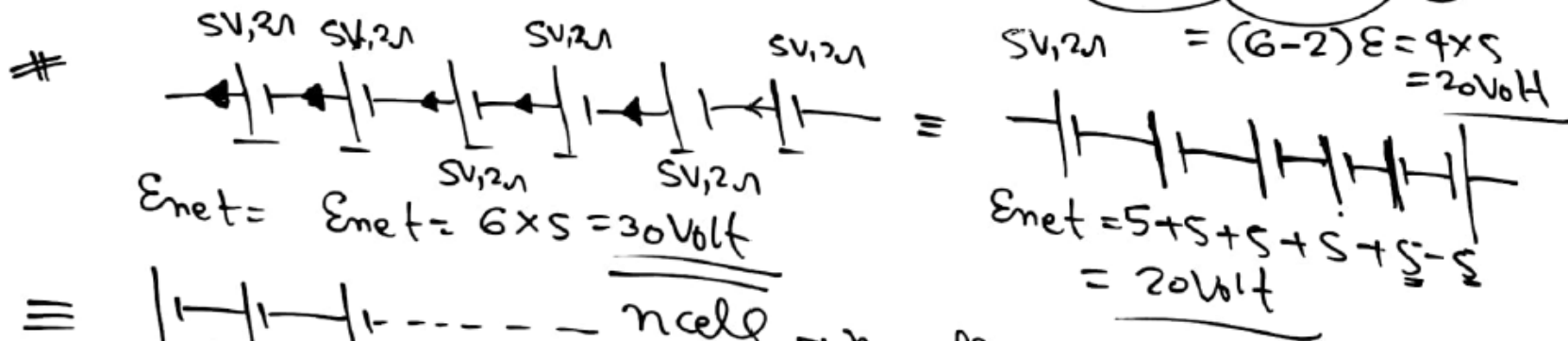

* Series Connection of battery


= 20 cell each of Emf 10 Volt & internal resistance 2Ω connected in series. Find E_{net} & r_{net} .

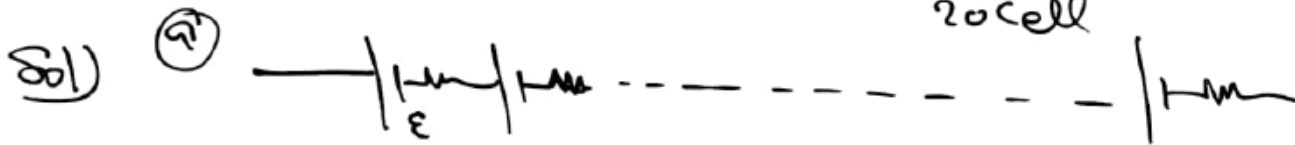(b) If 4 cell is connect opposite polarity in out of 20 then find a net Emf of combination of cell, E_{net} .



$$E_{net} = 20 \times 10 = 200 \text{ Volt}$$


$$r_{eq} = 20 \times 2 = 40 \Omega$$

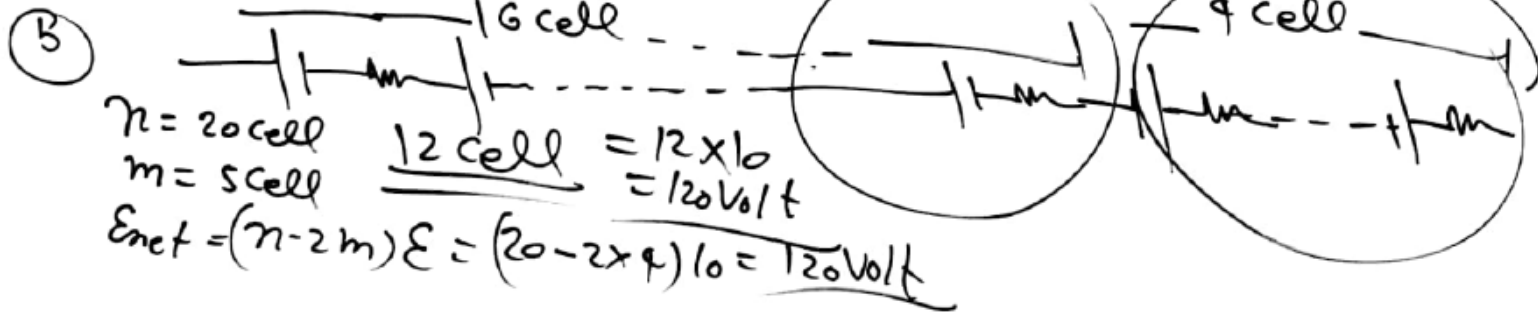

Series Connection of battery

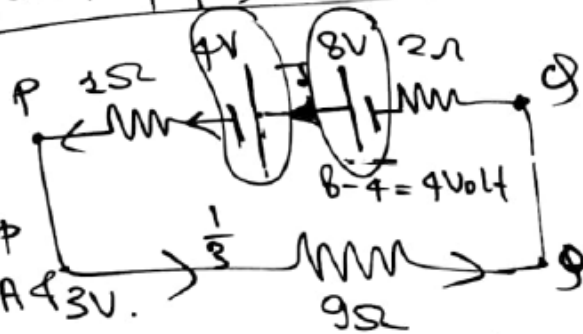Q. 12 PMT


Q) Two batteries of emf 4V & 8V with internal resistance 1Ω & 2Ω are connected in a ckt with resistance of 9Ω as shown in figure. The current & potential difference b/w the point P & Q are.




$$E_{net} = 8 - 4 = 4 \text{ Volt}$$

$$R_{eq} = 12 \Omega$$
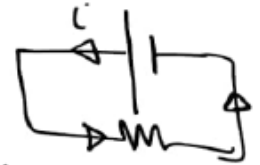
$$i = \frac{E_{net}}{R_{net}} = \frac{4}{12} = \frac{1}{3} \text{ Amp}$$



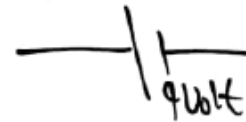
$$V_P - V_Q = \frac{1}{3} \times 9 = 3 \text{ Volt}$$



- (a) $\frac{1}{3} \text{ A}$ & 3V.
- (b) $\frac{1}{6} \text{ A}$ & 4V.
- (c) $\frac{1}{9} \text{ A}$ & 8V.
- (d) $\frac{1}{12} \text{ A}$ & 12V.

Series Connection of battery - 1

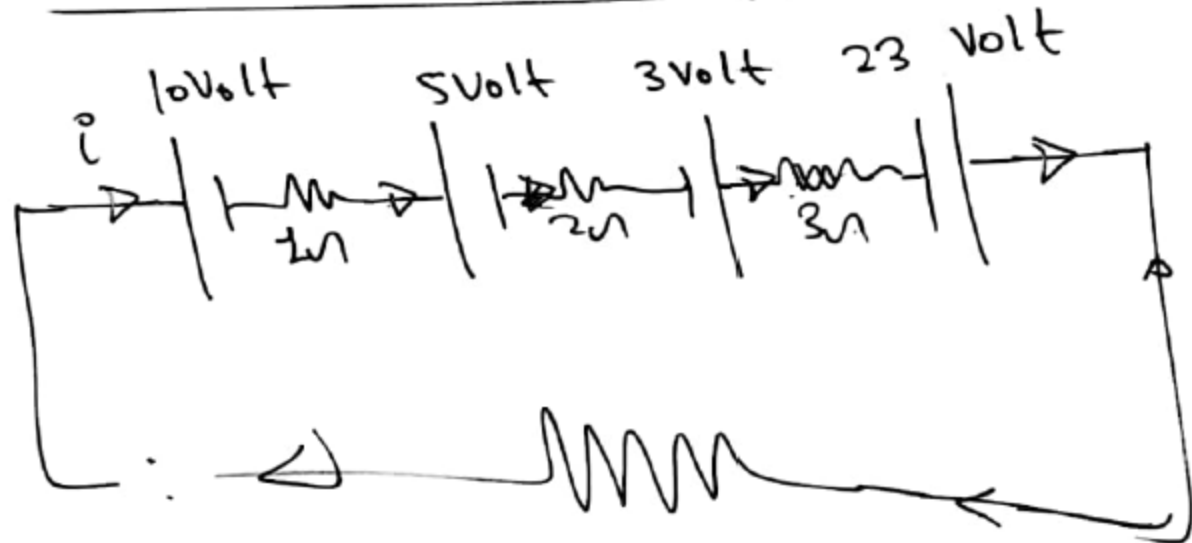

$$E_{net} = 23 + 3 - 5 - 10 = 11 \text{ Volt}$$


$$R_{eq} = 2\Omega + 2\Omega + 3\Omega = 8\Omega$$

$$i = \frac{E_{net}}{R_{eq}} = \frac{11}{8} \text{ Amp}$$

$E_{net} = 11 \text{ Volt}$

$i = \frac{11}{8} \text{ Amp}$

Parallel Connection

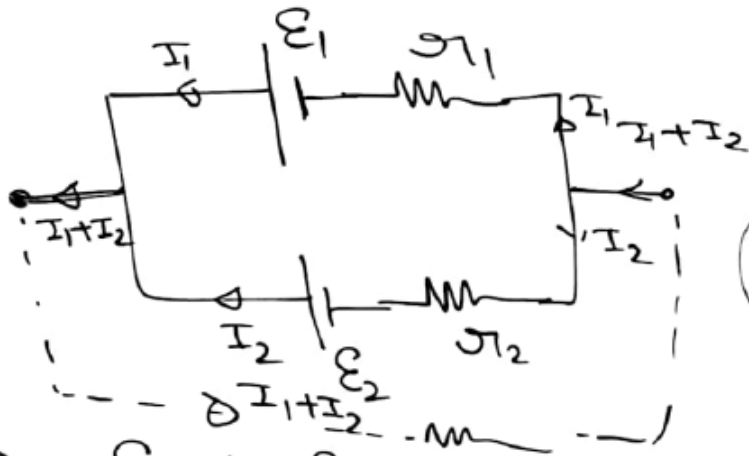

$$r_{eq} = ?$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} \Rightarrow r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$


$$E_{net} = \frac{\frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}}$$

$$E_{net} = \frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 r_2} = \frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 + r_2}$$


$$E_{net} = \frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 + r_2}$$

$$E_{net} = \frac{\frac{\epsilon_1}{r_1} - \frac{\epsilon_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} = \frac{\epsilon_1 r_2 - \epsilon_2 r_1}{r_1 + r_2}$$

⇒ $E_{net} = ?$

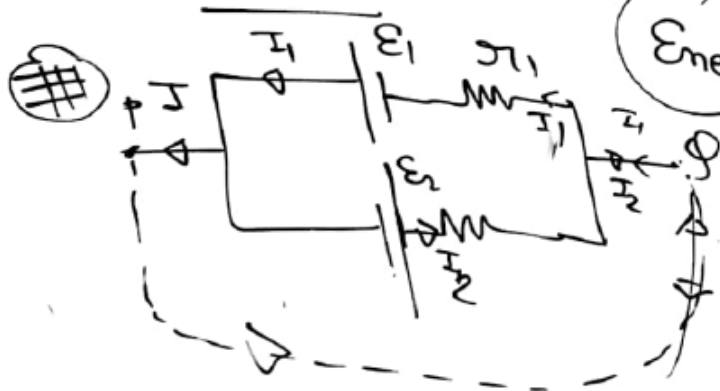


Parallel Connection

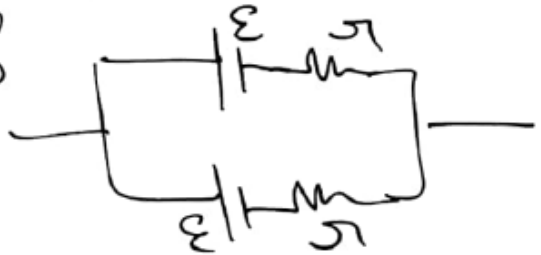



$$\Rightarrow E_{net} = \frac{\epsilon r + \epsilon r}{r + r} \left[\frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 + r_2} \right]$$

$$E_{net} = \frac{2\epsilon r}{2r} = \underline{\underline{\epsilon}}$$
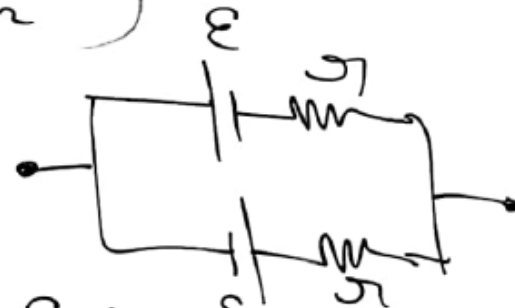
$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} \Rightarrow r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$


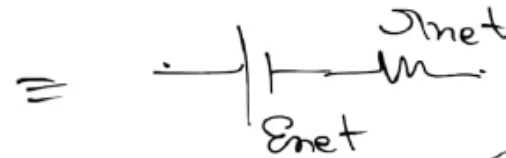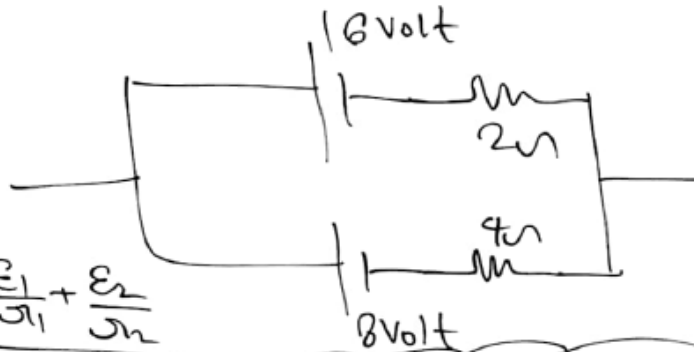
$$E_{net} = \frac{\epsilon_1 r_2 - \epsilon_2 r_1}{r_1 + r_2} = \underline{\underline{0}}$$




$$E_{net} = \frac{E_1 + E_2}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$E_{net} = \frac{E_1 R_2 + E_2 R_1}{R_1 + R_2}$$

$$\begin{aligned} E_1 &= 16 \text{ Volt} & R_1 &= 2 \Omega \\ E_2 &= 8 \text{ Volt} & R_2 &= 4 \Omega \\ &= \frac{16 \times 4 + 8 \times 2}{6} = \frac{64 + 16}{6} = \frac{80}{6} \\ &= \frac{40}{3} = \underline{\underline{13.33 \text{ Volt}}} \end{aligned}$$

Q2)

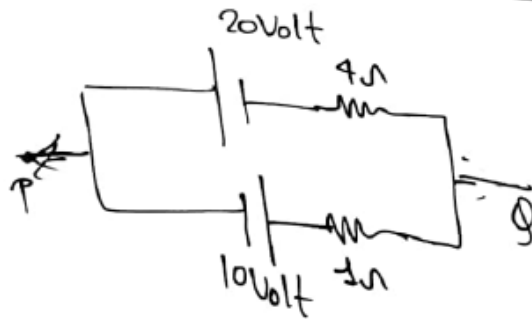

$$\equiv \underline{\underline{E_{net} \text{ f } R_{net}}}$$

$$E_1 = 20 \text{ Volt} \quad E_2 = -10 \text{ Volt}$$

$$R_1 = 4 \Omega \quad R_2 = 1 \Omega$$

$$\frac{20 \times 1 + (-10) \times 4}{4 + 1} = \frac{20 - 40}{5}$$


$$= \frac{-20}{5} = \underline{-4 \text{ Volt}}$$

$$R_{eq} = \frac{4 \times 1}{4 + 1} = \frac{4}{5} = \underline{0.8 \Omega}$$

$$\frac{E_1 R_2 + E_2 R_1}{R_1 + R_2} = E_{net}$$

Q2)



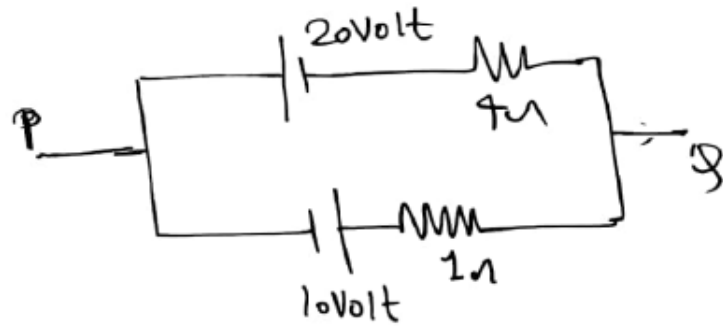

Let current flow from P to Q.

$$E_1 = 20 \text{ Volt} \quad r_1 = 4 \Omega$$

$$E_2 = -10 \text{ Volt} \quad r_2 = 1 \Omega$$

$$E_{\text{net}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} = \frac{20 \times 1 - 10 \times 4}{5}$$

$$E_{\text{net}} = \underline{\underline{-4 \text{ Volt}}}$$

Let dirⁿ of current from ϕ to ϕ

$$E_1 = -20 \quad r_1 = 4 \Omega$$

$$E_2 = 10 \text{ Volt} \quad r_2 = 1 \Omega$$


$$\Rightarrow E_{\text{net}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$= \frac{-20 \times 1 + 10 \times 4}{4 + 1}$$

$$= \underline{\underline{+20}} = 4 \text{ Volt}$$

Q2)

n-Cell

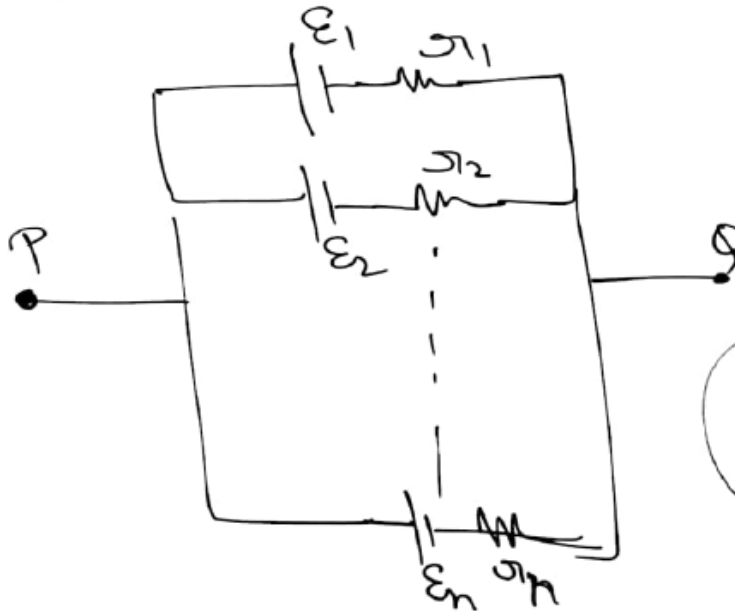



Connected with parallel combination
in same polarity.

$$E_{net} = \frac{E_1}{r_1} + \frac{E_2}{r_2} + \dots + \frac{E_n}{r_n}$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

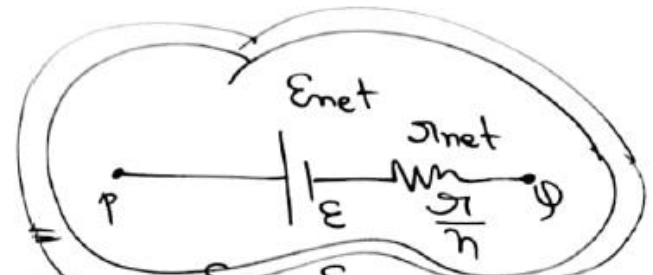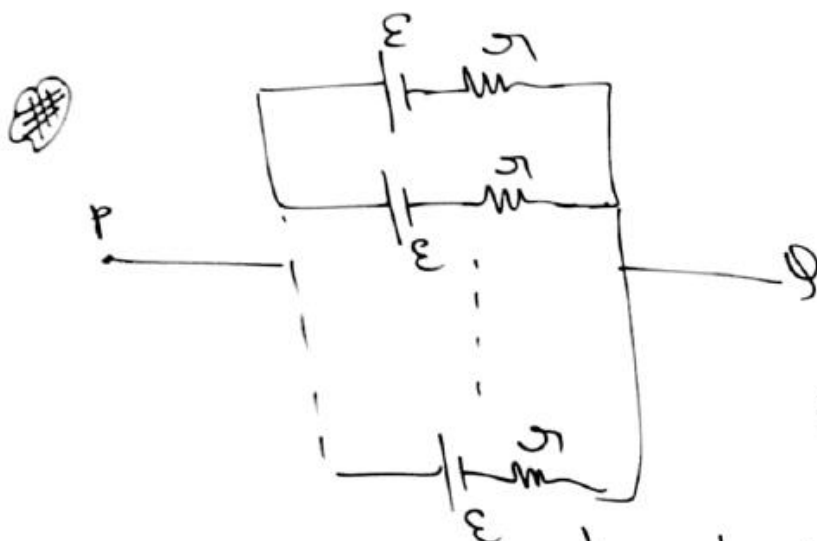If n cells have same Emf & same internal resistance.
 Find Equivalent Emf & Equivalent resistance.



$$E_{net} = \frac{E}{\frac{1}{n} + \frac{1}{n} + \dots + \frac{1}{n}}$$

$$E_{net} = \frac{nE}{\frac{1}{n} + \frac{1}{n} + \dots + \frac{1}{n}} = E_{net}$$

$$\frac{1}{r_{net}} = \frac{1}{r} + \frac{1}{r} + \dots + \frac{1}{r}$$

$$r_{net} = \frac{r}{n}$$