
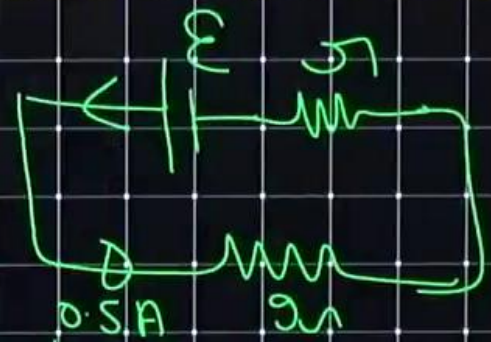


~~Q1~~

Q1: A Current of 2A flow through a  $2\Omega$  resistor when connected across a battery. The same battery supplies a current of 0.5A when connected across a  $9\Omega$  resistor. The internal resistance of battery.

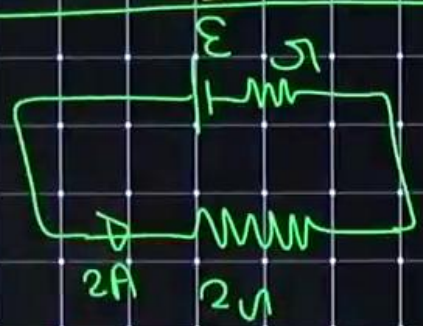- (a)  $0.5\Omega$
- (b)  $1/3\Omega$
- (c)  $2/3\Omega$
- (d)  $1\Omega$



$$R_{eq} = r + 2$$

$$E_{net} = E$$

$$i = \frac{E}{r + 2}$$

$$2A = \frac{E}{r + 2} \quad (1)$$

$$E = 2(r + 2)$$

$$2(r + 2) = 0.5(r + 9)$$

$$2r + 4 = 0.5r + 4.5$$

$$1.5r = 0.5$$

$$r = \frac{1}{3} \Omega$$

$$E_{net} = E$$

$$R_{net} = r + 9$$

$$i = \frac{E}{r + 9}$$

$$\Rightarrow 0.5 = \frac{E}{r + 9}$$

$$E = 0.5(r + 9)$$

1/3

Q1) NEET 2013


The internal resistance of a 2.1V cell which gives a current of 0.2A through a resistance of 10Ω is.

a) 0.8Ω

b) 1.0Ω

c) 0.2Ω

d) 0.5Ω

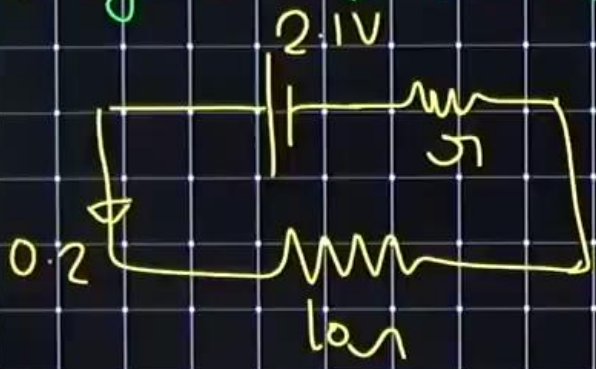

$$E_{net} = 2.1 \text{ Volt}$$

$$R_{eq} = r + 10$$

$$i = \frac{E_{net}}{R_{eq}} \Rightarrow 0.2 = \frac{2.1}{r + 10}$$

$$0.2r + 2 = 2.1$$



$$0.2r = 0.1$$

$$r = \frac{0.1}{0.2} = \frac{1}{2} = \underline{\underline{0.5\Omega}}$$

83) AI PM 7

For a cell terminal potential difference is 2.2V when ckt is open & reduce to 1.8V when cell is connected a resistance of 5Ω. Determine internal resistance of cell

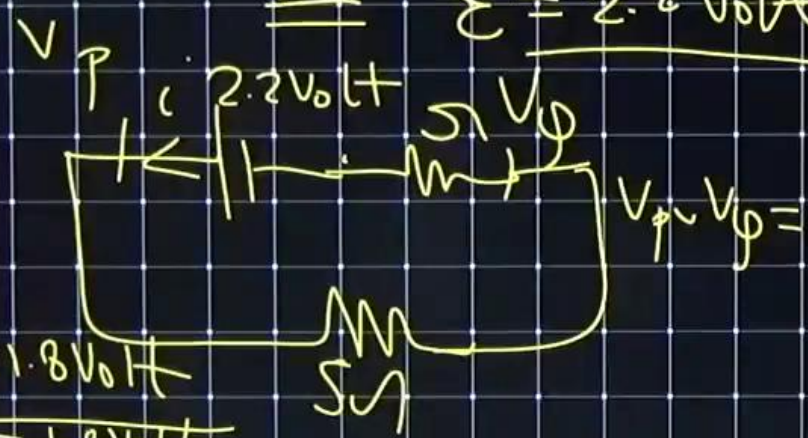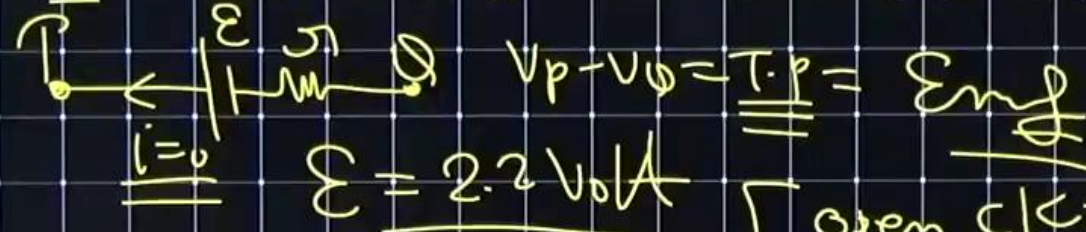
- (a) 1/9 Ω
- (b) 9/16 Ω
- (c) 11/9 Ω
- (d) 8/9 Ω



open ckt  
 $\text{T.P.} = \epsilon$   
 discharging  
 $\text{T.P.} = \epsilon - i r$   
 $\text{T.P.} < \epsilon$


charging  
 $\text{T.P.} = \epsilon + i r$   
 $\text{T.P.} > \epsilon$

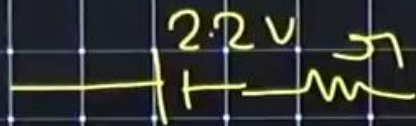$V_p - V_q = 1.8 \text{ Volt}$   
 $\frac{\epsilon - i r}{\epsilon - 0.5 r} = 1.8 \text{ Volt}$



$$\mathcal{E} = 2.2 \text{ Volt}$$

$$\mathcal{E} - i r = 1.8 \text{ Volt}$$

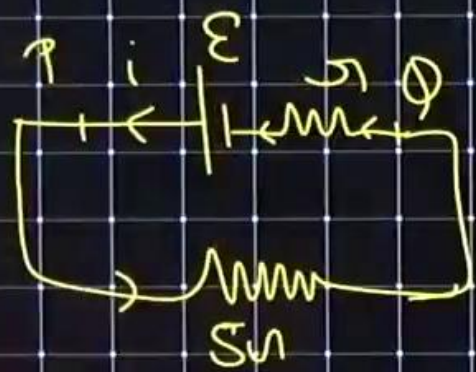

$$V_P - V_\phi = T.P.$$

$$V_P - V_\phi = 1.8 \text{ Volt}$$

$$V_P - \mathcal{E} + i r = V_\phi$$

$$V_P - V_\phi = \mathcal{E} - i r$$

$$r = \frac{20}{18}$$

$$r = \frac{10}{9} \Omega$$

$$i = \frac{\mathcal{E}}{r + 5}$$

$$2.2 - \left( \frac{2.2}{5 + r} \right) r = 1.8 \text{ Volt}$$






$$2.2 - 1.8 = \frac{2.2 r}{5 + r}$$

$$\Rightarrow 0.4 r + 2 = 2.2 r$$

$$2 = 1.8 r$$

$$.4 = \frac{2.2 r}{5 + r}$$

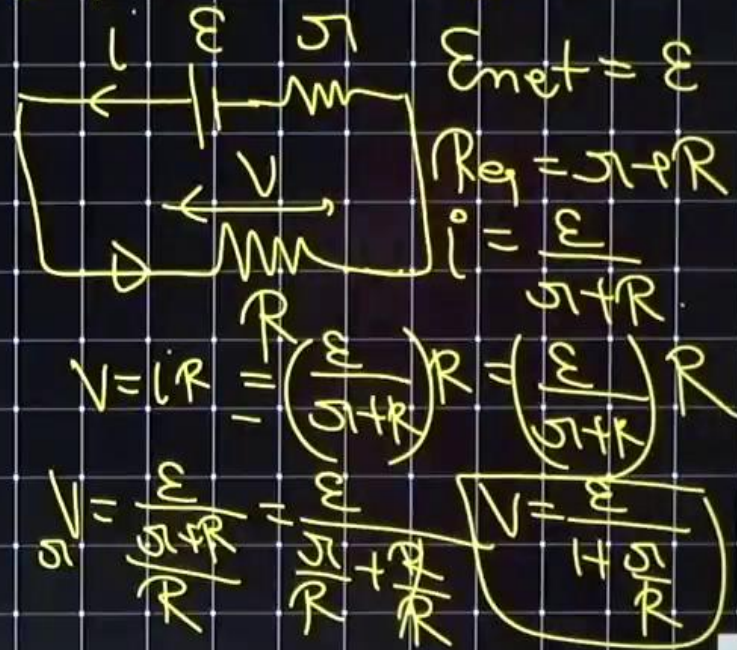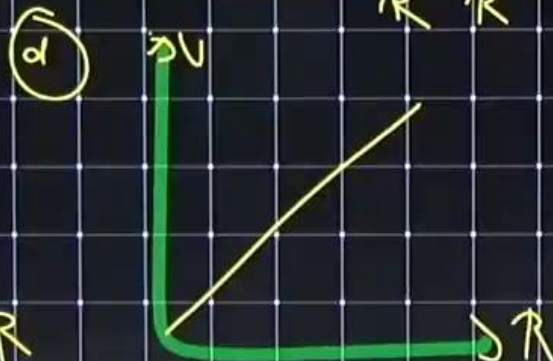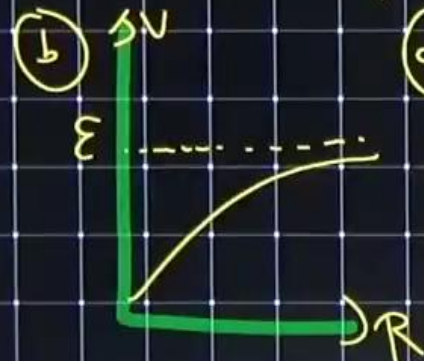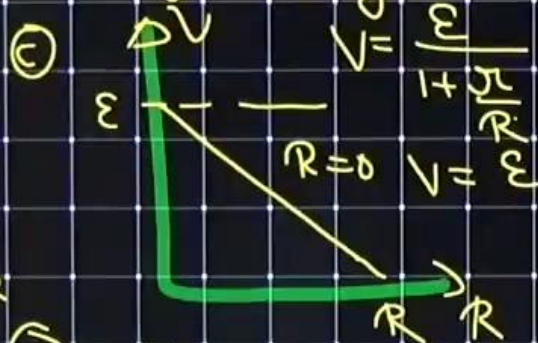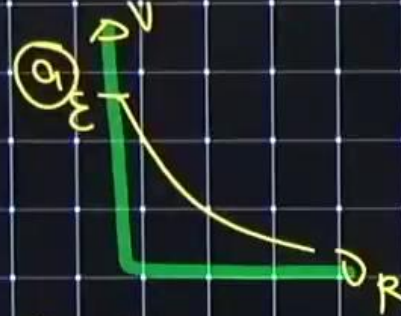Q) A Cell having an emf  $\epsilon$  & internal resistance  $r$  is connected across a variable external resistance  $R$ . As the Resistance  $R$  is increased, the plot of potential difference  $V$  across  $R$  is given by



# Two battery, one of Emf 18 Volt & internal resistance  $2\Omega$  other of Emf 12 Volt & internal resistance  $1\Omega$ , are connected as shown. The Voltmeter V will record of

(a) 30V.

(b) 18 Volt.


(c) 15 Volt

~~(d) 19 Volt.~~

$$E_{\text{net}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$= \frac{18 \times 1 + 12 \times 2}{2 + 1}$$
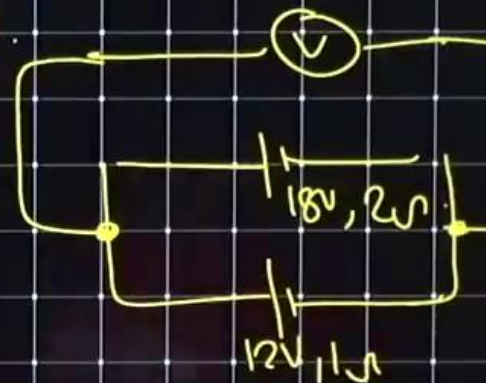
$$= \frac{18 + 24}{3} = 6 + 8 = 14 \text{ Volt}$$



**14 Volt**