
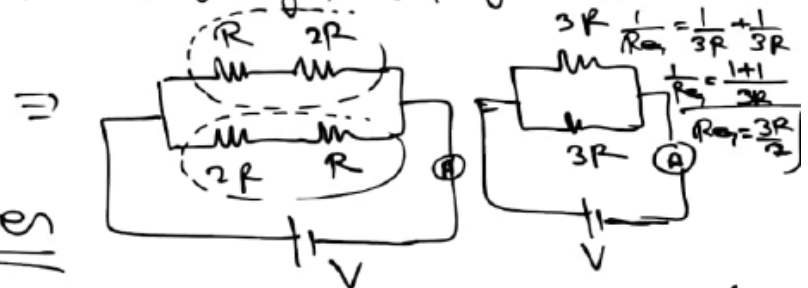


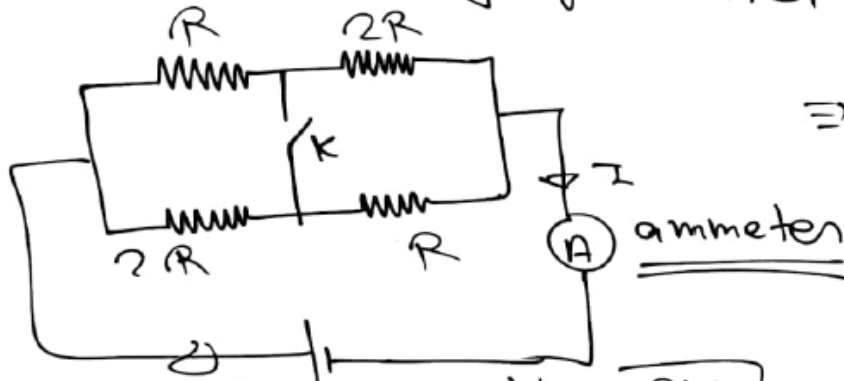Q21: How will the reading of ammeter change if the key K is closed.



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3R \times 3R}{3R + 3R} = \frac{3R}{2}$$




- (a) increases [✓]
- (b) Decrease.
- (c) Remains same.
- (d) Information insufficient.

When key is closed

$$I = \frac{V}{\frac{5R}{2}} = \frac{2V}{5R}$$

$$I' = \frac{3V}{4R}$$


$$I = 0.75 \frac{3V}{4R}$$

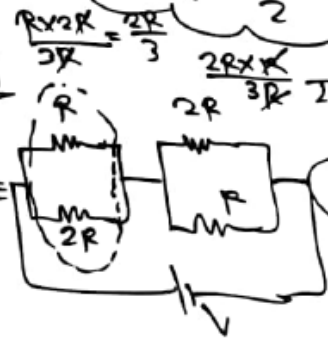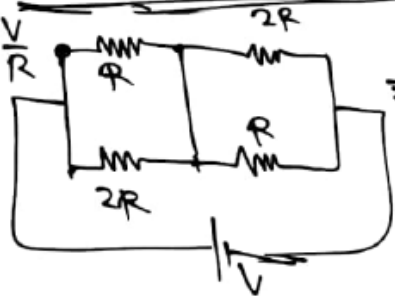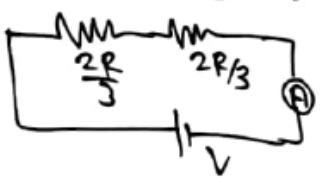


$$I = \frac{2V}{\frac{3R}{2}} = 0.67 \frac{V}{R}$$

32) Five equal resistance each of resistance R are connected as shown in figure. A battery of voltage V is connected A & B. The current flowing in AFCEB will be.


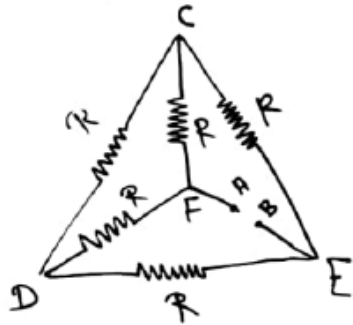
- (a) $\frac{V}{R}$
- (b) $\frac{V}{2R}$ ←
- (c) $\frac{2V}{R}$
- (d) $\frac{3V}{R}$



≡

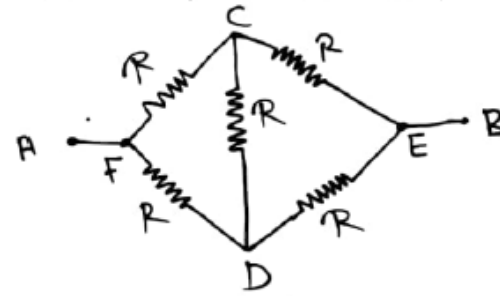


≡

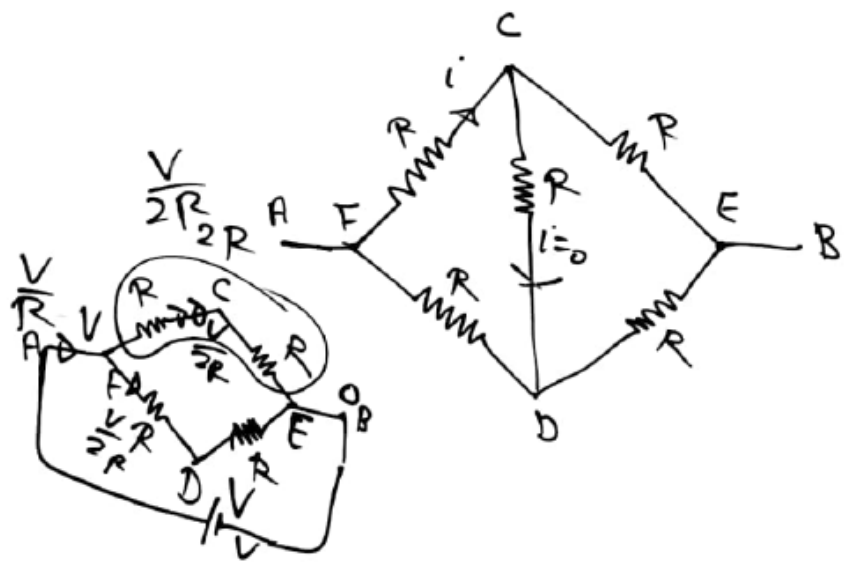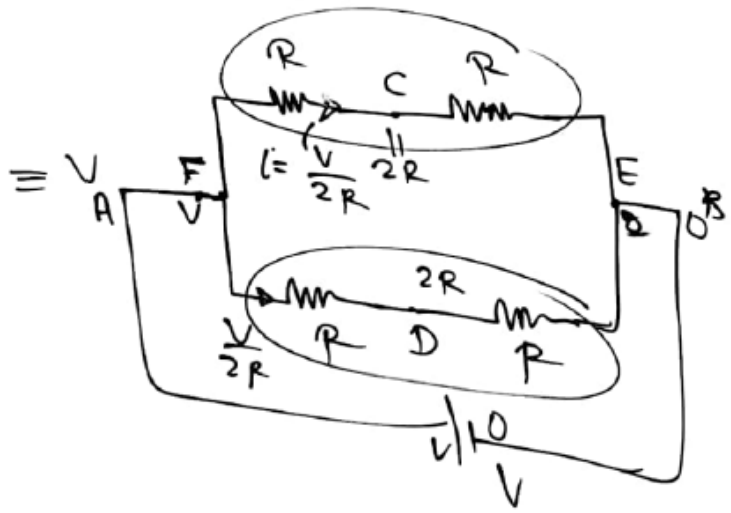

Q3) For the Network shown in figure the value of the current i is.

$\frac{4}{6} = \frac{2}{3}$

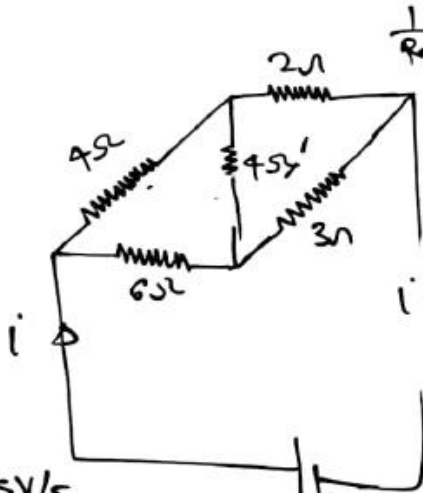

$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{9}$
 $R_p = \frac{18}{5} \Omega$




$V_x = V_y$

$i = \frac{V}{18/5}$

$i = \frac{5V}{18}$

$\frac{2 \times 9}{2+9} = \frac{18}{11}$
 $R = \frac{18}{5}$

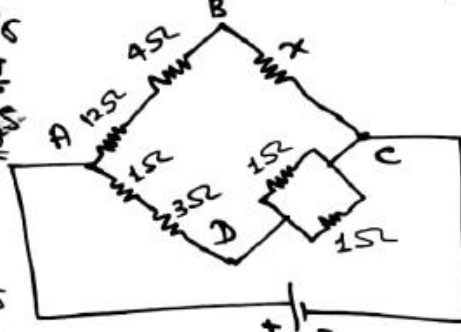Q4) In the arrangement of resistance shown in the ckt. the potential difference b/w points B & P will be zero. when the unknown resistance is





- (a) 9Ω
- (b) 3Ω
- (c) 2Ω
- (d) 1Ω

- (a) 15V/5.
- (b) 5V/9.
- (c) 9V/35.
- (d) $\frac{5V}{18}$.


$\frac{4}{6} = \frac{2}{3}$

$4 \times 3 = 12$

$6 \times 2 = 12$

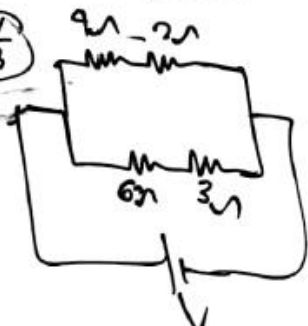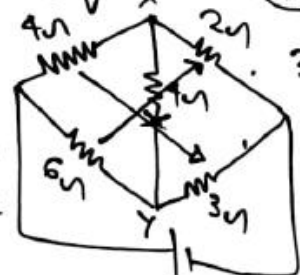

(#)

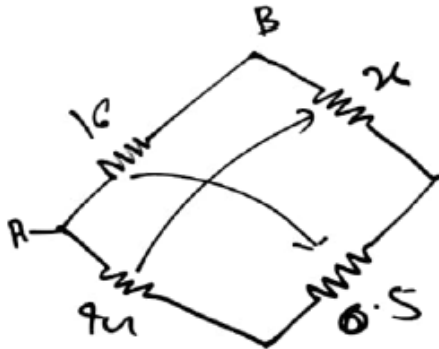

Try $V_B = V_D$

B.W.S.R


$$\frac{16}{9} = \frac{x}{0.5}$$

$$16 \times 0.5 = 9x$$

$$4 \times 0.5 = x \quad x = 2\Omega$$

$$x = \underline{\underline{2\Omega}}$$

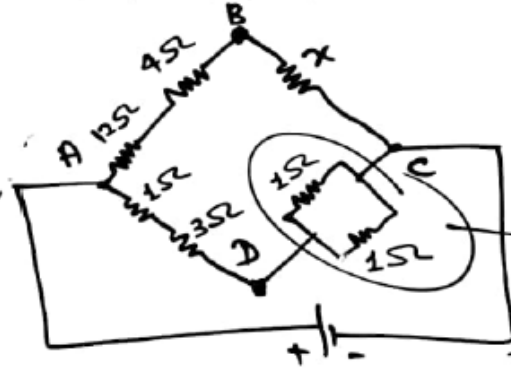Q9) In the arrangement of resistance shown in the ckt. the potential difference b/w points B & D will be zero. when the unknown resistance



$V_B - V_D = 0$ $V_B = V_D$

(a) 9Ω (b) 3Ω


(c) 2Ω (d) 1Ω

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{1}$$

$$\frac{1}{R_{eq}} = 1 + 1$$

$$\frac{1}{R_{eq}} = 2 \quad R_{eq} = \frac{1}{2}$$
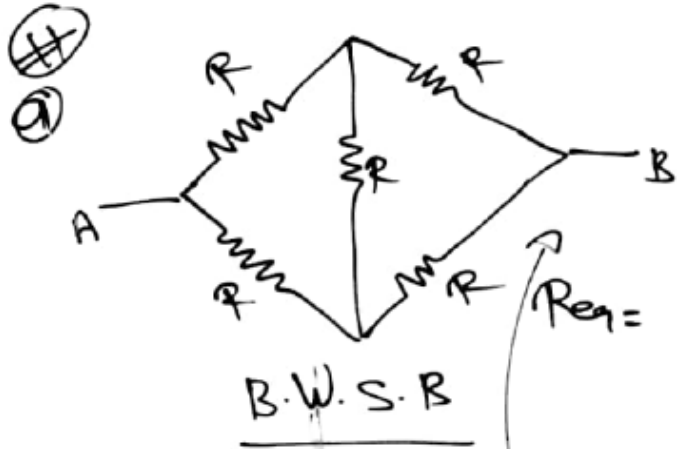
$$R_{eq} = 0.5 = \underline{\underline{0.5}}$$



(b)



B.W.S.B

(c)

