
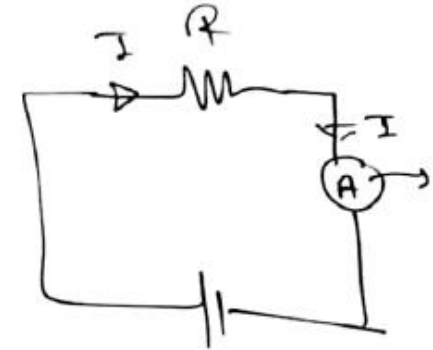


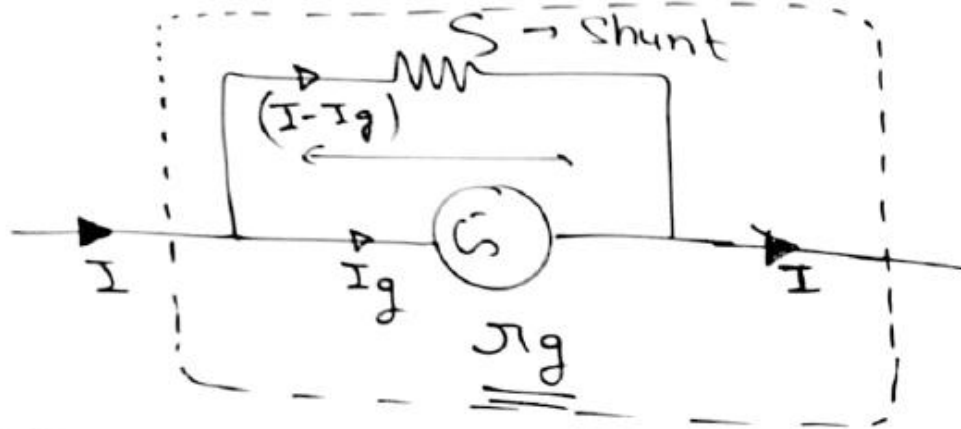Q. Conversion of Galvanometer into ammeter:-



$I_g \rightarrow$ maximum current in galvanometer

$S \rightarrow$ very low resistance.

$$(I - I_g)S = I_g r_g$$

$$IS - I_g S = I_g r_g$$


$$IS = I_g r_g + I_g S$$

$$I = \frac{I_g (r_g + S)}{S}$$


Q1) Conversion of Galvanometer into ammeter:-

Q1) A galvanometer having a coil of resistance 60ohm shows full deflection when a current of 1amp passes through it. it can be converted into an ammeter to read current upto 5amp by

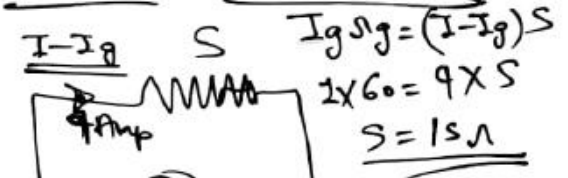- a) putting in series a resistance of 15Ω .
- b) putting in series a resistance of 29Ω .




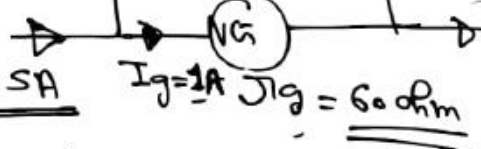- c) putting in parallel a resistance of 15Ω .



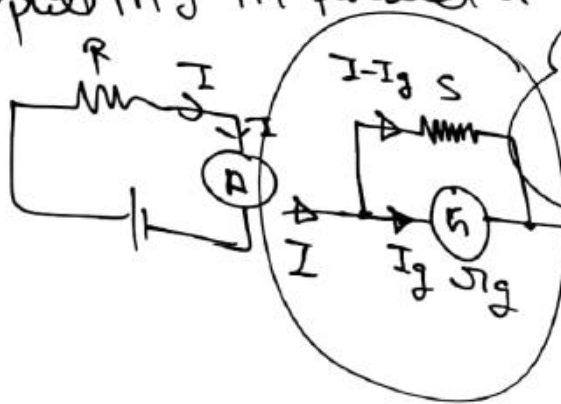- d) putting in parallel a resistance of 29Ω .

$4 \times S = 1 \times 60$
 $S = 15\Omega$




$(I - I_g) S = I_g \Omega_g$
 $I_g \rightarrow$ maximum deflection current in Galvanometer
 $I_g \Omega_g = (I - I_g) S$

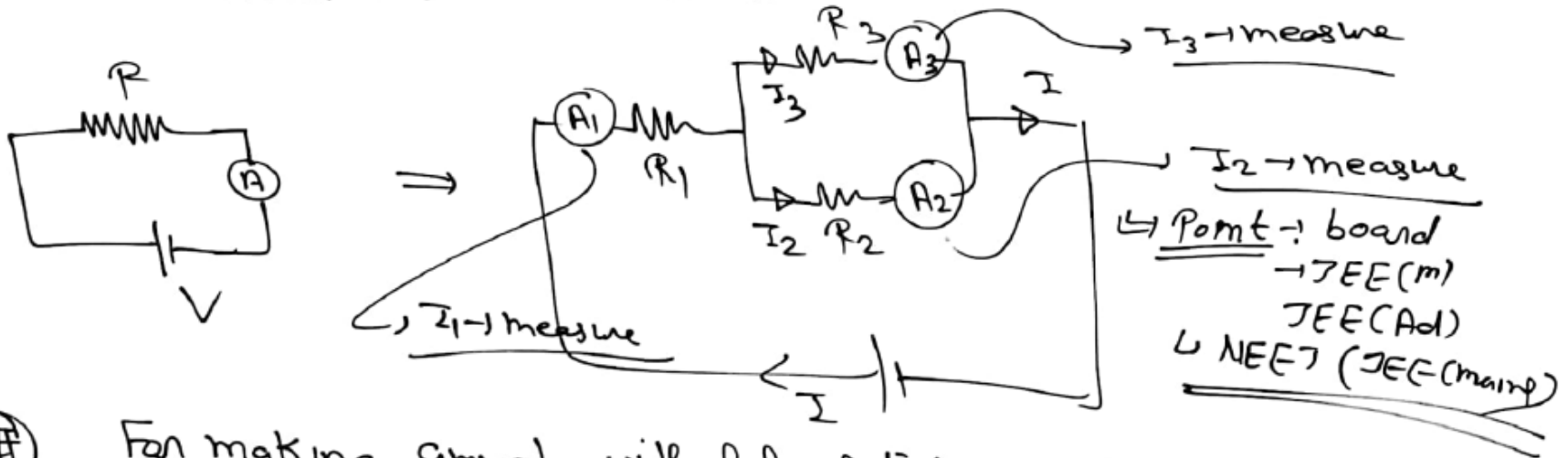Q2 Conversion of Galvanometer into ammeter:-


① Ammeter :- It is a device which measure current in ckt.

⇒ Ammeter is connected in series with circuit.



②

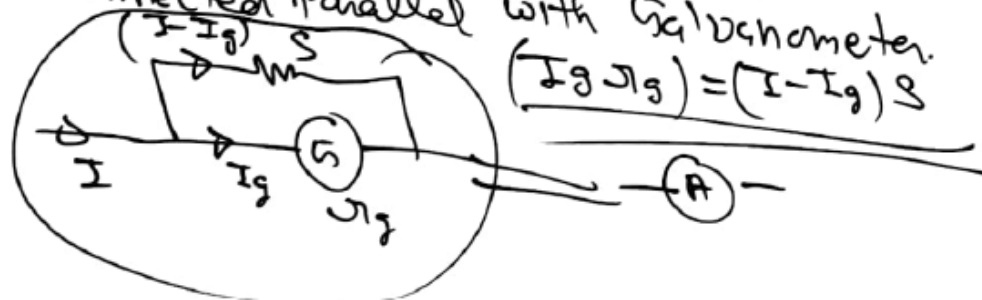For making ammeter with help of galvanometer, connected parallel with galvanometer.




$$(I_g r_g) = (I - I_g) S$$

Shunt is

##

Ammeter

$(I - I_g) S \rightarrow$ Low resistance

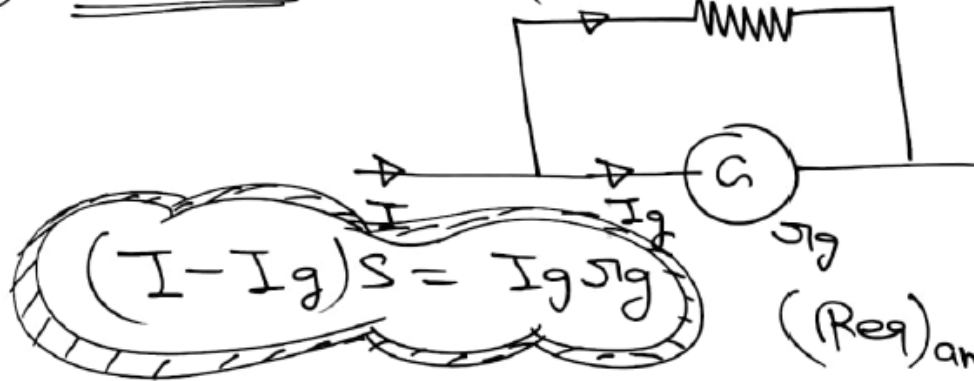

$(I - I_g)S = I_g S_g$

∴ $I_g \rightarrow$ It is maximum current which can flow through Galvanometer

$(R_{eq})_{\text{ammeter}} = \frac{S_g \cdot S}{(S_g + S)}$ NICE RT
↓
Reading

$R_A = \frac{S_g S}{S_g + S} \Rightarrow R_A = \frac{S}{\frac{S_g + S}{S_g}}$


$R_A = \frac{S}{\frac{S_g}{S_g} + \frac{S}{S_g}}$

$R_A = \frac{S}{1 + \frac{S}{S_g}}$

$R_A < S$

Ideal ammeter
 $R_A = 0$

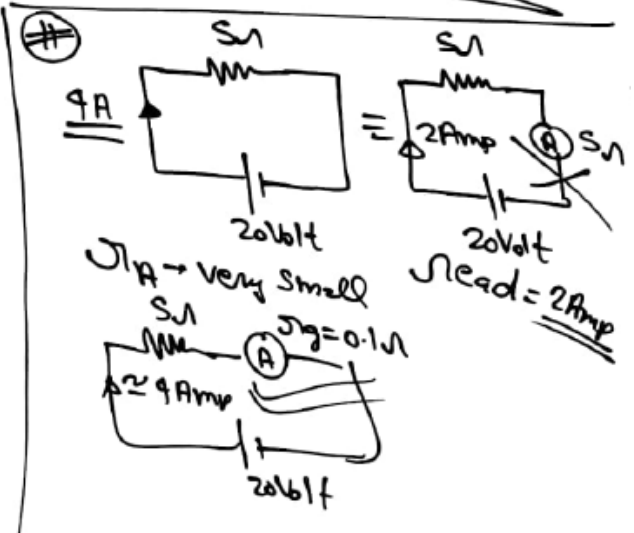
For good ammeter S_g is very small, Shunt $S \rightarrow$ is very small



Q) A galvanometer of resistance G , is shunted by a resistance S . To keep the main current in the circuit unchanged, the resistance to be put in series with galvanometer

Q3) In an ammeter 0.2% of main current passes through the galvanometer. If resistance of galvanometer is G , the resistance of ammeter will be. [2019]

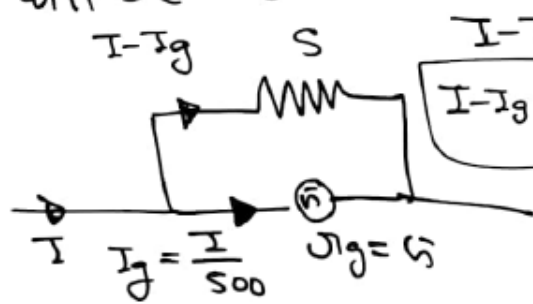- a) $\frac{1}{499} G$.
- b) $\frac{499}{500} G$.
- c) $\frac{1}{500} G$ [✓]
- d) $\frac{500}{499} G$.



$$I - I_g = I - \frac{I}{500}$$

$$I - I_g = \frac{499 I}{500}$$

$$I_g = I \times \frac{0.2}{100} = I \times \frac{2}{1000}$$

$$= \frac{I}{500}$$

$$R_A = \frac{G \times S}{G + S} = \frac{G \times \frac{G}{499}}{G + \frac{G}{499}}$$

$$(I - I_g)S = I_g G$$

$$\frac{499 I}{500} \times S = \frac{I}{500} \times G$$

$$S = \frac{G}{499}$$

$$R_A = \frac{G \times \frac{G}{499}}{\frac{500 G}{499}} = \frac{G}{500}$$

Q) ATPMT 2-H

A galvanometer of Resistance G , is shunted by a resistance S .
 ohm. To keep the main current in the circuit unchanged, the
 resistance to be put in series with galvanometer



Main current = 2 Amp.

$I_g = 0.1 \text{ Amp. } (I - I_g)S = I_g G$

$G = 1000 \Omega$

Find Value of shunt resistance

↳ Short Notes

$\Rightarrow \frac{W_{all} \rightarrow I}{I}$



$I = 2 \text{ Amp}$

$I_g = 0.1 \text{ Amp}$

$I - I_g = 2 - 0.1 = 1.9 \text{ Amp}$

$(I - I_g)S = I_g G$

$1.9 \times S = 0.1 \times 10$

$1.9S = 10$

$S = \frac{10}{1.9} = \frac{100}{19} = 5.2 \dots \Omega$

Main current = 2 Amp

$I_g = 1 \text{ mA}$

$G = 1000 \Omega$

$S = ?$

$(I - I_g)S = I_g G$

$(2 - 1 \times 10^{-3})S = 10^{-3} \times 1000$

$(2 - 0.001)S = 1$

$2S = 1$

$S = \frac{1}{2} = 0.5 \Omega$

Q) ^{17pm} A galvanometer of resistance G , is shunted by a resistance S .
 $0 \text{ } \Omega$. To keep the main current in the circuit unchanged, the
 resistance to be put in series with galvanometer ~~is~~

\Rightarrow $I_g \rightarrow 0.01\%$ of main current.
 $G \rightarrow$ low and Shunt resistance

Solve:- let's main current is I

$$I_g = I \times \frac{0.01}{100} = \underline{\underline{I \times 10^{-4}}}$$

$$\underline{\underline{I - I_g \approx I}}$$

$$(I - I_g)S = I_g G$$

$$I \times S = 10^{-4} \times I \times 10$$

$$\underline{\underline{S = 10^3 \Omega}}$$

$$\underline{\underline{S = 0.001 \Omega}}$$