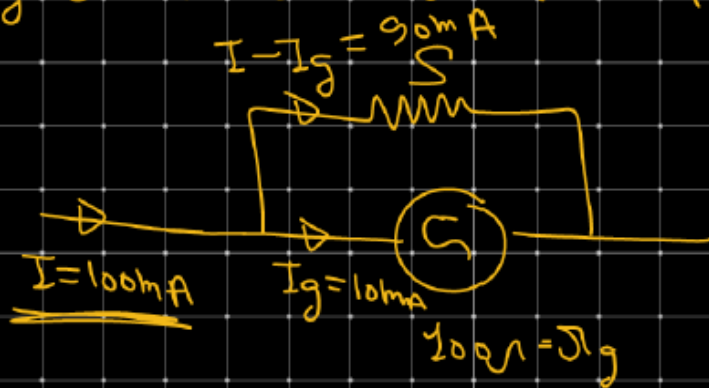


Q1:- A galvanometer of 100Ω resistance yields complete deflection when 10mA current flows. What should be the value of shunt so that it can measure currents up to 100mA ?

- (a) 9.9Ω
 (b) 9.5Ω
 (c) 11.11Ω
 (d) 11Ω



$$(I - I_g)S = I_g R_g$$

$$(100 - 10)S = 10\text{mA} \times 100$$


$$90\text{mA} \times S = 10\text{mA} \times 100$$

$$S = \frac{100}{9} \Omega$$

$$S = 11.11\Omega$$

Conversion of Galvanometer into voltmeter :-

↳ for ideal voltmeter resistance is ∞

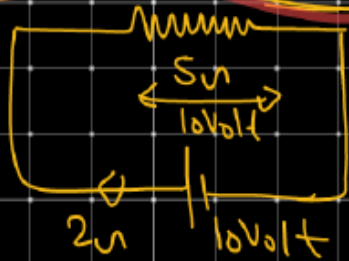

$\Rightarrow 5\text{V} \Rightarrow$



\Rightarrow Voltmeter connected with resistance in parallel.

$$R_{eq} = \frac{5\text{V} \times 5}{5\text{V} + 5} = \frac{5}{\frac{5+5}{5\text{V}}}$$

$$R_{eq} < 5\Omega$$

$$R_{eq} = \frac{5}{\frac{5}{5\text{V}} + 5} = \frac{5}{\frac{5}{5\text{V}} + 5} = \frac{5}{1 + \frac{5}{5\text{V}}}$$

$$\underline{\underline{5\text{V} \rightarrow \infty}} \quad R_{eq} = \frac{5}{1 + \frac{5}{\infty}} = \frac{5}{1} = 5\Omega$$

#



ideal voltmeter

$$R_{eq} = \frac{r_v \times R}{r_v + R}$$

$$R_{eq} = \frac{R}{\frac{r_v}{R} + 1}$$

$$R_{eq} = \frac{R}{\frac{r_v}{R} + 1} = \frac{R}{\frac{r_v}{R} + \frac{R}{R}} = \frac{R}{\frac{r_v + R}{R}} = \frac{R \times R}{r_v + R}$$


$$\frac{r_v}{R} = \frac{1}{\frac{R}{r_v}} = \frac{1}{R \parallel r_v}$$

$$\frac{1}{R \parallel r_v} + 1 = \frac{1}{R \parallel r_v} + \frac{R \parallel r_v}{R \parallel r_v} = \frac{1 + R \parallel r_v}{R \parallel r_v}$$

$$R_{eq} = \frac{R}{\frac{1 + R \parallel r_v}{R \parallel r_v}} = \frac{R \times (R \parallel r_v)}{1 + R \parallel r_v}$$

Q AIPMT To Convert a galvanometer into a ammeter, one ~~needs~~ needs to convert a.

~~(A)~~ Low resistance in Parallel

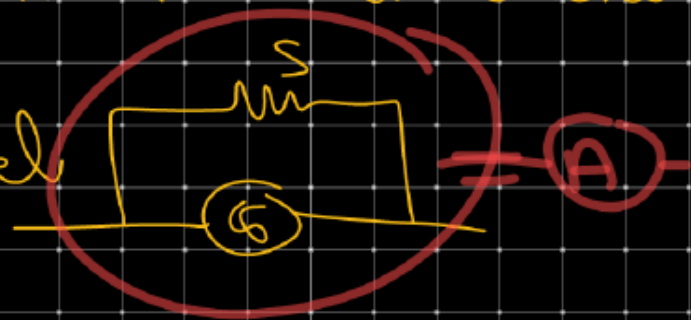

(B) high resistance in parallel


(C) low resistance in series.

(D) high resistance in series.


⇒ Conversion of Galvanometer into voltmeter,

↳ For ideal Voltmeter resistance is (∞)

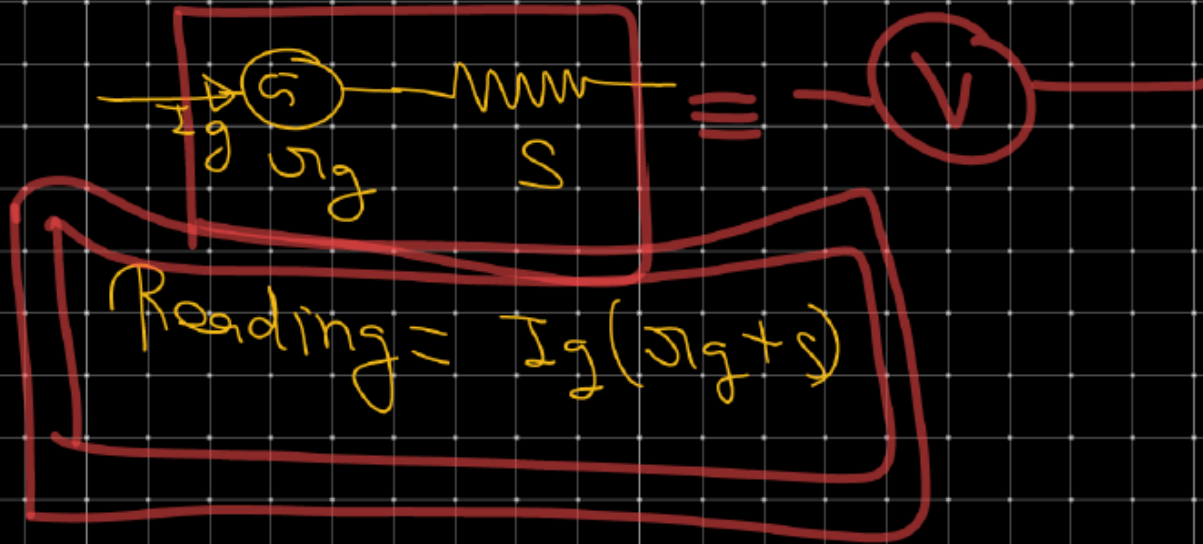↳ of practical voltmeter resistance is very high.




~~##~~ #

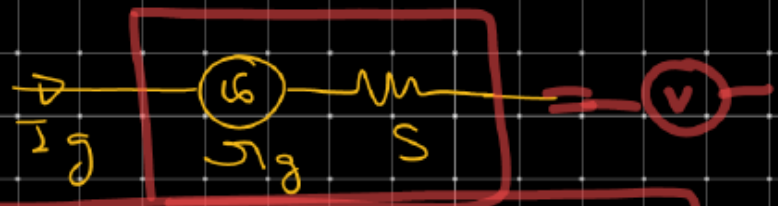


S → Shunt resistance is very high

Reading = $I_g (r_g + S)$

##

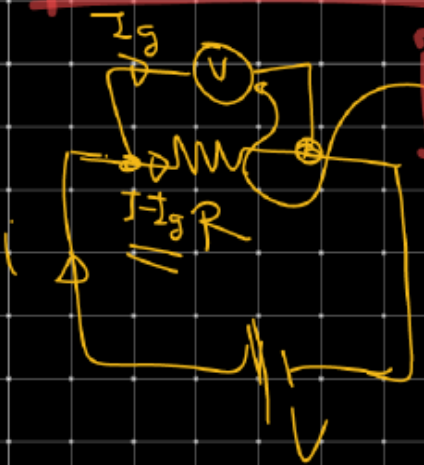

$V = I_g (r_g + S)$

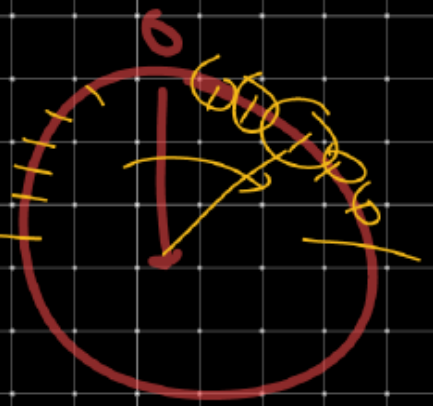



8) The resistance of galvanometer is $5\ \Omega$ and its range is $1\ \text{V}$. The value of resistance (in Ω) used to convert it into voltmeter of range $10\ \text{V}$ is

(a) $9\ \Omega$

(b) $5\ \Omega$


(c) $\frac{1}{9}\ \Omega$

(d) $10\ \Omega$

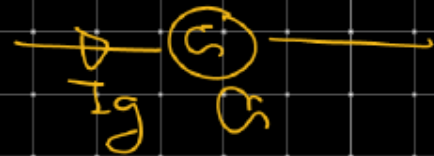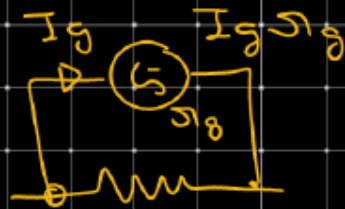

$$I_g \times 5\ \Omega = 1\ \text{V}$$

$$I_g \times 5 = 1\ \text{V}$$

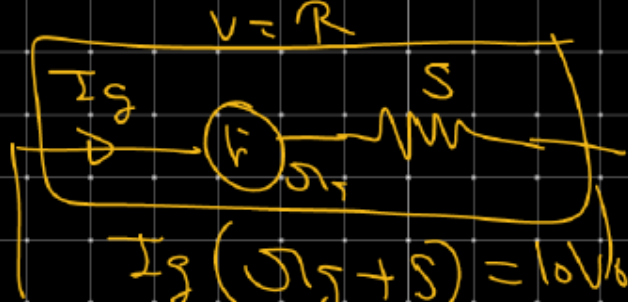

$$I_g (5\ \Omega + S) = 10\ \text{V}$$

$$\frac{1}{5} (5 + S) = 10$$

$$(5 + S) = 10\ \Omega$$

$$S = 5\ \Omega$$

5\ \Omega


Q2) A 1Ω Voltmeter has a range of 1 V . Find the additional resistance which has to be joined with the series in voltmeter to increase the range of Voltmeter to 100 V .

(a) 10Ω .

(b) $\frac{1}{99} \Omega$.

~~(c) 99Ω~~

(d) 100Ω .

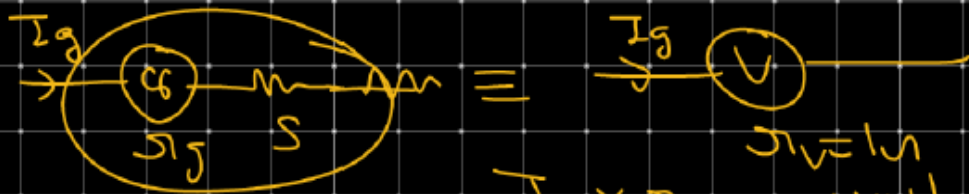

$I_g \times 1 \Omega = 1 \text{ Volt}$. $I_g = \frac{1}{1 \Omega}$

$I_g \times (1 \Omega + R) = 100 \text{ Volt}$

$\frac{1}{1 \Omega} (1 + R) = 100$

$\therefore (1 + R) = 100$ $R = 99 \Omega$