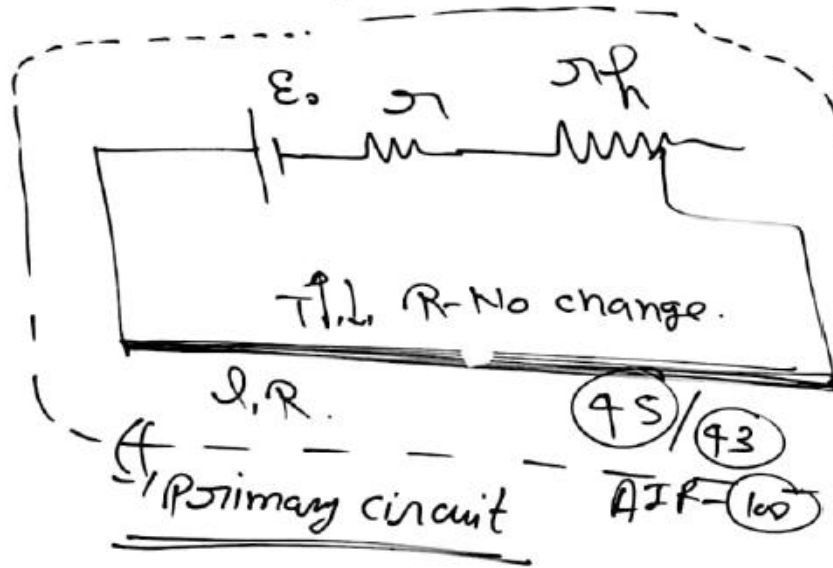


Necessity of potentiometer



$\frac{95}{93}$   
 $\frac{AIF-100}{}$

⇒ Potentiometer wire

⇒ Made of Manganin, Eureka,

$S = \frac{m}{ne^2 \tau}$

Constantan

Alloy

⇒ due to high specific resistance / resistive


$S \rightarrow$  high

⇒ Manganin, Eureka

$\alpha \rightarrow$  very low

$T \uparrow \text{ or } T \downarrow - S \text{ almost No change}$

(#) Primary circuit of Potentiometer:-

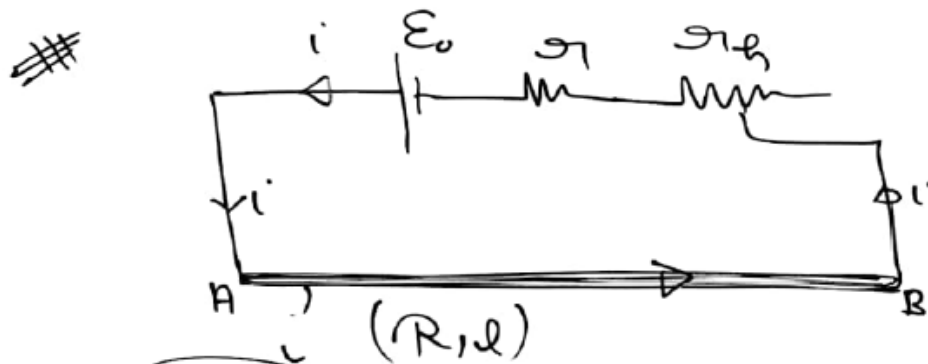


(i) 
$$i = \frac{\epsilon_0}{r + R + rR}$$

(ii) Potential difference across AB,

$$V_{AB} = iR = \frac{\epsilon_0}{(r + R + rR)} \times R$$

(iii) Potential gradient  $\alpha = \frac{V_{AB}}{l}$

Ex

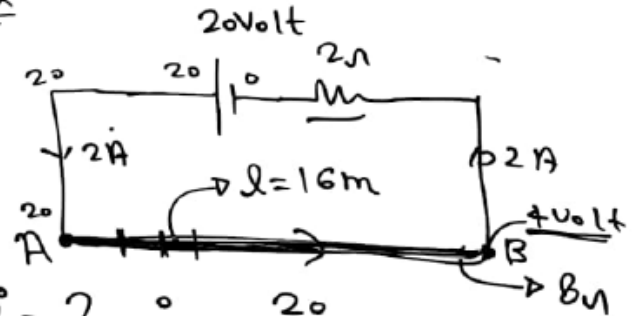

(i)  $i = ? \quad i = \frac{20}{10} = 2 \text{ Amp}$

(ii)  $V_{AB} = 2 \times 8 = 16 \text{ Volt}$

(iii) Potential gradient  $\alpha = \frac{V_{AB}}{l}$


$$\alpha = \frac{16 \text{ Volt}}{16 \text{ m}} = 1 \text{ Volt/m}$$

$$\alpha = \frac{\Delta V}{-l} = \frac{V_B - V_A}{l} = \frac{-16 \text{ V}}{16 \text{ m}} = -1 \text{ Volt/m}$$

Primary circuit of Potentiometer:-



$x \Rightarrow$  Potential gradient.

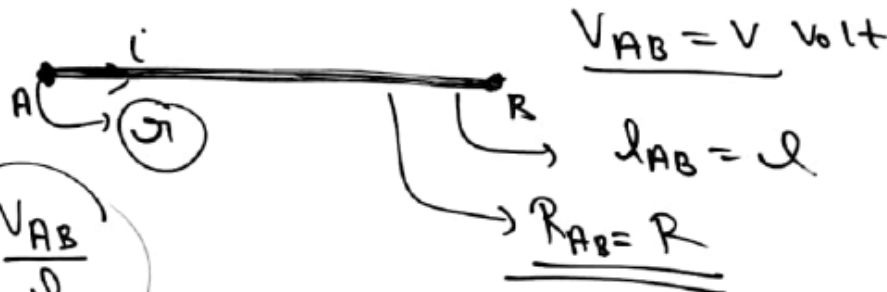

NCE RT  
↓  
given

$X = \frac{V_{AB}}{l}$

$X = \frac{iR}{l}$


Potential gradient  $X \rightarrow \rho, \sigma,$

$R = \frac{\rho l}{A}$   
 $\rho = \frac{R A}{l}$

$x \propto \frac{1}{(\text{radius})^2}$

Application of potentiometer:-

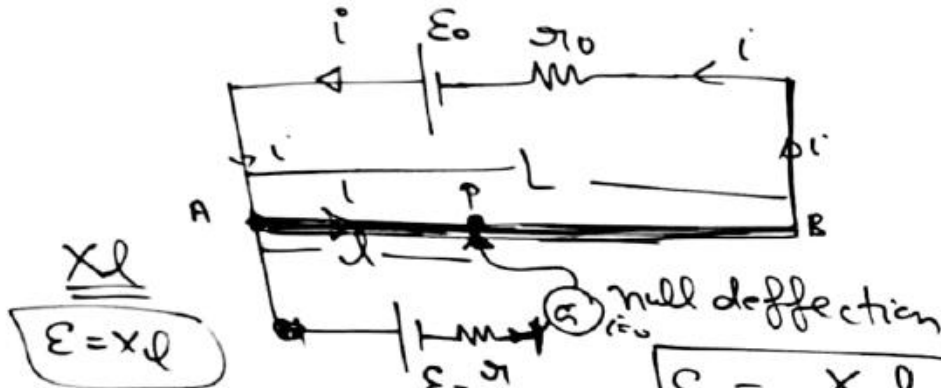ii) To find Emf of cell.  $(\mathcal{E} = X \cdot l)$




$\mathcal{E} = X \cdot l$

$T.P = \mathcal{E}$

$X \rightarrow \frac{V_{AB}}{L}$

$X \rightarrow$  Potential gradient

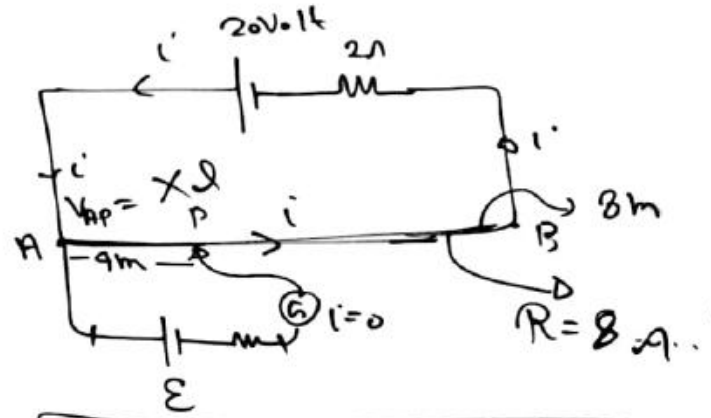$V_{AP} = X \cdot l$   
 $\mathcal{E} = X \cdot l$



$\Rightarrow$   $i$  in primary circuit

$i = \frac{20}{10} = 2 \text{ Amp}$   $\mathcal{E} = 8 \text{ Volt}$

$V_{AB} = 2 \times 8 = 16 \text{ Volt}$

$X = \frac{V_{AB}}{l} = \frac{16}{8} = 2 \text{ Volt/m}$

$\mathcal{E} = X \cdot l = \frac{2 \text{ Volt}}{1 \text{ m}} \times 4 \text{ m} = 8 \text{ Volt}$

Application of potentiometer:-

(b) Compare of Emf of two cell:-

