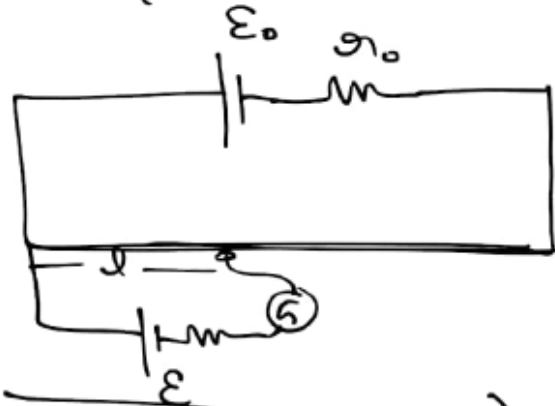



⇒ Potentiometer ⇒

(i) Emf of the cell.



$$\mathcal{E} = \frac{\mathcal{E}_0}{l_0} l$$

(ii) 2021 NEET

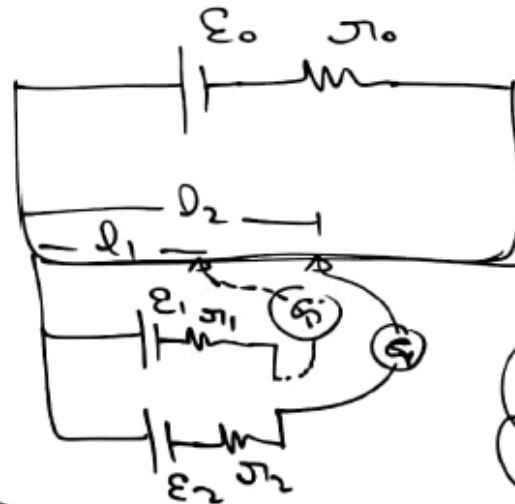

$$\frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{l_1}{l_2}$$

$$\mathcal{E}_1 = \frac{\mathcal{E}_0}{l_0} l_1$$

$$\mathcal{E}_2 = \frac{\mathcal{E}_0}{l_0} l_2$$

$$\frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{l_1}{l_2}$$

X

- Potential gradient

2021 NEET

Q. In a potentiometer circuit a cell of emf 1.5V gives balance point at 36cm length of wire. If another cell of emf 2.5V replace the first cell, then at what length of the wire, the balance point occurs?

- (a) 62 cm
- (b) 60 cm
- (c) 21.6 cm
- (d) 64 cm



$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\frac{1.5}{2.5} = \frac{36}{l_2}$$

$$l_2 = \frac{36 \times 2.5}{1.5}$$

$$l_2 = \frac{36 \times 5}{3}$$

$$l_2 = 60 \text{ cm}$$

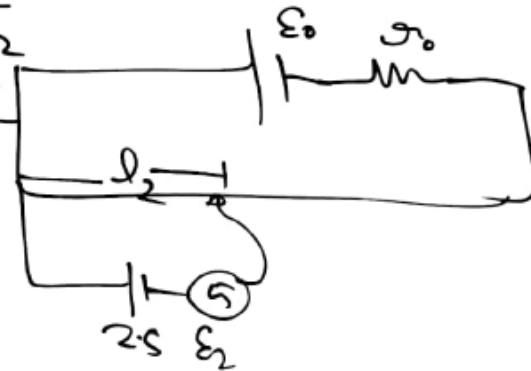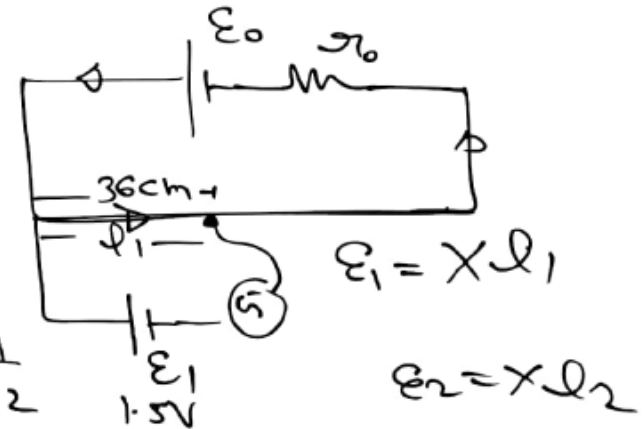

Q2) AIEET 2017

A potentiometer is an accurate & versatile device to make electrical instruments of emf because the method involve.

a) potential gradients.


Null deflection

b) A condition of no current flow through the galvanometer.


c) a combination of cells, galvanometer & resistance.

is based on null deflection

d) cells.

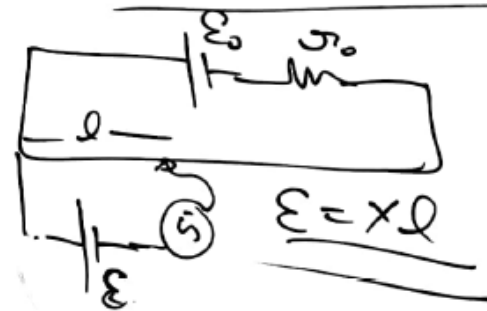

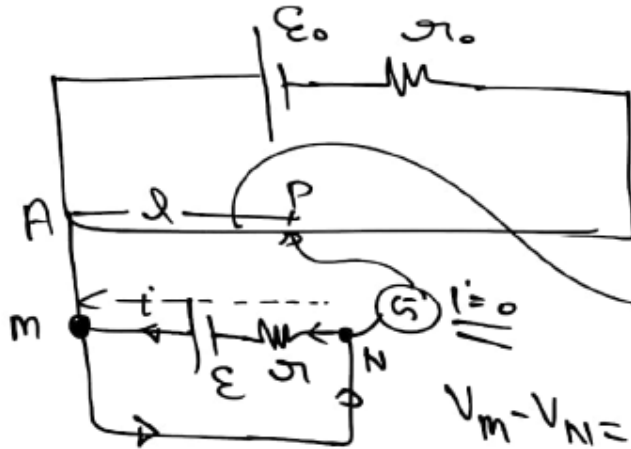(ii) To find internal resistance of cell -




V.P.D b/w  
 $AP = x \rho$   
 $V_M - V_N = \epsilon - ir$

$$V_N - ir + \epsilon = V_M$$


$$V_M - V_N = \epsilon - ir$$

$$\epsilon - ir = x \rho$$


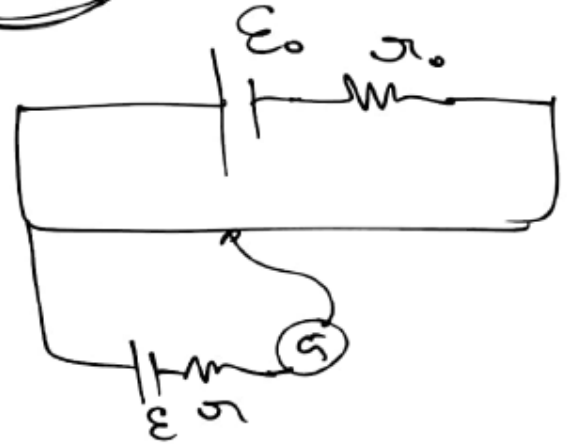




Power, Energy Consume by resistance:-

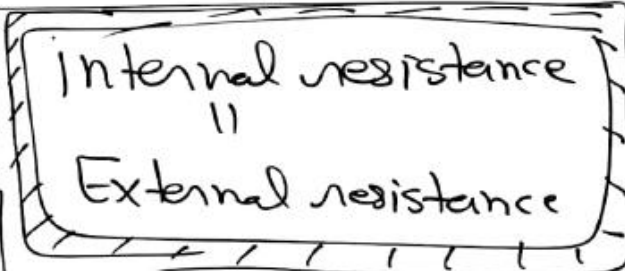

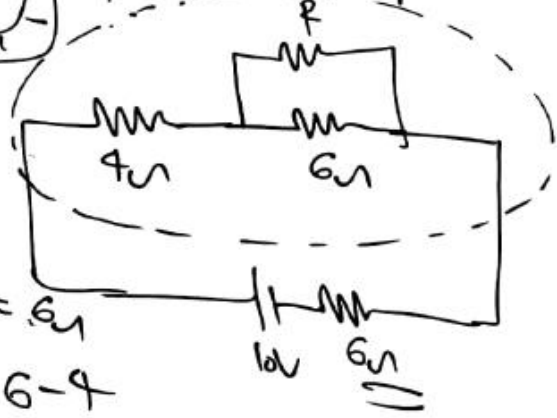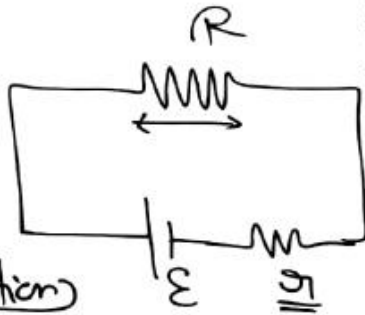Q) Find value of R such that maximum power consumption.



Condition)

for maximum power dissipation / consume / provide by external Resistance,  $r = R$

$$4 + \frac{6R}{6+R} = 6$$

$$\frac{6R}{6+R} = 6 - 4$$


$$\frac{6R}{6+R} = 2 \Rightarrow 6R = 12 + 2R$$

$$4R = 12$$

$$R = 3\Omega$$



Power, Energy Consume by resistance:-

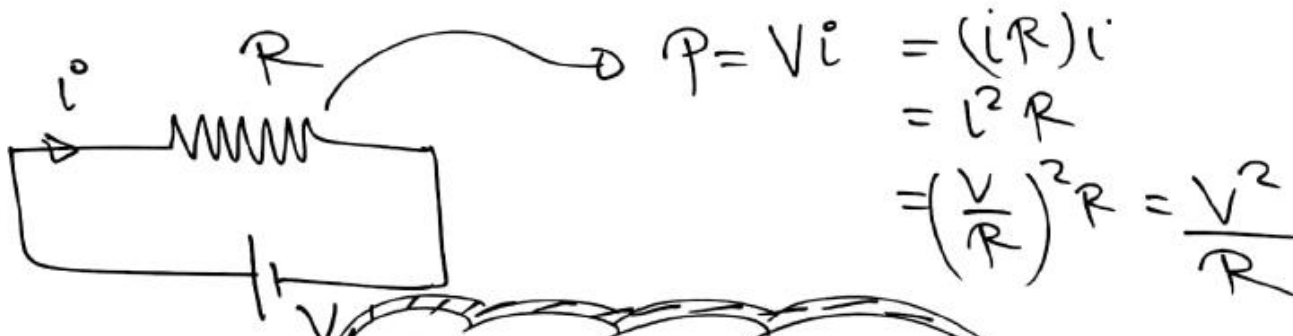

$$\begin{aligned}
 P &= Vi = (iR)i \\
 &= i^2 R \\
 &= \left(\frac{V}{R}\right)^2 R = \frac{V^2}{R}
 \end{aligned}$$

$P = Vi = i^2 R = \frac{V^2}{R}$



Power =  $\frac{\text{Energy}}{\text{time}}$

$P = \frac{E}{t}$

$E = P \cdot t$



Energy Consume/Radiate in t -


$E = Vit = i^2 R t = \frac{V^2}{R} t$

Power, Energy Consume by resistance:-

$$P = VI = I^2R = \frac{V^2}{R} \quad V = IR$$

Mains 2012

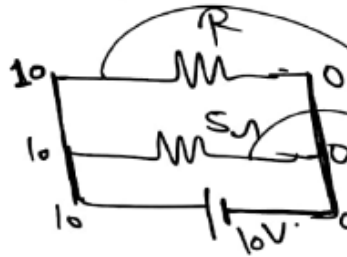- (a) 20Ω.
- (b) 15Ω.
- (c) 10Ω.
- (d) 30Ω.



Power dissipated in ckt is 30 watt. The value of R.

$$P_1 + P_2 = 30 \text{ watt}$$

$$\frac{10^2}{R} + \frac{10^2}{5} = 30$$

$$\frac{100}{R} + \frac{100}{5} = 30$$

$$\frac{100}{R} = 30 - 20$$


$$\frac{100}{R} = 10 \quad \underline{\underline{R = 10\Omega}}$$

AIPMT 2011 | If the Power dissipated in the 9Ω resistor in the circuit shown is 36 W, The potential difference across the

2Ω resistor.

- (a) 4V
- (b) 8V
- (c) 16V
- (d) 2Volt.



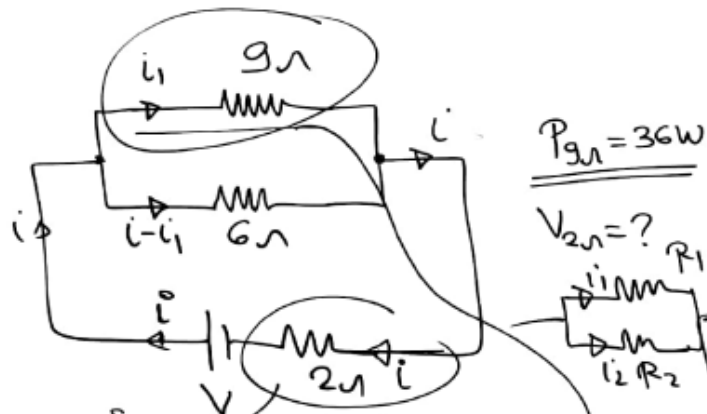

- (i) Read Question
  - (ii) Write what is given
  - (iii) Find  $\rightarrow$ ?
  - (iv) Think about formula
- or write -

ATPMT 2011 | If the Power dissipated in the 9Ω resistor in the circuit shown is 36W, The potential difference across the

(L) First How to find, net current through cell,

$$i_1 \times 9 = (i - i_1) 6$$

$$\frac{i_1}{i - i_1} = \frac{6}{9} = \frac{2}{3}$$

$$3i_1 = 2i - 2i_1 \quad \boxed{i_1 = \frac{2}{5}i}$$

$$5i_1 = 2i$$

$$\rightarrow V = iR = 5 \times 2 = 10 \text{ Volt}$$

$$P = i_1^2 R = 36$$

$$= \left(\frac{2i}{5}\right)^2 \times 9 = 36$$

$$\left(\frac{2i}{5}\right)^2 = (2)^2$$

$$\frac{2i}{5} = 2$$

$$i = 5 \text{ Amp}$$

2Ω resistor:

- (a) 4V
- (b) 8V
- (c) 10V
- (d) 20V

