

#



[220V, 50W]

Indian System of Electricity:-


Home supply \rightarrow 220 Volt, 50 Hz

\rightarrow with help of Reading we find
Resistance of bulb, $\left[P = \frac{V^2}{R} \right]$

$$R = \frac{V^2}{P}$$

\rightarrow Meaning of Reading [220V, 50W]

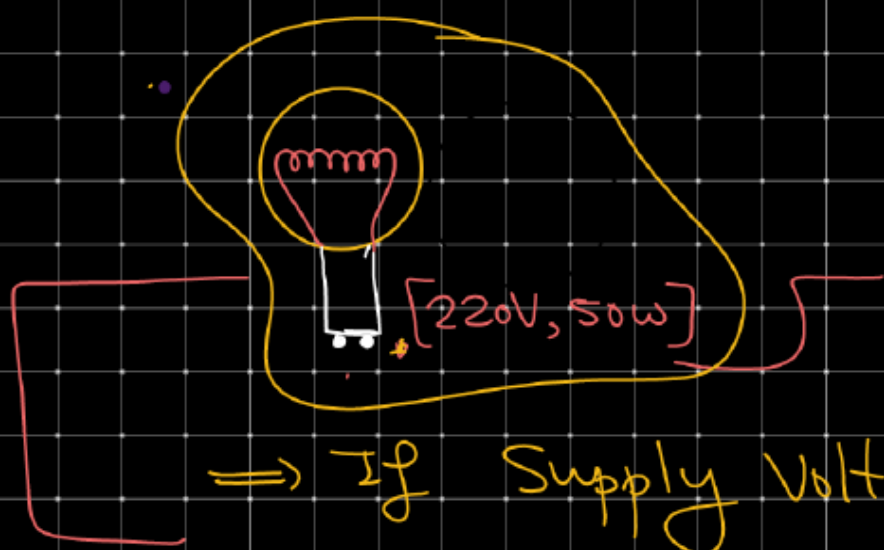this bulb operate 220 volt supply with full brightness
that's means power dissipated is 50W [50 J/sec]




⇒ If Supply Voltage

$V_{\text{supp}} < V_{\text{Reading}} \rightarrow$ Low brightness.

$V_{\text{supp}} = V_{\text{Reading}} \rightarrow$ full brightness.

$V_{\text{supply}} > V_{\text{Reading}} \rightarrow$ bulb will be fuse.

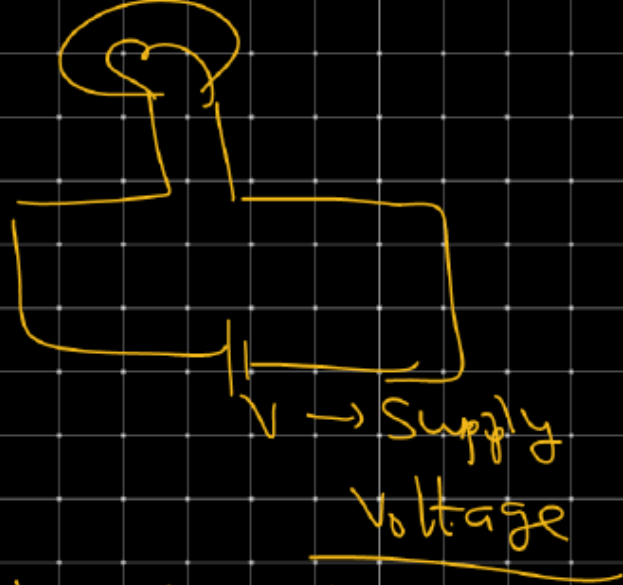

NEET 16) A filament bulb (500W, 100V) is to be used in 230V main supply. When a resistance R is connected in series, it works perfectly & the bulb consumes 500W. The value of R .

(a) 230Ω .

(b) 96Ω .

~~(c) 26Ω .~~

(d) 13Ω .


$$i \times 20 = 100$$

$$i = 5 \text{ Amp}$$

$$iR = 130$$

$$5 \times R = 130$$

$$R = 26\Omega$$

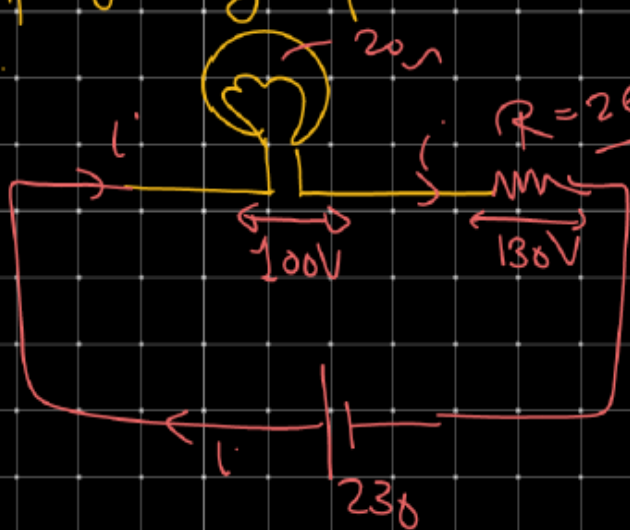

Reading [500W, 100V]

$$R = \frac{V^2}{P}$$

$$R = \frac{100 \times 100}{500}$$

$$R = 20\Omega$$


Q Two electric bulb, rated at (25W, 220V) and (100W, 220V) are connected in series across a 220V source. If the 25W & 100W bulbs draw powers P_1 & P_2 respectively, then

(a) $P_1 = 9W, P_2 = 16W$

(b) $P_1 = 16W, P_2 = 9W$

(c) $P_1 = 9W, P_2 = 16W$

(d) $P_1 = 16W, P_2 = 9W$

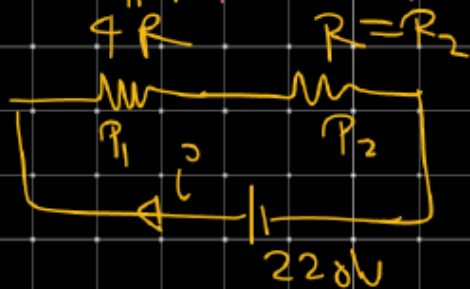

$$I = \frac{220}{5R}$$

$$P_2 = I^2 \times R_2$$

$$\left[\begin{array}{l} 25W \\ 220V \end{array} \right]$$

$$R_1 = \frac{V^2}{P_1} = \frac{220 \times 220}{25}$$

$$R_1 = 4R \quad (R_1 = 4R)$$

$$\left[\begin{array}{l} 100W \\ 220V \end{array} \right]$$

$$R_2 = \frac{220 \times 220}{100}$$

$$(R_2 = R)$$

$$P_2 = 9Watt$$

$$P_1 = \frac{220 \times 220}{25R^2} \times 4R$$

$$P_1 = \frac{220 \times 220 \times 4}{25 \times \frac{220 \times 220}{100}} = \frac{4 \times 100}{25} = 16Watt$$

#


Three bulb, ($P = 110W, 220V$) → Reading:

$$R = \frac{V^2}{P} = \frac{220 \times 220}{110} = 440 \Omega$$

⇒ Power emission by P_1, P_2 & P_3 .

OR Which bulb is operate with full brightness.

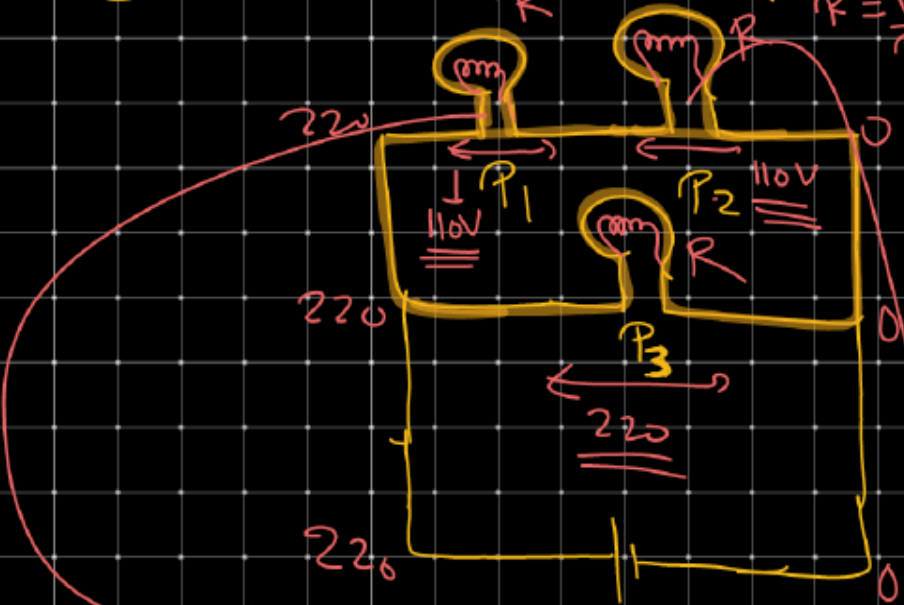P_3 → gives full brightness
bcz potential across P_3 is 220 Volt



$$P_{\text{acty}} = \frac{V^2}{R} = \frac{110 \times 110}{440} = \frac{110}{4} = \underline{\underline{27.5 \text{ Watt}}}$$

⊙ Some Important points of NCERT



For Conductor, $R = R_0(1 + \alpha T)$

$\hookrightarrow \alpha \rightarrow$ Co-ef of Thermal resistance

$\rho = \rho_0(1 + \alpha \Delta T)$ and vice versa

$\alpha = +ive, T \uparrow R \uparrow \rho \uparrow$ and vice versa


NCERT

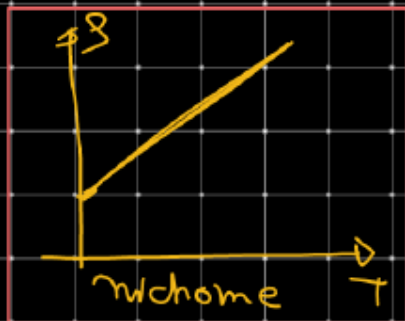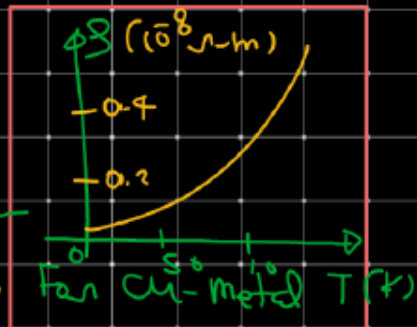

For Semiconductor, $\alpha = -ive$

$R_f = R_0(1 - \alpha \Delta T)$

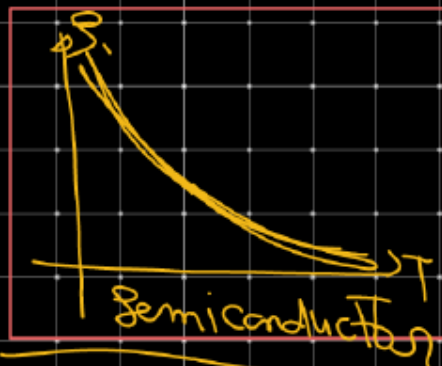$T \uparrow R \downarrow, \rho \downarrow, T \downarrow R \uparrow, \rho \uparrow$



For Insulator $\alpha = -ive$

NCERT 2020

Imp graph

NCEERS

Imp

