

☞ Complete :


Q2) A wire of resistance 12Ω per meter is bent to form a complete circle of radius 10 cm . The resistance b/w its two diametrically opposite points, A & B are as shown in figure is


(a) 3Ω [AIPMT 2009]

(b) $6\pi \Omega$.


(c) 6Ω .

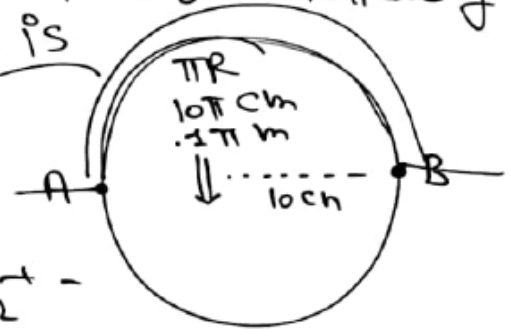(d) $0.6\pi \Omega$

$2\pi R$ 
 $20\pi \text{ cm}$ $2 \text{ m} \rightarrow 12 \Omega$
 $\Rightarrow 20\pi \times 10^{-2} \text{ m}$ $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
 $= 0.2\pi \text{ m}$



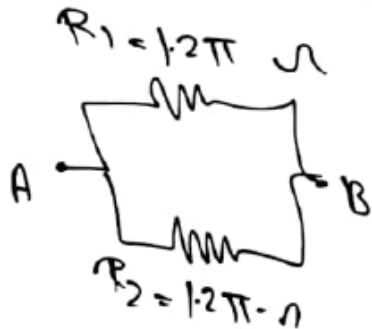Resistance = $0.2\pi \times 12$
 $= 1.2\pi \Omega$





$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1.2\pi \times 1.2\pi}{2.4\pi}$
 $= 0.6\pi \Omega$

NCFRT
(9)

~~Q1~~ I-I-T

R_{AB}

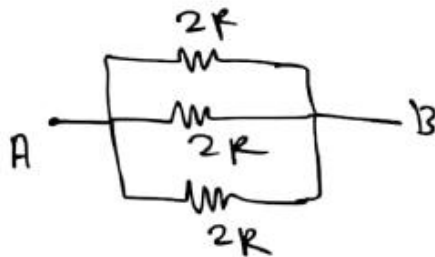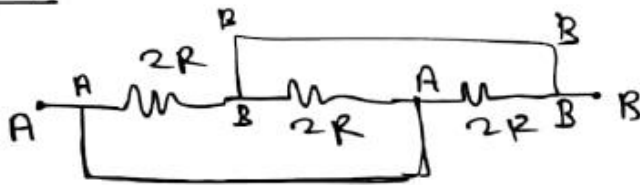

$$\frac{1}{R_{eq}} = \frac{1}{2R} + \frac{1}{2R} + \frac{1}{2R} = \frac{1+1+1}{2R}$$


$$\frac{1}{R_{eq}} = \frac{3}{2R}$$

$$R_{eq} = \frac{2R}{3}$$






Q2)

I-T-T

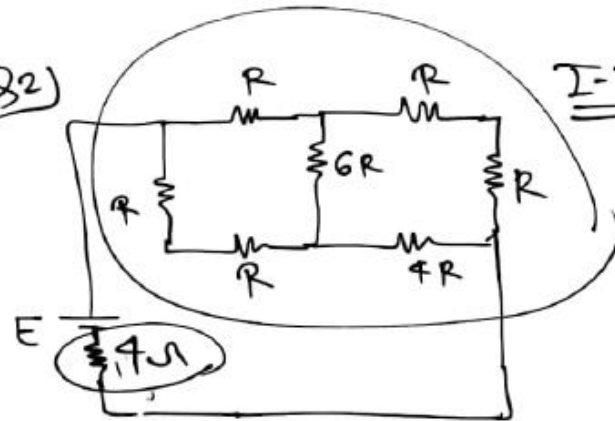

Find the value of R for maximum power delivered.

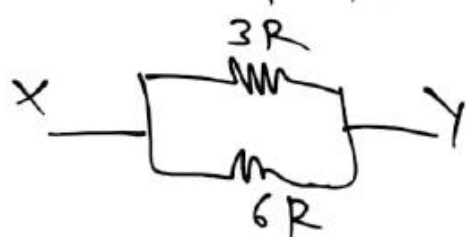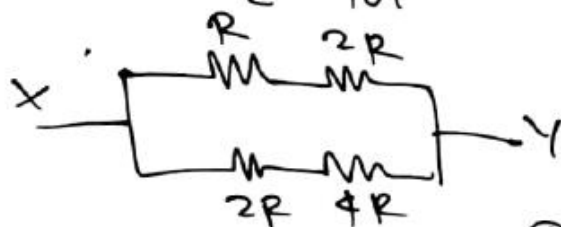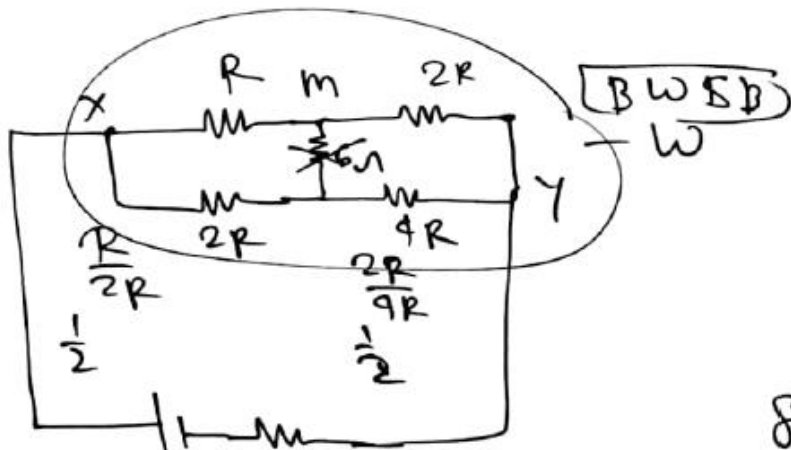When Internal resistance equal to external resistance




$$R_{xy} = \frac{3R \times 6R}{3R + 6R} = \frac{18R}{9} = 2R$$

$$2R = 9\Omega$$


$$2R = 9\Omega$$

$$R = 2\Omega$$

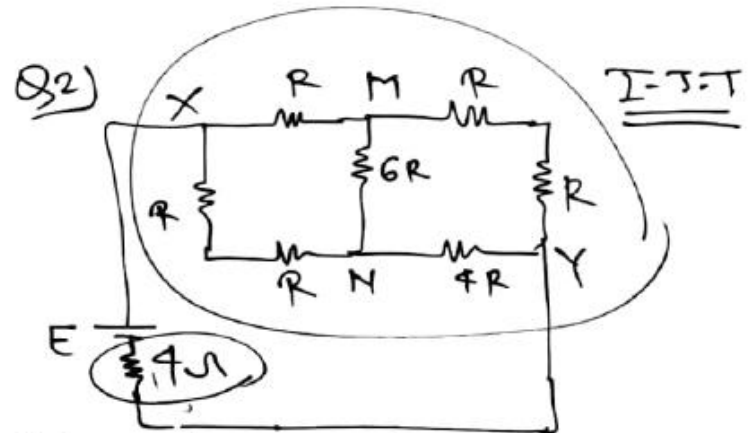

Find the value of R for maximum power delivered.

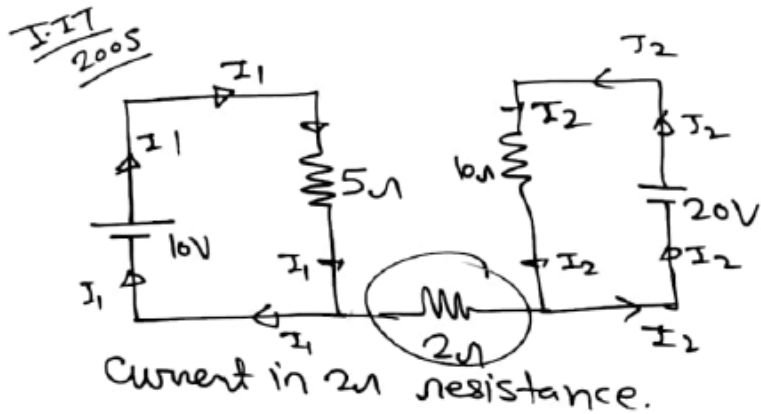When Internal resistance equal to external resistance




- (a) 2A (b) zero (c) 5A (d) 4A

↳ Current never re-trace its path,


↳ battery से जितना charge निकलेगा, same amount of charge वापस आयेगा battery में।

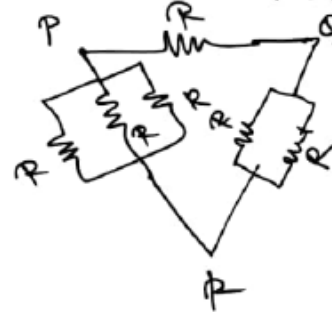I-I-1 2007
Six identical resistance connected as shown in figure. The equivalent resistance will be.





- (a) Maximum b/w P & Q
(b) Maximum b/w Q & R
(c) Maximum b/w P & R.
(d) All are equal.

JEE (Adv) 2015

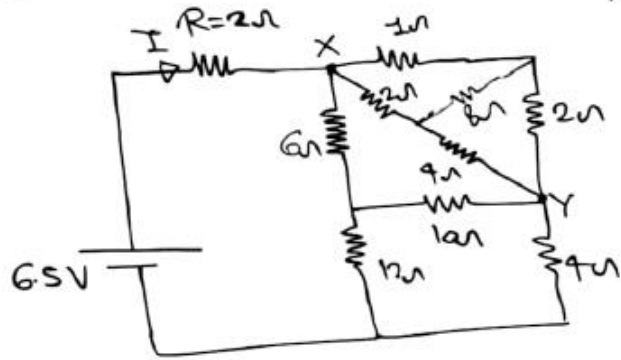

≡

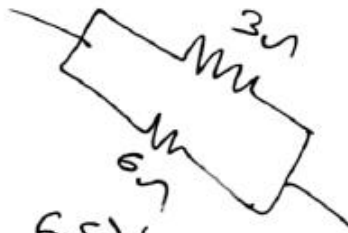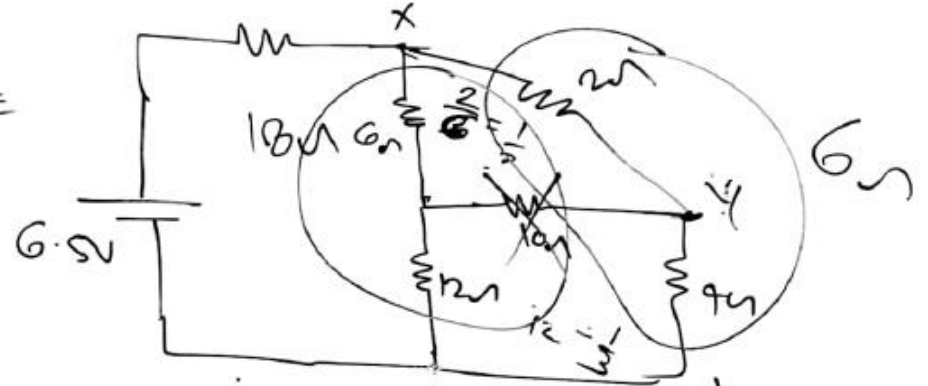


$$R_{eq} = \frac{3 \times 6}{3 + 6}$$

$$= 2\Omega$$

$$I = \frac{6.5V}{6.5\Omega}$$

$$= 1 \text{ Amp}$$

$$R_{eq} = 6.5\Omega$$

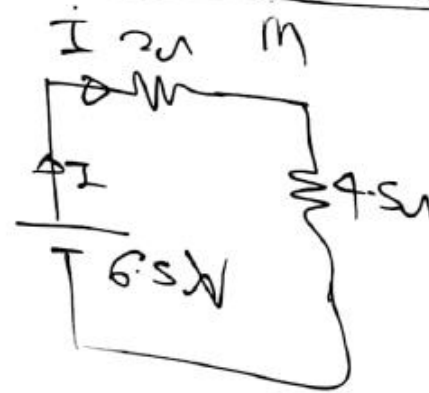

$$R_{eq} = \frac{6 \times 18}{6 + 18}$$

$$= \frac{6 \times 18}{24}$$

$$= \frac{9}{2} = 4.5\Omega$$