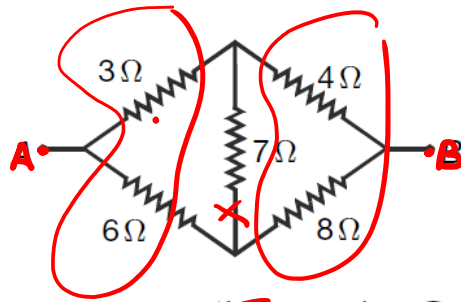


The net resistance of the circuit between A and B is



$$\frac{3}{6} = \frac{1}{2}$$

$$\frac{4}{8} = \frac{1}{2}$$


BWSB

(a) $8/3 \Omega$

(b) $14/3 \Omega$

(c) $16/3 \Omega$

(d) $22/3 \Omega$

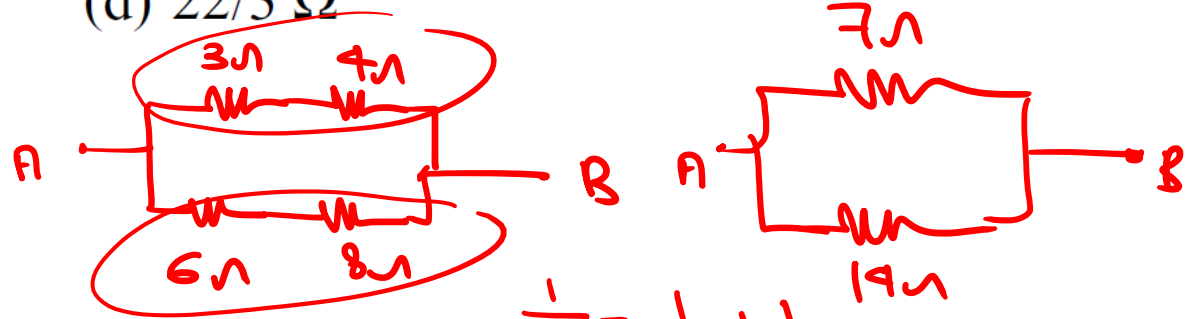

$$R_{AB} = \frac{7 \times 14}{7 + 14}$$

$$= \frac{7 \times 14}{2 \times 3}$$

$$R_{AB} =$$

$$R_{eq} = \frac{1}{7} + \frac{1}{14}$$

$$R_{eq} = \frac{14}{3} \Omega$$

A car battery of emf 12 V and internal resistance $5 \times 10^{-2} \Omega$, receives a current of 60 amp, from external source, then terminal potential difference of battery is

- (a) 12 V (b) 9 V
(c) 15 V (d) 20 V

$$V_p - V_q = \mathcal{E} + i r$$

$$= 12 + 60 \times 5 \times 10^{-2}$$

$$= 12 + 3000 \times 10^{-2}$$

$$= 12 + 3 = \underline{\underline{15 \text{ Volt}}}$$

$$\mathcal{E}_{\text{emf}} = 12 \text{ V}$$

$$r = 5 \times 10^{-2} \Omega$$

$$i = 60 \text{ amp}$$

charging of battery.



⑭ Practical The earth's surface has a negative surface charge density of 10^{-9} C/m^2 . The P.D of 400KV b/w the top of the atmosphere & the surface results [due to the low conductivity of the lower atmosphere] in a current of only 1800 A over the entire globe.



Neer2 chapter

$$Q = \sigma \times A = 10^{-9} \times [4\pi \times (6.37 \times 10^6)^2]$$

$$Q = 509.8 \times 10^3 \text{ C}$$

$$I = \frac{Q}{t}$$

$$t = \frac{Q}{I} = \frac{509.8 \times 10^3}{1800}$$

For a cell terminal potential difference is 2.2 V when circuit is open and reduces to 1.8 V when cell is connected to a resistance of $R=5 \Omega$. Determine internal resistance of cell (r)

- (a) $10/9 \Omega$ ✓ (b) $9/10 \Omega$
 (c) $11/9 \Omega$ (d) $5/9 \Omega$

$$i = \frac{2.2}{5+r}$$


$$2.2 - 1.8 = \frac{2.2r}{5+r}$$

$$0.4 = \frac{2.2r}{5+r}$$

$$r = \frac{2}{1.8} = \frac{20}{18} = \frac{10}{9}$$


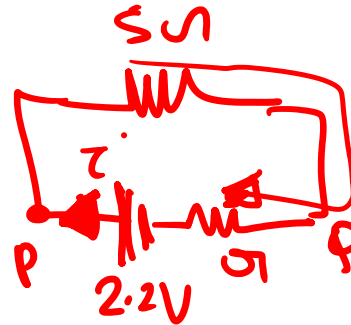
$$\underline{V_p - V_q = \epsilon = 2.2V}$$



$$V_p - V_q = 1.8V$$

$$\epsilon - ir = 1.8V$$

$$2.2 - \left(\frac{2.2}{5+r}\right)r = 1.8V$$

$$\Rightarrow 2 + 0.4r = 2.2r$$


$$2 = 1.8r$$

In a Wheatstone's bridge all the four arms have equal resistance R . If the resistance of the galvanometer arm is also R , the equivalent resistance of the combination as seen by the battery is

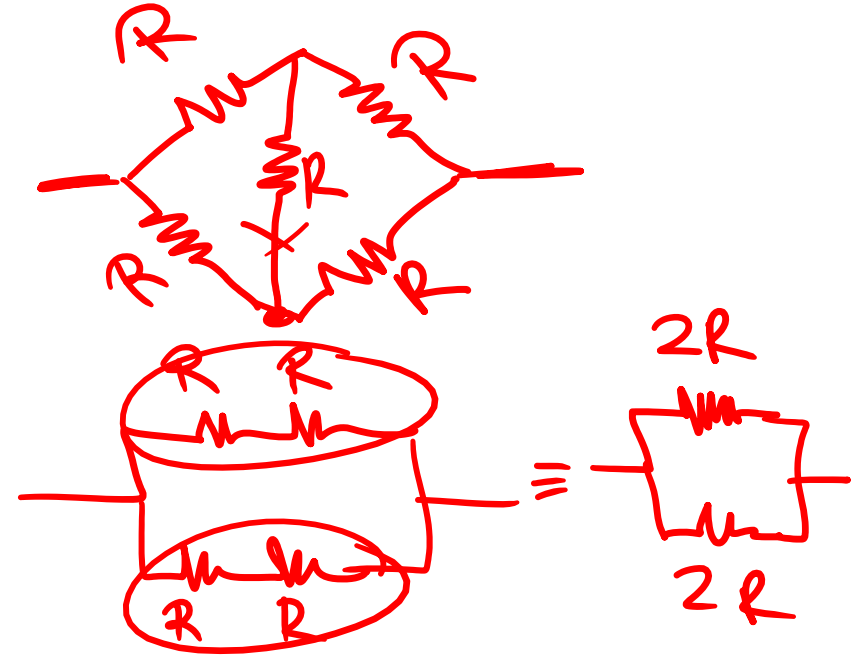- (a) $R/4$ (b) $R/2$
 (c) R (d) $2R$

$R_{eq} = R$

$$\frac{1}{R_{eq}} = \frac{1}{2R} + \frac{1}{2R}$$



$$\frac{1}{R_{eq}} = \frac{1+1}{2R} \quad \frac{1}{R_{eq}} = \frac{2}{2R}$$

Ohm's law is not obeyed by

- (a) electrolytes
- (b) discharge tube
- (c) vacuum tubes
- (d) all of these ✓



Kirchhoff's I and II laws are based on conservation of

- (a) energy and charge
- (b) charge and energy ✓
- (c) mass and charge
- (d) none of these

Ⓘ

Conservation of [Reverse] Charge.

Ⓜ

Energy Conservation

Resistance n , each of r ohm, when connected in parallel give an equivalent resistance of R ohm. if these resistances were connected in series, the combination would have a resistance in ohms, equal to

- (a) $n^2 R$
- (c) R/n

- (b) R/n^2
- (d) nR

[NCEET]



$$R = \frac{r}{n}$$

$$\frac{r}{n} = R$$

$$r = nR$$




$$R_{eq} = nr$$

$$= n[nR] = \underline{\underline{n^2 R}}$$

Five equal resistances each of resistance R are connected as shown in the figure. A battery of V volts is connected between A and B . The current flowing in $AFCEB$ will be



(a) $\frac{3V}{R}$

(c) $\frac{V}{2R}$

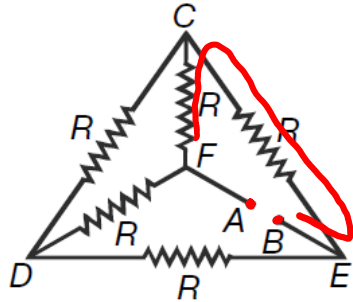


(b) $\frac{V}{R}$

(d) $\frac{2V}{R}$

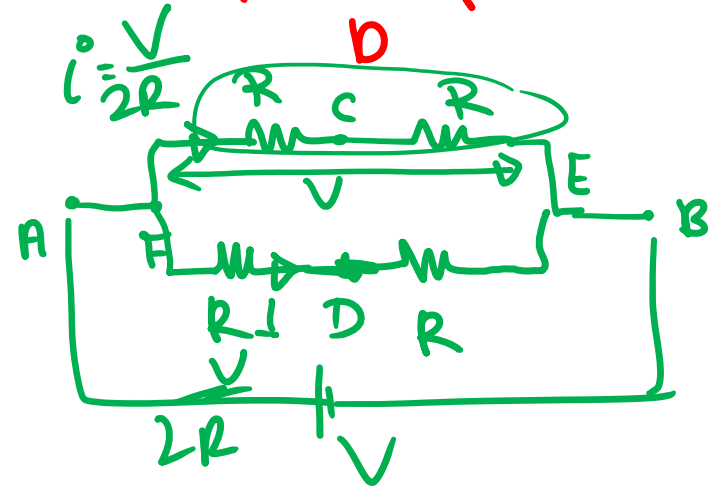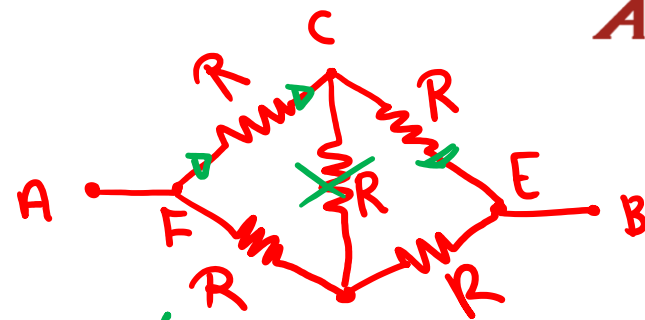

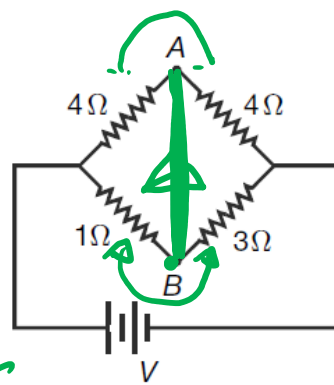In the circuit shown, if a conducting wire is connected between points A and B , current in this wire will



- (a) flow from B to A . ✓
 (b) flow from A to B .
 (c) flow in the direction which will be decided by the value of V .
 (d) be zero.

$$4:4 = \underline{\underline{1}}$$

$$1:3 = 0.33$$

$$\underline{\underline{V_B > V_A}}$$

[Yaad Karna]


JEE (main)

Two cells, having the same e.m.f. are connected in series through an external resistance R . Cells have internal resistances r_1 and r_2 ($r_1 > r_2$) respectively. When the circuit is closed, the potential difference across the first cell is zero. The value of R is

- (a) $r_1 + r_2$ (b) $r_1 - r_2$
 (c) $\frac{r_1 + r_2}{2}$ (d) $\frac{r_1 - r_2}{2}$

[good]
 good

$r_1 > r_2$

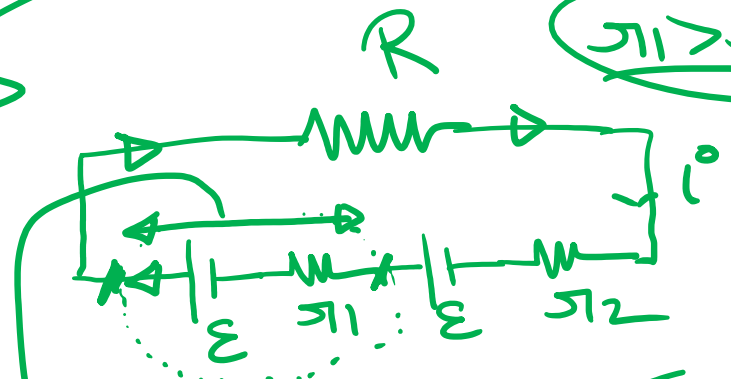

$$i = \frac{2\epsilon}{R + r_1 + r_2} \quad [L]$$

P.D $\Rightarrow \epsilon - i r_1 = 0$

$$\epsilon - \frac{2\epsilon}{R + r_1 + r_2} \times r_1 = 0$$

$$\underline{\underline{R = r_1 - r_2}}$$

$$\epsilon = \frac{2\epsilon}{R + r_1 + r_2} \times r_1$$

$$R + r_1 + r_2 = 2r_1$$

$$R = 2r_1 - r_1 - r_2$$

$$R = r_1 - r_2$$

1	2	3	4	5	6	7	8	9	10
B	C	A	C	D	B	A	C	A	B