

The masses of the wires of copper is in the ratio of 1 : 3 : 5 and their lengths are in the ratio of 5 : 3 : 1. The ratio of their electrical resistance is

- (a) 1 : 3 : 5
- (b) 5 : 3 : 1
- (c) 1 : 25 : 125
- (d) 125 : 15 : 1


$m, 3m, 5m$
 $5l, 3l, l$

$$R_1 : R_2 : R_3 = \frac{l_1^2}{m_1} : \frac{l_2^2}{m_2} : \frac{l_3^2}{m_3}$$

$$= \frac{25l^2}{m} : \frac{9l^2}{3m} : \frac{l^2}{5m}$$

$$= 25 : 3 : \frac{1}{5}$$

$= 125 : 15 : 1$

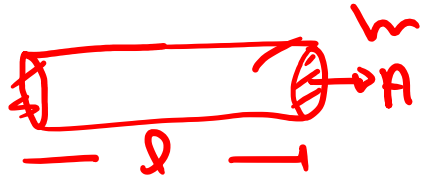

$$\text{density} = \frac{m}{Al}$$

$$m = \underline{A \cdot l} \times \text{density}$$

$$R = \frac{\rho l}{A} = \frac{\rho l^2}{Al}$$

$$= \frac{\rho l^2}{m / \text{density}}$$

$$R = \frac{\rho l^2 (\text{density})}{m}$$

$$R \propto \frac{l^2}{m}$$

$$R \propto \frac{l^2}{m}$$

A charged particle having drift velocity of $7.5 \times 10^{-4} \text{ m s}^{-1}$ in an electric field of $3 \times 10^{-10} \text{ V m}^{-1}$, has a mobility in $\text{m}^2 \text{ V}^{-1} \text{ s}^{-1}$ of

- (a) 2.25×10^{15}
 (c) 2.5×10^{-6}

- ~~(b) 2.5×10^6~~
 (d) 2.25×10^{-15}

NEET 2020

$$v_d = 7.5 \times 10^{-4} \text{ m/s}$$

$$E = 3 \times 10^{-10} \text{ V/m}$$

$$\begin{aligned}
 H &= \frac{v_d}{E} = \frac{7.5 \times 10^{-4}}{3 \times 10^{-10}} \\
 &= \frac{7.5 \times 10^{-4} \times 10^{10}}{3} \\
 &= \underline{\underline{2.5 \times 10^6 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}}}
 \end{aligned}$$

The color code of a resistance is given below



Yellow Violet Brown Gold
~~X~~ ~~Y~~ ~~Z~~ ~~T~~

The values of resistance and tolerance, respectively, are

- (a) 470 kΩ, 5%
- (b) 47 kΩ, 10%
- (c) 4.7 kΩ, 5%
- ~~(d) 470 Ω, 5%~~

$$\cdot (X \cdot Y + 10^Z \pm T)$$

$$\Rightarrow 47 + 10^1 \pm 5\%$$

$$= (470 \pm 5\%)$$




• BBROY
 ↓ ↓ ↓ ↓ ↓
 0 1 2 3 4
 Circuit → S
 Boy → G
Very → 7
 Gold → 8
 wide → 5
 Gold → 5%
 Silver → 10%
 No color → 20%

An electric bulb is rated 60 W, 220 V. The resistance of its filament is

- (a) 870 Ω (b) 780 Ω
 (c) 708 Ω (d) ~~807 Ω~~

Rating 60W, 220V

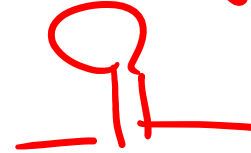

$$P = \frac{V^2}{R}$$

$$R = \frac{220 \times 220}{60}$$

$$\frac{2420}{3}$$

$$= 806.66 = \underline{\underline{807 \Omega}}$$

If 220 Volt apply
 || across the filament of bulb
 then bulb gives power
 60 J/s = 60 watt

Two metal wires of identical dimensions are connected in series. If σ_1 and σ_2 are the conductivities of the metal wires respectively, the effective conductivity of the combination is

(a) $\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2} \quad R = \frac{3l}{A}$

(b) $\frac{\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$

(c) $\frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$



(d) $\frac{\sigma_1 + \sigma_2}{2\sigma_1 \sigma_2}$

$R = \frac{l}{\sigma A}$

$R = \frac{3l}{A}$

$S = \frac{1}{R}$

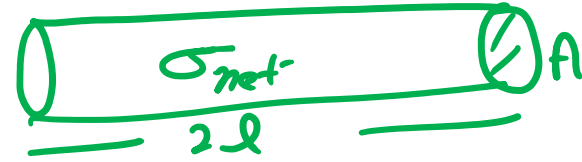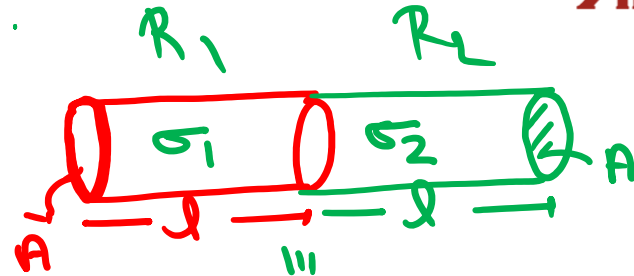$\sigma = \frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$




$$R_{eq} = R_1 + R_2$$

$$\frac{2l}{\sigma \cdot A} = \frac{l}{\sigma_1 A} + \frac{l}{\sigma_2 A}$$

$$\frac{2}{\sigma} = \frac{1}{\sigma_1} + \frac{1}{\sigma_2}$$

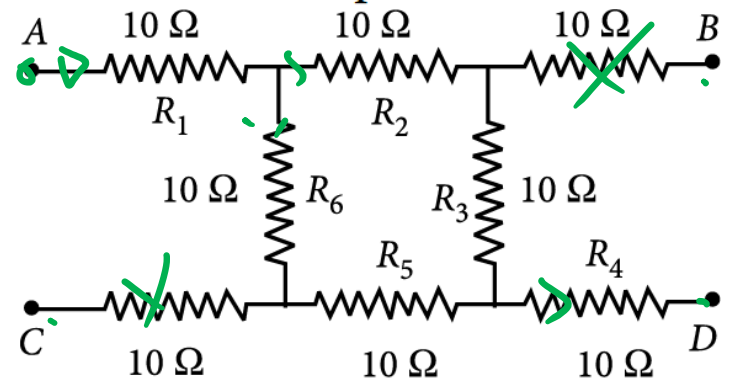
What will be the equivalent resistance between the two points A and D?



- (a) $30\ \Omega$
- (c) $20\ \Omega$


$R_{AD} = 30\ \Omega$

- (b) $40\ \Omega$
- (d) $10\ \Omega$

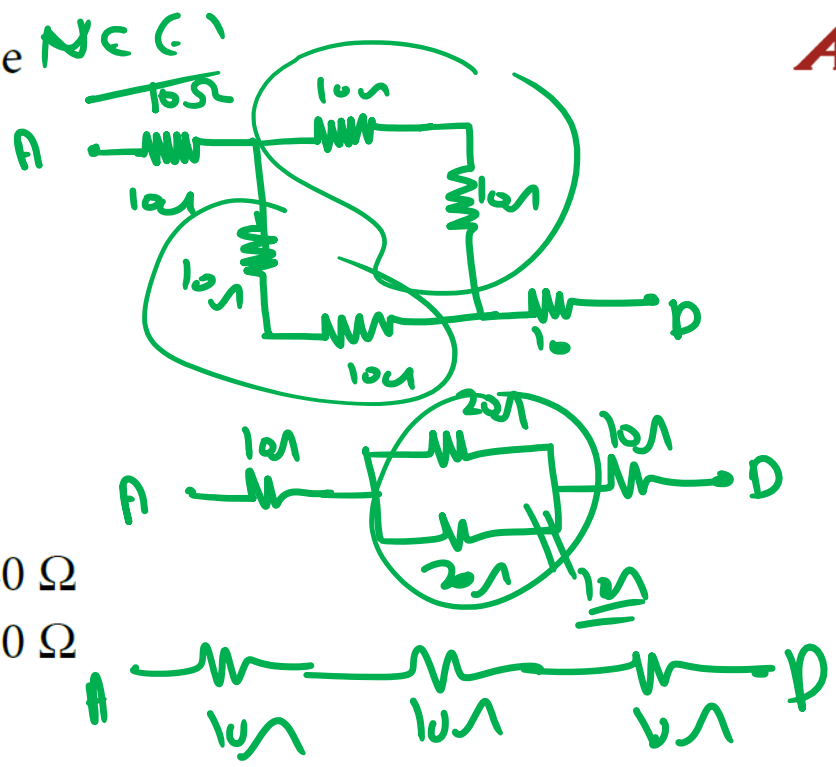


The internal resistance of a cell of e.m.f. 2 V is 0.1Ω . It is connected to a resistance of 3.9Ω . The voltage across the cell will be

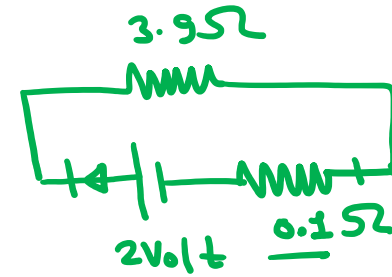- (a) 1.95 V  (b) 1.9 V
 (c) 0.5 V (d) 2 V



$$\begin{aligned}
 T.P &= \mathcal{E} - iR \\
 &= 2\text{V} - \frac{2}{4} \times 0.1 \\
 &= 2 - \frac{1}{2} \times 0.1 \\
 &= 2 - 0.05 \\
 &= \underline{\underline{1.95 \text{ Volt}}}
 \end{aligned}$$

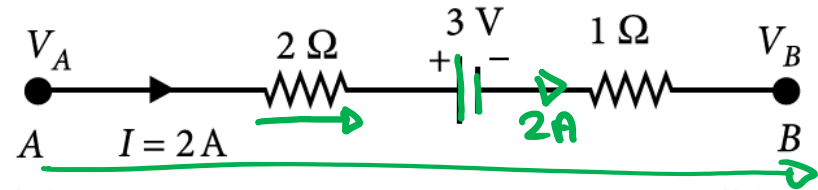The potential difference ($V_A - V_B$) between the points A and B in the given figure is





- (a) -3 V
- (b) $+3\text{ V}$
- (c) $+6\text{ V}$
- ~~(d) $+9\text{ V}$~~

$$V_A - 2 \times 2 - 3 - 2 \times 1 = V_B$$

$$V_A - V_B = 4 + 3 + 2 = 9\text{ Volt}$$

$$V_A - V_B = 9\text{ Volt}$$

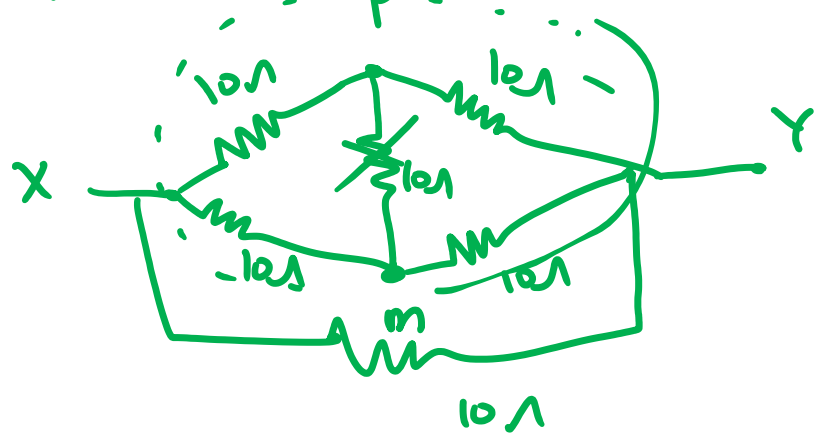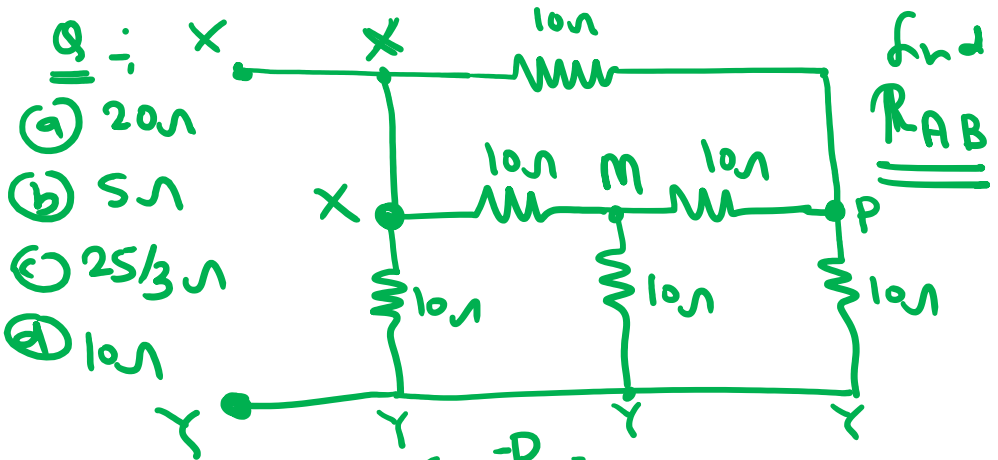


A potentiometer wire of length L and a resistance r are connected in series with a battery of e.m.f. E_0 and a resistance r_1 . An unknown e.m.f. E is balanced at a length l of the potentiometer wire. The e.m.f. E will be given by

(a) $\frac{E_0 l}{L}$

(b) $\frac{LE_0 r}{(r + r_1) l}$

(c) $\frac{LE_0 r}{r_1 L}$

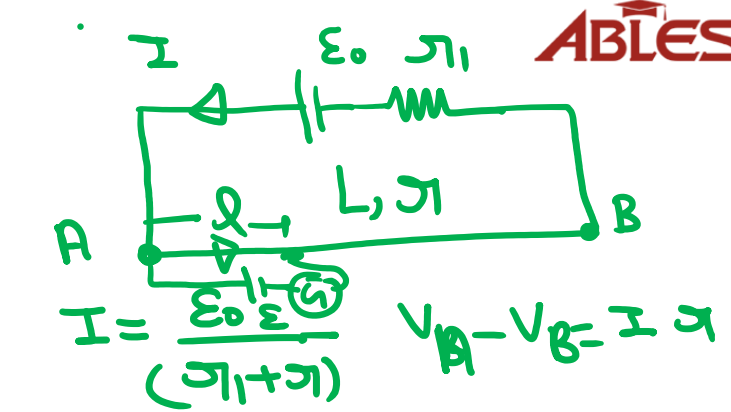(d) $\frac{E_0 r}{(r + r_1)} \cdot \frac{l}{L}$



$V_A - V_B = \left(\frac{E_0}{r_1 + r} \right) r$

$x = \frac{V_{AB}}{L} = \left[\left(\frac{E_0 r}{r_1 + r} \right) \times \frac{1}{L} \right]$

$E = x l$

$E = \frac{E_0 r}{(r_1 + r) L} \times l \times 1 = \frac{E_0 r l}{(r_1 + r) L}$

9) Two bulbs are of (40W, 200V) & (100W, 200V). The correct relation for their resistance.

Ⓐ $R_{40} < R_{100}$ $R_{40} = \frac{V^2}{P} = \frac{200 \times 200}{40}$

~~Ⓑ $R_{40} > R_{100}$ $R_{40} = 1000 \Omega$~~

Ⓒ $R_{40} = R_{100}$

Ⓓ no relation can be predicted.

$R_{100} = \frac{200 \times 200}{100} = \underline{\underline{400 \Omega}}$

R

If specific resistance of a potentiometer wire is $10^{-7} \Omega \text{ m}$ and current flow through it is 0.1 amp., cross-sectional area of wire is 10^{-6} m^2 then potential gradient will be

- (a) 10^{-2} volt/m
- (b) 10^{-4} volt/m
- (c) 10^{-6} volt/m
- (d) 10^{-8} volt/m

$\rho \rightarrow 10^{-7} \Omega\text{-m}$
 $i = 0.1 \text{ amp}$
 $A = 10^{-6} \text{ m}^2$



$$\alpha = \frac{V_A - V_B}{l} = \frac{l[\rho i]}{A \times l}$$

$$V_A - V_B = i \times R$$

$$V_A - V_B = i \left(\frac{\rho l}{A} \right)$$

$$= \frac{i \rho}{A} = \frac{0.1 \times 10^{-7}}{10^{-6}} = 0.1 \times 10^{-7} \times 10^6 = 1 \times 10^{-2} \text{ Volt/m}$$


Q1: A (100W, 200) Volt bulb is connected to a 160V supply. The power consumption would be.

- 80
- (a) 100W.
- (b) 125W.
- (c) 64W.
- (d) 80W.

Rating से ज्ञात किया करते हैं। Resistance

$$P = \frac{V^2}{R} \quad R = \frac{200 \times 200}{100}$$

$$R = 400 \Omega$$

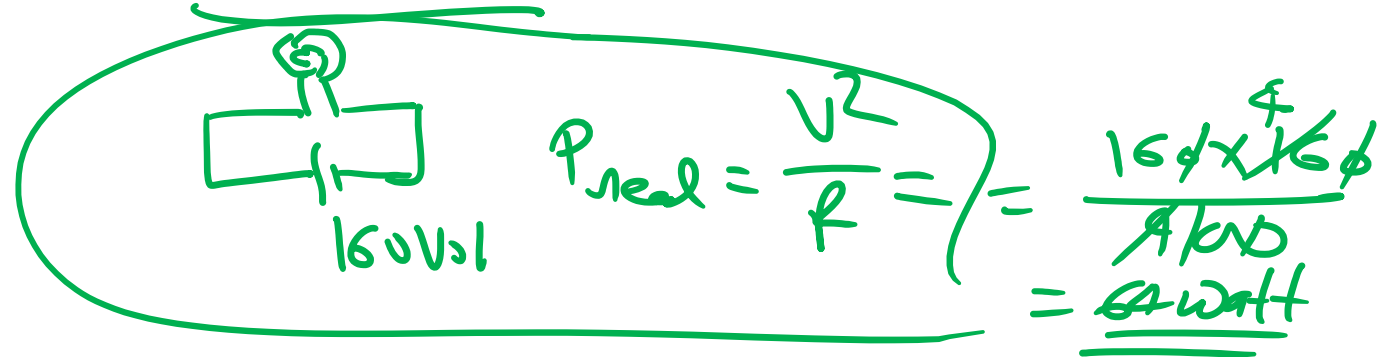

1	2	3	4	5	6	7	8	9	10
D	B	D	D	C	A	A	D	D	A