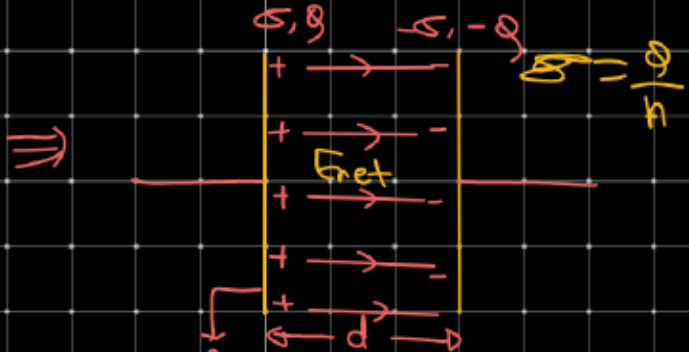


# ↳ Parallel Plate Capacitor (PPC)




$$E_{\text{in}} = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0}$$


$$(\Delta V)_{\text{b/w plate}} = E d = \frac{\sigma d}{\epsilon_0} = \frac{Q d}{A\epsilon_0}$$

$$C = \frac{+Q}{\Delta V} = \frac{A\epsilon_0}{d}$$
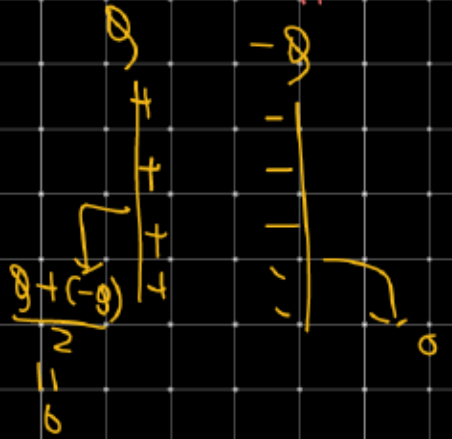
$$C_m = \frac{A\epsilon_0\epsilon_r}{d}$$



⇒ when PPC Connected with battery:

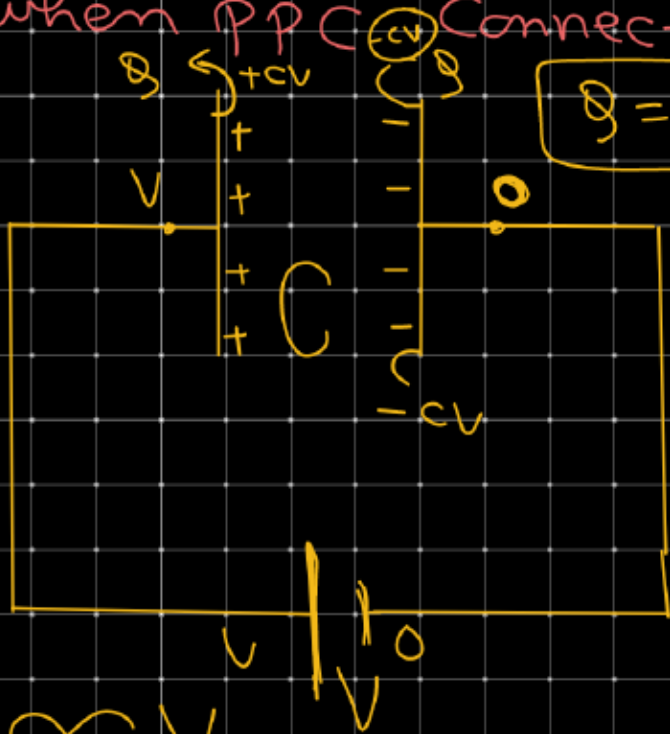

$$Q = CV$$


↳ Potential across the Capacitor is V

↳ C is the Capacitance of Capacitor.

$$\underline{\underline{Q = CV}}$$
$$\underline{\underline{Q = CV}}$$

$$\underline{\underline{Q = CV}}$$

Q1)

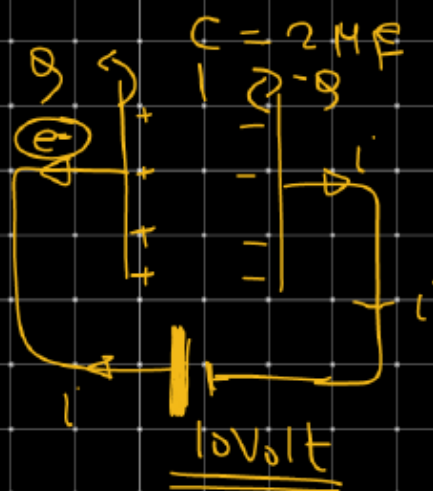

$$Q = ?$$

$$Q = CV$$

$$Q = (2\mu F) \times 10$$

$$Q = 20\mu C$$


$$Q = \underline{\underline{20\mu C}}$$

$$Q = 20 \times 10^{-6} C$$
$$Q = 2 \times 10^{-5} C$$


$$\Rightarrow \boxed{Q = PC}$$

$$Q \propto \Delta V$$
$$\boxed{Q = C \Delta V}$$

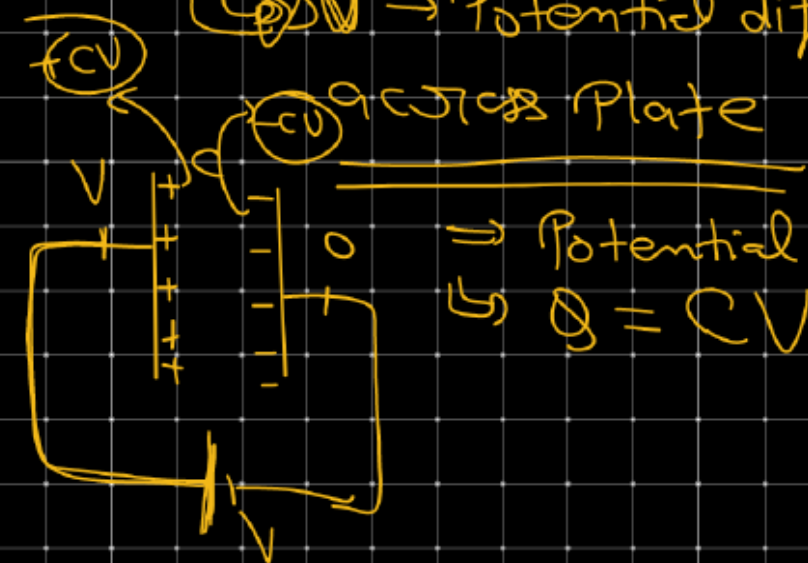$\Delta V$  → Potential diff  
C → Capacitance of Capacitor.



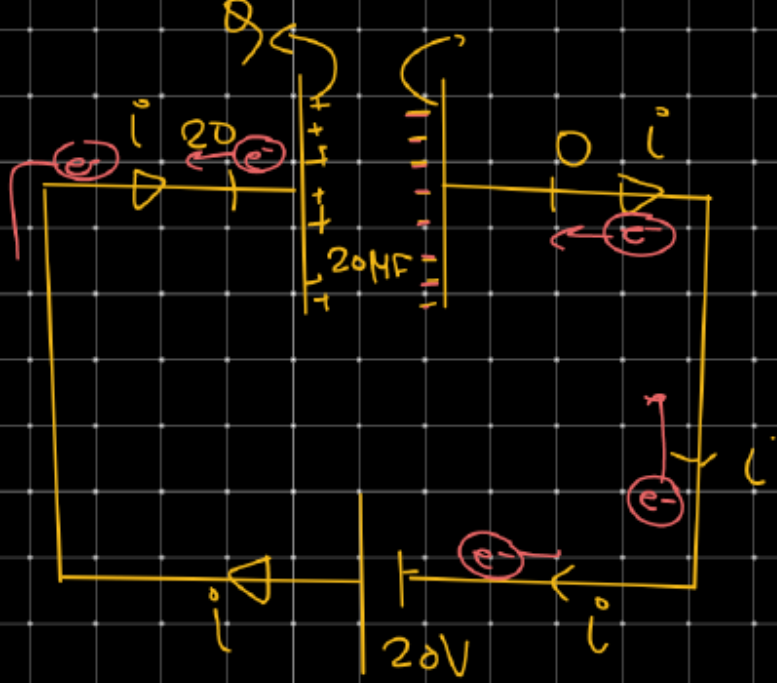⇒ Potential across the plate = V.  
↳  $Q = CV$



$$\hookrightarrow Q = CV$$


$$= CV$$

$$Q = CV$$

$$= (20\text{mF})(20\text{V})$$

$$= 400\text{mC}$$
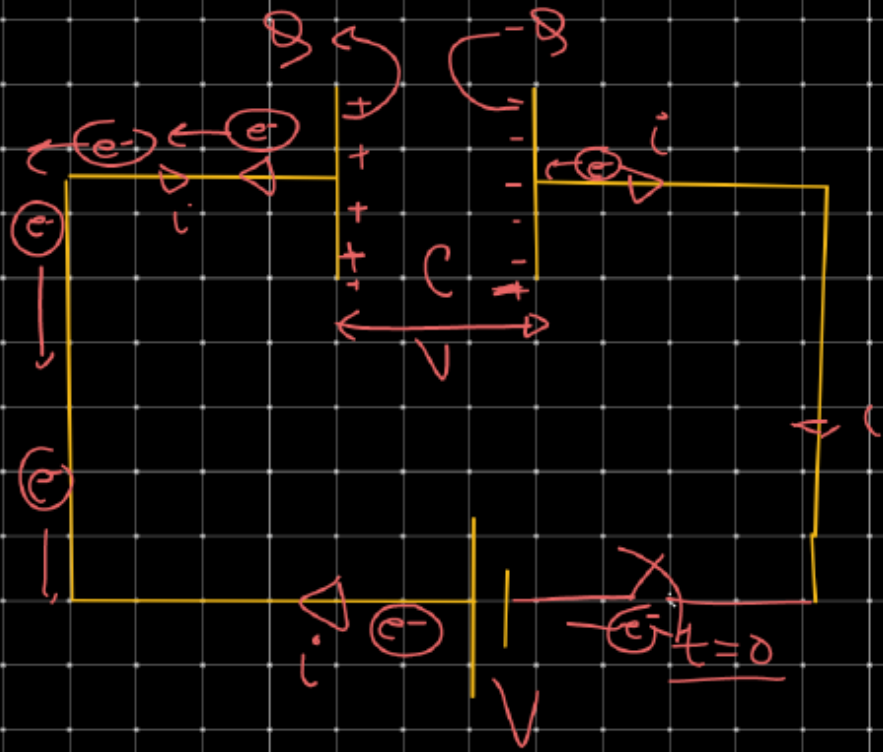
$$= \underline{\underline{4 \times 10^{-4}\text{C}}}$$



$t=0$ , Switch is closed.

$t \rightarrow \infty$  Steady state.

$$Q = CV$$

## ⇒ Energy Store in Capacitor:-

↳ at  $t=0^+$  Switch is on

at any instant, charge on Capacitor is  $q$

↳ Potential drop across the Capacitor  $[q = CV]$

$$V' = \frac{q}{C}$$


work done to increase  $dq$  charge on Capacitor


$$dW = (dq) V' = dq \times \frac{q}{C}$$

$$W = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \int_0^Q q dq$$

$$W = \frac{1}{C} \left[ \frac{q^{1+1}}{1+1} \right]_0^Q$$
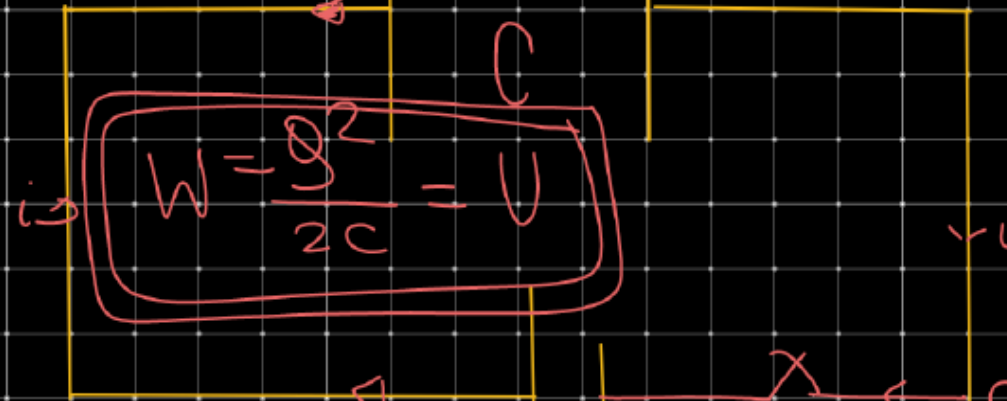
$$W = \frac{1}{C} \left[ \frac{q^2}{2} \right]_0^Q = \frac{1}{C} \left[ \frac{Q^2}{2} - \frac{0}{2} \right] = \frac{1}{C} \frac{Q^2}{2} = \boxed{W = \frac{Q^2}{2C}}$$



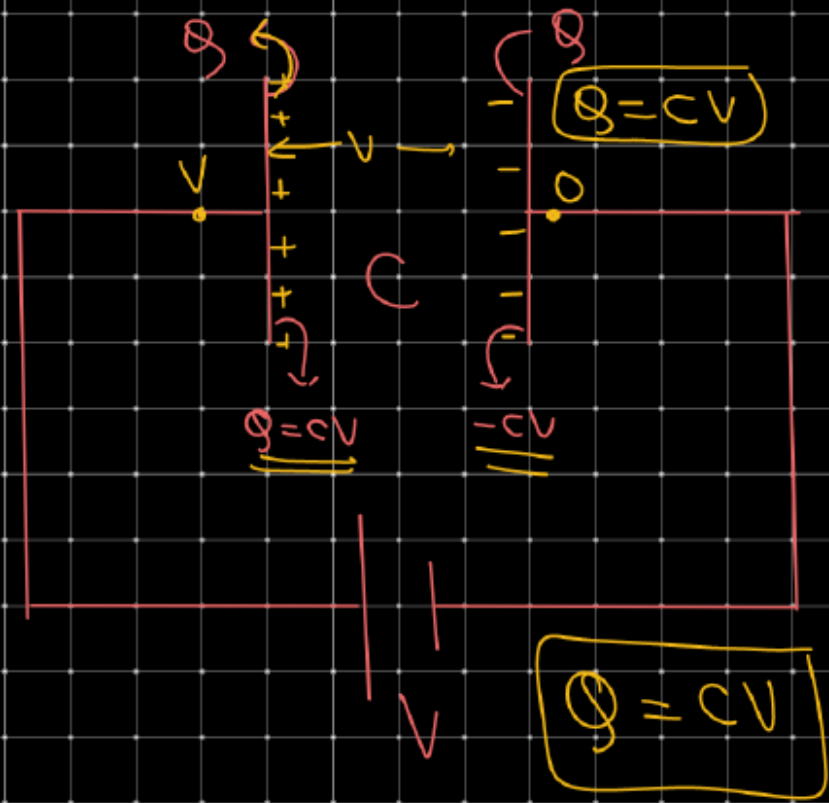

At steady state -  $t = \infty$

$$\text{Energy stored} = \frac{Q^2}{2C}$$

$$Q = CV$$

$$U = \frac{Q^2}{2C} = \frac{(CV)^2}{2C} = \frac{1}{2} CV^2$$


$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{QV}{2}$$

$$U = \frac{1}{2} (CV)V = \frac{1}{2} QV = \frac{QV}{2}$$



Q1) At steady state find (i) Q, (ii) E=?, (iii) U

(iv) U

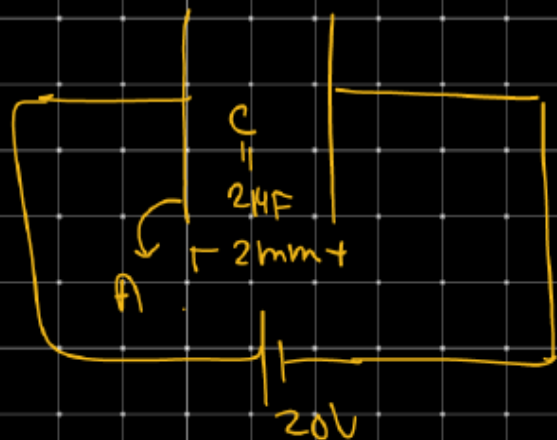

$$\begin{aligned} \text{(i) } Q &= CV = (2\mu\text{F}) 20\text{V} \\ &= 40\mu\text{F-V} \\ &= 40\mu\text{C} \\ &= 40 \times 10^{-6} \text{C} = 4 \times 10^{-5} \text{C} \end{aligned}$$

$$\text{(ii) } E = \frac{Q}{A\epsilon_0} = \frac{Q}{\epsilon_0}$$

$$\begin{aligned} U &= \frac{1}{2} CV^2 \\ &= \frac{Q^2}{2C} \Rightarrow \frac{1}{2} QV \end{aligned}$$

$$\begin{aligned} \text{(iii) } U &= Ed = \frac{Qd}{A\epsilon_0} \\ &= \frac{1}{2} \times 4 \times 10^{-5} \text{C} \times 20 \\ &= 40 \times 10^{-5} = 4 \times 10^{-4} \text{J} \end{aligned}$$

↳ Energy store inside the Capacitor & Energy density:

$u =$

$$\frac{U}{Ad} = \frac{1}{2} \epsilon_0 E^2$$

$$\frac{U}{V} = u = \frac{1}{2} \epsilon_0 E^2$$

$$u = \frac{Q^2}{2CA d}$$

$$U = \frac{1}{2} \epsilon_0 E^2 Ad$$


$$\frac{U}{Ad} = \frac{1}{2} \epsilon_0 E^2$$

$$u = \frac{1}{2} \epsilon_0 E^2$$

$$U = \frac{(E A \epsilon_0)^2}{2 A \epsilon_0 d}$$

$$U = \frac{E^2 A^2 \epsilon_0^2 \times d}{2 A \epsilon_0}$$

$$U = \frac{1}{2} \epsilon_0 E^2 Ad$$

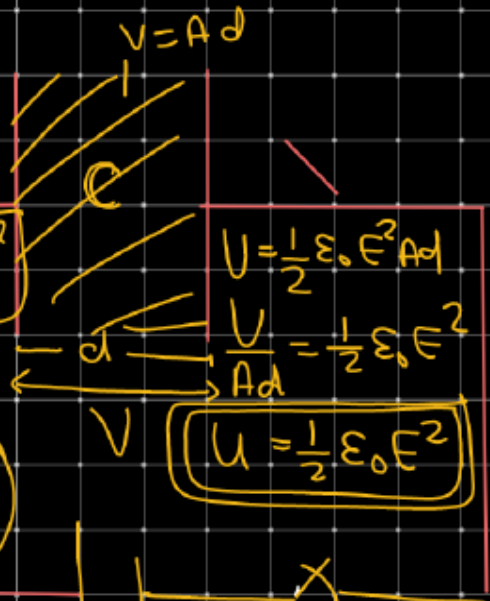

(i) at steady state ( $i=0$ )

(ii) Charge store on Capacitor.

$$Q = CV$$

(iii) Energy store by Capacitor

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

$$U = \frac{E^2 \epsilon_0 Ad}{2}$$

$$E = \frac{Q}{A \epsilon_0}$$


$$Q = E A \epsilon_0$$

$$Q = E A \epsilon_0$$

$$C = \frac{A \epsilon_0}{d}$$

$$U = \frac{(E A \epsilon_0)^2}{2 A \epsilon_0 d} = \frac{E^2 A^2 \epsilon_0^2 d}{2 A \epsilon_0}$$

#

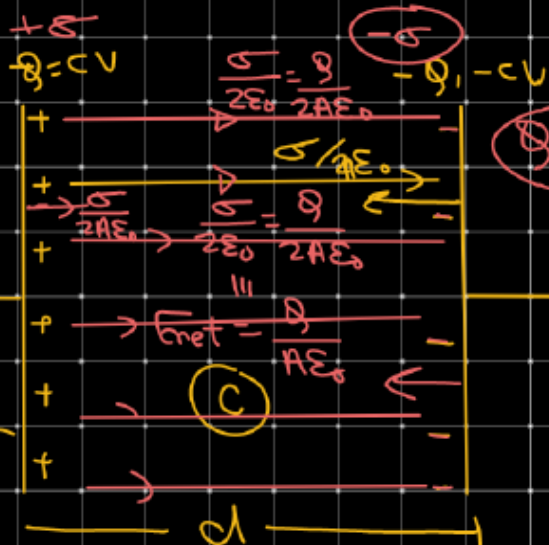

$$Q = \sigma A$$

At Steady state ( $t = \infty$ )

$$C = \frac{A\epsilon_0}{d}$$

$$Q = CV$$

# Force on (+ve) Plate

$$F = Q [E]$$

$$= Q \left[ \frac{Q}{2A\epsilon_0} \right]$$

$$\text{Force} = \frac{Q^2}{2A\epsilon_0} = \frac{\sigma^2 A^2}{2A\epsilon_0}$$

$$\text{Force} = \frac{\sigma^2 A}{2\epsilon_0}$$

Force on positive Plate = Force on -ve plate

$$= \frac{Q^2}{2A\epsilon_0} = \frac{\sigma^2 A}{2\epsilon_0}$$

\*\*

① Pressure on Plate

$$P = \frac{F}{A} = \frac{\sigma^2 A}{2\epsilon_0 \times A} = \frac{\sigma^2}{2\epsilon_0}$$

⇒ The two PPC connected by 300V battery, Charge collected at each plate of PPC is 1nC. Find Energy store in PPC.


Sol) Solve  $U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV.$

$$= \frac{1}{2} \times 1 \times 10^{-6} \text{ C} \times 300 \text{ V}$$

$$= 1.5 \times 10^{-6+2} \text{ J}$$

$$= \underline{\underline{1.5 \times 10^{-4} \text{ J}}} = \underline{\underline{150 \mu\text{J}}}$$
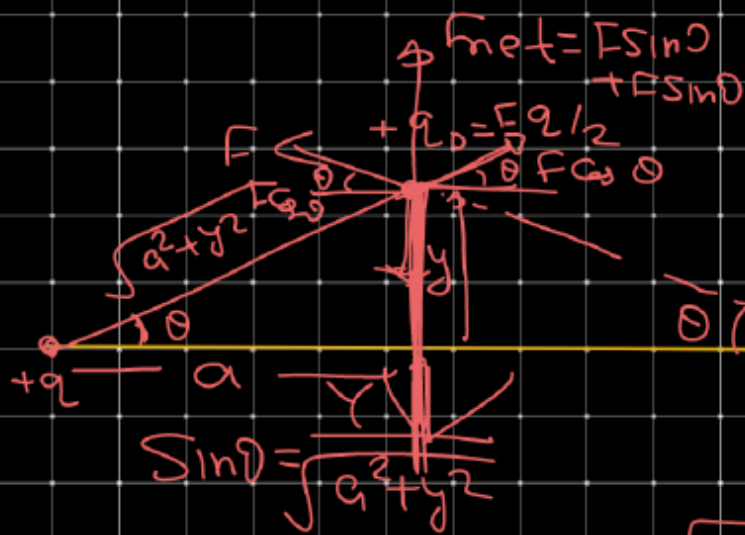
$$= \underline{\underline{.15 \text{ mJ}}}$$



$$F = \frac{kq_0 q_0}{(\sqrt{a^2 + y^2})^2} = \frac{kq_0 q_0}{(a^2 + y^2)}$$

$$F_{net} = 2F \sin \theta$$


$$\sin \theta = \frac{y}{\sqrt{a^2 + y^2}}$$

$$F = \frac{2kq_0 q_0 y}{(a^2 + y^2)}$$

$$F = \frac{2kq^2 y}{(a^2 + y^2)^{3/2}} = \frac{2kq^2 y}{a^3} = \frac{2kq^2 y}{(a^2 + y^2)(a^2 + y^2)^{1/2}}$$

$y \ll a$  given  $F \propto y$   $F \propto -y$

$$(a^2)^{3/2} = a^3$$

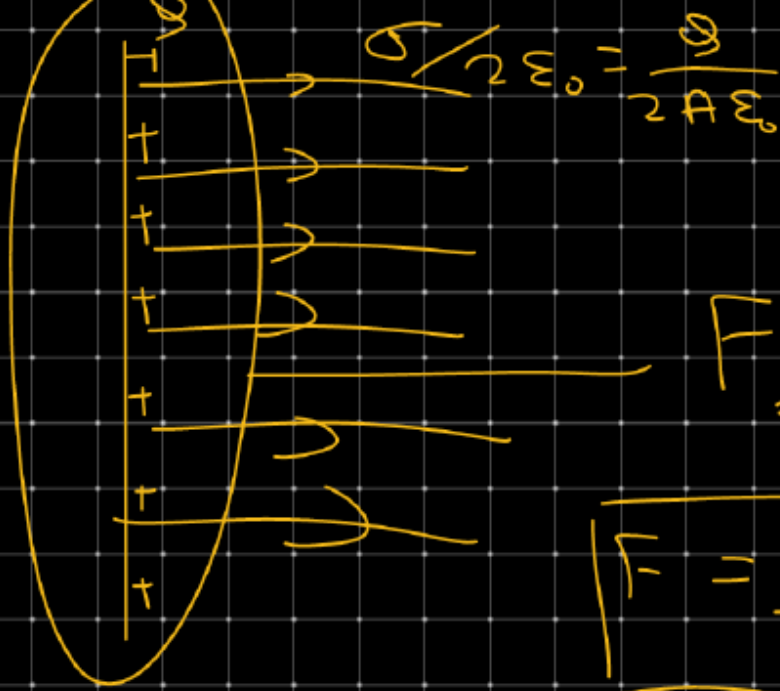

$$F = qE$$
$$= Q \times \frac{Q}{2A\epsilon_0}$$

$$F = \frac{Q^2}{2A\epsilon_0}$$