

# # Parallel Connection of Capacitors:-


↳ Potential across each capacitor is same.

$$q = q_1 + q_2 + q_3$$


$$C_{eq}V = C_1V + C_2V + C_3V$$

$$(C_{eq})V = (C_1 + C_2 + C_3)V$$

$$C_{eq} = C_1 + C_2 + C_3$$

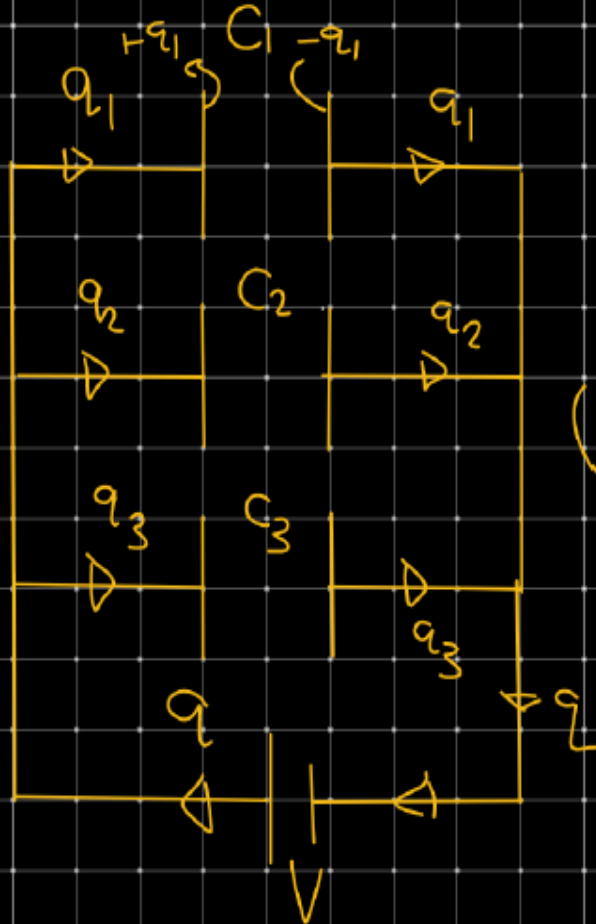



## Series connection:-

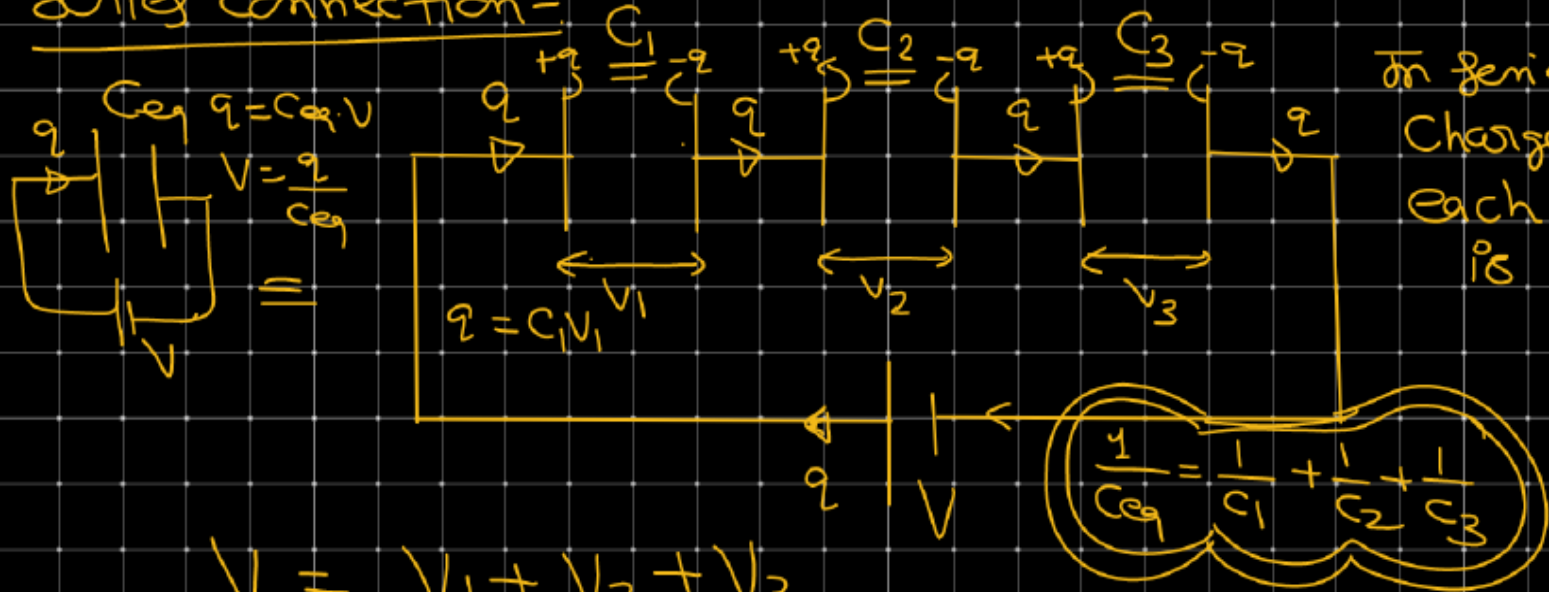

In series connection  
Charge flow on  
each capacitor  
is same.

$$V = V_1 + V_2 + V_3$$

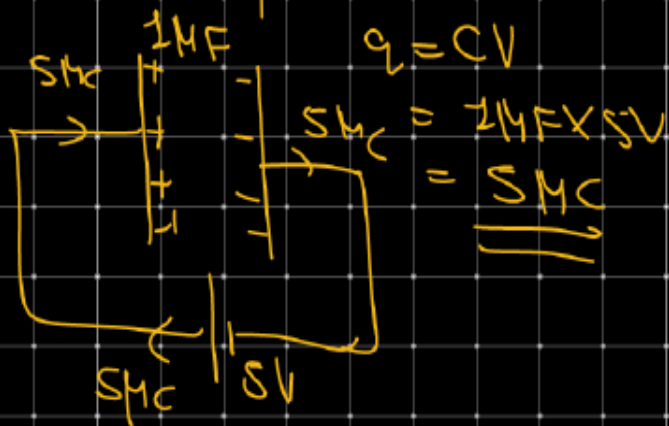
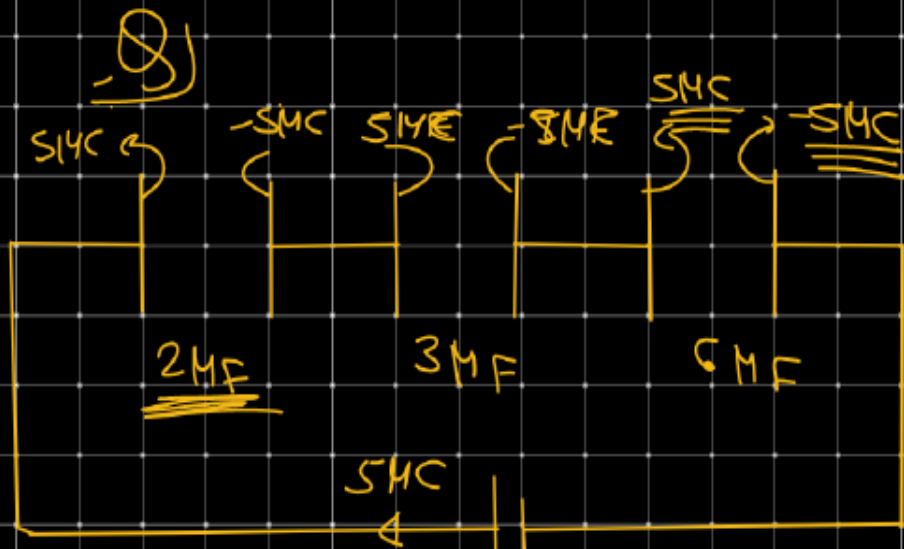
$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3} = q \left[ \frac{1}{C_{eq}} \right] = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right] q$$



- ⑨ Find  $C_{eq}$ .  
 ⑩ Charge flow through the battery.  
 ⑪ Charge on each capacitor.

$C_{eq} = 2MF$

Q)

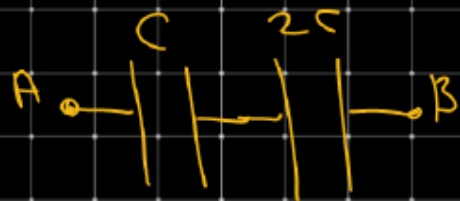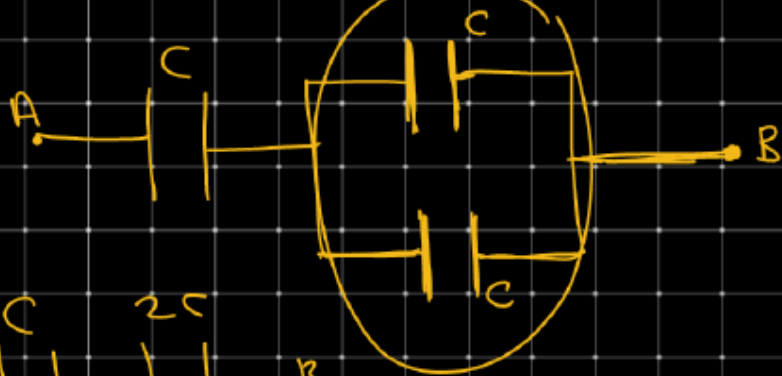

Parallel

$$C_{eq} = C_1 + C_2 \\ = C + C = \underline{\underline{2C}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} = \frac{2+1}{2C}$$


$$\frac{1}{C_{eq}} = \frac{3}{2C}$$

$$\Rightarrow C_{eq} = \frac{2C}{3}$$

 $C_{eq}$  b/w A & B.

$$C_{eq} = \frac{2C}{3}$$

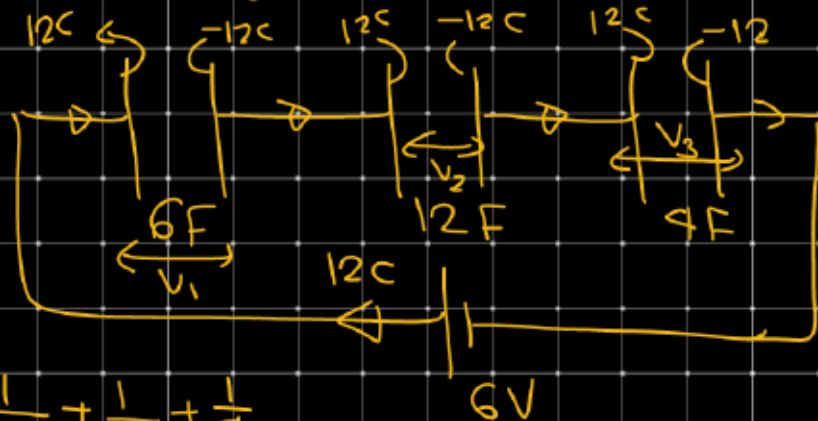Q) Find charges & Potential across each Capacitor.



Step 1)  $C_{eq}$ .


Step 2) Charge flow through battery

$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{12} + \frac{1}{4}$$

$$\frac{1}{C_{eq}} = \frac{2+1+3}{12} = \frac{6}{12}$$

$$C_{eq} = 2F$$
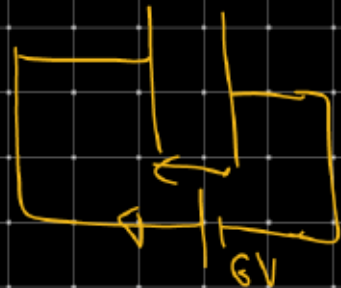
$$Q = C_{eq} \cdot V = 2 \times 6 = 12C$$



$$Q = C_1 V_1$$

$$12 = 6 V_1$$

$$V_1 = 2 \text{ Volt}$$

$$12 = 12 \times V_2 \quad 12 = 4 V_3$$



$$V_2 = 1 \text{ Volt}$$

$$V_3 = 3 \text{ Volt}$$

$$V_1 + V_2 + V_3 = 6$$

$$2 + 1 + 3 = 6 \text{ Volt}$$

9) Find  $C_{eq}$  b/w A & B

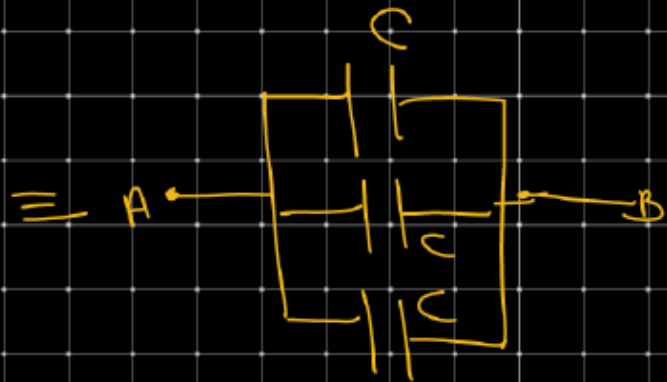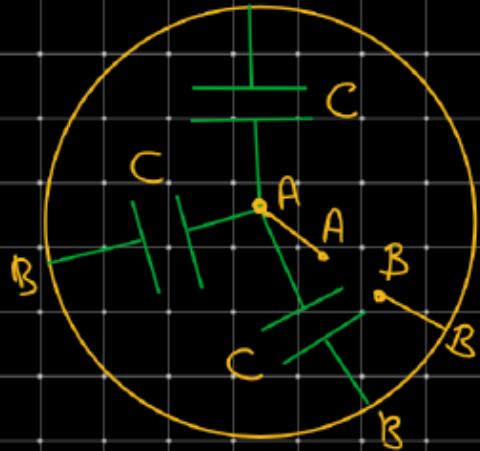


$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = 3C$$

# WSB:-

find  $C_{eq}$


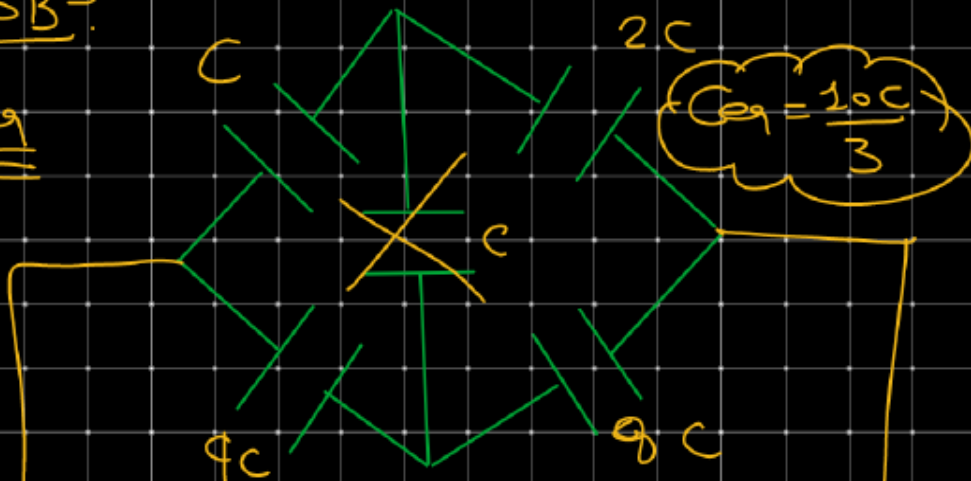


$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} = \frac{2+1}{2C}$$

$$C_{eq} = \frac{2C}{3}$$

$$\frac{1}{C_{eq}} = \frac{1}{8C} + \frac{1}{4C} = \frac{1+2}{8C}$$

$$C_{eq} = \frac{8C}{3}$$

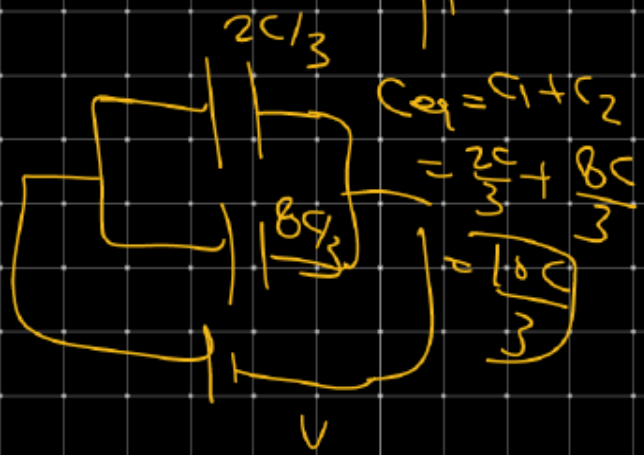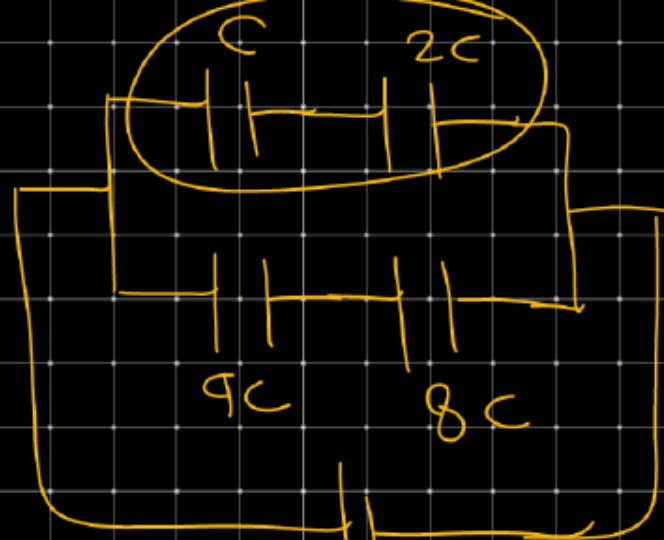

$$C_{eq} = C_1 + C_2$$

$$= \frac{2C}{3} + \frac{8C}{3}$$

$$= \frac{10C}{3}$$



Q) Five Capacitors, each of capacitance value  $C$  are connected as shown in figure. The ratio of Capacitance b/w P & R, and the Capacitance b/w P & Q is [AIEEE 2008]

$$\frac{C_{PR} = 5C \times 4}{6 \times 5C}$$

- (a) 3:1
- (b) 5:2
- (c) 2:3
- (d) 1:1

$$= \frac{2}{3}$$

$$C_{PR} = \frac{5C}{6}$$

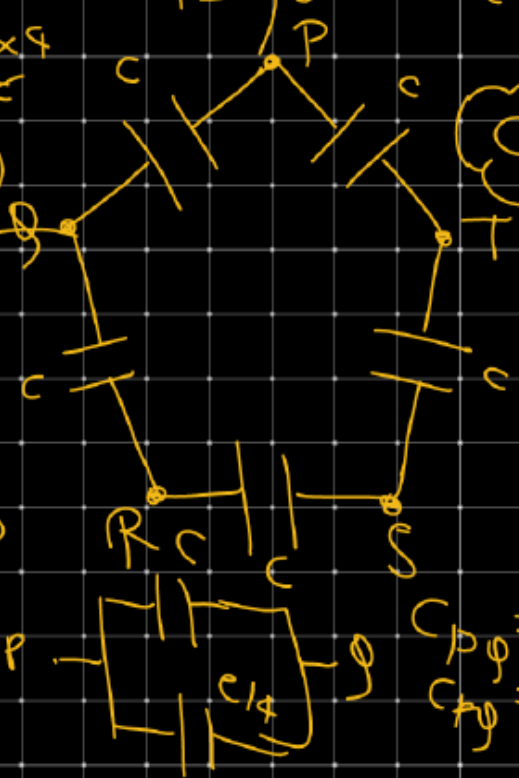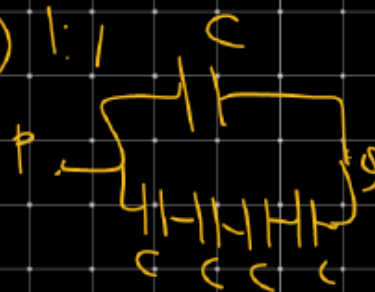

$$C_{PQ} = \frac{5C}{4}$$


$$C_{PQ} = \frac{5C}{4}$$






$$C_{PQ} = C_1 + C_2 = \frac{C}{2} + \frac{C}{3} = \frac{5C}{6}$$



Q) Cap b/w P & Q.

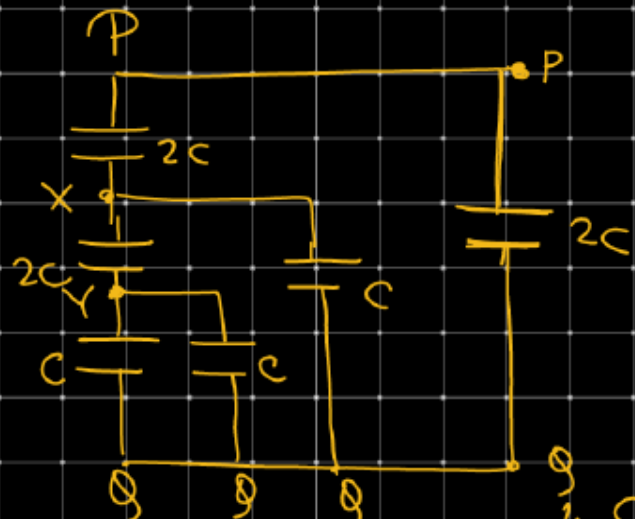

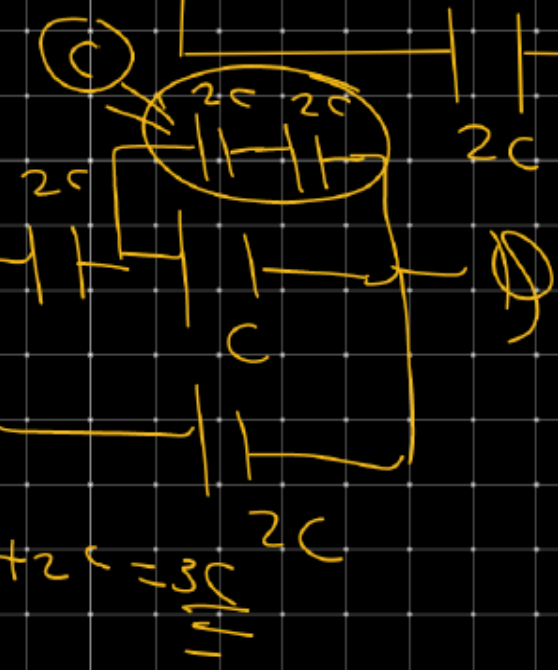
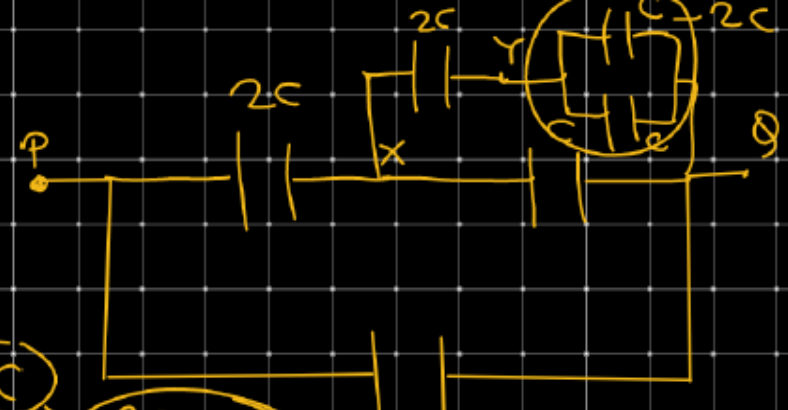
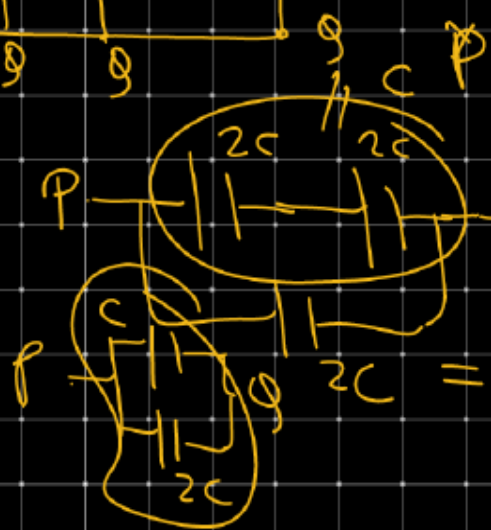
- (a)  $C/3$
- (b)  $C$
- (c)  $3C$
- (d)  $2C$



$$\frac{1}{C_1} = \frac{1}{2C} + \frac{1}{2C} = \frac{2}{2C}$$

$C_1 = C$

Cap b/w A & B.

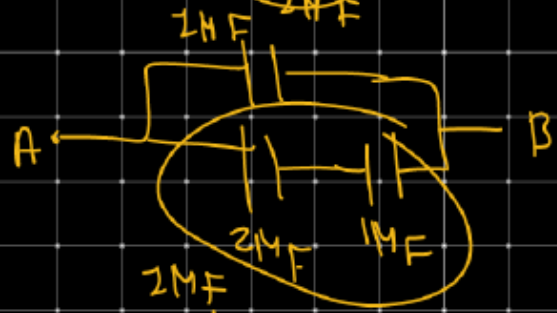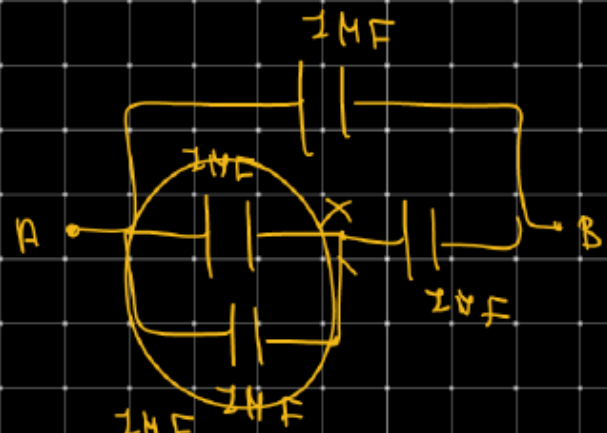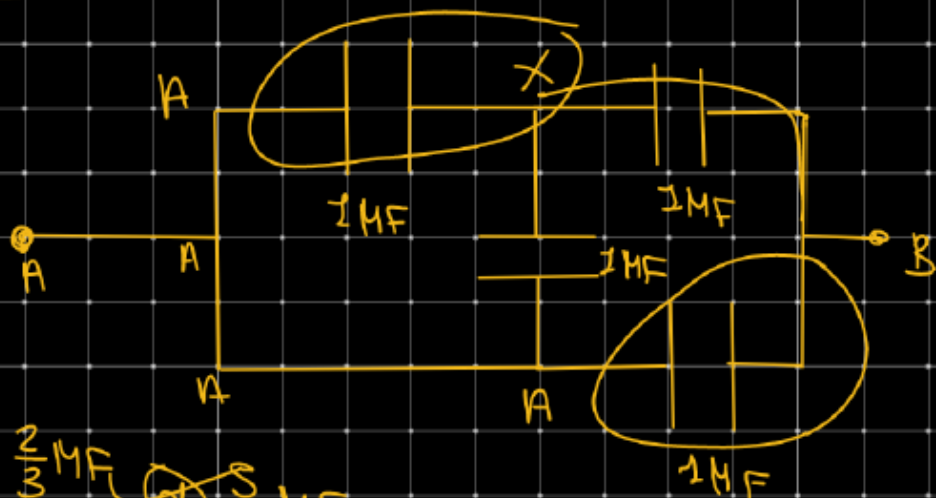

(a)  $\frac{2}{3} MF$  (d)  $\frac{5}{3} MF$

(b)  $\frac{7}{3} MF$

(c)  $\frac{8}{3} MF$

$$\frac{1}{C_{eq}} = \frac{1}{2} + \frac{1}{1} = \frac{3}{2}$$

$$C_{eq} = \frac{2}{3} MF$$

$$C_{eq} = C_1 + C_2 = 1 + \frac{2}{3} = \frac{5}{3} MF$$