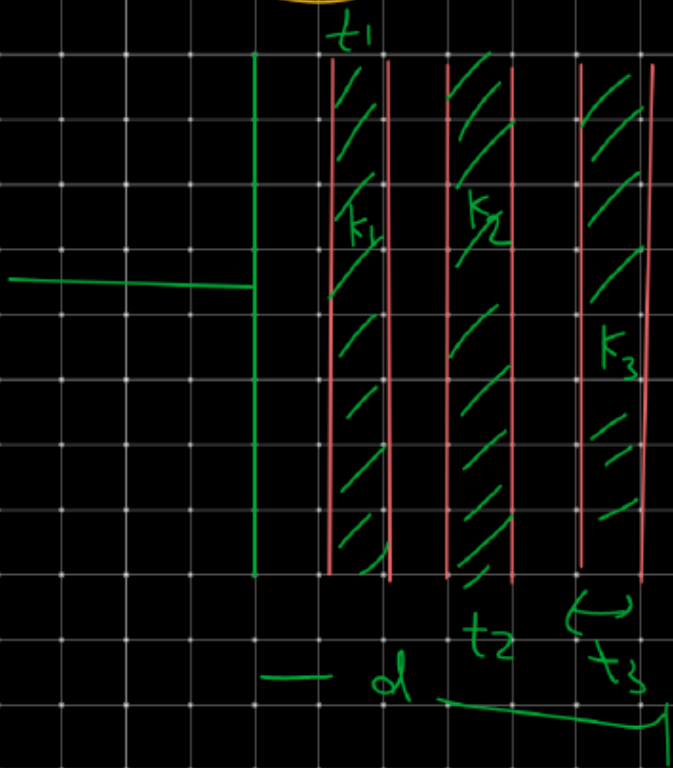


⇒ dielectric inside PPC:



$$C = \frac{A \epsilon_0 k}{d}$$


⇒ Partial (OR) different-? dielectric part inside? PC-1





$$C = \frac{A\epsilon_0}{(d - t_1 - t_2 - t_3) + \frac{t_1}{K_1} + \frac{t_2}{K_2} + \frac{t_3}{K_3}}$$

$$C = \frac{Q}{\Delta V}$$
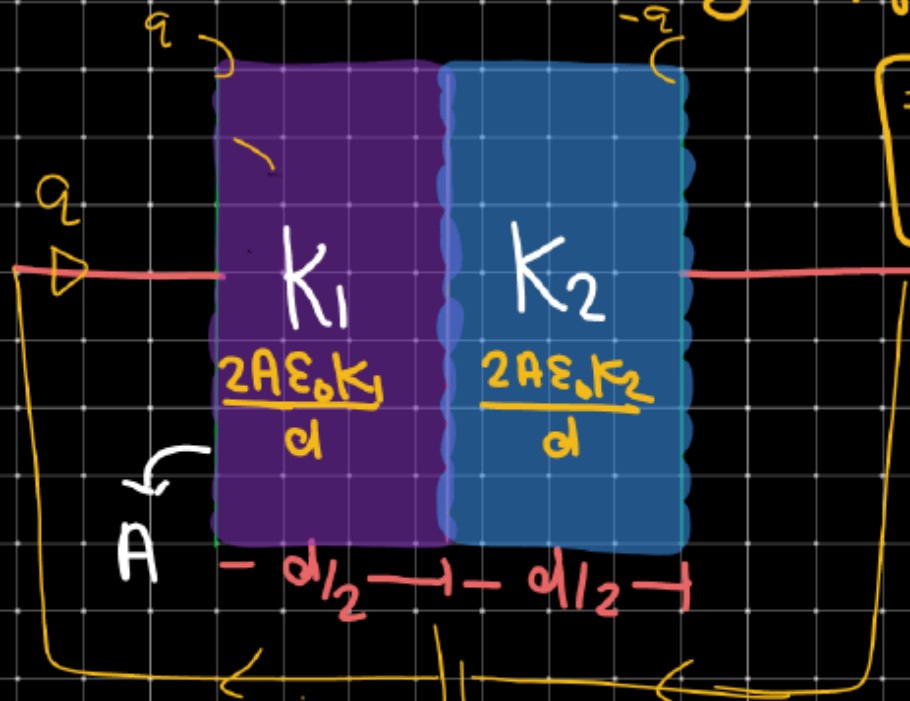
# Equivalent Capacitance of different PPC System



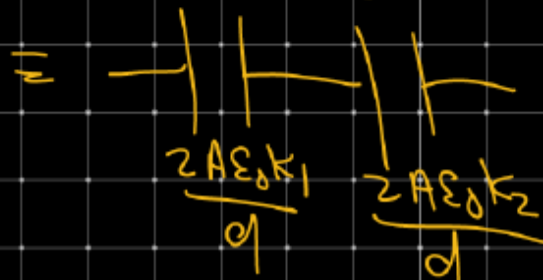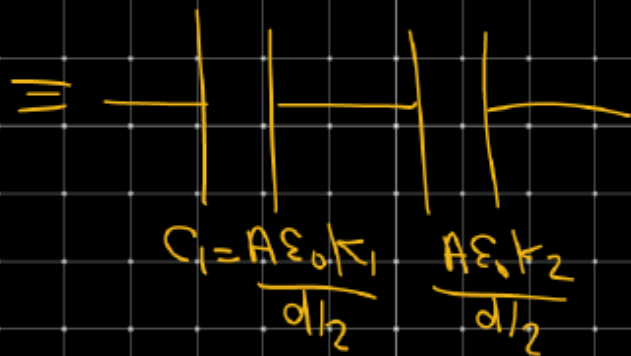⇒ In Series bcz charge flow on both are same.



$$\frac{1}{C_g} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C_g} = \frac{d}{2A\epsilon_0 K_1} + \frac{d}{2A\epsilon_0 K_2}$$



$$\frac{1}{C_{eq}} = \frac{d}{2A\epsilon_0 K_1} + \frac{d}{2A\epsilon_0 K_2}$$

$$\frac{1}{C_{eq}} = \frac{d}{2A\epsilon_0} \left[ \frac{1}{K_1} + \frac{1}{K_2} \right]$$

$$\frac{1}{C_{eq}} = \frac{d}{2A\epsilon_0} \left[ \frac{K_2 + K_1}{K_1 K_2} \right]$$

$$C_{eq} = \frac{2A\epsilon_0}{d} \left[ \frac{K_1 K_2}{K_1 + K_2} \right]$$

$$K_{eq} = \frac{2K_1 K_2}{K_1 + K_2}$$

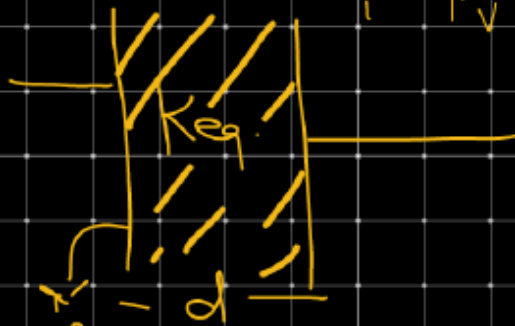
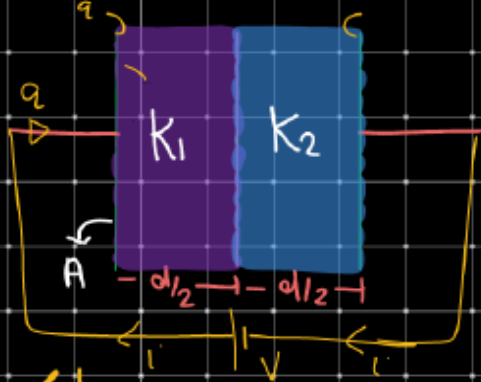


$$\cancel{\frac{A\epsilon_0}{d} K_{eq}} = \frac{2A\epsilon_0}{d} \left[ \frac{K_1 K_2}{K_1 + K_2} \right]$$

# Find  $C_{eq}$  &  $K_{eq}$   $\frac{A/2 \epsilon_0 K_1}{d/2} = \frac{A \epsilon_0 K_1}{d}$

$$\frac{1}{C_1} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} P$$

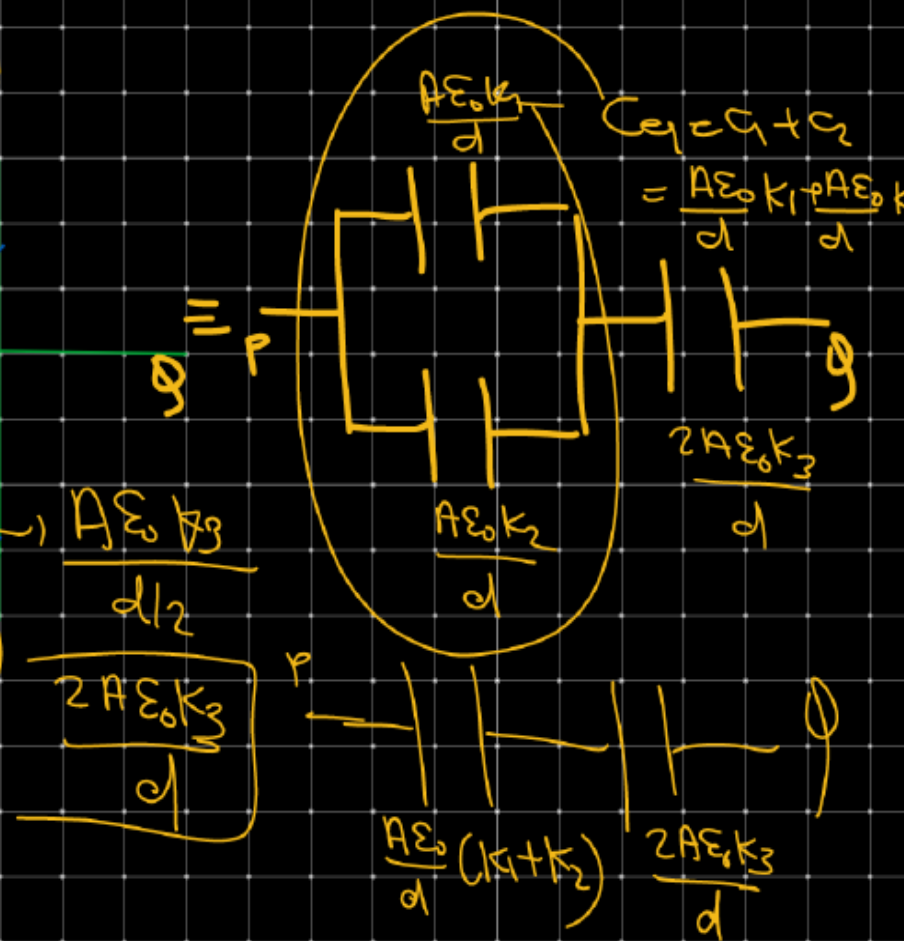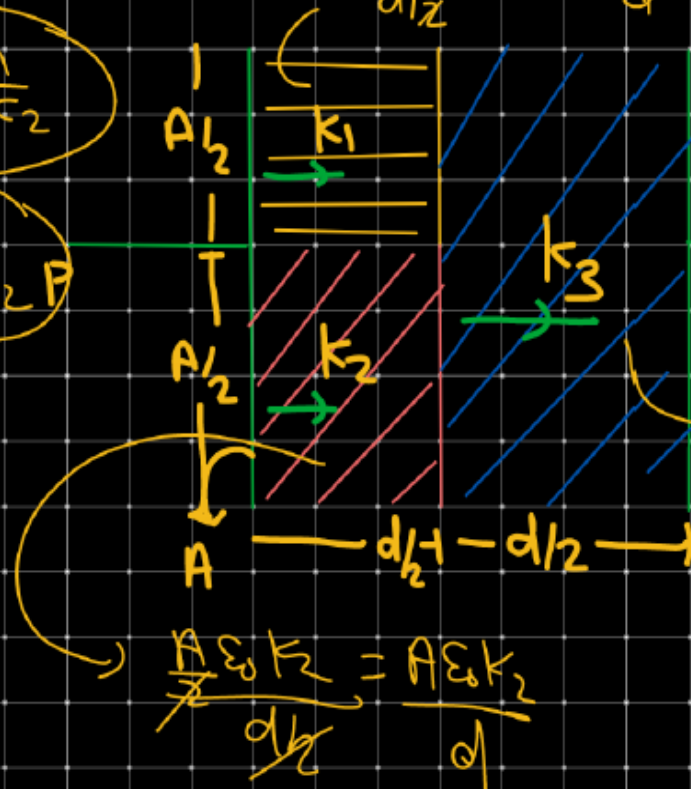


$$\frac{A \epsilon_0 K_2}{d/2} = \frac{A \epsilon_0 K_2}{d}$$


$$\frac{2 A \epsilon_0 K_3}{d}$$

$$\frac{A \epsilon_0}{d} (K_1 + K_2)$$

$$\frac{2 A \epsilon_0 K_3}{d}$$

# ⊛ Connection of Capacitors:

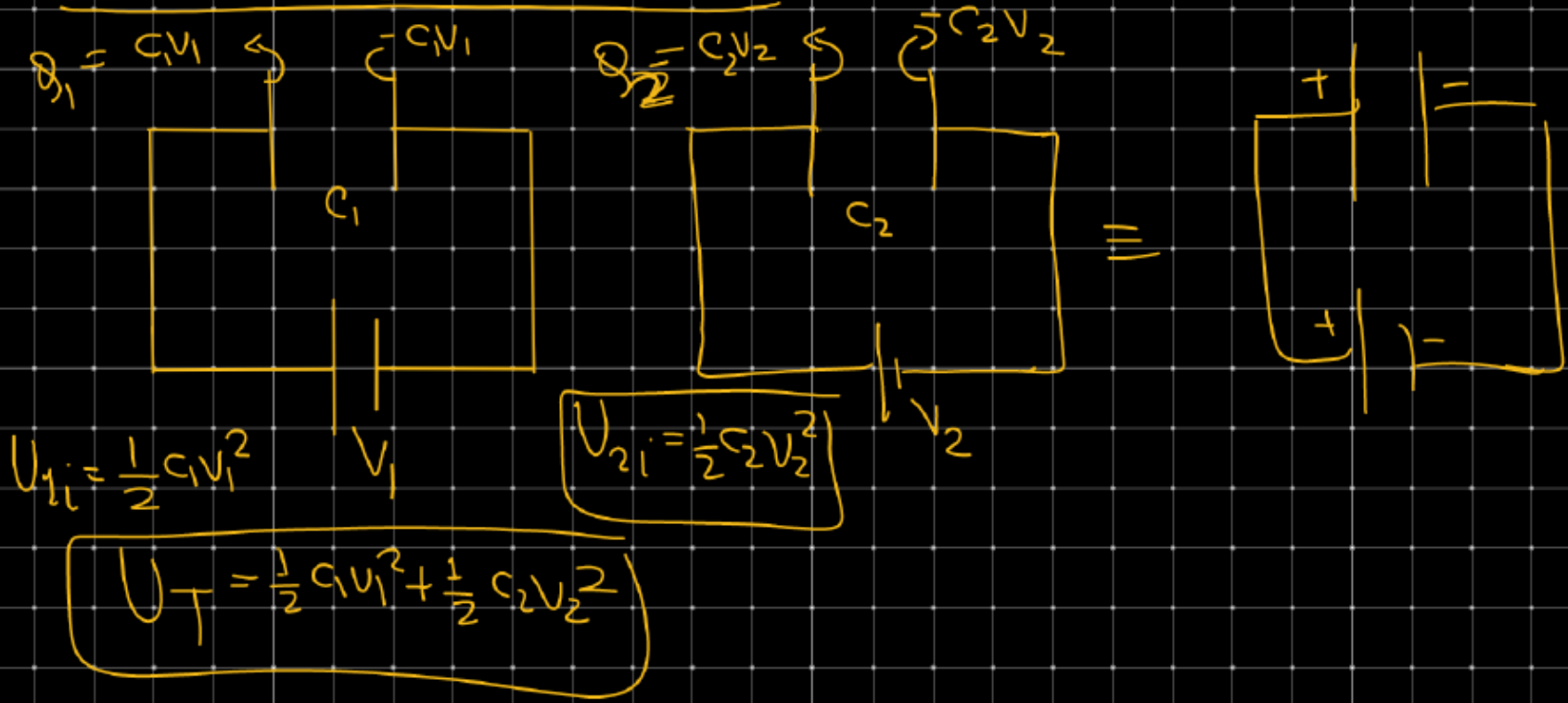

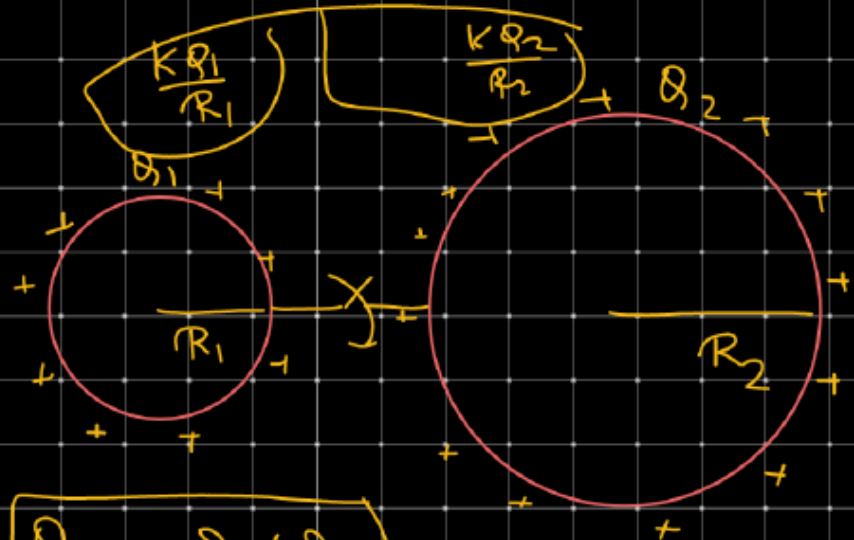

$$Q_{iT} = Q_1 + Q_2$$


$$Q_1 + Q_2 = Q_1' + Q_2'$$

$$Q_1 + Q_2 = \frac{Q_2' R_1}{R_2} + Q_2'$$

$$Q_2' = \left( \frac{R_2}{R_1 + R_2} \right) (Q_1 + Q_2)$$

$$\frac{KQ_1'}{R_1} = \frac{KQ_2'}{R_2}$$

$$Q_1' = \frac{Q_2' R_1}{R_2}$$

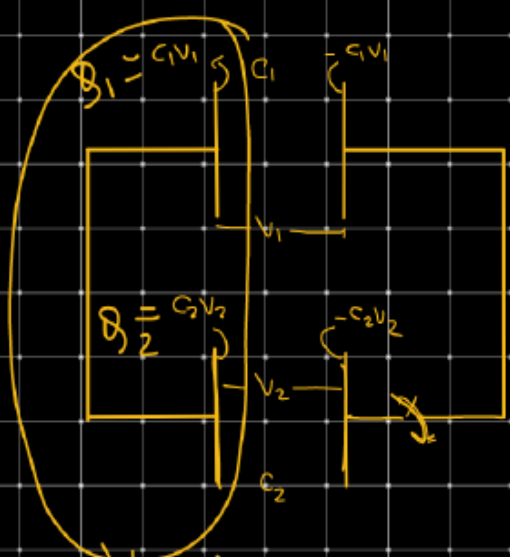


$V_1 < V_2$

$$Q_1 + Q_2 = C_1V_1 + C_2V_2$$

$$C_1V_1 + C_2V_2 = C_1V + C_2V$$
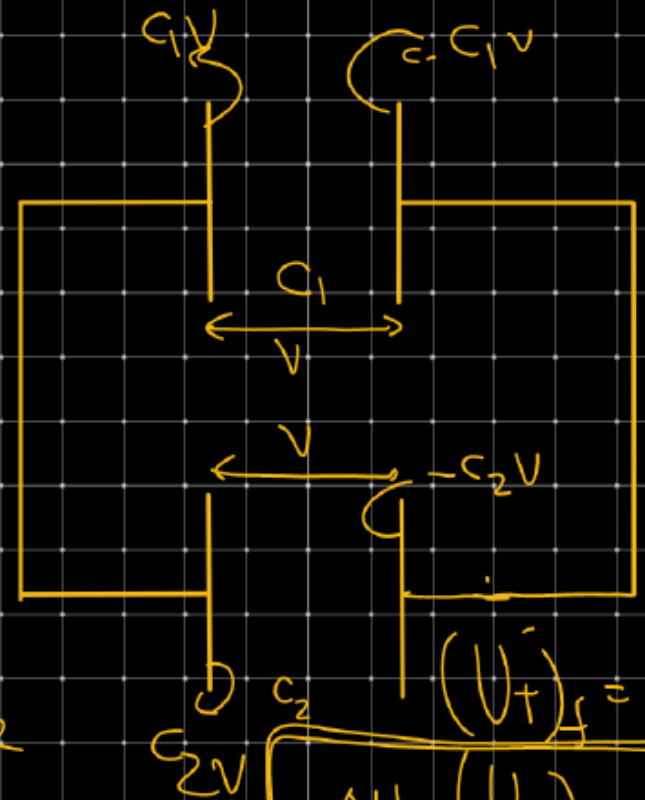
$$(U_T)_i = \frac{1}{2}C_1V_1^2 + \frac{1}{2}C_2V_2^2$$






$$V_{\text{Common}} = \frac{C_1V + C_2V}{C_1 + C_2}$$

$$V_{\text{Common}} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

$$(U_T)_f = \frac{1}{2}C_1V^2 + \frac{1}{2}C_2V^2$$

$$\Delta H = (U_T)_i - (U_T)_f$$



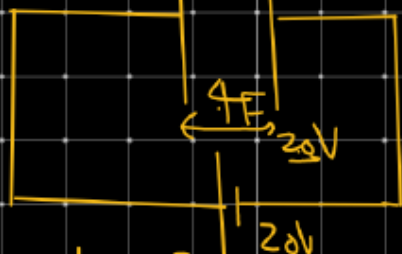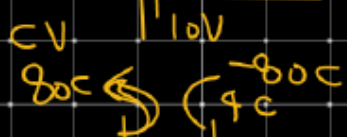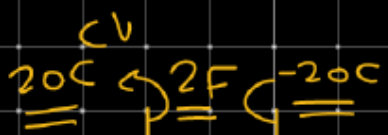

$$\begin{aligned}
 (U_f)_i &= \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \\
 &= \frac{1}{2} \times 2 \times 10^2 + \frac{1}{2} \times 2 \times 20^2 \\
 &= 100 + 2 \times 200 = 500 \text{ J}
 \end{aligned}$$

Q1) +ve plate of Capacitor 1 is connected with +ve plate of Capacitor 2.

- ① find  $V_{\text{common}}$  ②  $\Delta H$ . ③ final charge on Capacitors.


$$\begin{aligned}
 \frac{50}{3} \times 2 & \leftarrow 2V \\
 & = 100/3
 \end{aligned}$$

$$\Delta H = (U_f)_f - (U_f)_i$$

$$\begin{aligned}
 &= 900 - 833 \\
 &= 67.7 \text{ J}
 \end{aligned}$$

$$\frac{4 \times 50}{3}$$

$$\frac{200}{3}$$

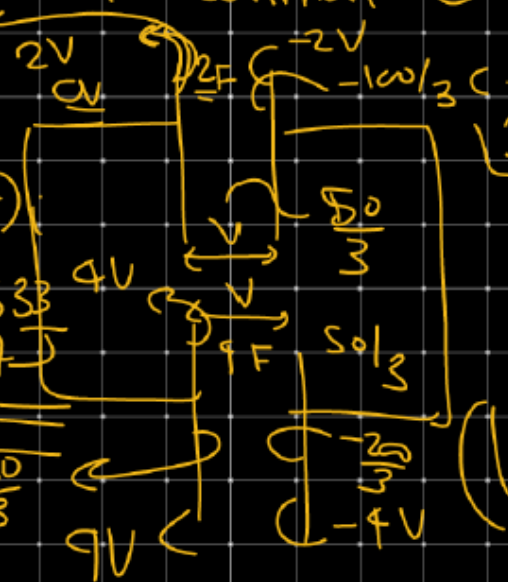

$$20 + 80 = 2V + 4V$$

$$100 = 6V$$


$$V = \frac{100}{6} = \frac{50}{3} \text{ Volt}$$

$$(U_f)_f = \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2$$


$$= \frac{1}{2} (C_1 + C_2) V^2$$

$$\begin{aligned}
 &= \frac{1}{2} \times 6 \times \left(\frac{50}{3}\right)^2 \\
 &= \frac{1}{2} \times \frac{2500}{3} = 833.33 \text{ J}
 \end{aligned}$$


# # Equivalent Capacitance:-

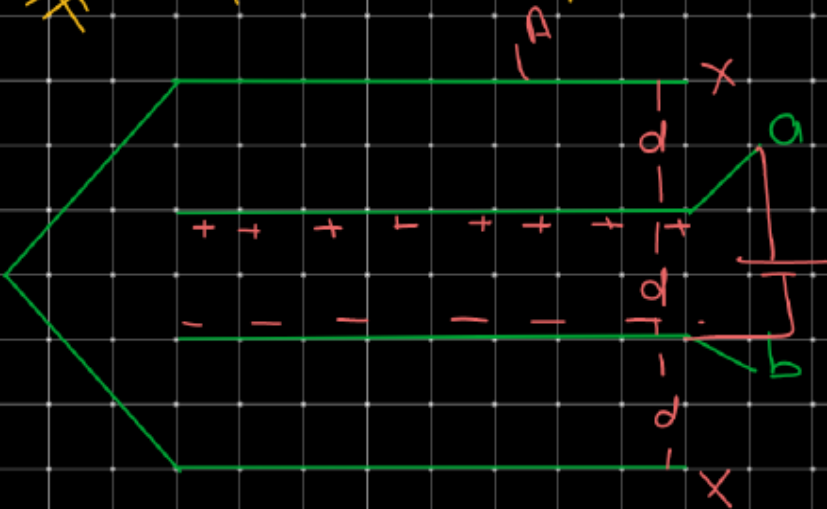


find  $C_{eq}$  b/w a & b.

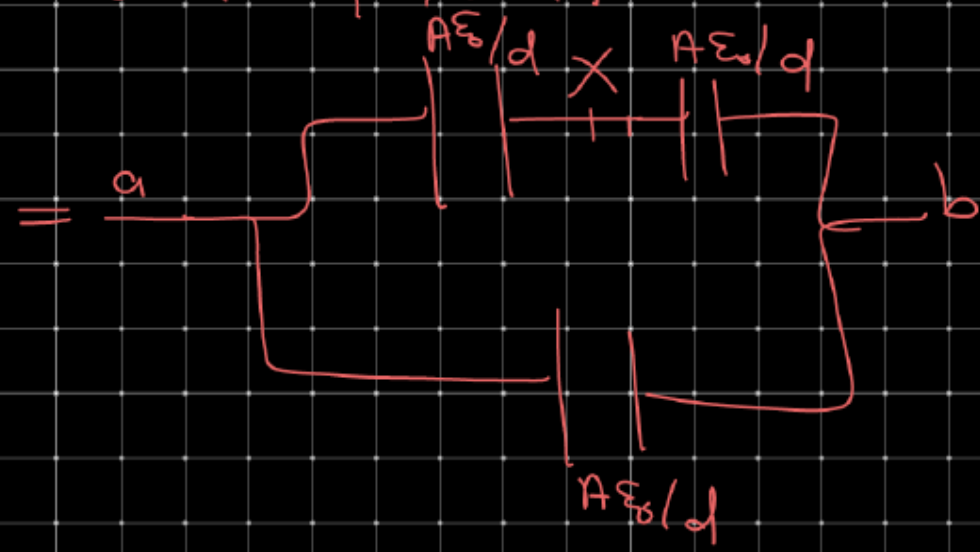

Find  $C_{eq}$  b/w a & b.

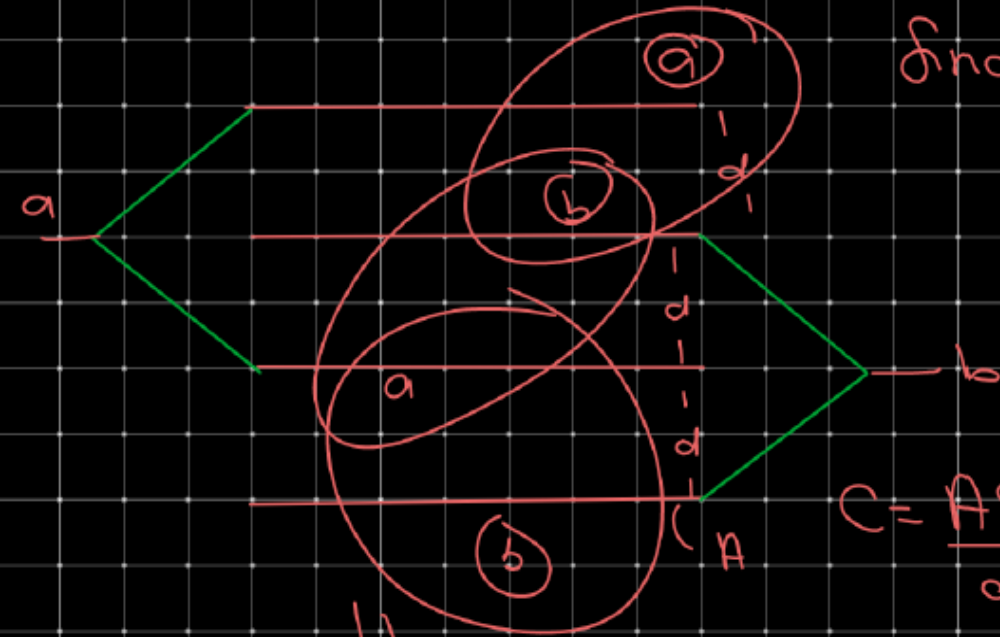

$$C = \frac{A\epsilon_0}{d}$$

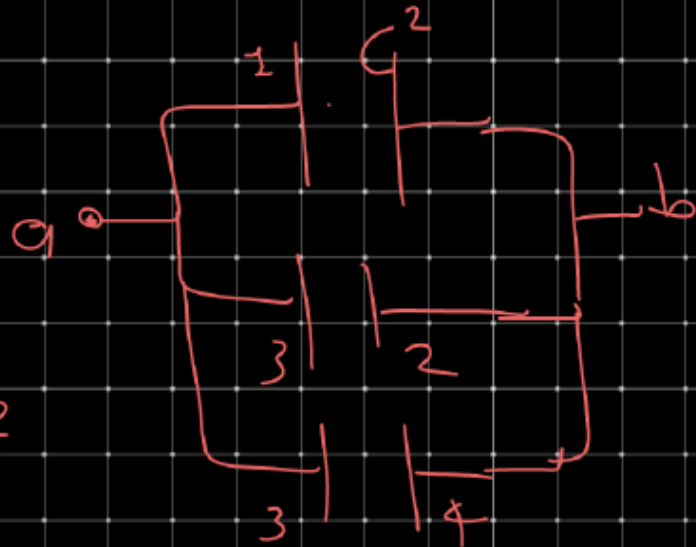

$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = \frac{3A\epsilon_0}{d}$$