

A flow of  $10^7$  electrons per second in a conducting wire constitutes a current of

- (a)  $1.6 \times 10^{-12}$  A                      (b)  $1.6 \times 10^{26}$  A  
 (c)  $1.6 \times 10^{-26}$  A                      (d)  $1.6 \times 10^{12}$  A

$$i = \frac{q}{t} = \frac{1.6 \times 10^{-12} \text{ e/sec}}{1} = \text{A}$$

$$i = 1.6 \times 10^{-12} \text{ A}$$

$10^7$  electron per second

$$q = ne$$

$$= 10^7 \times 1.6 \times 10^{-19} \text{ C}$$

$$q = 1.6 \times 10^{-12} \text{ C}$$

A charged particle having drift velocity of  $7.5 \times 10^{-4} \text{ m s}^{-1}$  in an electric field of  $3 \times 10^{-10} \text{ V m}^{-1}$ , has a mobility in  $\text{m}^2 \text{ V}^{-1} \text{ s}^{-1}$  of

(a)  $2.25 \times 10^{15}$

(c)  $2.5 \times 10^{-6}$

NEET-2020/19.

~~(b)  $2.5 \times 10^6$~~

(d)  $2.25 \times 10^{-15}$

$$V_d = 7.5 \times 10^{-4} \text{ m/s}$$

$$E = 3 \times 10^{-10} \text{ V/m}$$

$$M = \frac{V_d}{E} = \frac{7.5 \times 10^{-4}}{3 \times 10^{-10}}$$

$$M = \frac{7.5}{3} \times 10^{-4+10}$$

$$= \frac{7.5}{3} \times 10^6 = \underline{\underline{2.5 \times 10^6}}$$

Specific resistance of a conductor increases with

- ~~(a)~~ increase in temperature
- (b) increase in cross-section area
- (c) increase in cross-section and decrease in length
- (d) decrease in cross-section area.

$$g = \frac{m}{ne^2\tau}$$

$$\begin{array}{ccc} \tau \uparrow & \tau \downarrow & g \uparrow \\ \tau \downarrow & \tau \uparrow & g \downarrow \end{array}$$

Two bulbs are of (40 W, 200 V), and (100 W, 200 V). Then correct relation for their resistances is

- (a)  $R_{40} < R_{100}$
- ~~(b)~~  $R_{40} > R_{100}$
- (c)  $R_{40} = R_{100}$
- (d) no relation can be predicted.

$$R_{100} = \frac{200 \times 200}{100}$$

$$R_{100} = 400 \Omega$$

$$\boxed{40 \text{ W, } 200 \text{ V}}$$

$$P = \frac{V^2}{R} \quad R = \frac{V^2}{P}$$

$$R_{40} = \frac{200 \times 200}{40} = 1000 \Omega$$

An electric bulb is rated 60 W, 220 V.

The resistance of its filament is

(a)  $870 \Omega$

(b)  $780 \Omega$


(c)  $708 \Omega$

(d)  $807 \Omega$


$$R = \frac{220 \times 220}{60}$$

$$R = \frac{22 \times 110}{3}$$

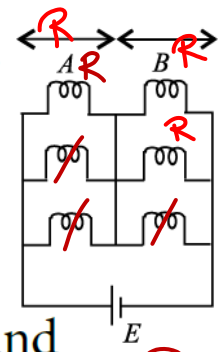Six similar bulbs are connected as shown in the figure with a DC source of emf  $E$ , and zero internal resistance. The ratio of power consumption by the bulbs when (i) all are glowing and (ii) in the situation when two from section A and one from section B are glowing, will be



$$P = \frac{V^2}{R}$$

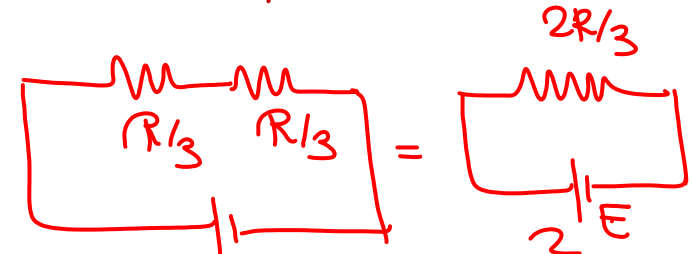


$$P = \frac{E^2 \times 3}{2R}$$

$$\frac{P_1}{P_2} = \frac{3E^2 \times 3 \times 2}{2R \times 2R} = \frac{9}{4}$$


$$P = \frac{3E^2}{2R}$$

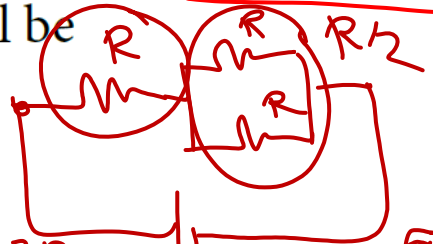- (a) 2 : 1
- (b) 4 : 9
- (c) 9 : 4
- (d) 1 : 2



$$R + \frac{R}{2} = \frac{3R}{2} \quad P_2 = \frac{E^2 \times 2}{3R}$$

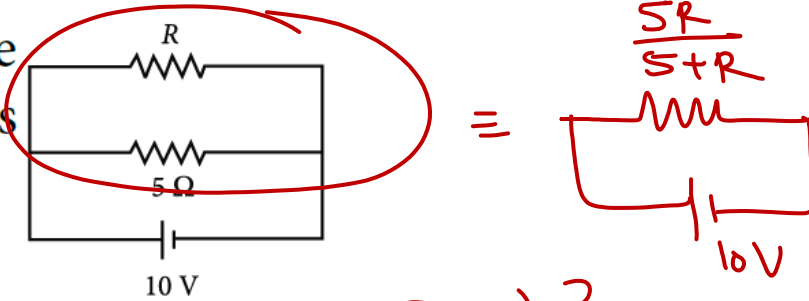The power dissipated in the circuit shown in the figure is 30 watts. The value of  $R$  is



- (a) 20  $\Omega$
- (b) 15  $\Omega$
- (c) 10  $\Omega$
- (d) 30  $\Omega$

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{5}$$

$$R_{eq} = \frac{SR}{(S+R)}$$

$$P = \frac{V^2}{R} = \frac{100(S+R)}{SR}$$

$$30 = \frac{500 + 100R}{SR}$$

$$150R = 500 + 100R$$


$$50R = 500$$

$$R = 10\Omega$$

# Rating

Two 220 volt, 100 watt bulbs are connected first in series and then in parallel. Each time the combination is connected to a 220 volt a.c. supply line. The power drawn by the combination in each case respectively will be

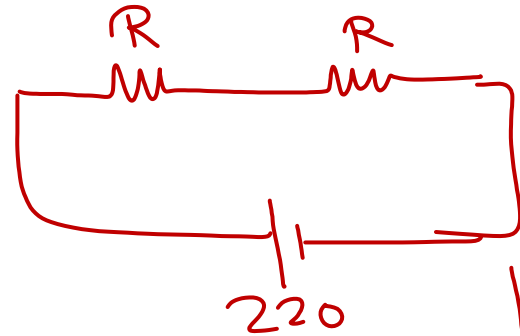
- (a) 50 watt, 100 watt
- (b) 100 watt, 50 watt
- (c) 200 watt, 150 watt
- (d) 50 watt, 200 watt



$$R = \frac{V^2}{P}$$

$$= \frac{220^2}{100}$$

$$R = 22 \times 22 \Omega$$

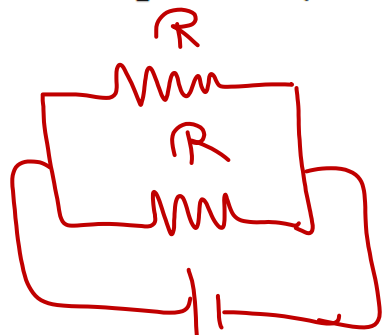

$$P_1 = \frac{V^2}{R}$$

$$= \frac{220^2}{22 \times 22}$$

$$= 100 \text{ W}$$



$$P_2 = \frac{220^2 \times 2}{10R}$$


$$= \frac{220^2 \times 2}{22 \times 22} = 100 \times 2 = 200 \text{ W}$$




A battery of e.m.f 10 V and internal resistance 0.5  $\Omega$  is connected across a variable resistance  $R$ . The value of  $R$  for which the power delivered in it is maximum is given by

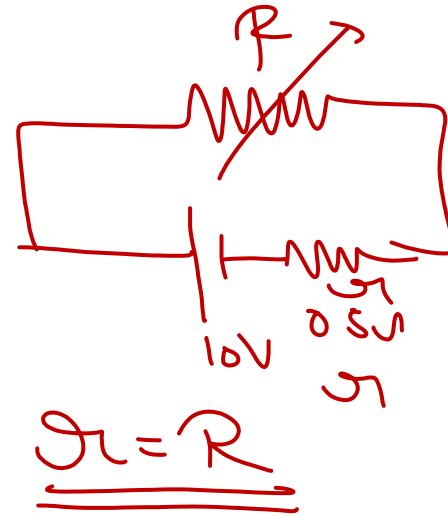- (a) 0.5  $\Omega$  (b) 1.0  $\Omega$   
(c) 2.0  $\Omega$  (d) 0.25  $\Omega$

$$\underline{\underline{R = 0.5 \Omega}}$$



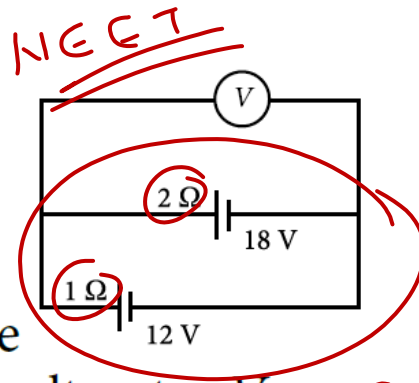Two batteries, one of emf 18 volts and internal resistance  $2\ \Omega$  and the other of emf 12 volts and internal resistance  $1\ \Omega$ , are connected as shown. The voltmeter  $V$  will record a reading of



$$E_{net} = \frac{E_1/r_1 + E_2/r_2}{\frac{1}{r_1} + \frac{1}{r_2}}$$


$$E_{net} = \frac{18/2 + 12/1}{\frac{1}{2} + \frac{1}{1}}$$

$$= \frac{(9+12) \cdot 2}{3}$$

$$= \frac{21 \times 2}{3} = \underline{\underline{14 \text{ Volt}}}$$

- (a) 30 volt
- (c) 15 volt


- (b) 18 volt
- (d) 14 volt

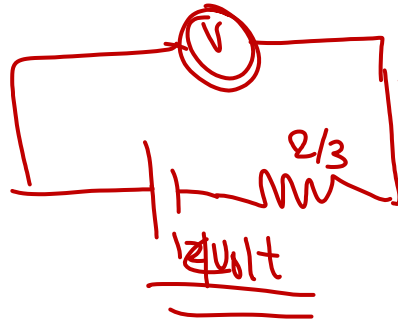

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>
<b>A</b>	<b>B</b>	<b>A</b>	<b>B</b>	<b>D</b>	<b>C</b>	<b>C</b>	<b>D</b>	<b>A</b>	<b>D</b>

# # Dielectric inside the PPC:-

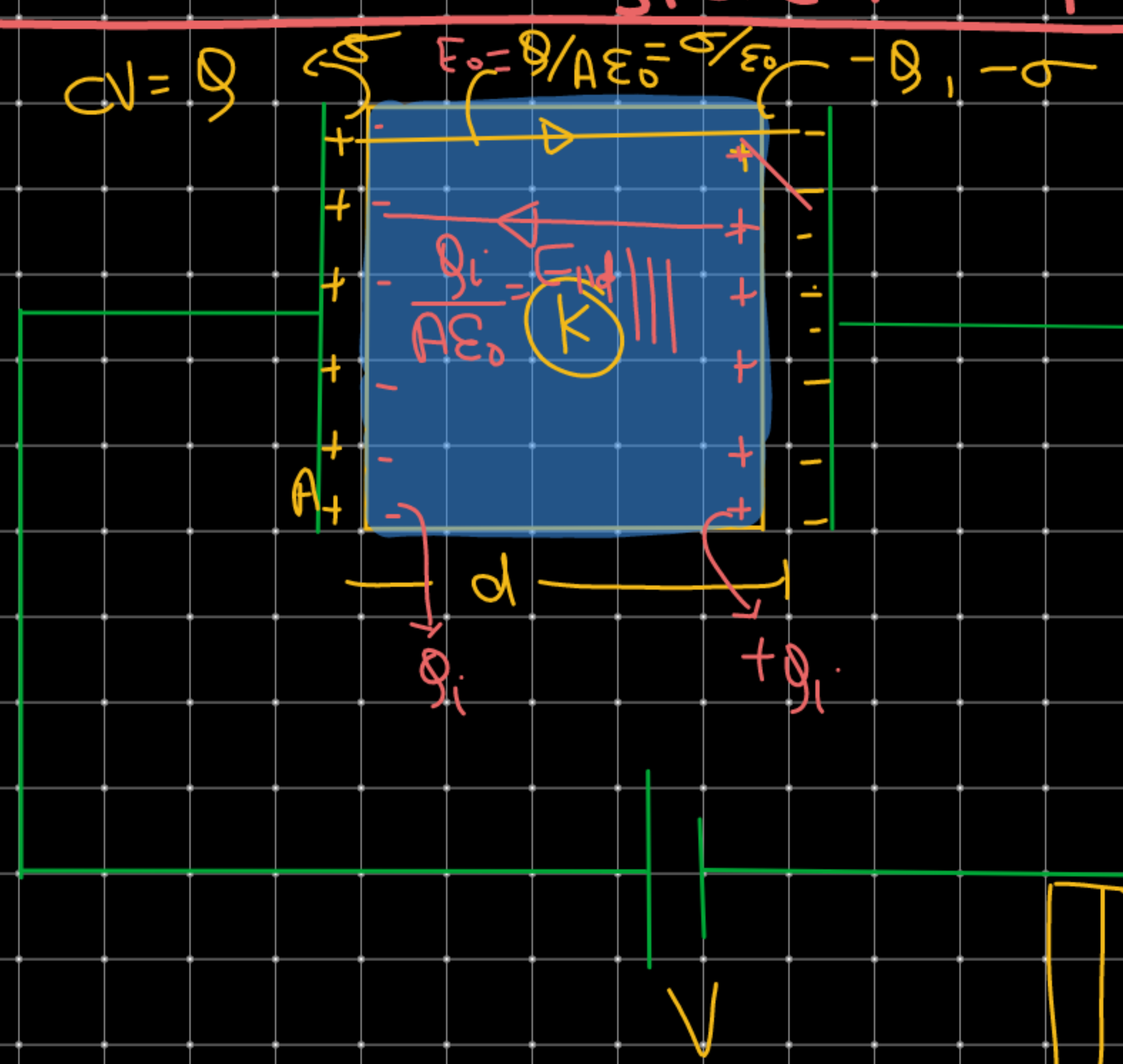

$$C = \frac{A\epsilon_0 K}{d}$$


$$\Rightarrow V = \frac{Q}{A\epsilon_0 K} = \frac{Q}{\epsilon_0 K}$$

$$E_{net} = E_0 - E_{ind}$$

$$Q_i = Q \left( \frac{1}{K} \right)$$

$$\frac{Q_i}{A} = \frac{Q}{A} \left( \frac{1}{K} \right)$$

$$Q_i = Q \left( \frac{1}{K} \right)$$

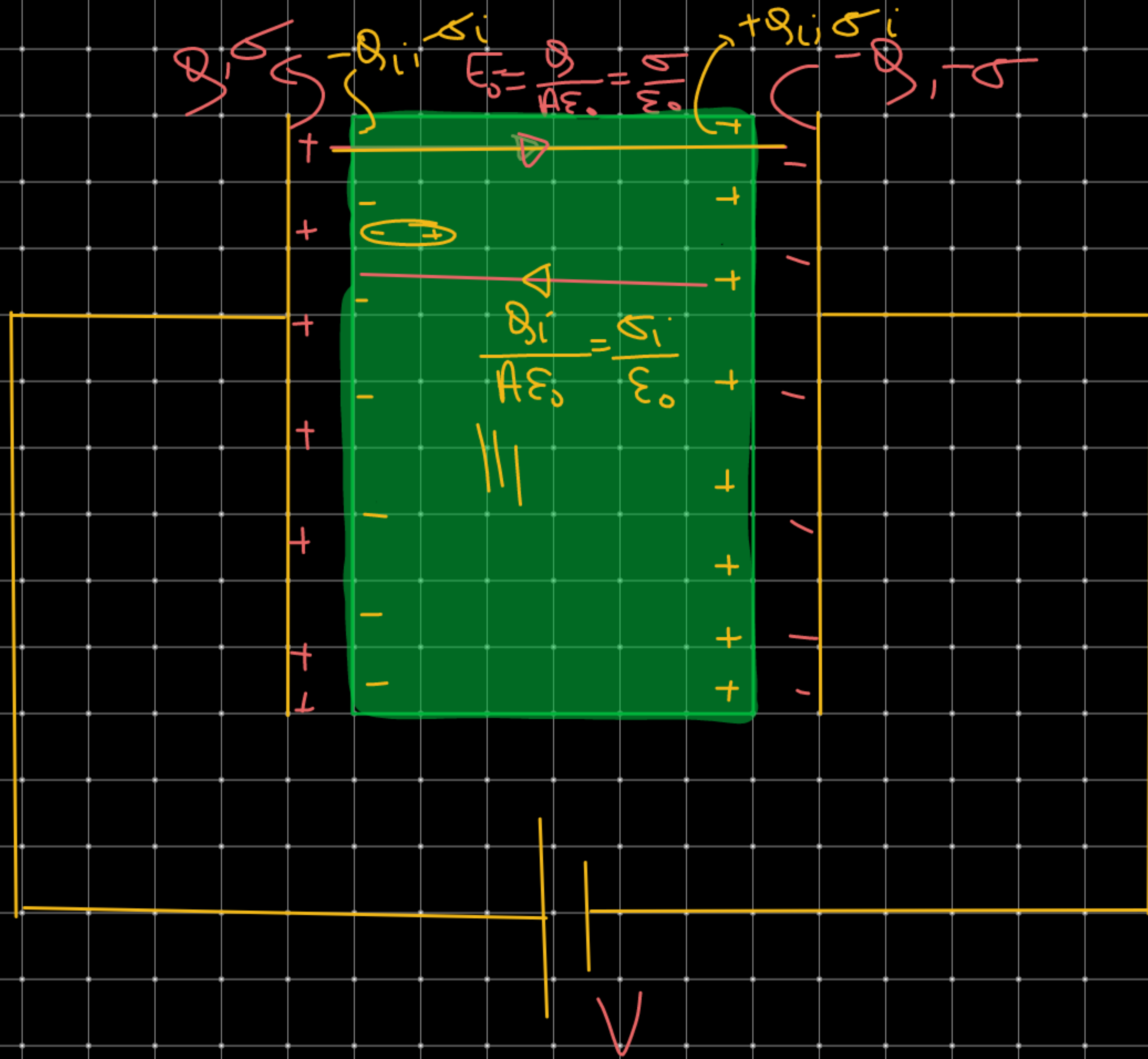


$$E_{med} = E_0 - E_{ind}$$

$$\frac{Q}{A \epsilon_0 K} = \frac{Q}{A \epsilon_0} - \frac{Q_{ind}}{A \epsilon_0}$$

$$Q/K = Q - Q_{ind}$$

$$Q_{ind} = Q - \frac{Q}{K}$$
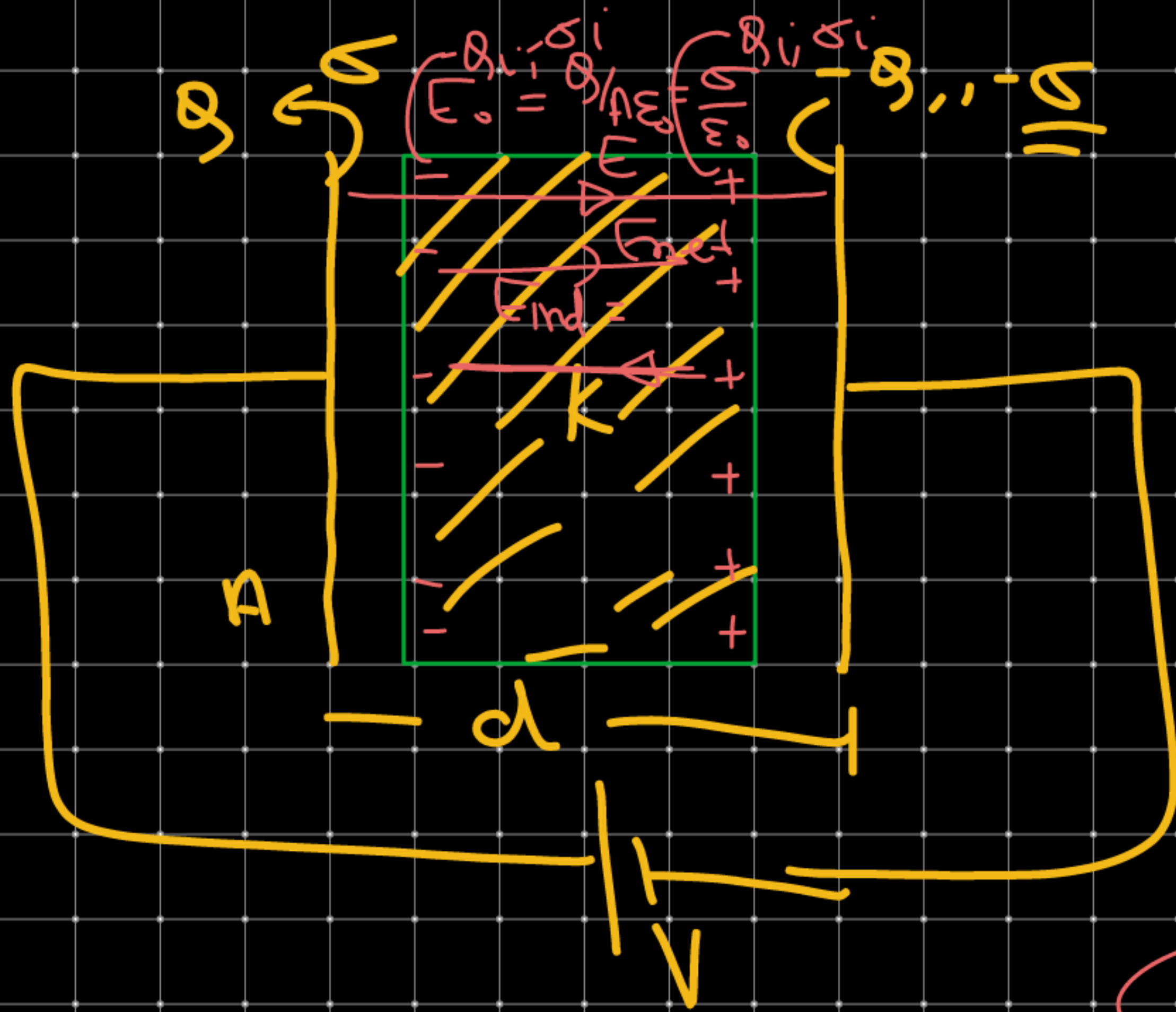
$$Q_{ind} = Q \left( 1 - \frac{1}{K} \right)$$



$$C = \frac{A\epsilon_0 K}{d}$$

$$E_{net} = E_0 - E_{ind}$$


$$\frac{Q}{A\epsilon_0 K} = \frac{Q}{A\epsilon_0} - \frac{Q_i}{A\epsilon_0}$$

$$\frac{Q_i}{A\epsilon_0} = \frac{Q}{A\epsilon_0} - \frac{Q}{A\epsilon_0 K}$$

$$Q_i = Q \left( 1 - \frac{1}{K} \right)$$

$$Q_i = Q \left( \frac{K-1}{K} \right)$$



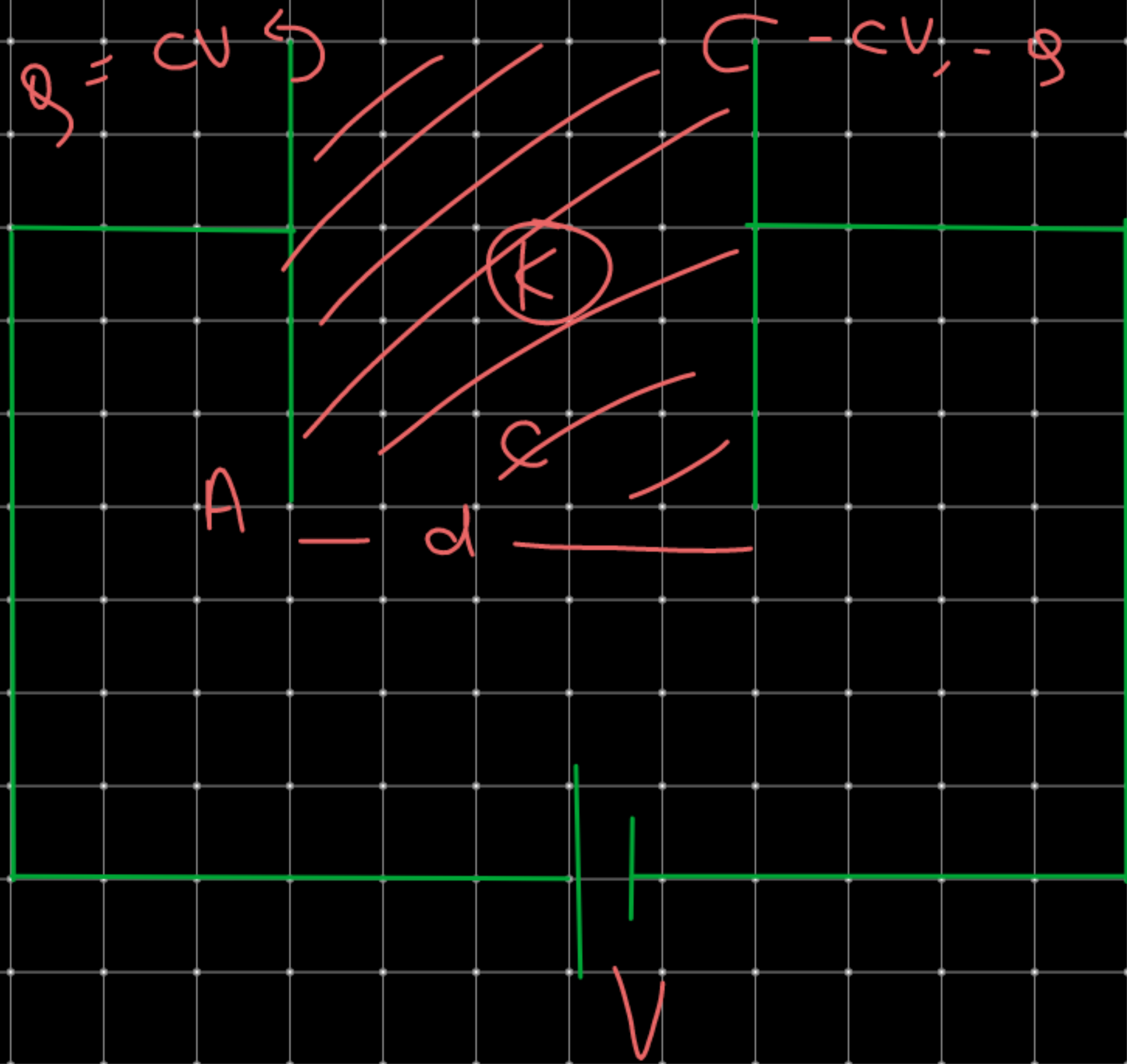



$$E = \frac{Q}{\epsilon_0 S} = \frac{Q}{\epsilon S}$$

$$U_0$$
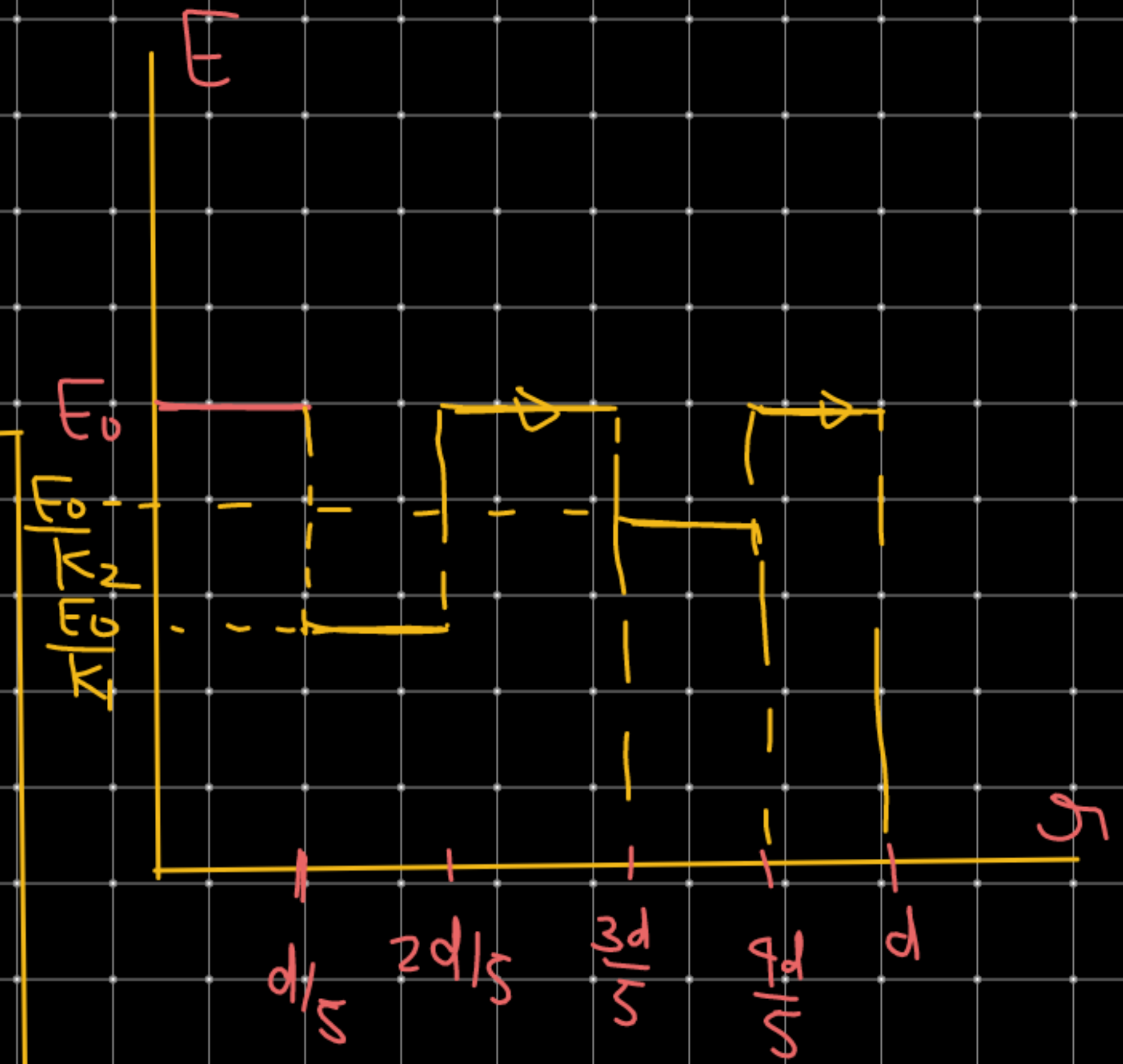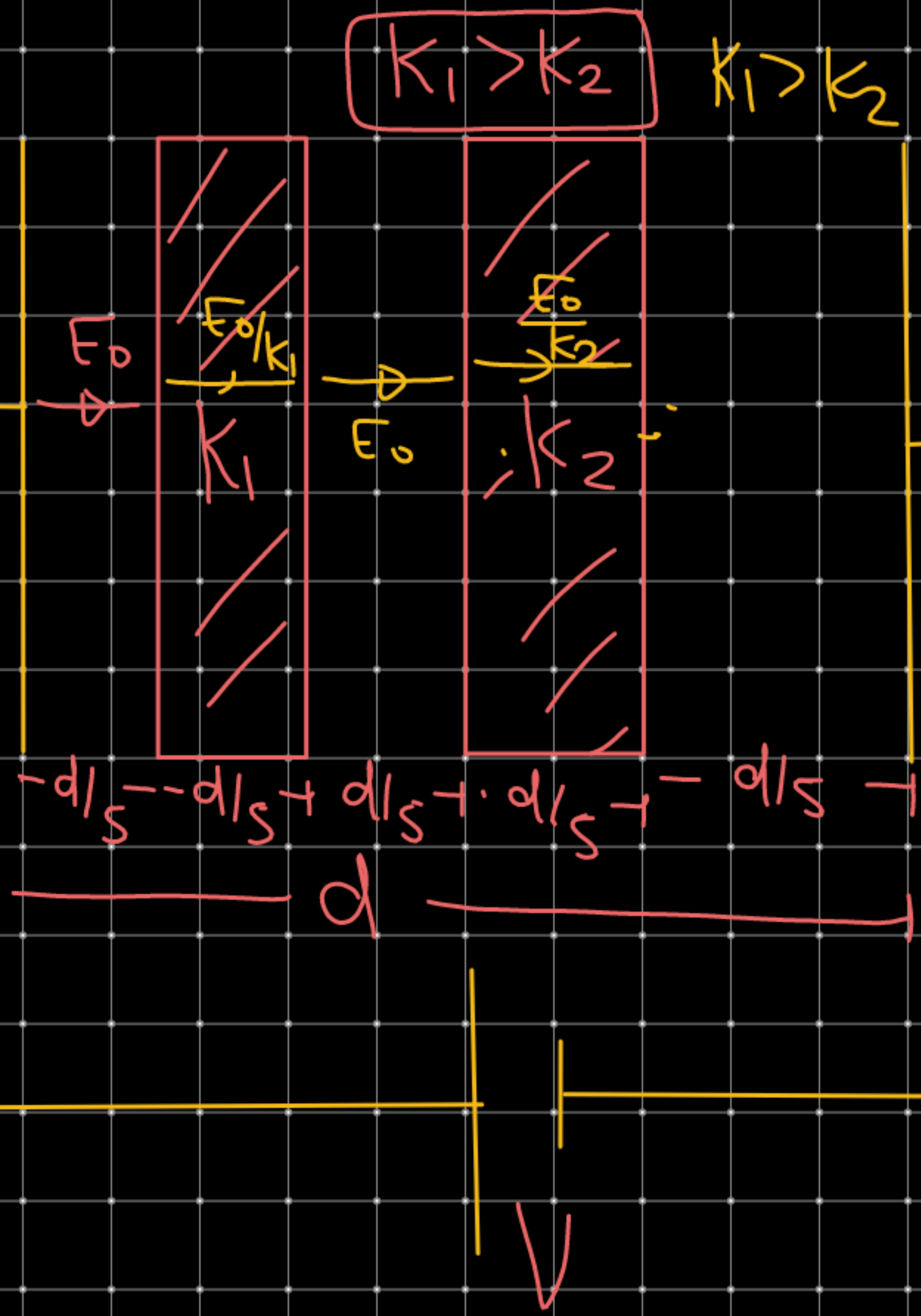
#1

$$E_{\text{net}} = \frac{Q}{\epsilon_0 K S}$$

$$E_0 = \frac{F_0}{AE_0} = \frac{\sigma}{E_0}$$






$$K_1 > K_2 > K_3$$

$$Q = CV$$


$$E_1 = E_4 > E_5 > E_3 > E_2$$

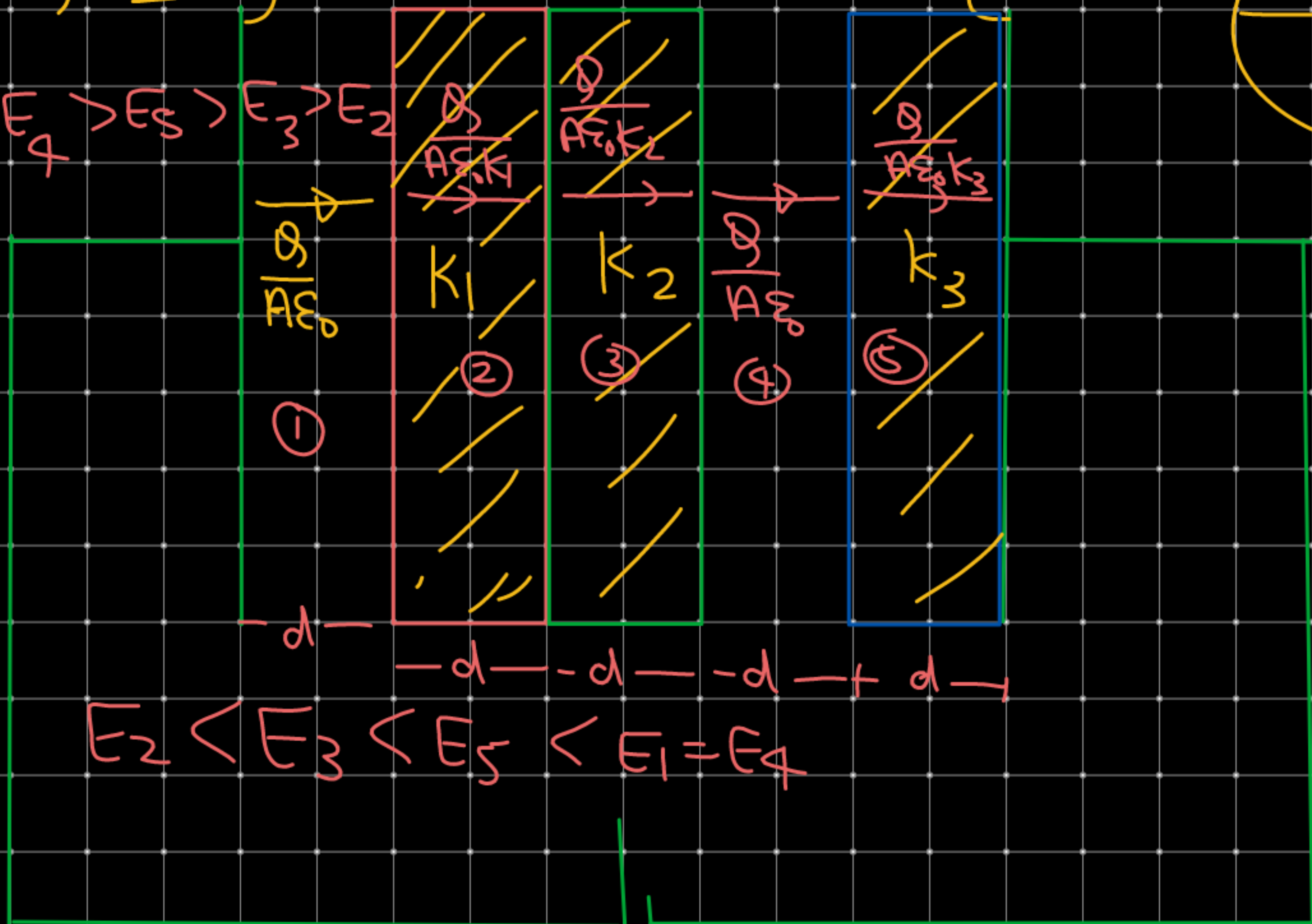


$$E_2 < E_3 < E_5 < E_1 = E_4$$



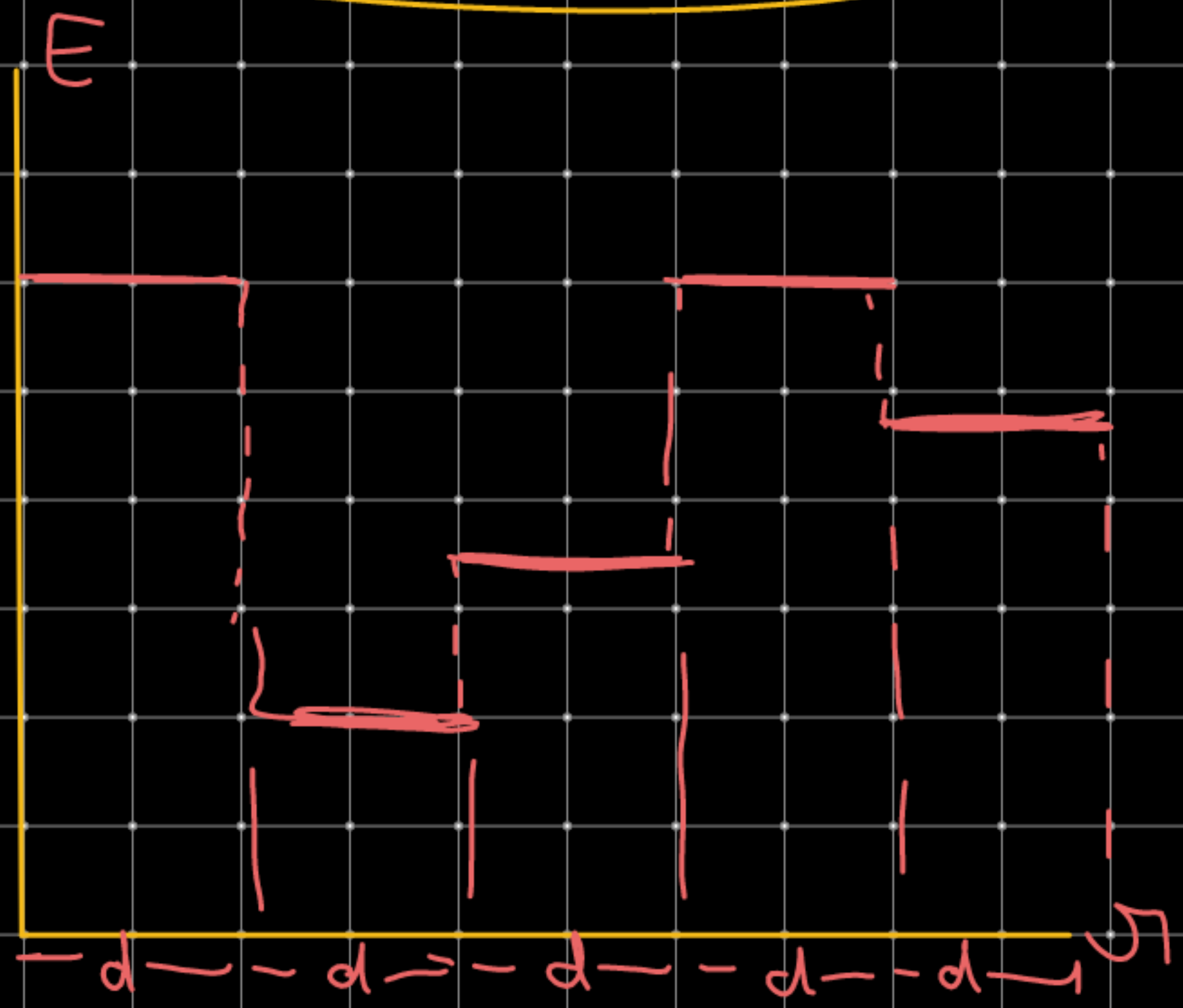
$$\frac{Q}{A} = \frac{Q}{A} = \frac{Q}{A}$$




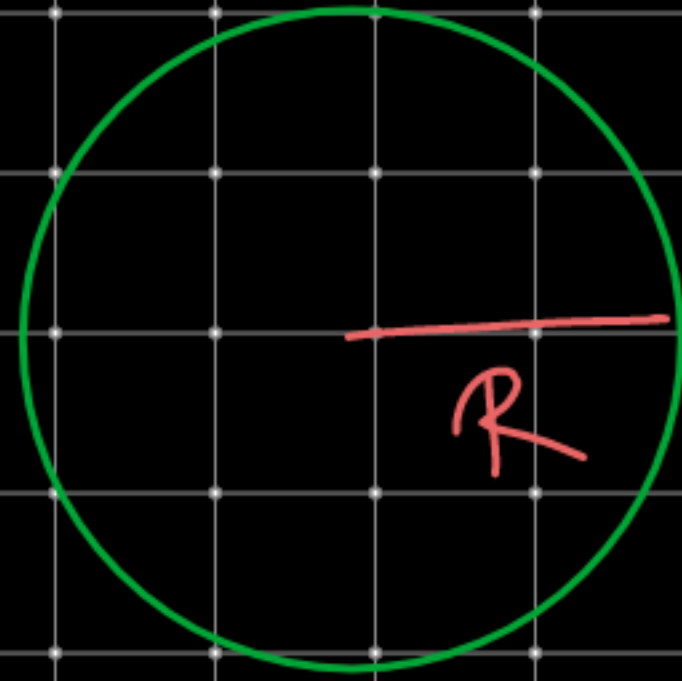

$$C = 4\pi\epsilon_0 R$$

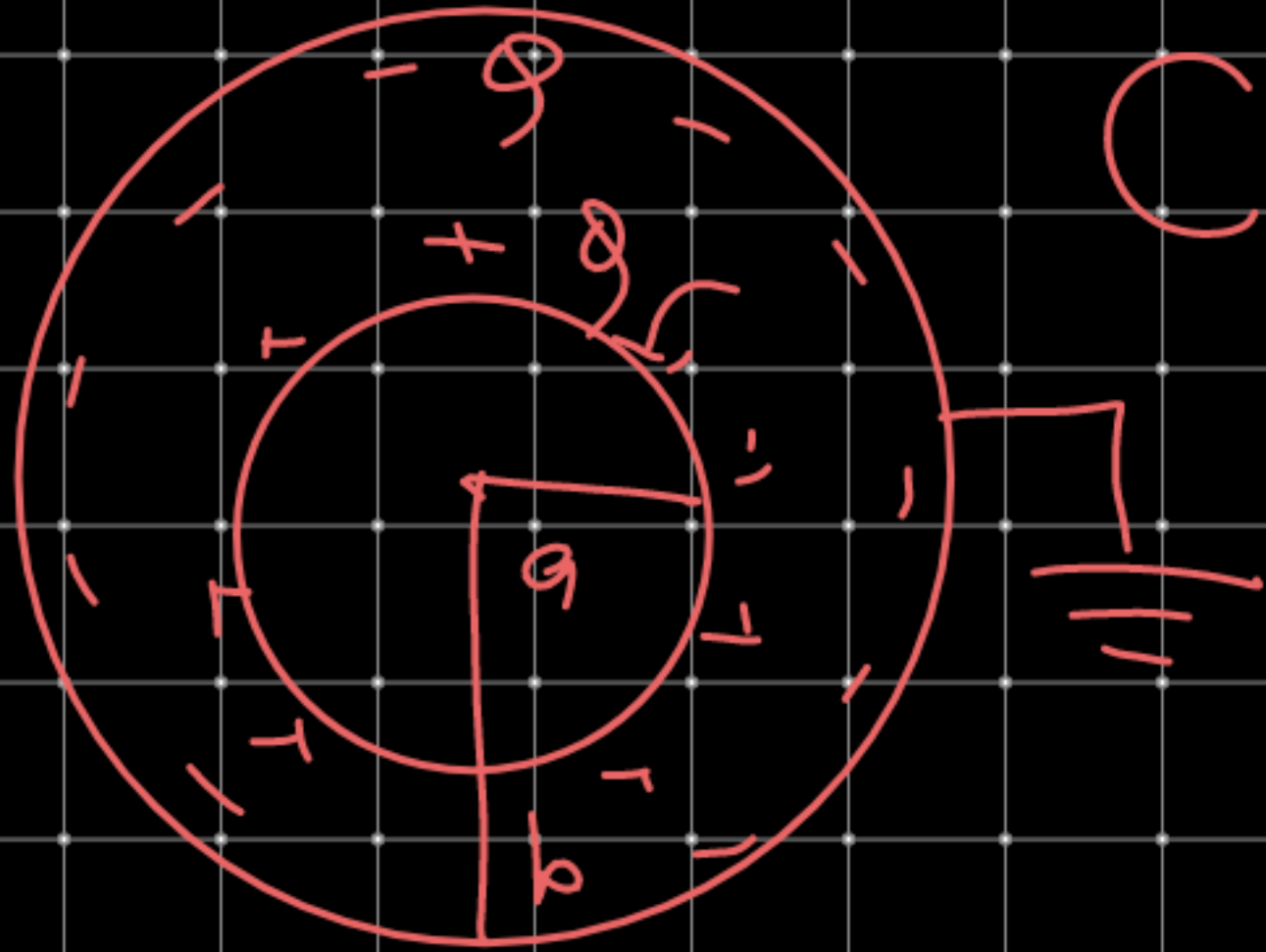
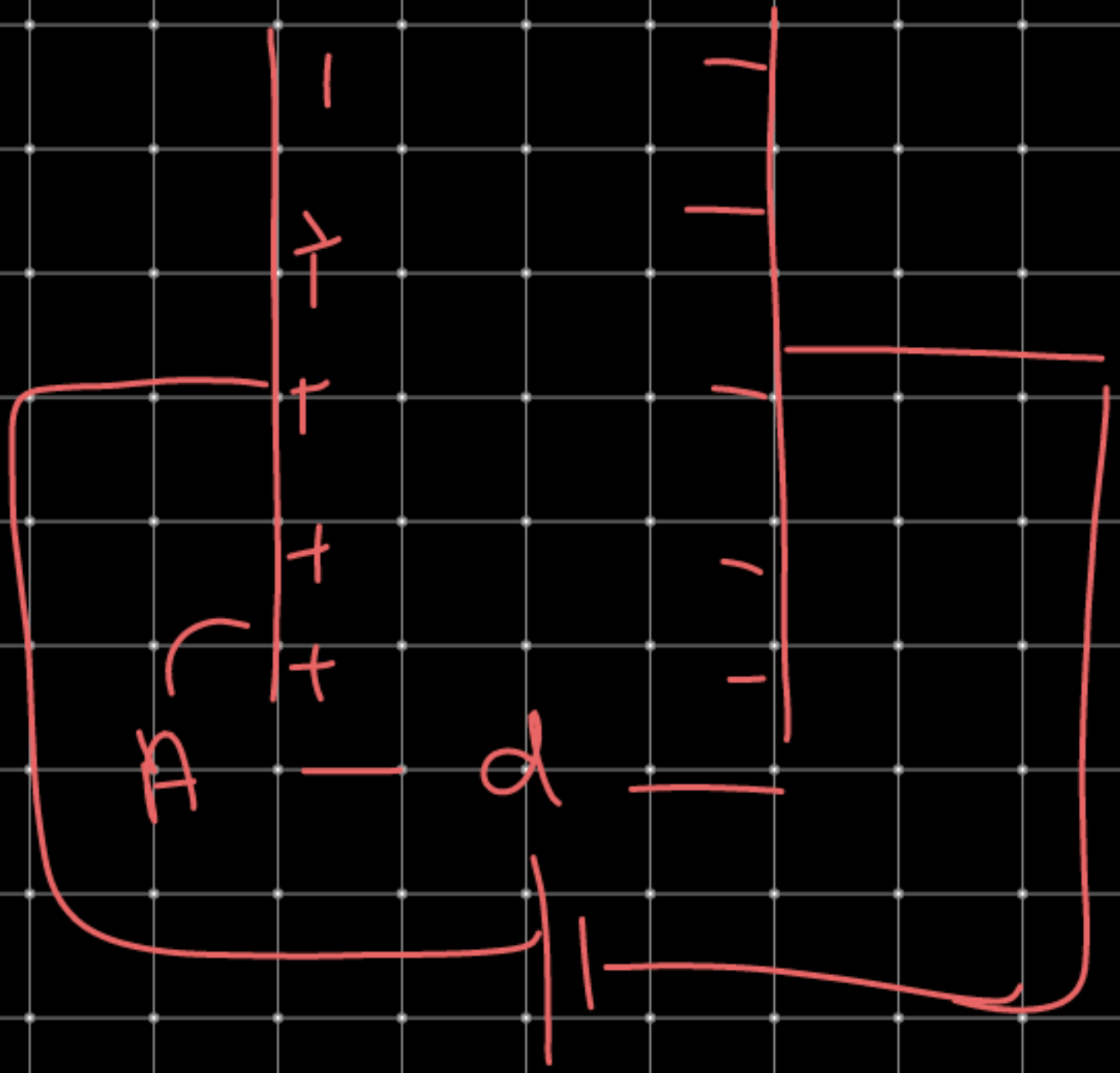
$$C = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$



$$C = \frac{A \epsilon_0}{d}$$
$$C_m = \frac{A \epsilon_0 K}{d}$$