

↳

$$q_i = \theta \left[1 - \frac{1}{\kappa} \right]$$

$$q_i = \theta \left(1 - \frac{1}{\kappa} \right)$$



Dielectric →

$$C_m = K C$$

Insulating material


Polar dielectric

Non-Polar dielectric

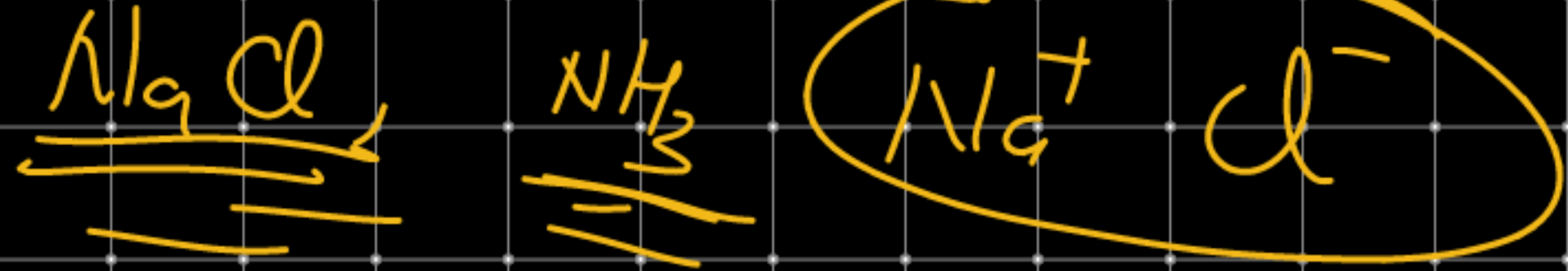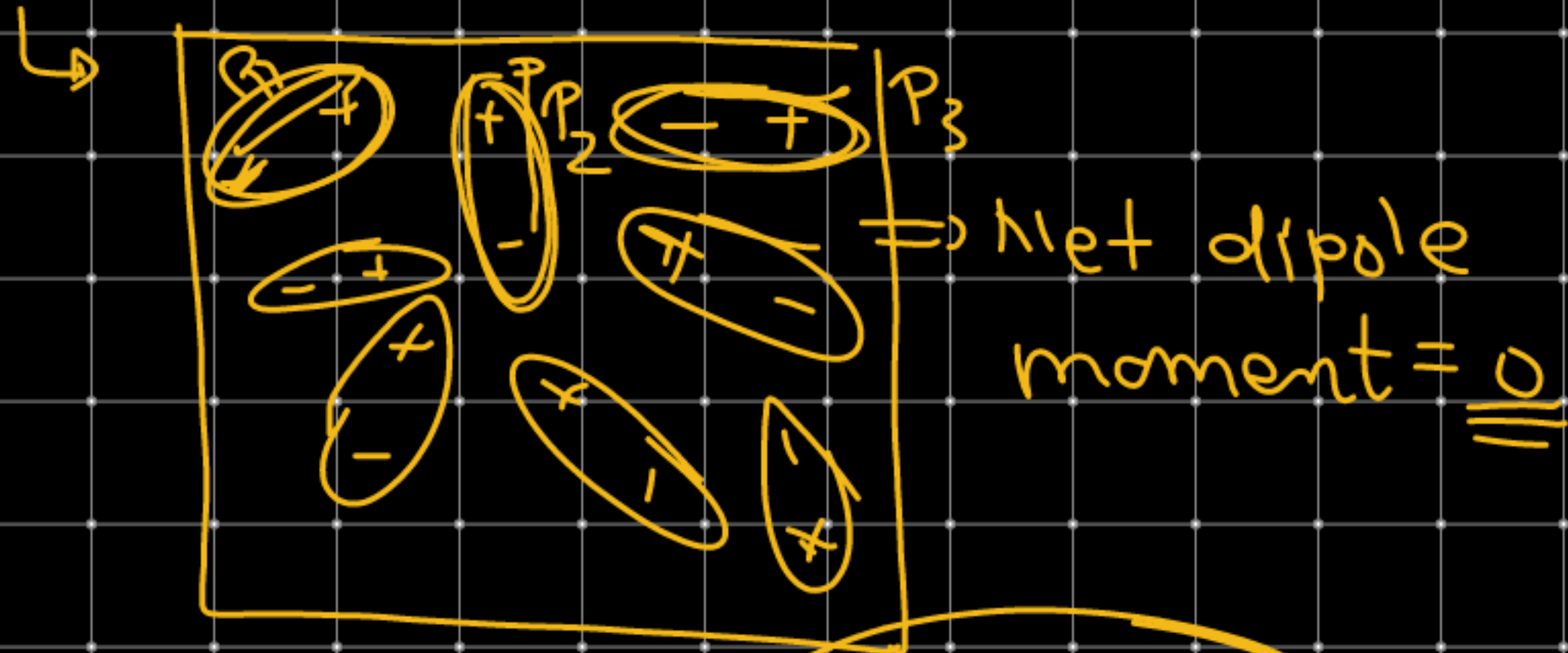


↳ When polar dielectric placed in uniform electric field.

$\text{Na}^+ \text{Cl}^-$

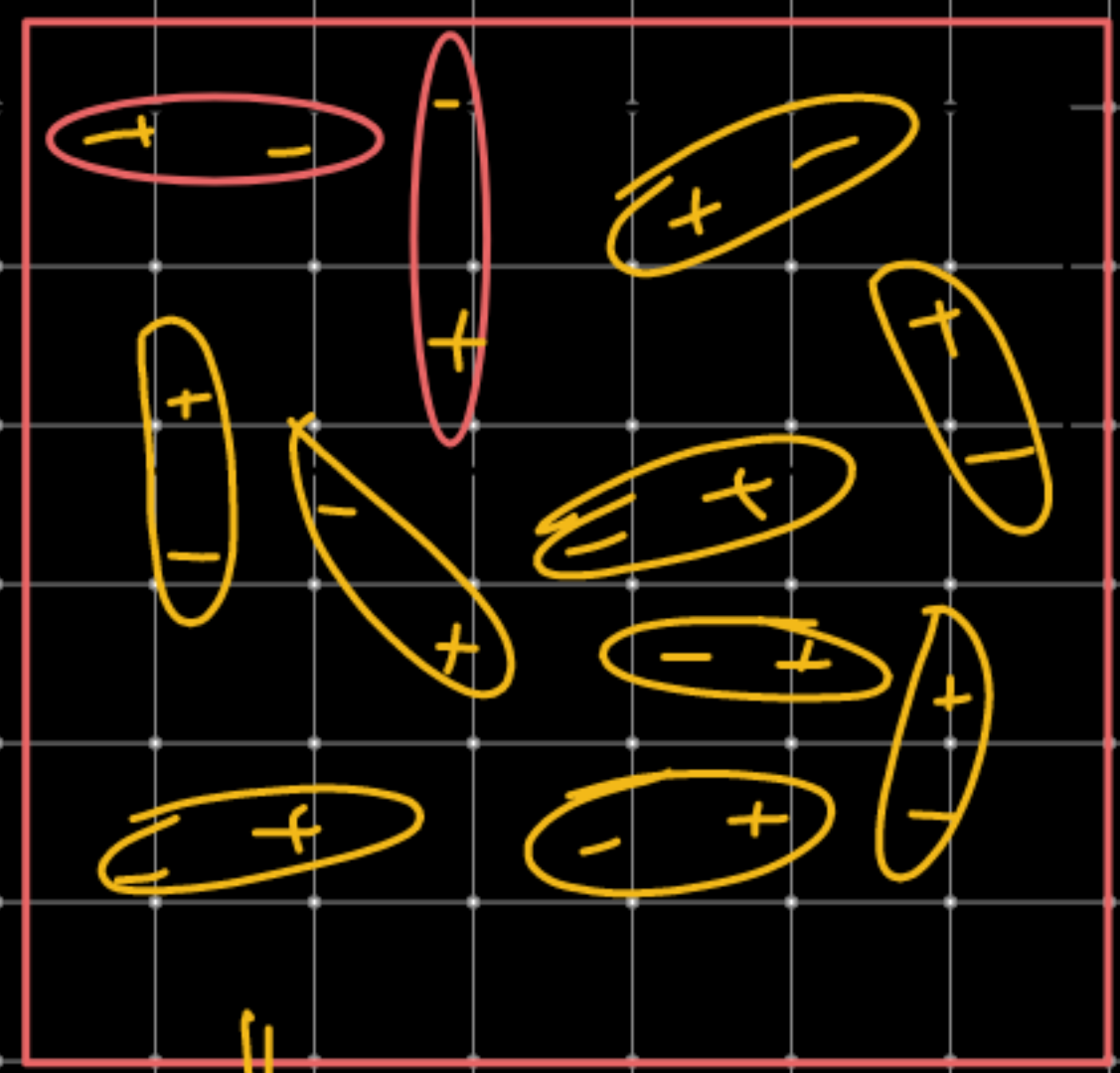


Net dipole moment
= 0

$\text{Cl}^- \text{Na}^+$

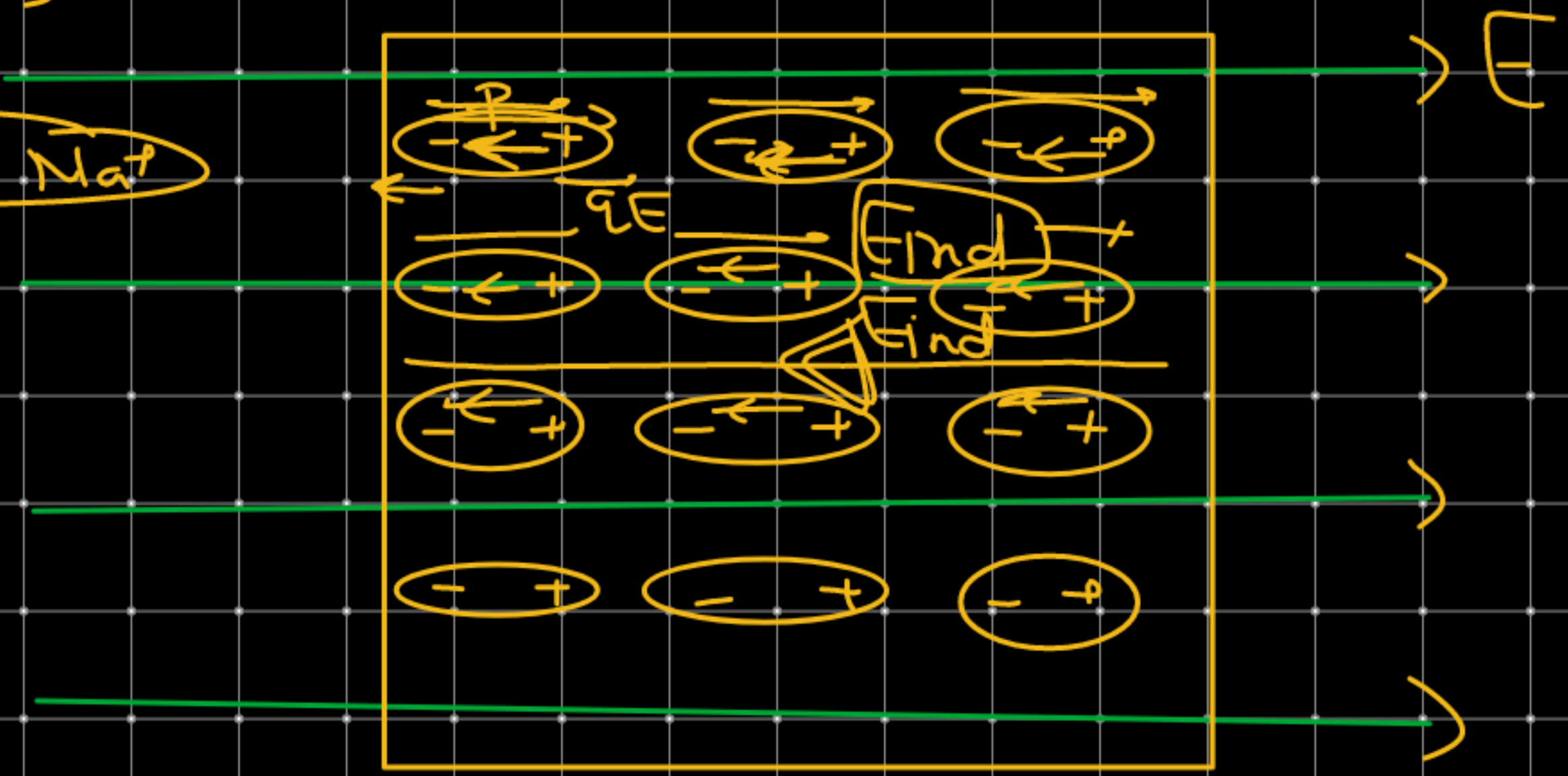

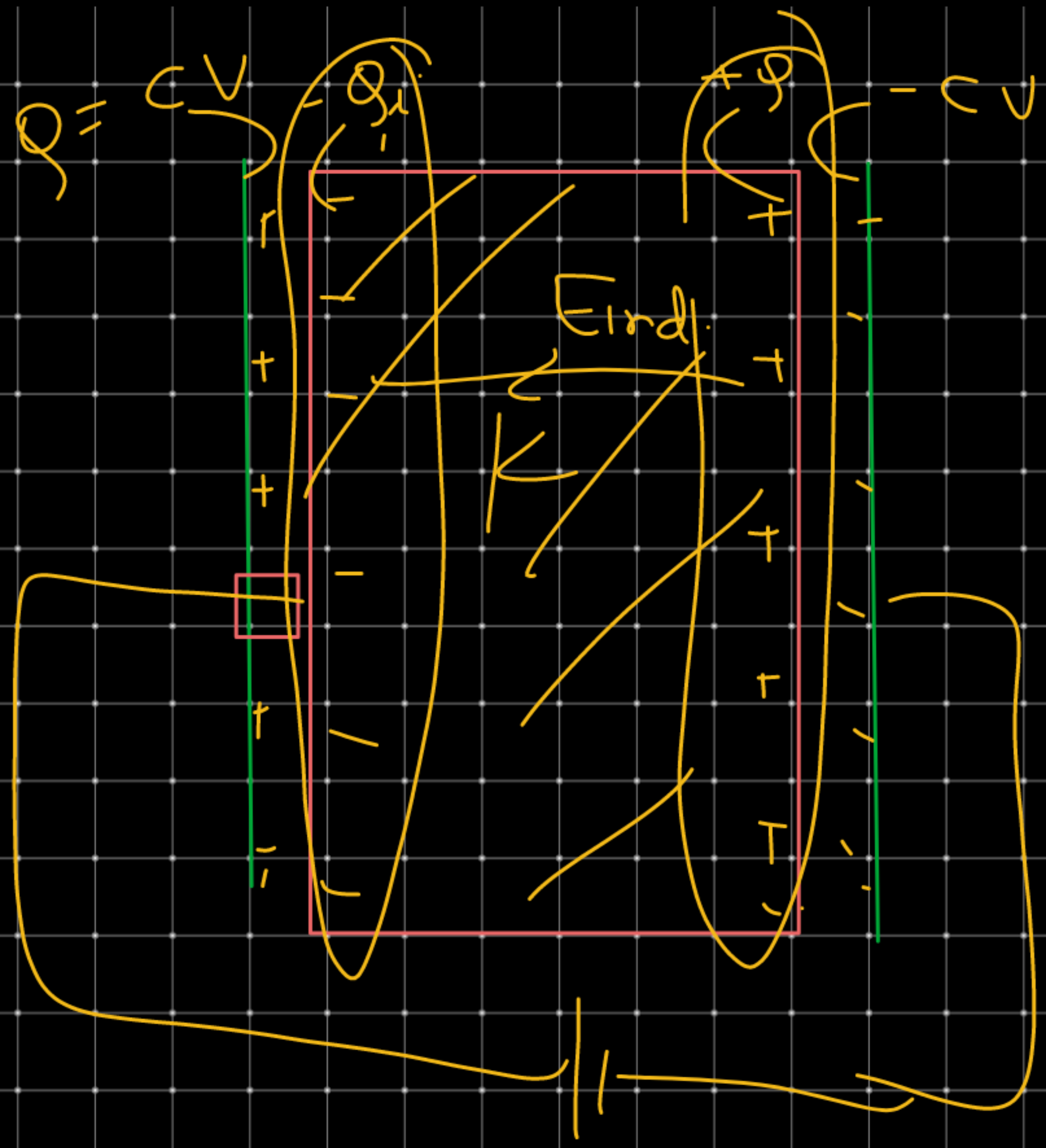Net dipole moment $\neq 0$
Total dipole moment = $n p$
 $n = \text{no of molecule}$





Non-polar dielectric:

↳ dipole moment of each molecule is zero.


Ex N_2 , CH_4 , C_6H_6 ,

non-polar.

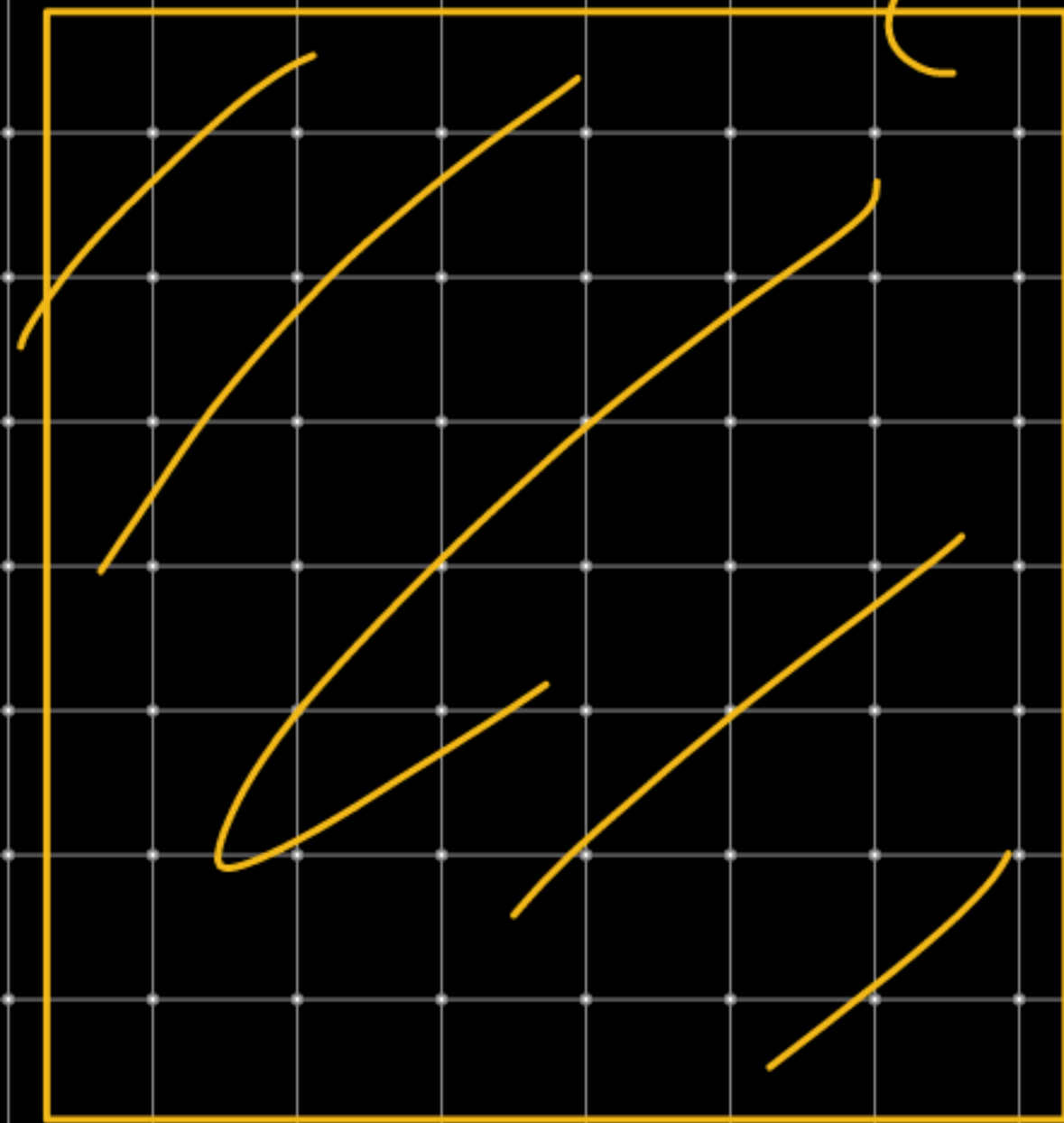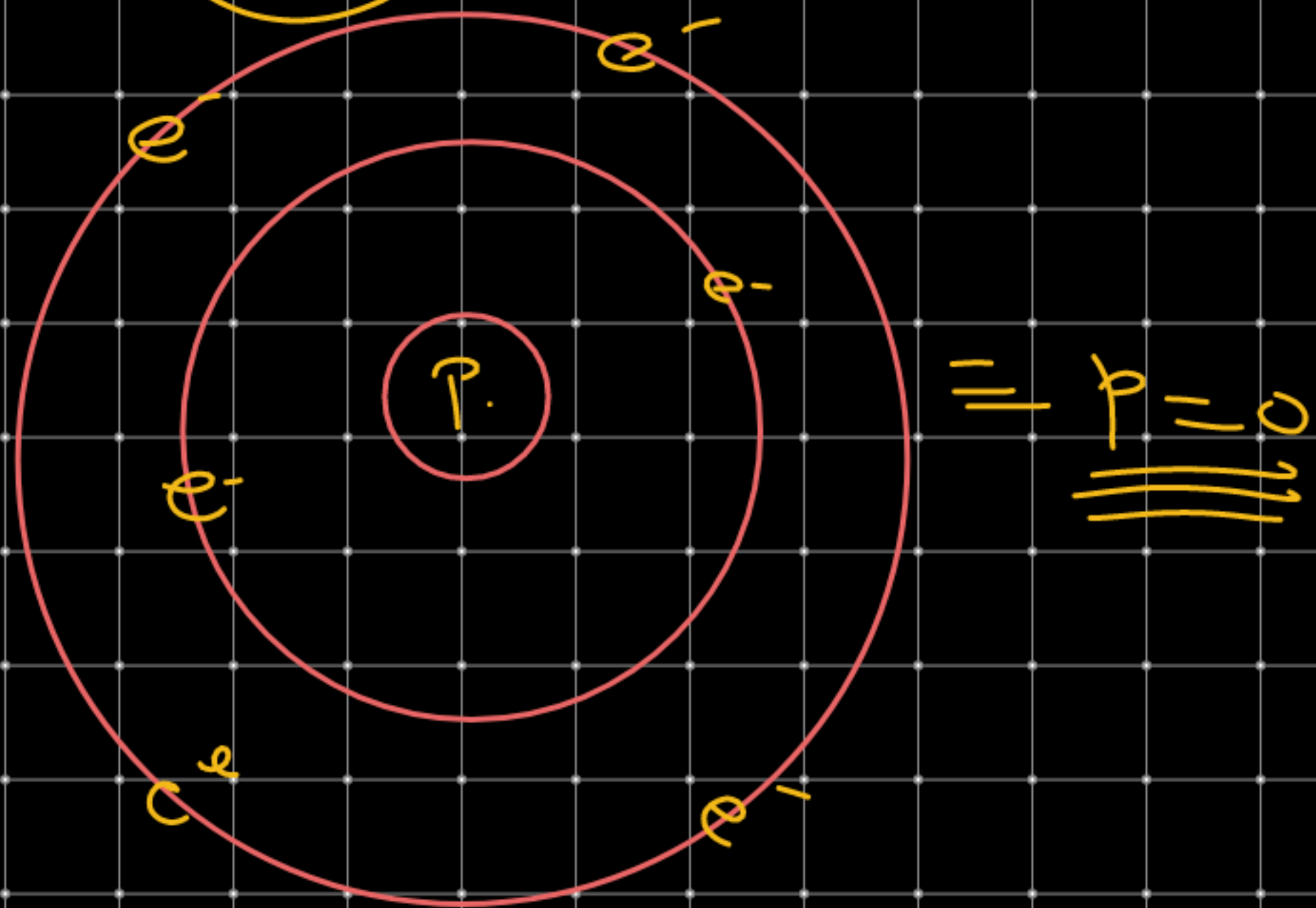


$P_{net} = 0$

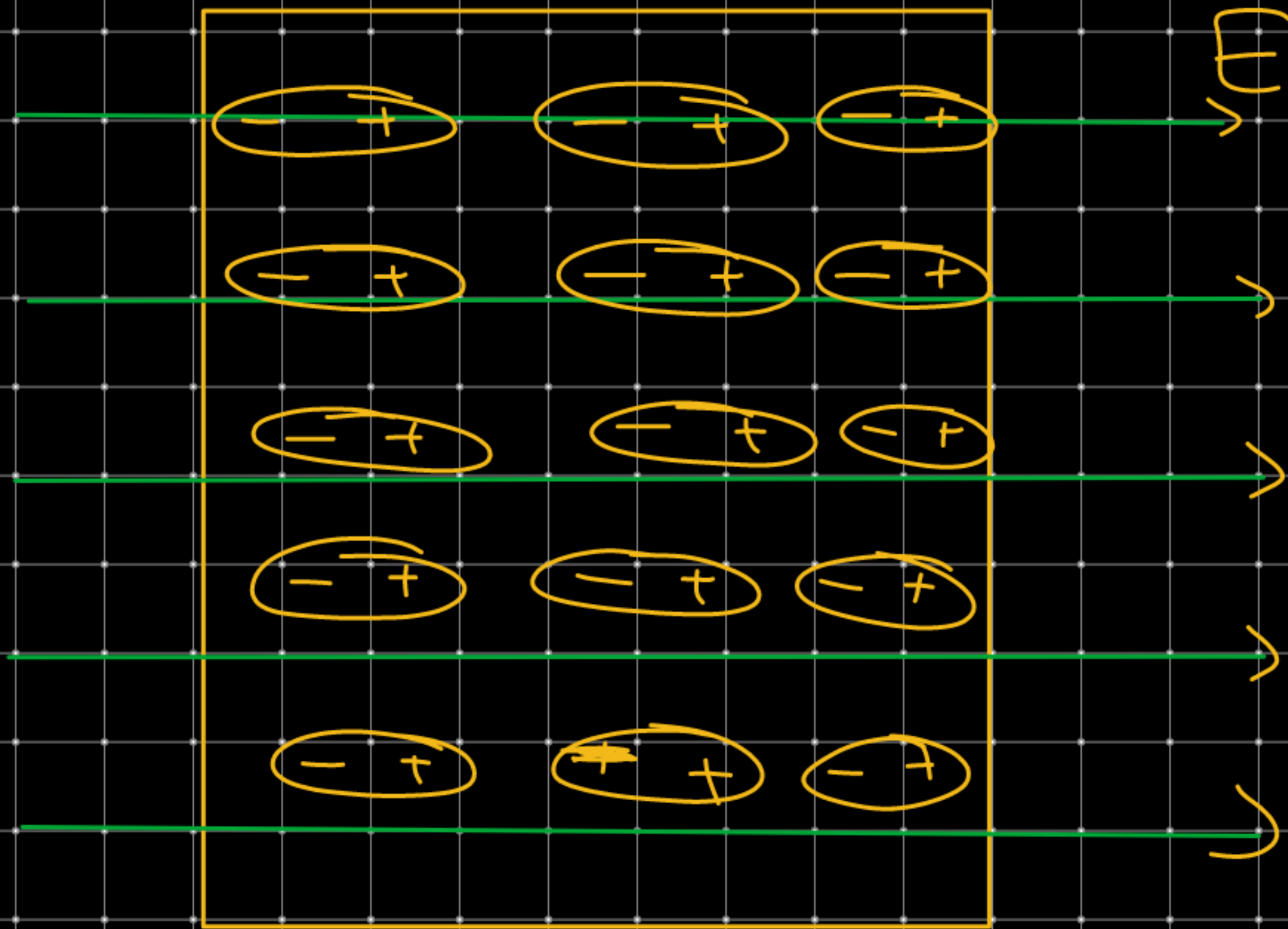When we placed non-polar dielectric in External Electric field.



$P_{net} \neq 0$ $P_i = nP$

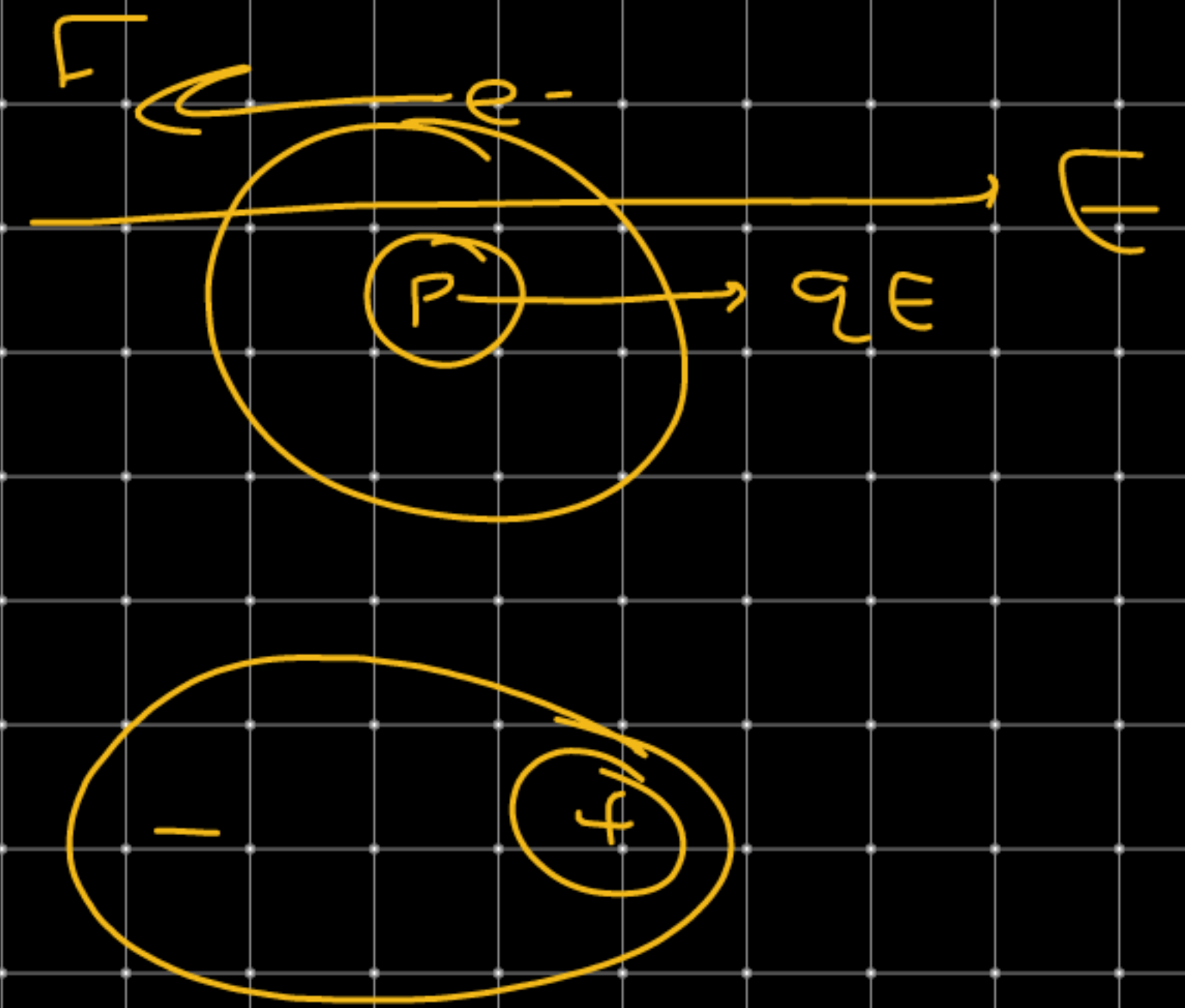

Polarization Vector

$$\text{Polarization} = \frac{P_T}{V} = \frac{nP}{Ad}$$

NET/JEE (m)


dimensional formula of

Polarization:

→


$$\frac{[AT]}{[L^2]} = \frac{[L^{-2} M^3]}{[AT]}$$
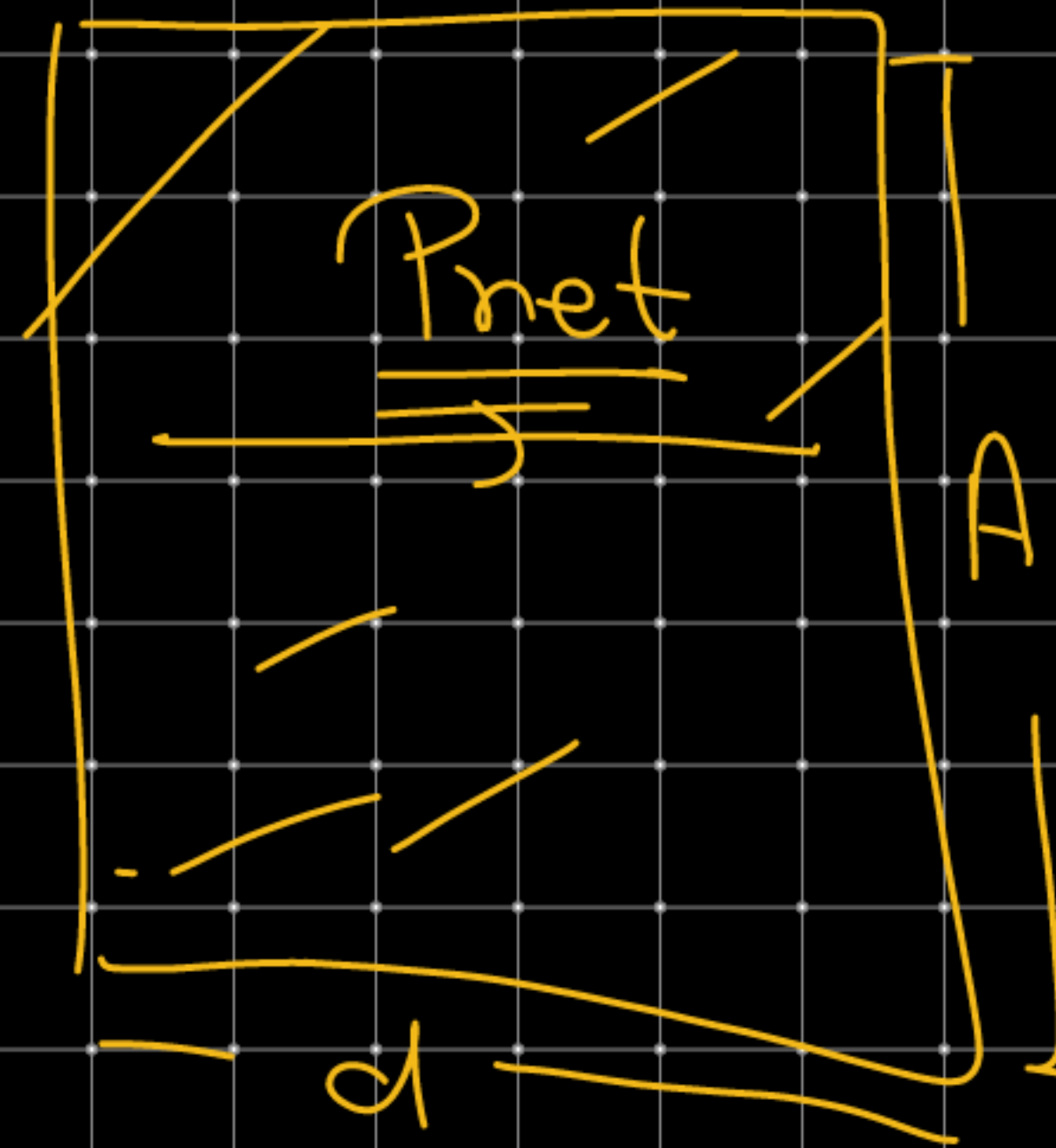
$$\frac{C \cdot m}{m^3} = \frac{C}{m^2}$$




↳ Dielectric strength of material:

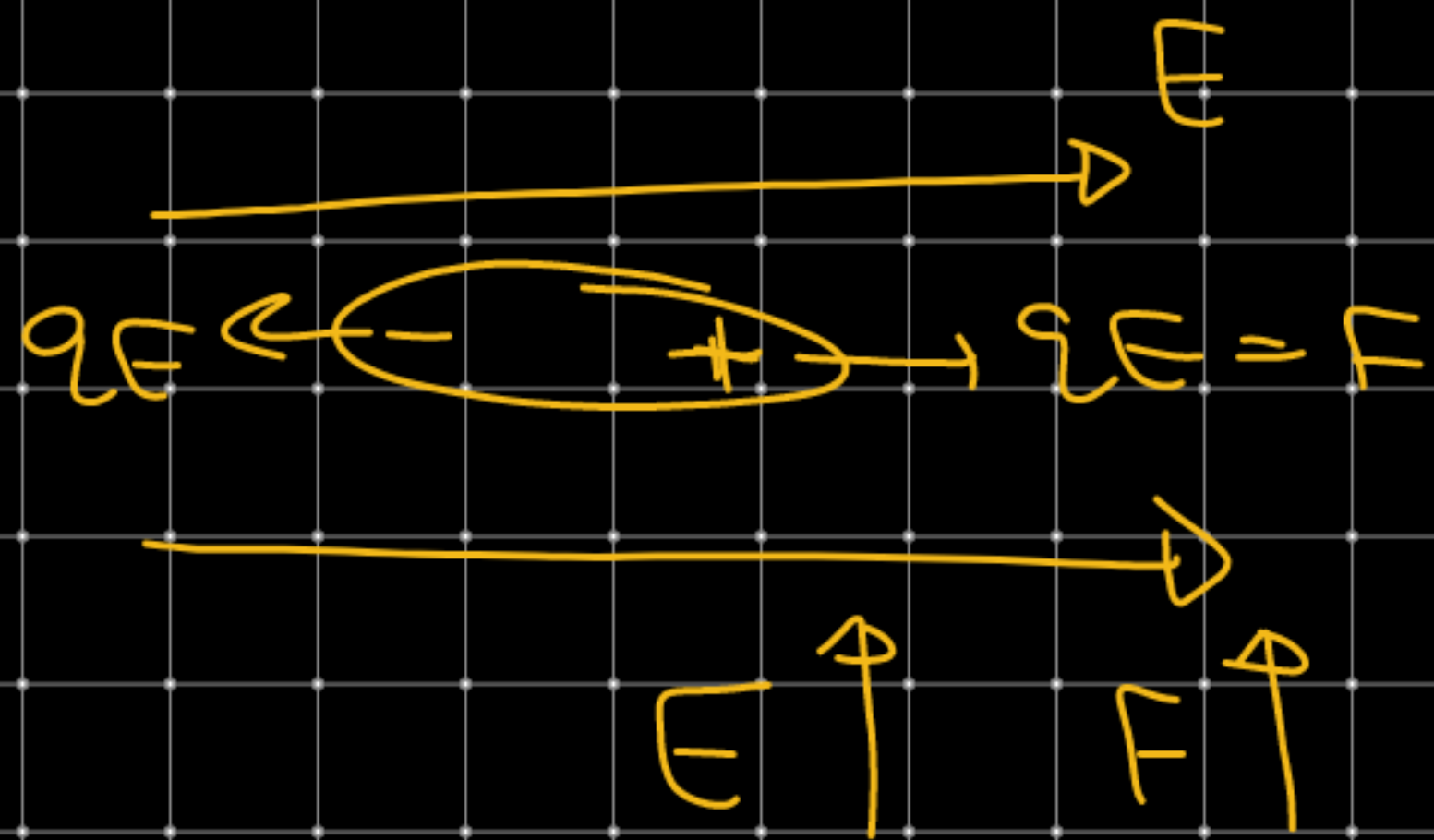⇒ $E = 3 \times 10^6 \text{ N/C}$ → for air.



At a certain value of electric field, dipole break,
This certain value of electric field is known as breakdown
Electric field & potential is called breakdown potential.

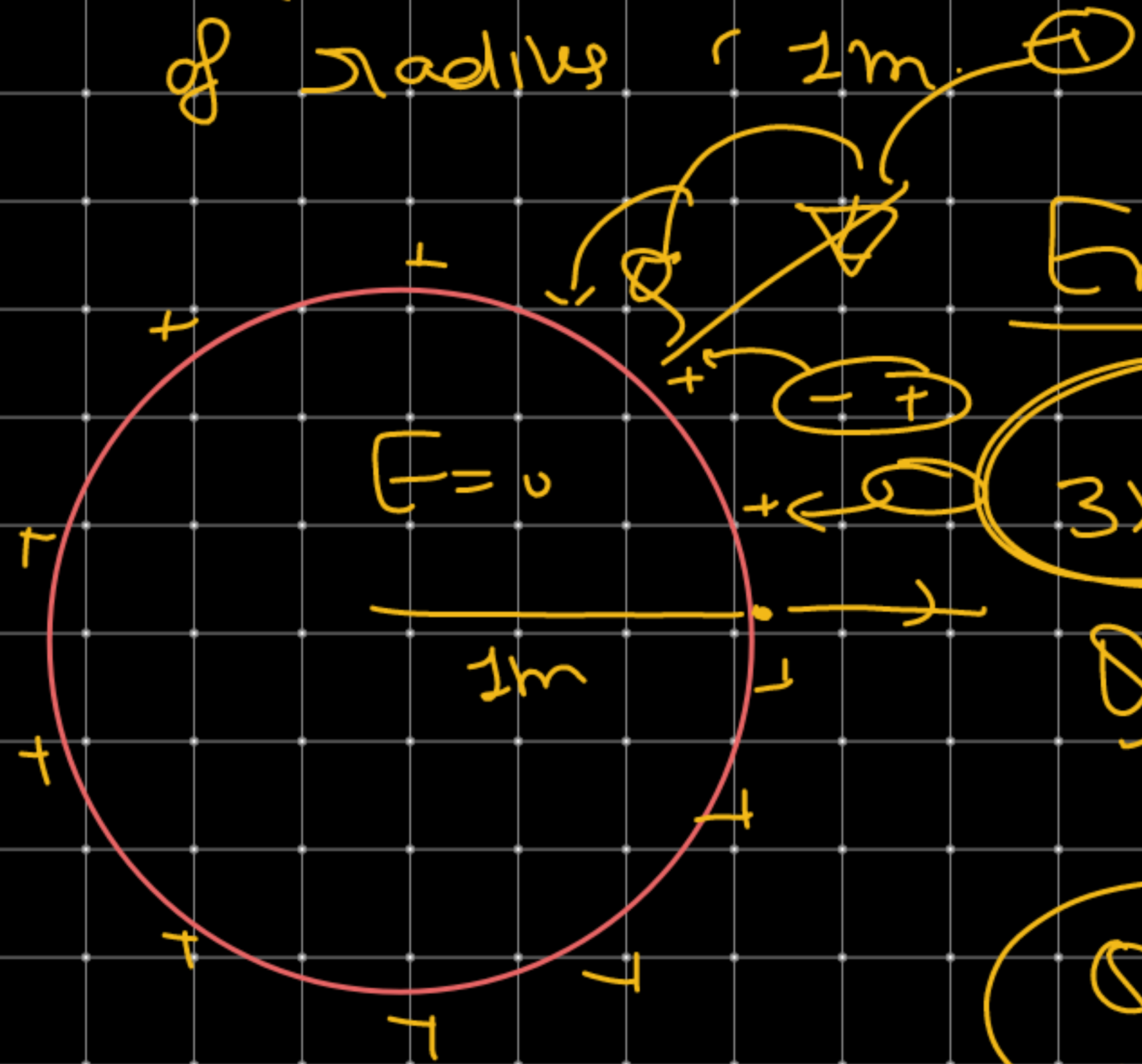Q1: Find the maximum charge on a sphere placed in air of radius 2m .



$$E_{\text{max}} = \frac{Kq}{R^2} = \frac{9 \times 10^9 \times q}{1}$$


$$q = \frac{3 \times 10^6}{9 \times 10^9}$$

$$q = \frac{1}{3} \times 10^{-3} \text{ C}$$

$$q = 3.33 \times 10^{-4} \text{ C}$$

Parallel Plate Capacitor:-

① Charging of Parallel plate Capacitor.

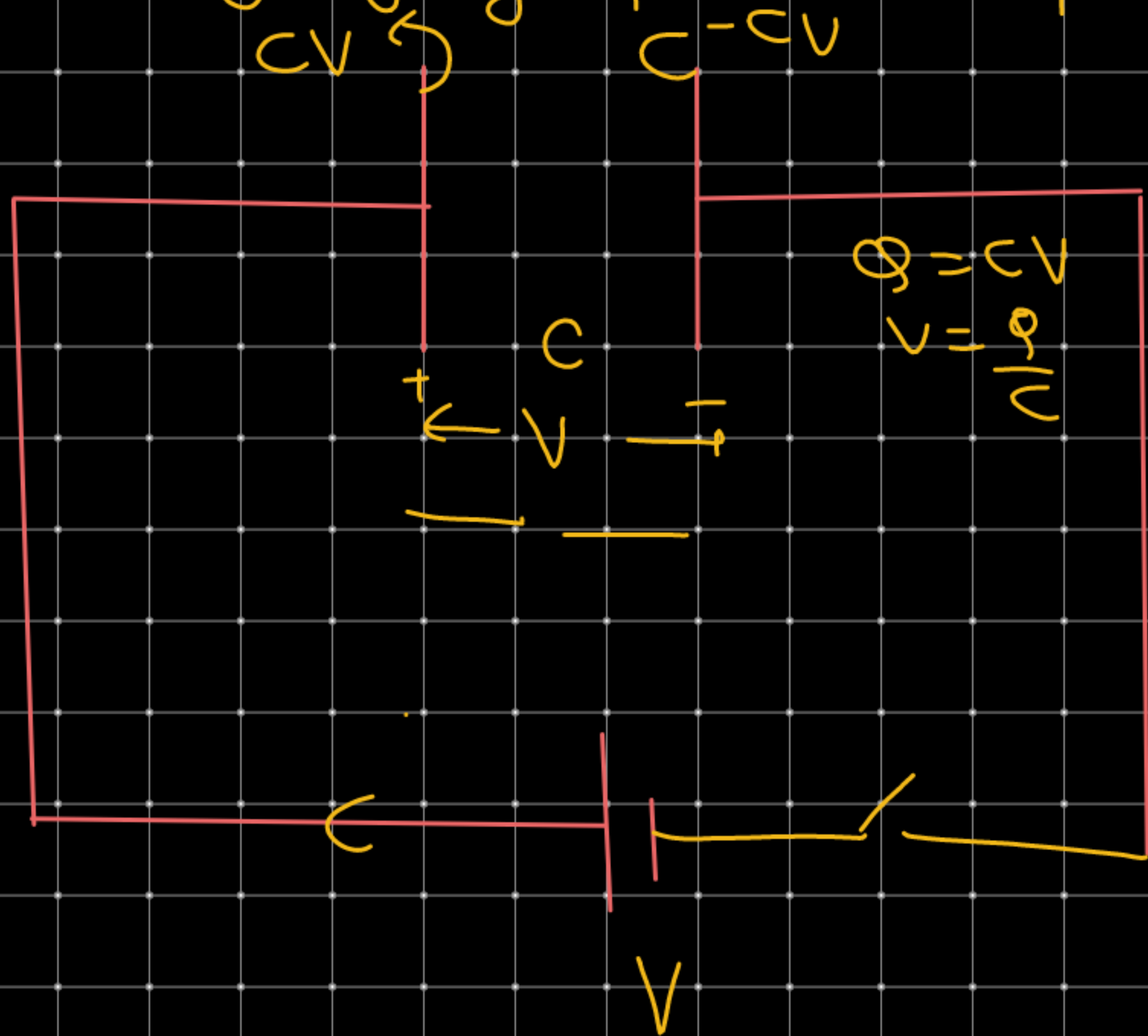


① $t=0$ Key is closed


↳ Charge on Capacitor



② $t=\infty$ (long time)
Steady State ($i=0$)

$Q=CV$

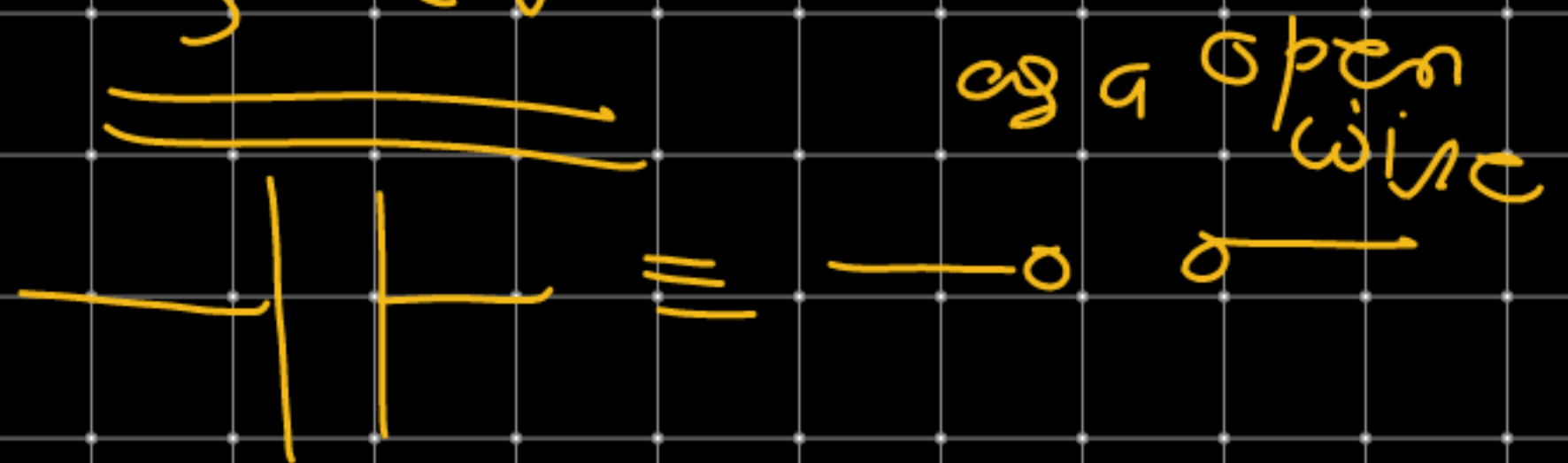

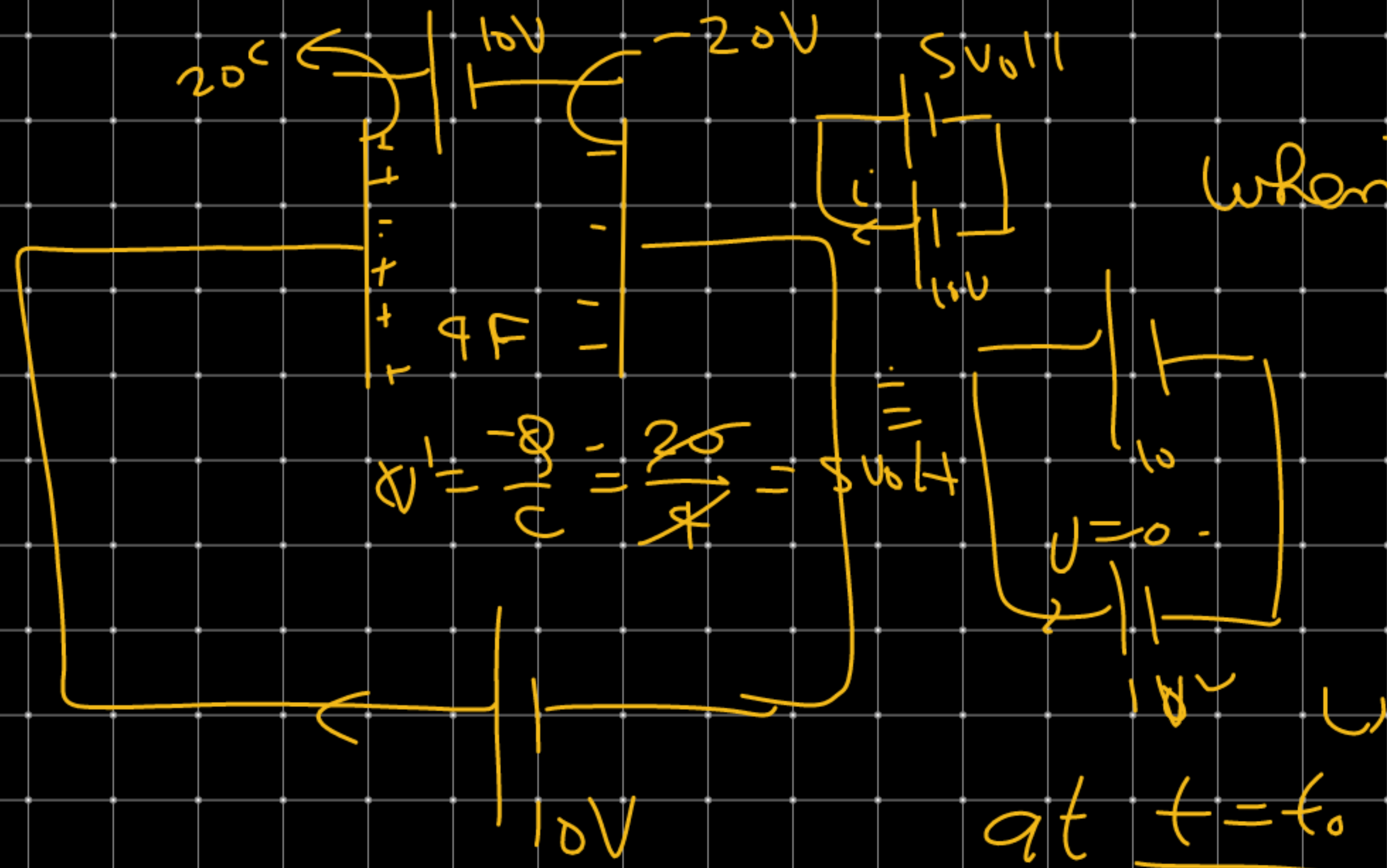

When capacitor is fully charged


$$Q = CV$$

$$= 4 \times 10$$


$$= 40C$$

at $t = t_0$, $Q = 20C$

$t = 0$


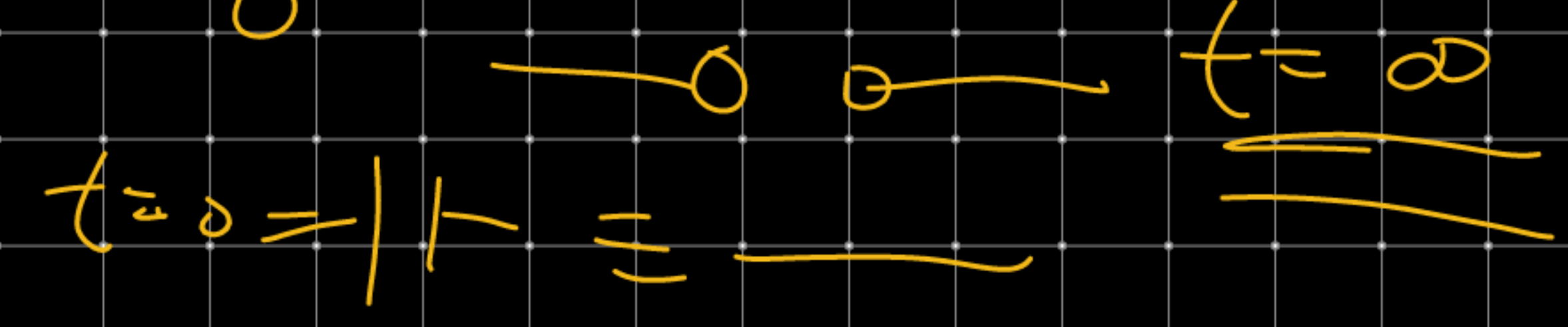


Q1) Find Current at $t=0$

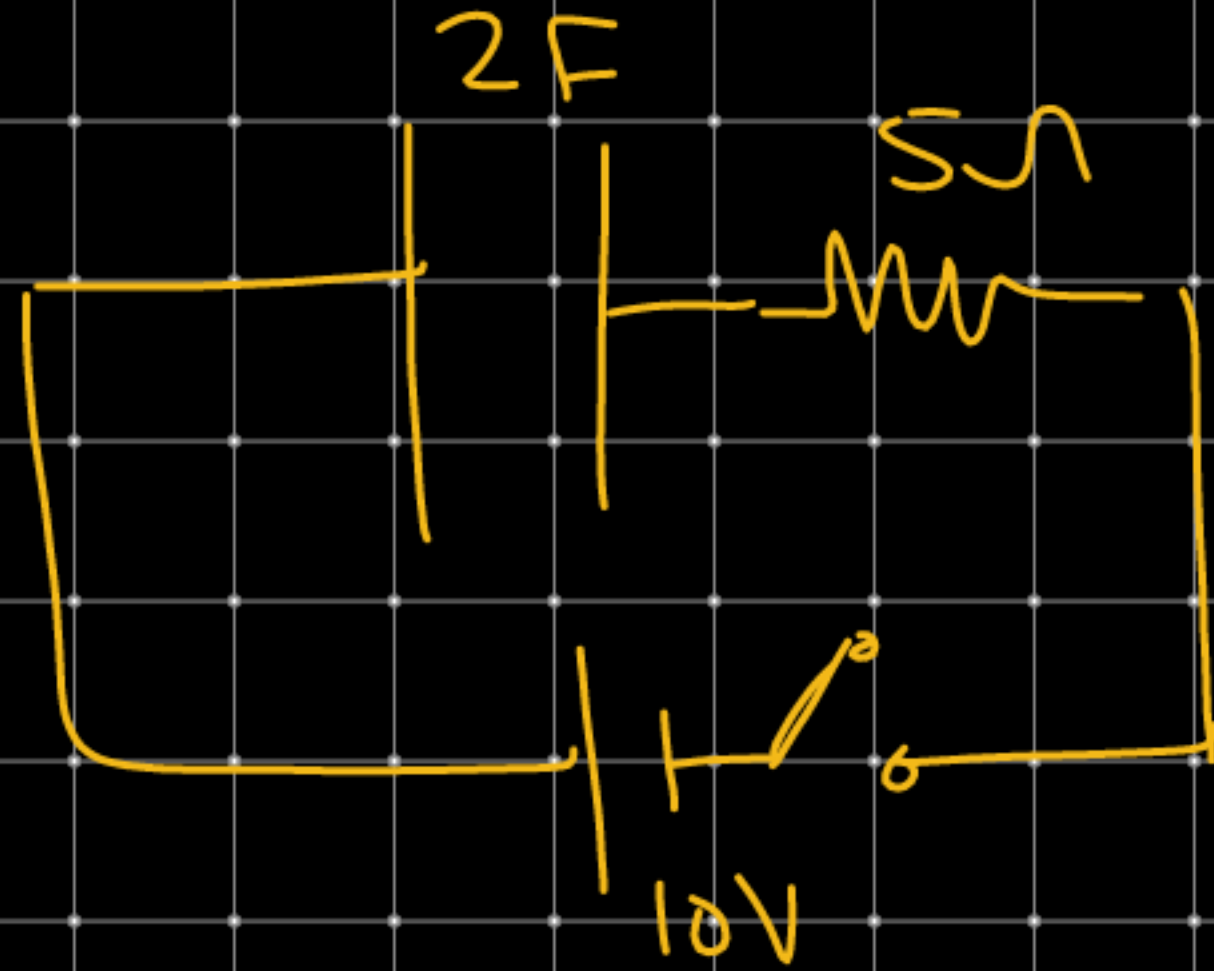


$$i = \frac{10}{5} = 2A$$

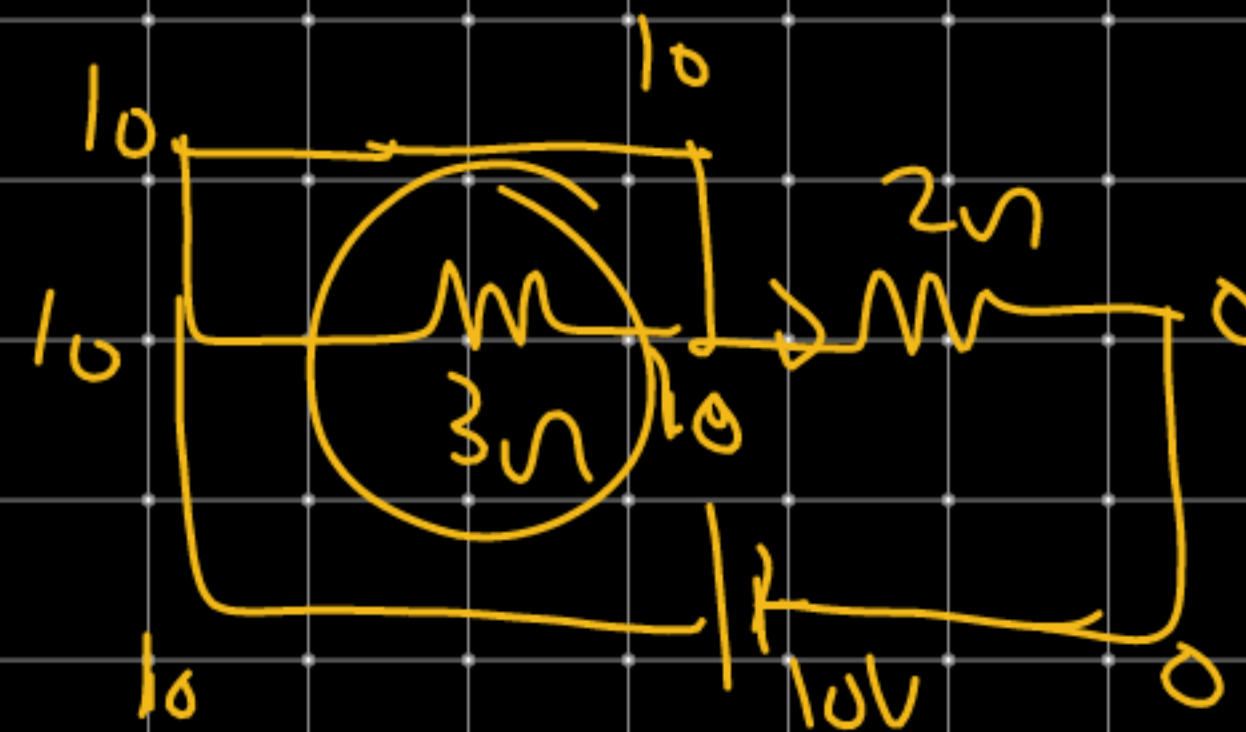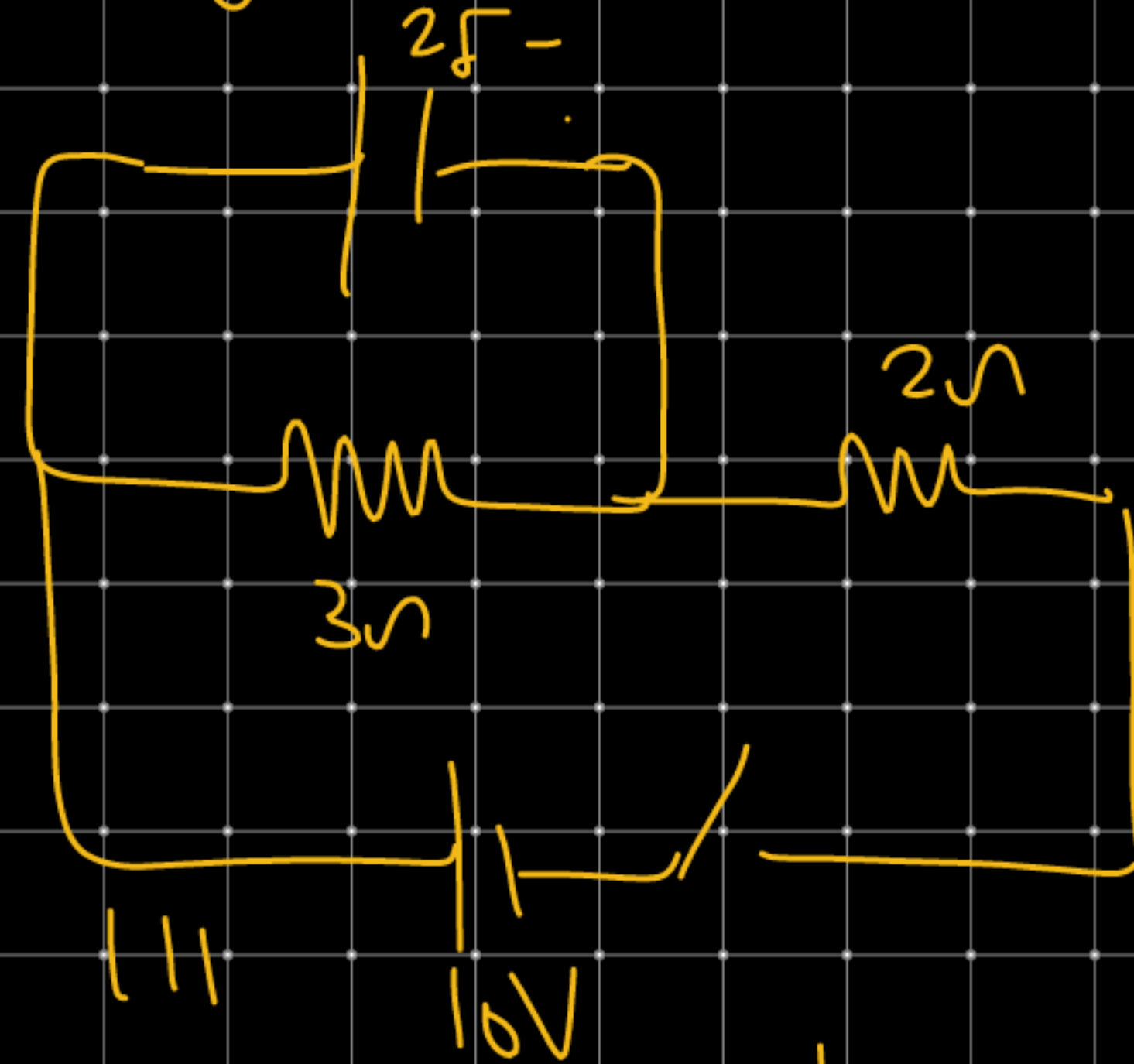Q2) Find Current Supplied by battery at $t=0$






$$\frac{10}{2} = 5A$$


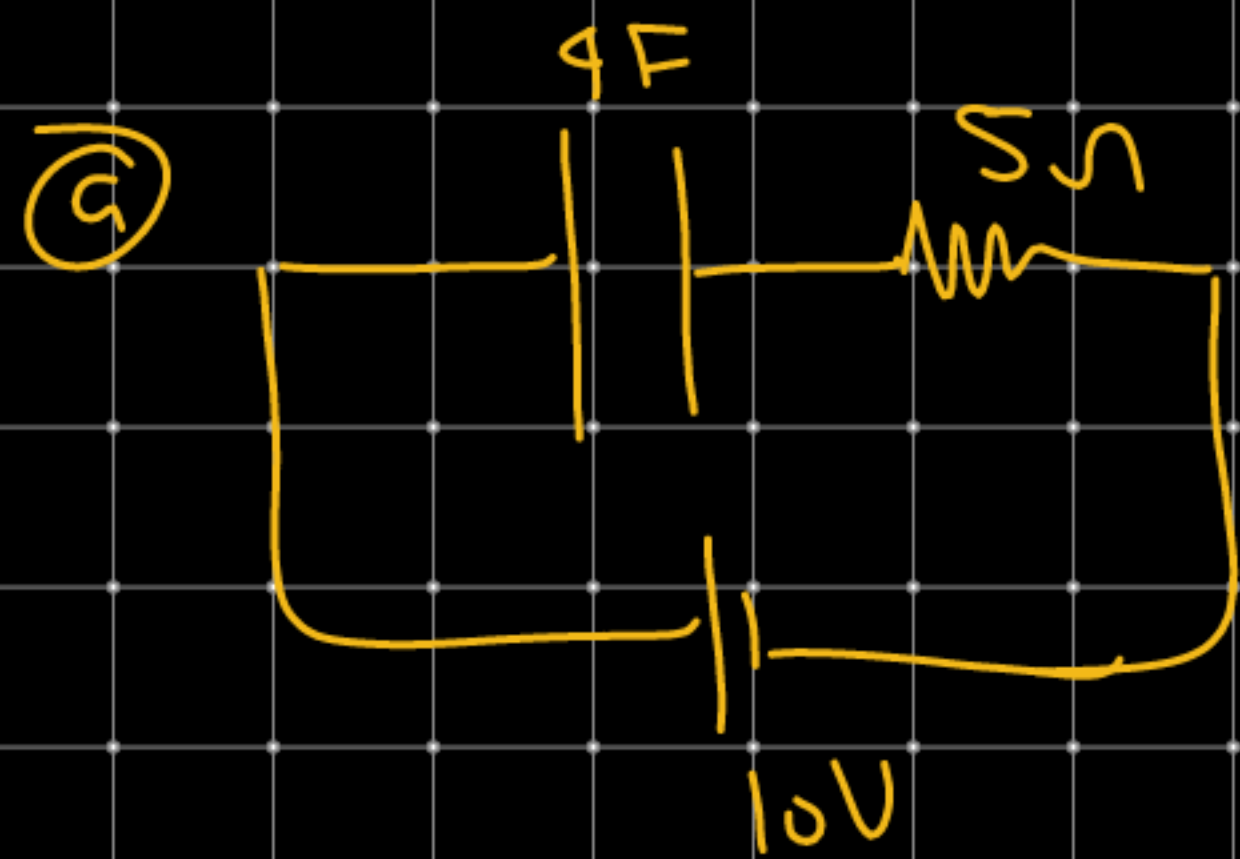
Find Current through battery at $t = \infty$.




$i = 0$, CKT is OPEN

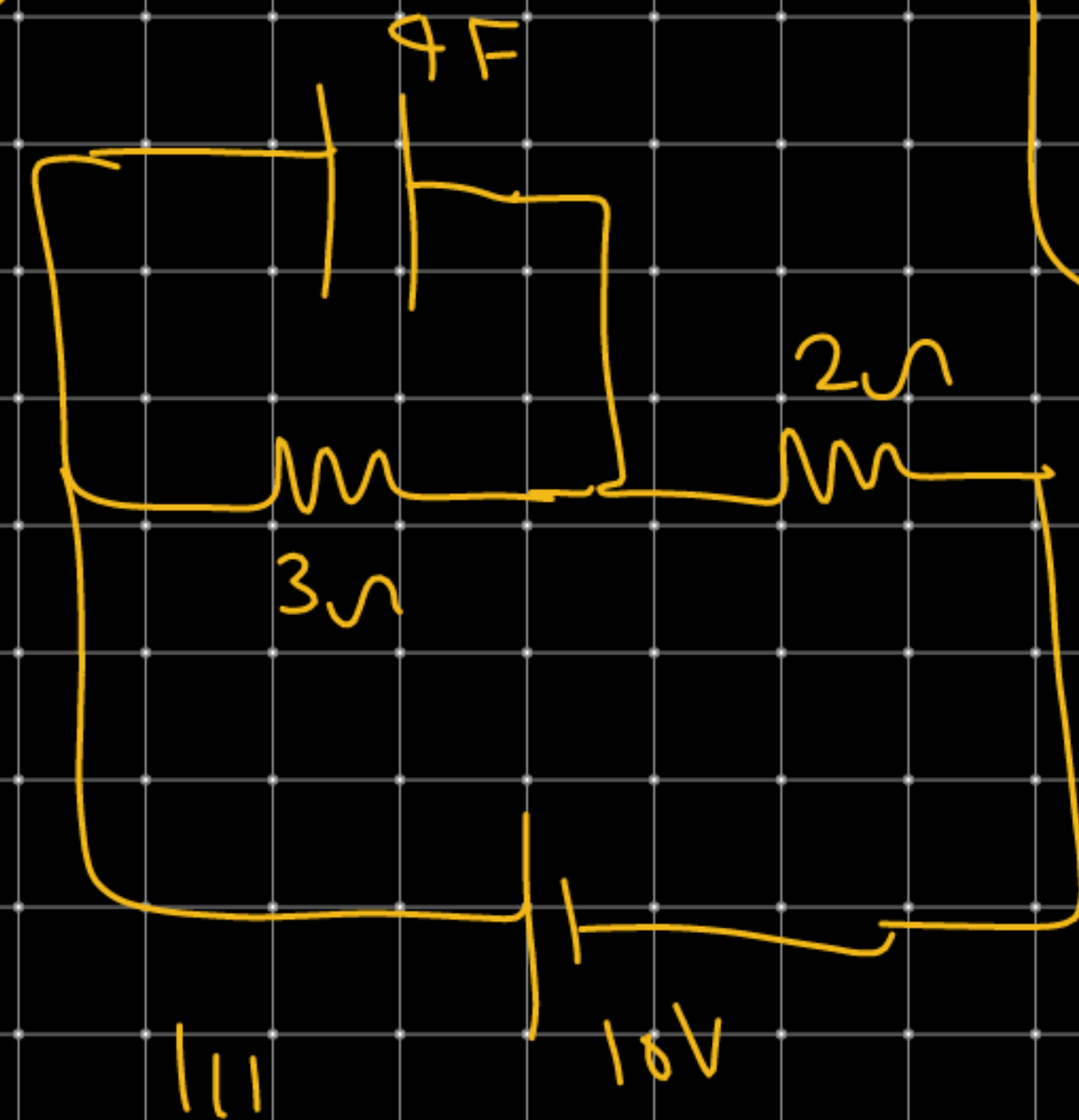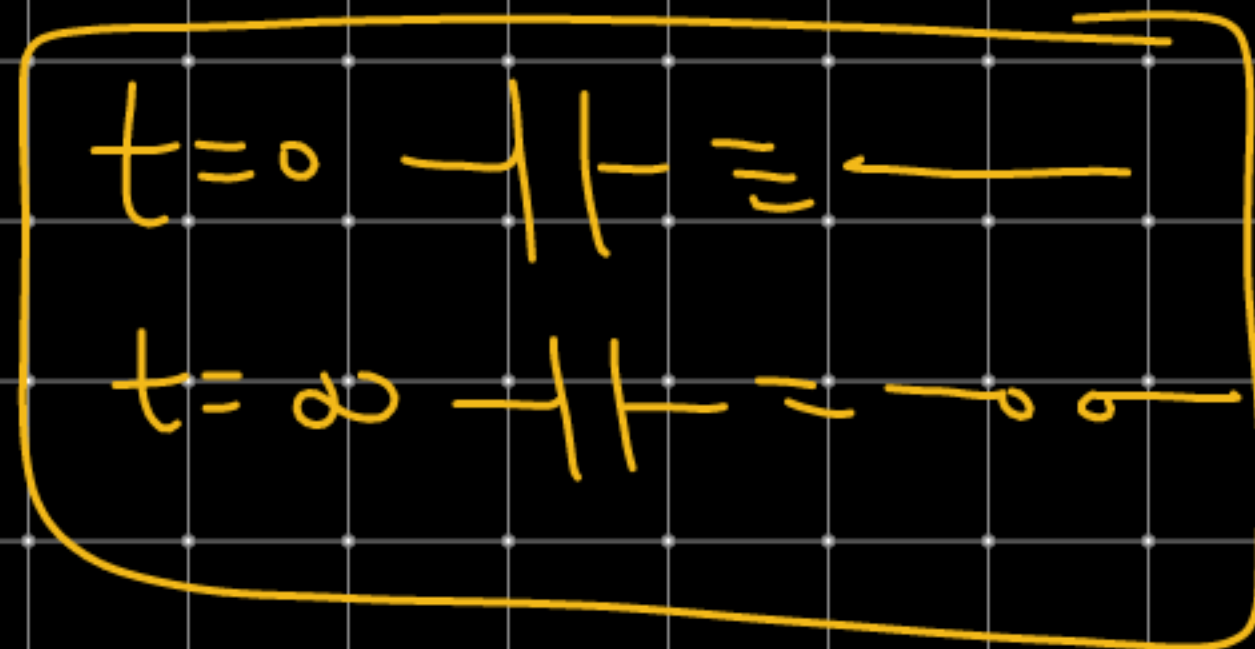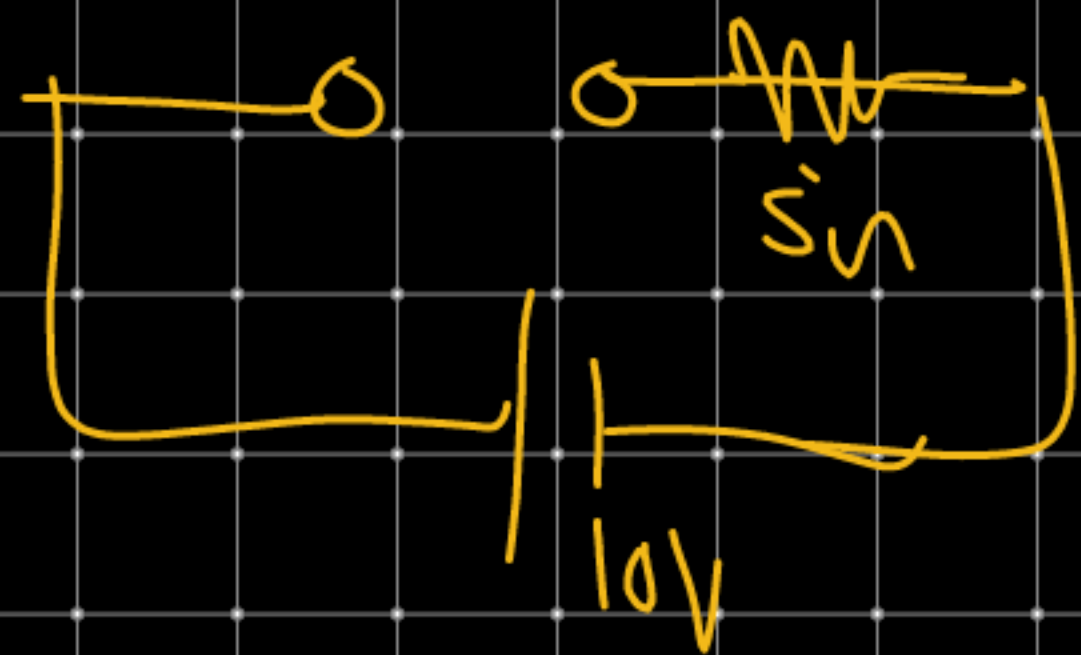

$t = \infty$

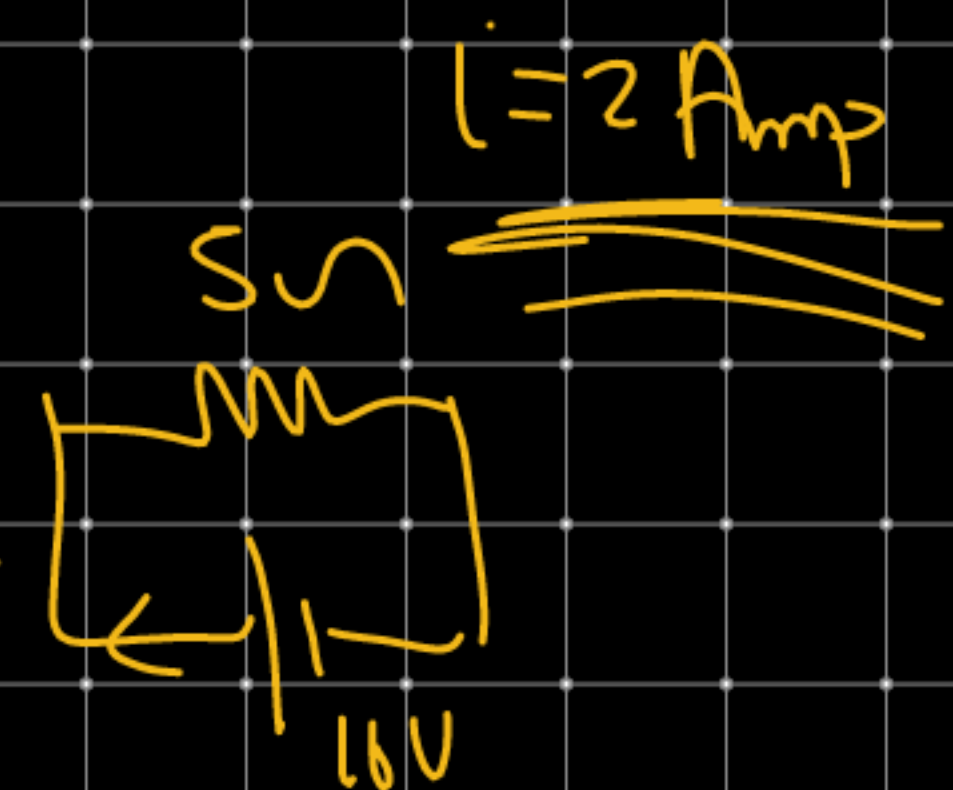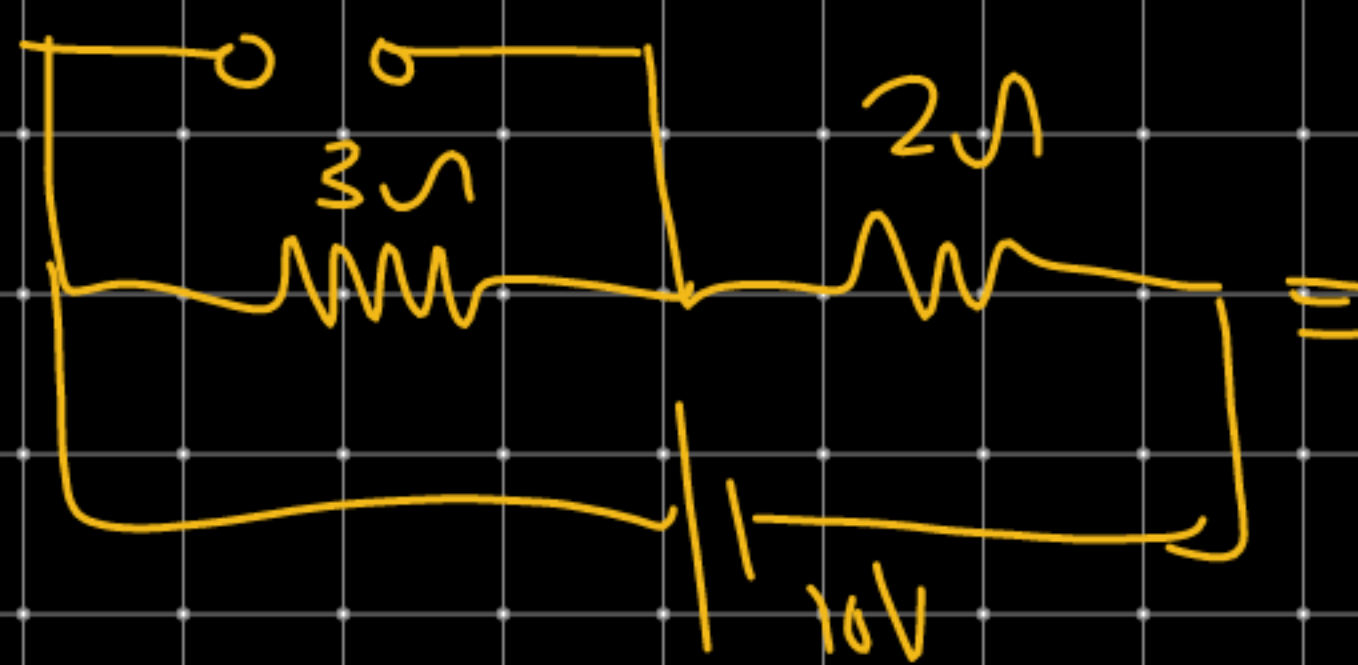


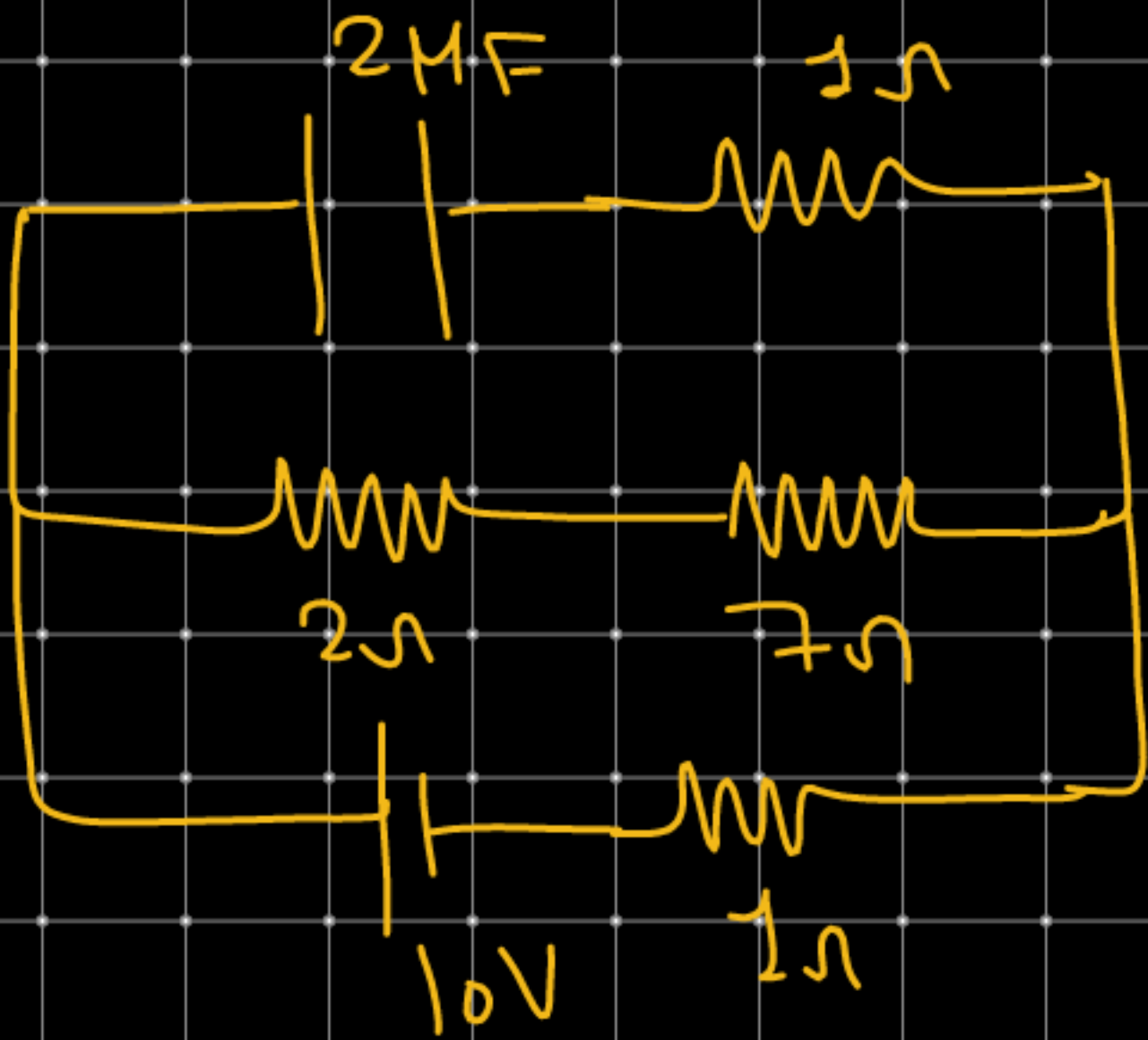

at $t=0$


$$R_{eq} = \frac{9 \times 1}{9+1}$$

$$= \frac{9}{10} = 0.9\Omega$$

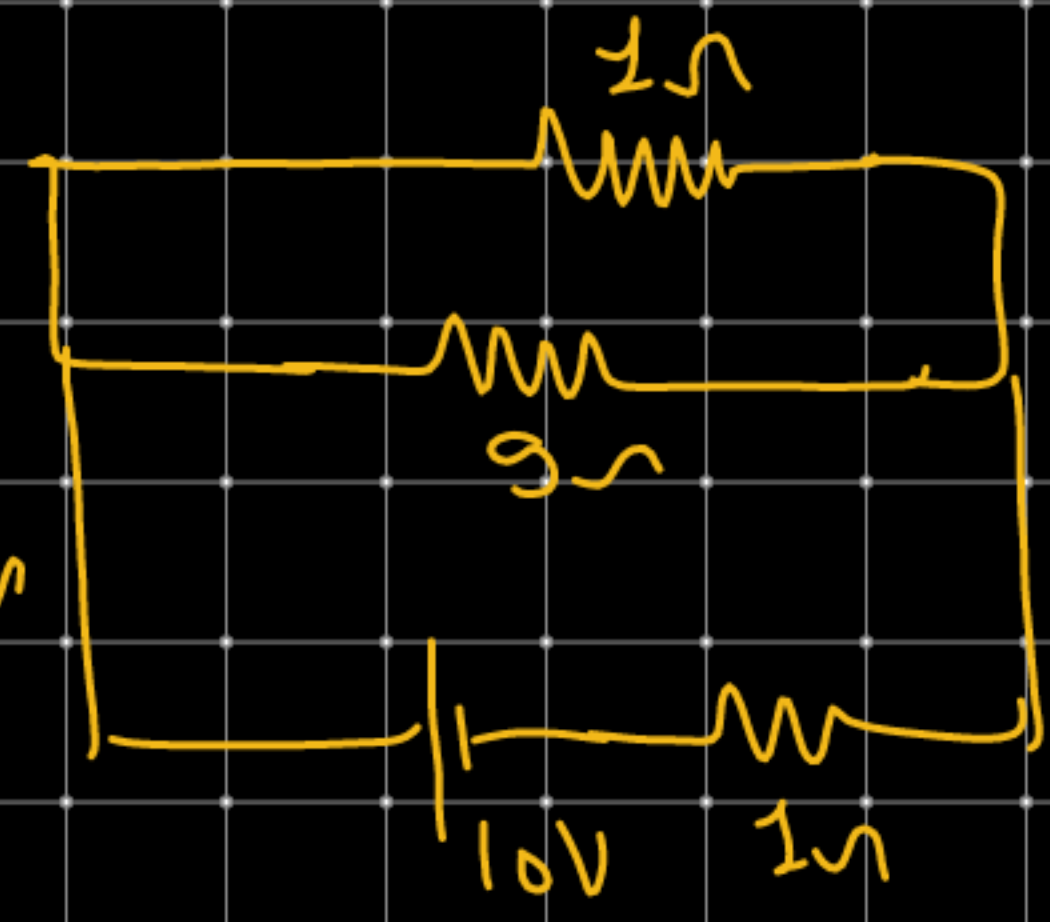


$$= \frac{0.9\Omega}{10V} = \frac{10}{1.9} \text{ Amp}$$

$t=\infty$ (Steady state)

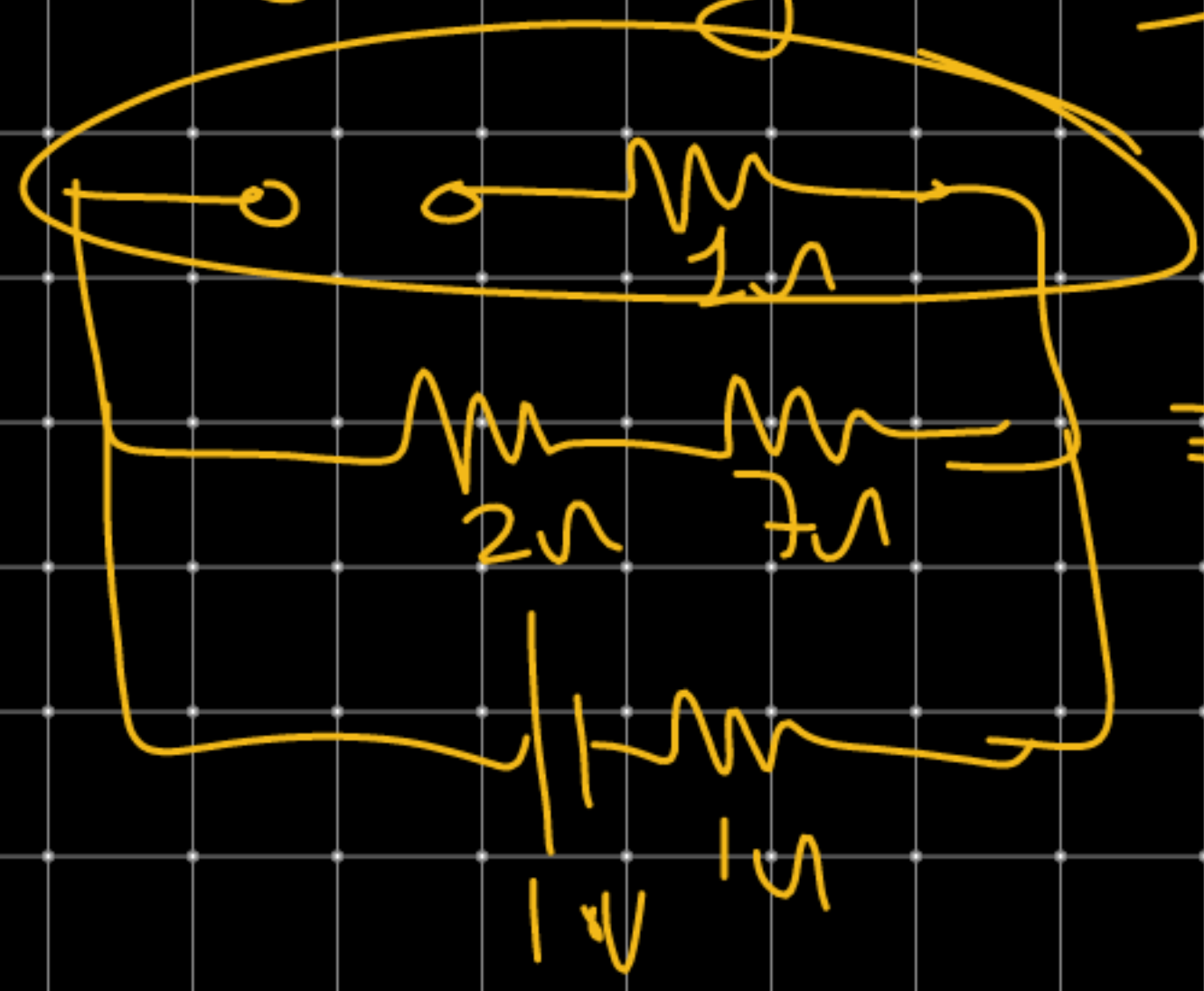

$$R_{eq} = 10\Omega$$


$$i = \frac{10}{10} = 1 \text{ Amp}$$

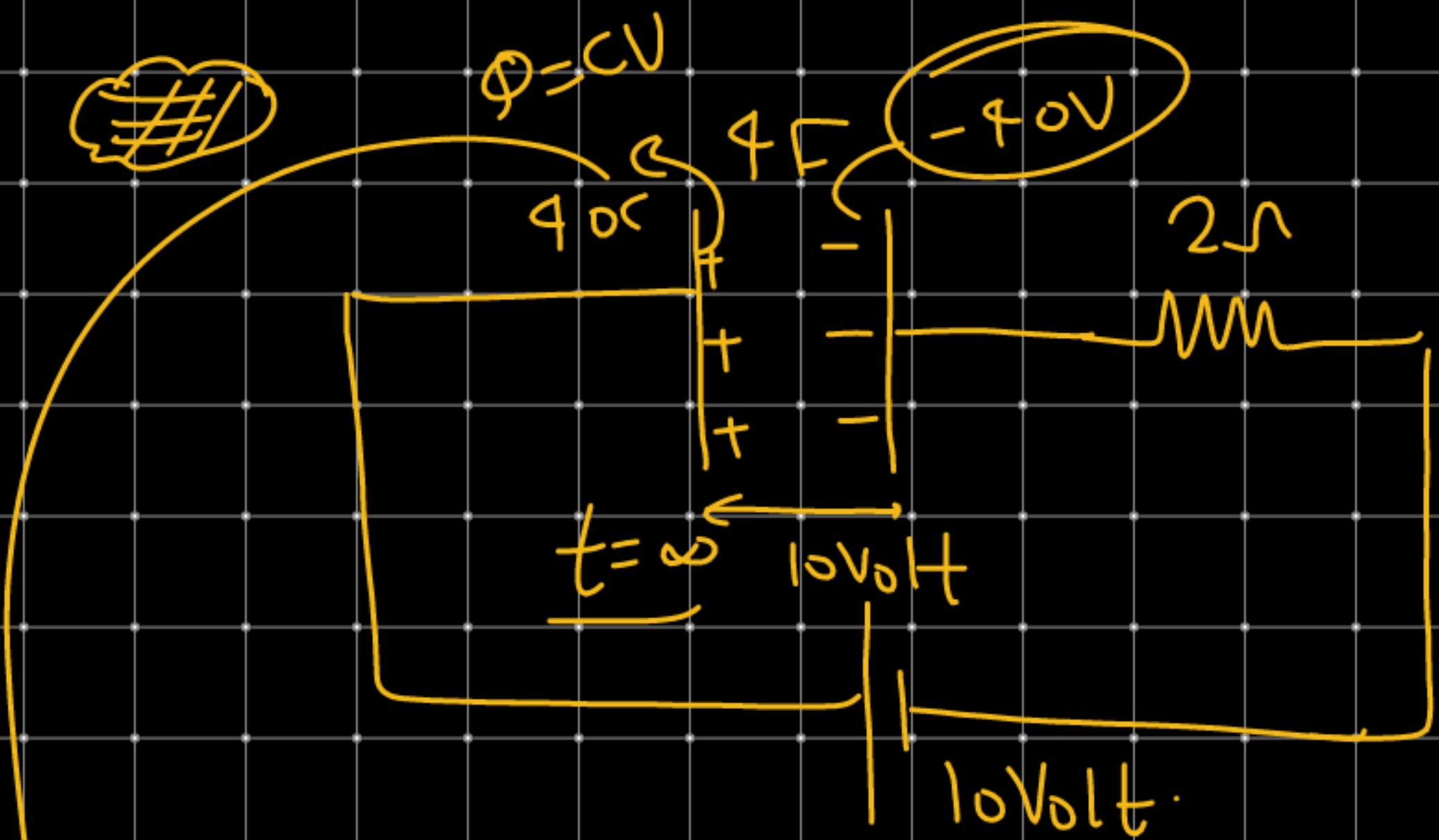

$\hookrightarrow t = \infty$, Steady state.
 Capacitor will fully charged




① $t = 0$

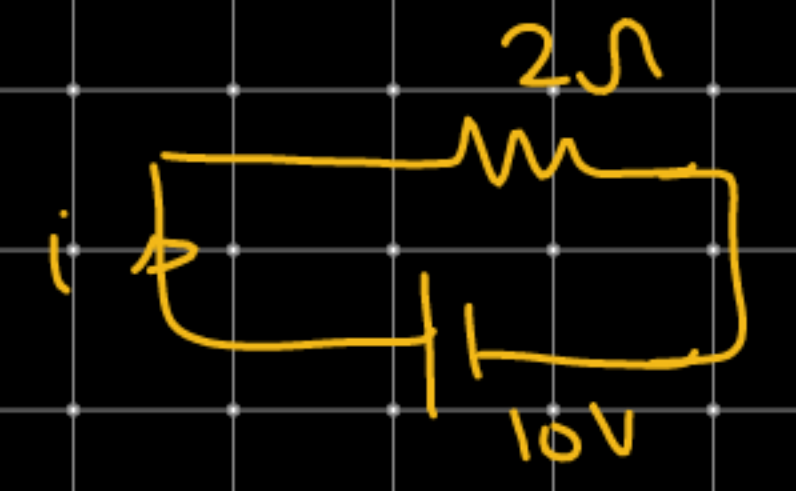


$i = \frac{10}{2} = 5 \text{ Amp.}$


② $t = \infty$

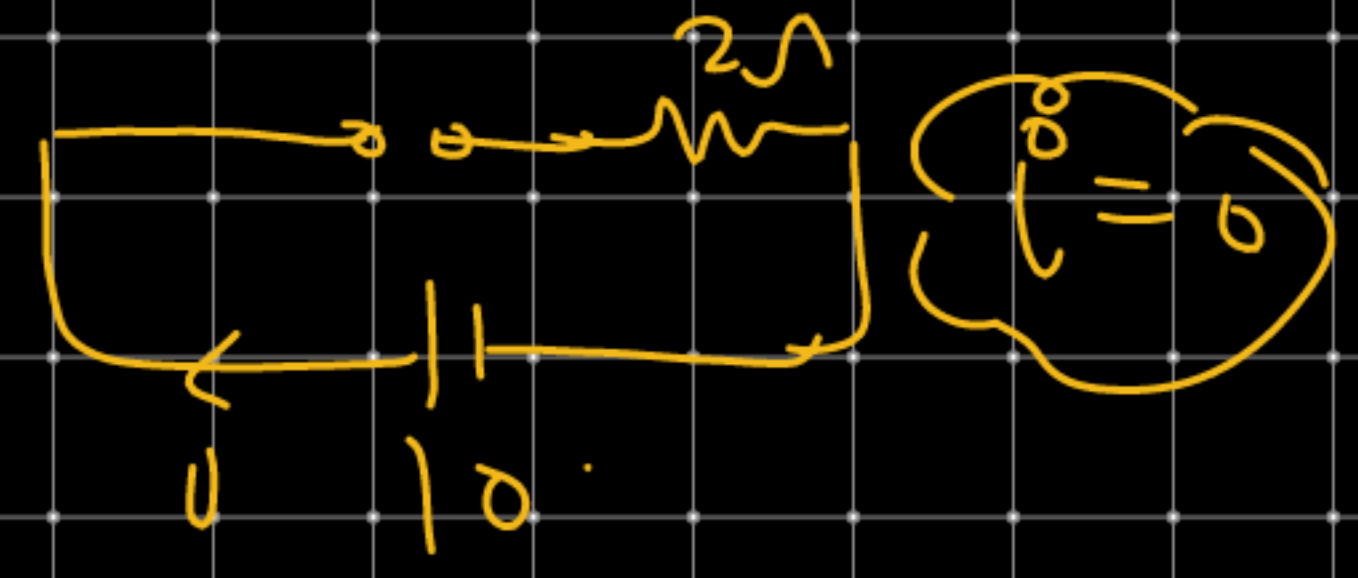

$t = 0$

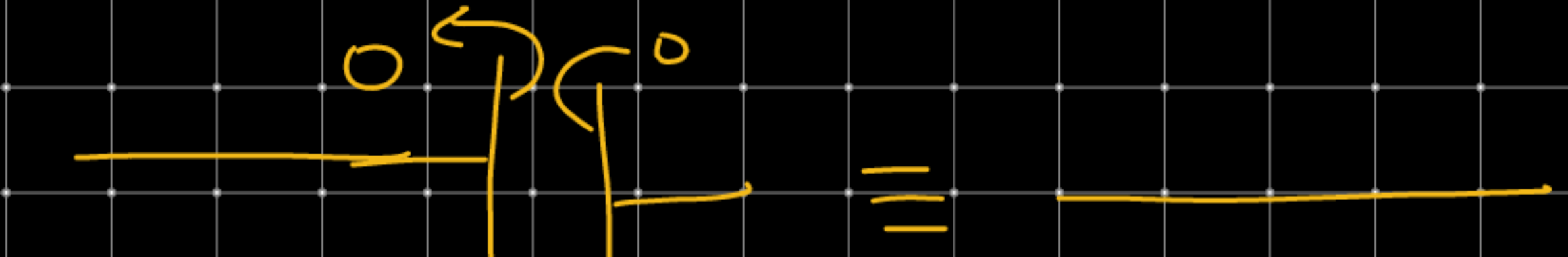


$t = \infty$

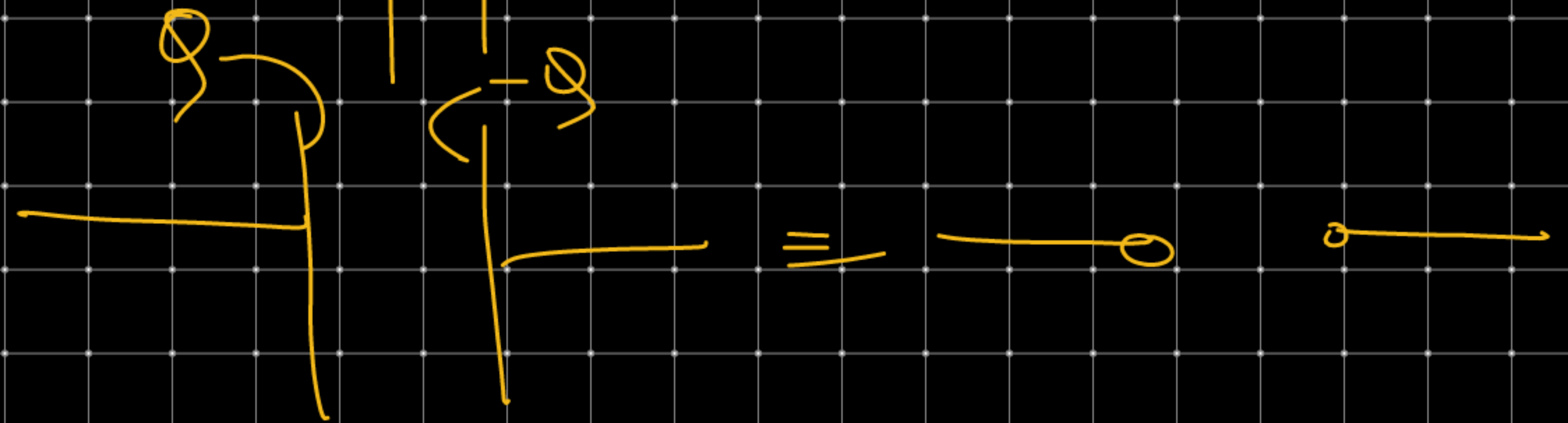


full charged

$t = t$ General time

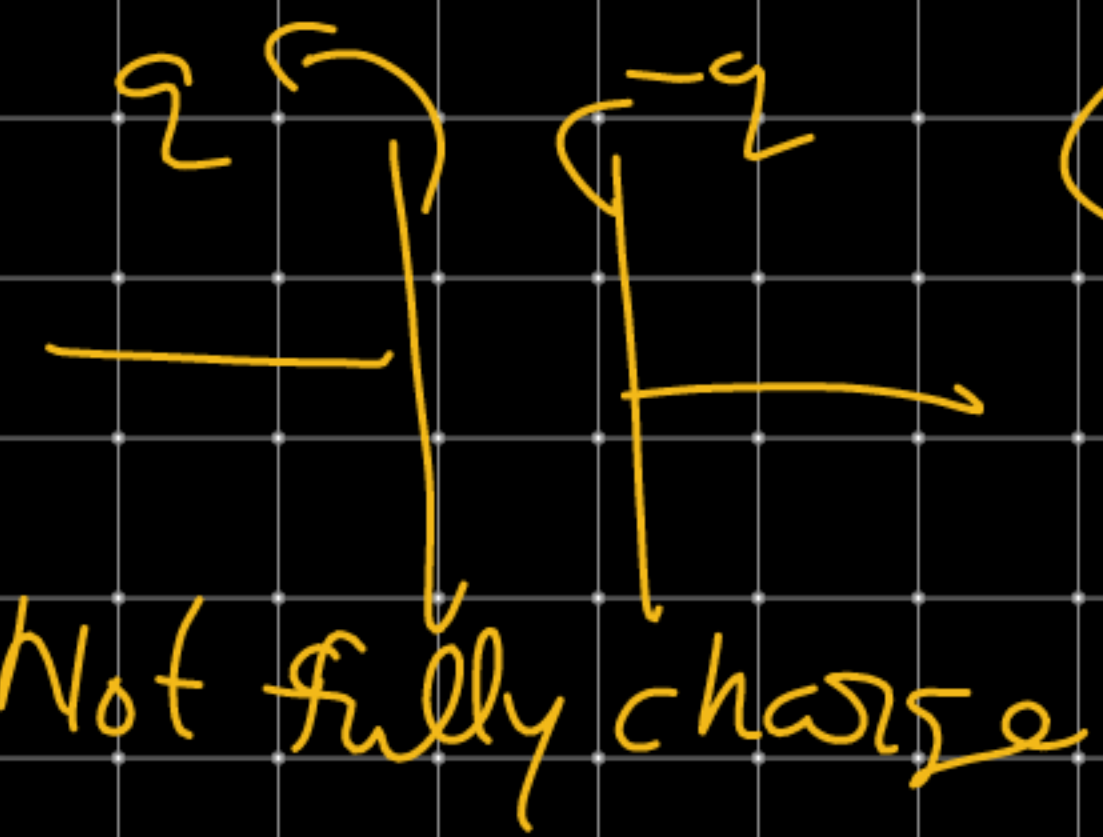

R-C circuit

$$Q = CV(1 - e^{-t/RC})$$

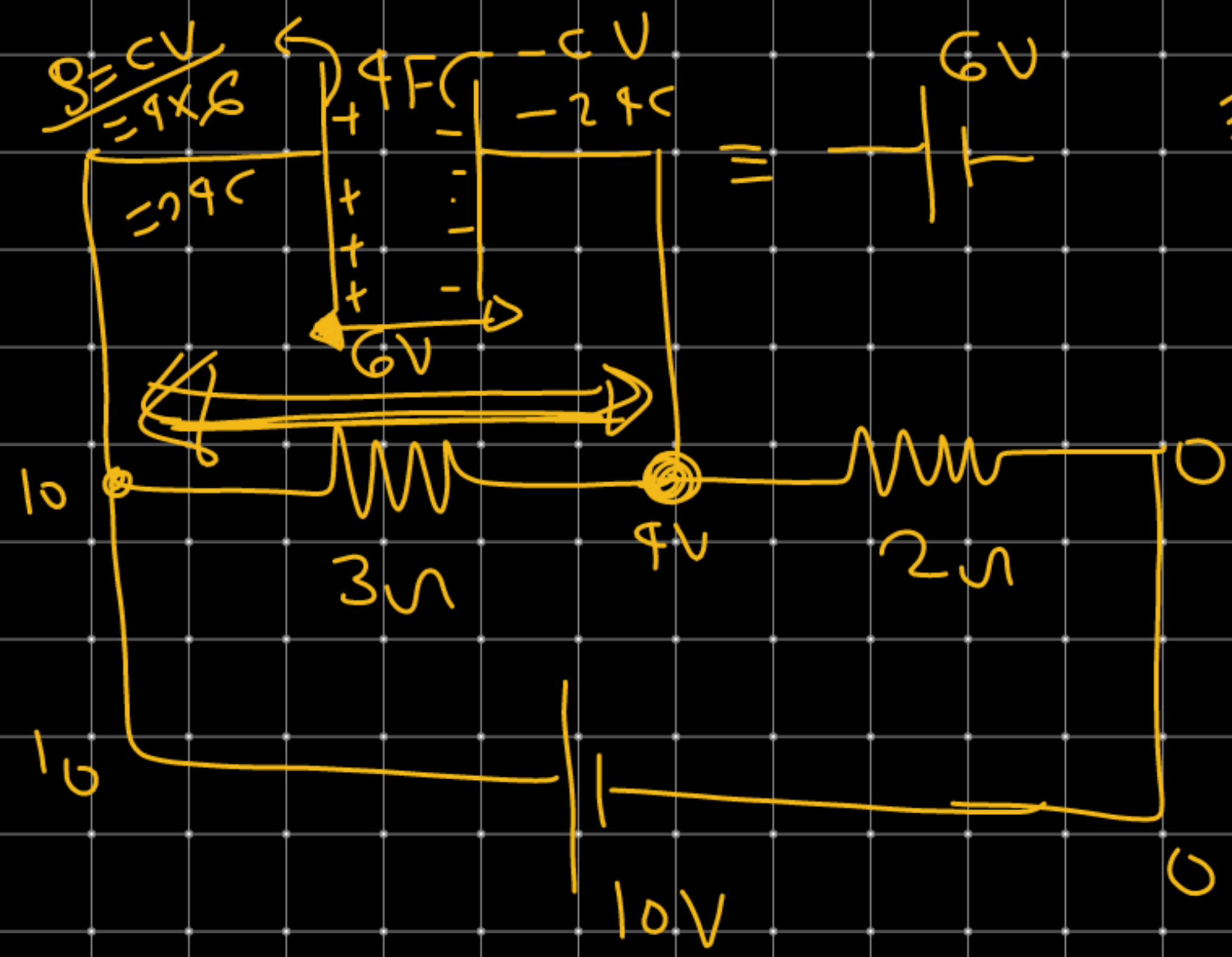

At Steady State charge on Capacitor [Steady state $t = \infty$]

↳ How to solve

