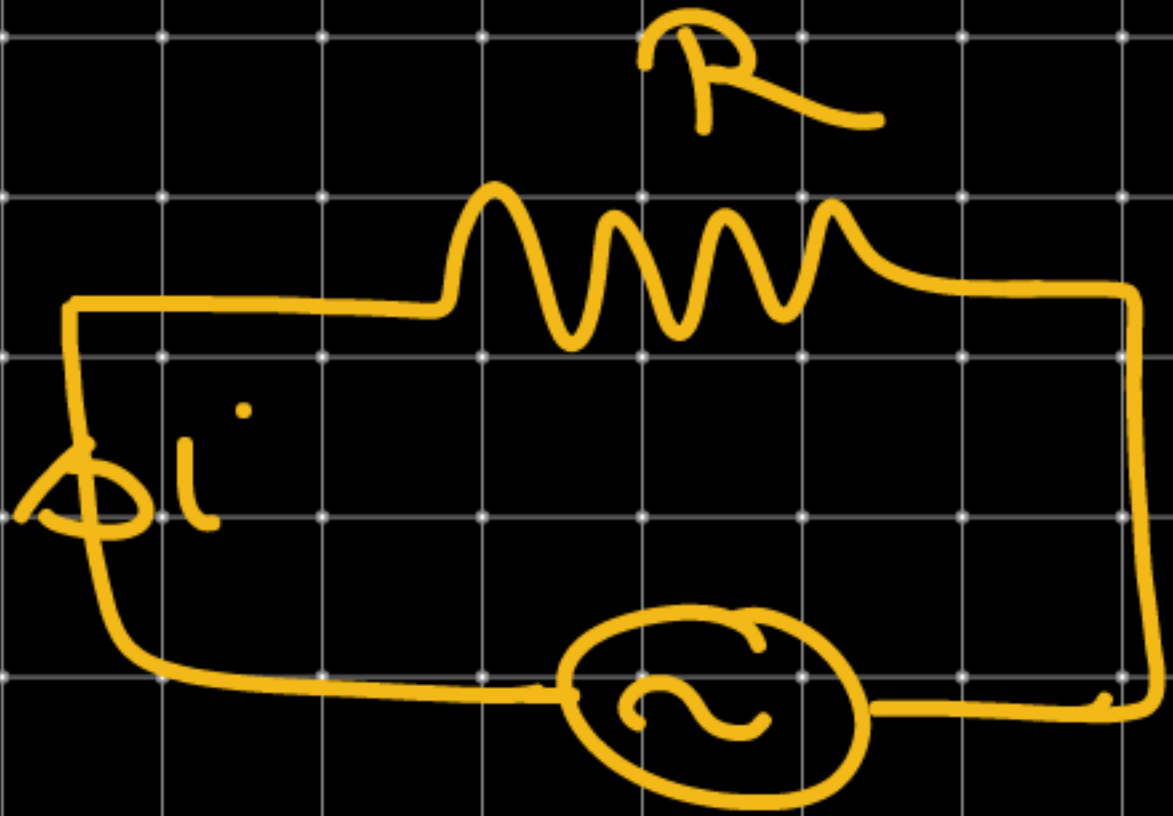


↳ **AC**

→ When AC source connect with R





$\epsilon = \epsilon_0 \sin \omega t$

Phase diff b/w ϵ & i


$i = i_0 \sin \omega t$

$i = i_0 \sin \omega t$

$i_0 = \frac{\epsilon_0}{R}$

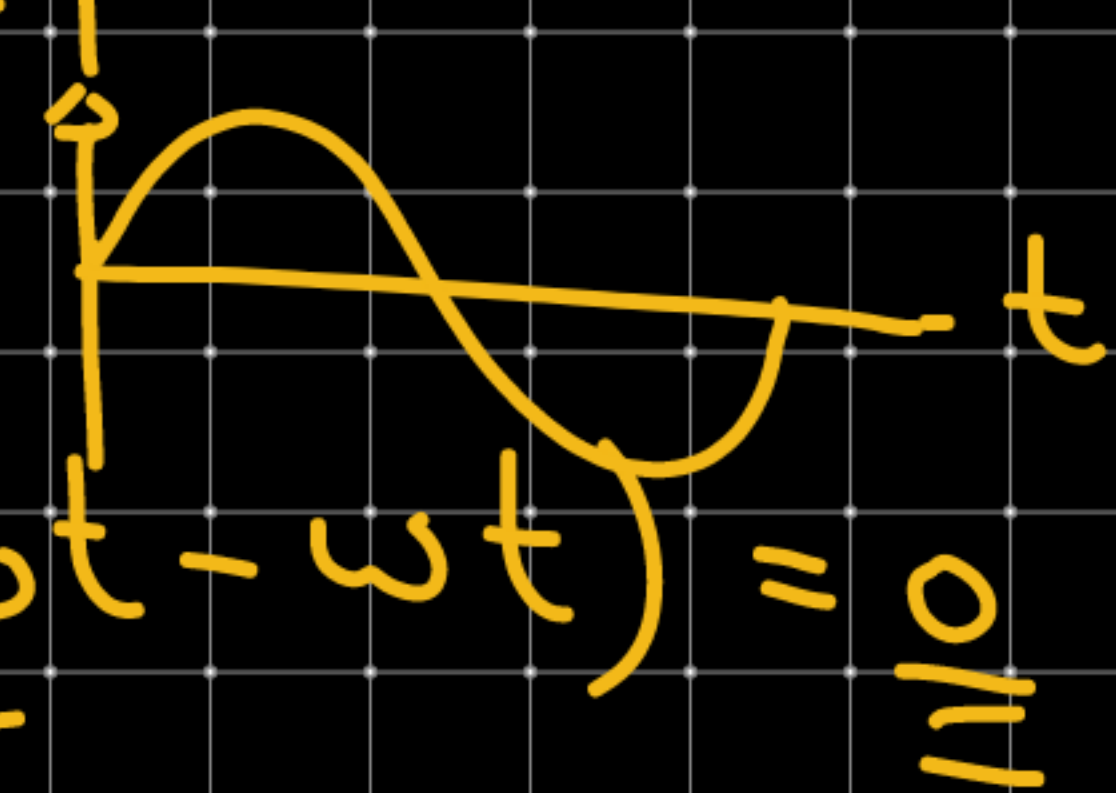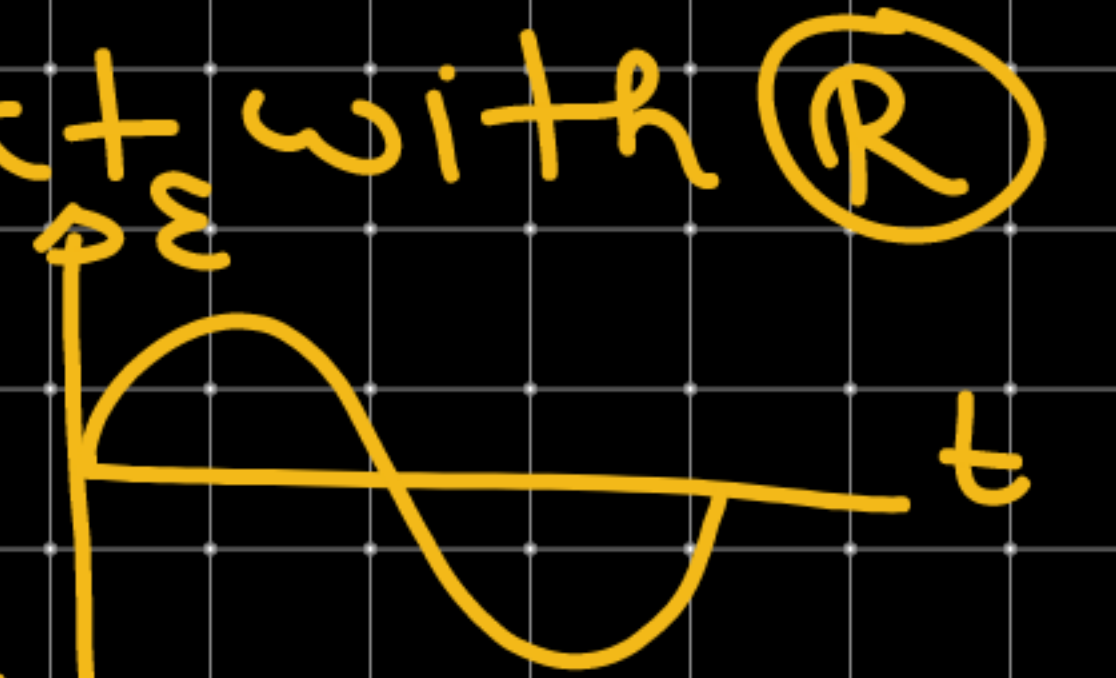


$\phi = (\omega t - \omega t) = 0$

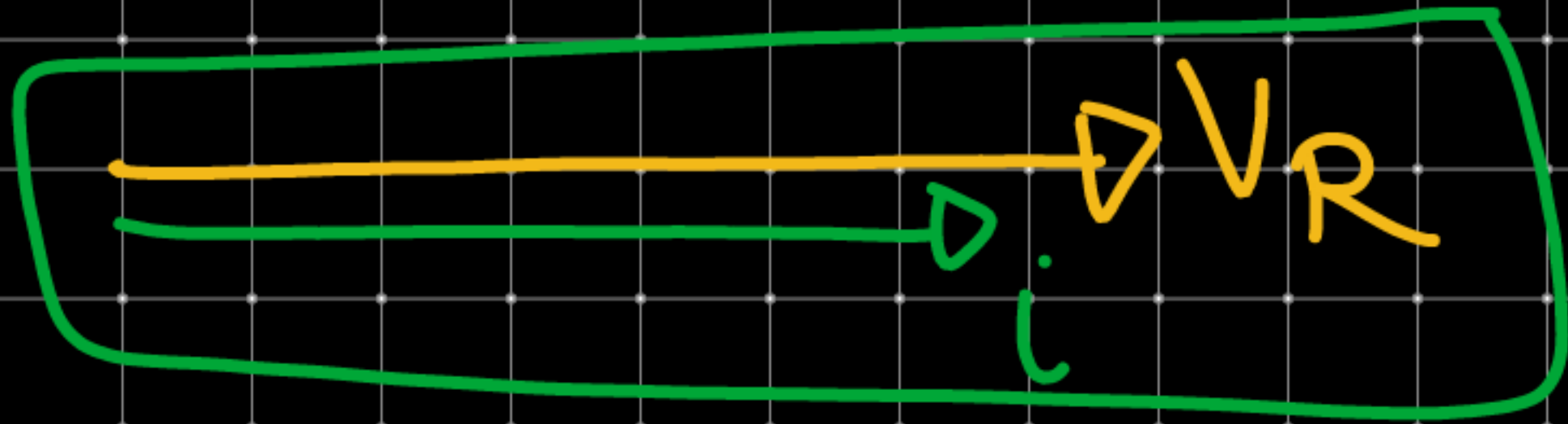

\bar{I}_m \textcircled{R}

\bar{E} \bar{f}_0
in same
Phase

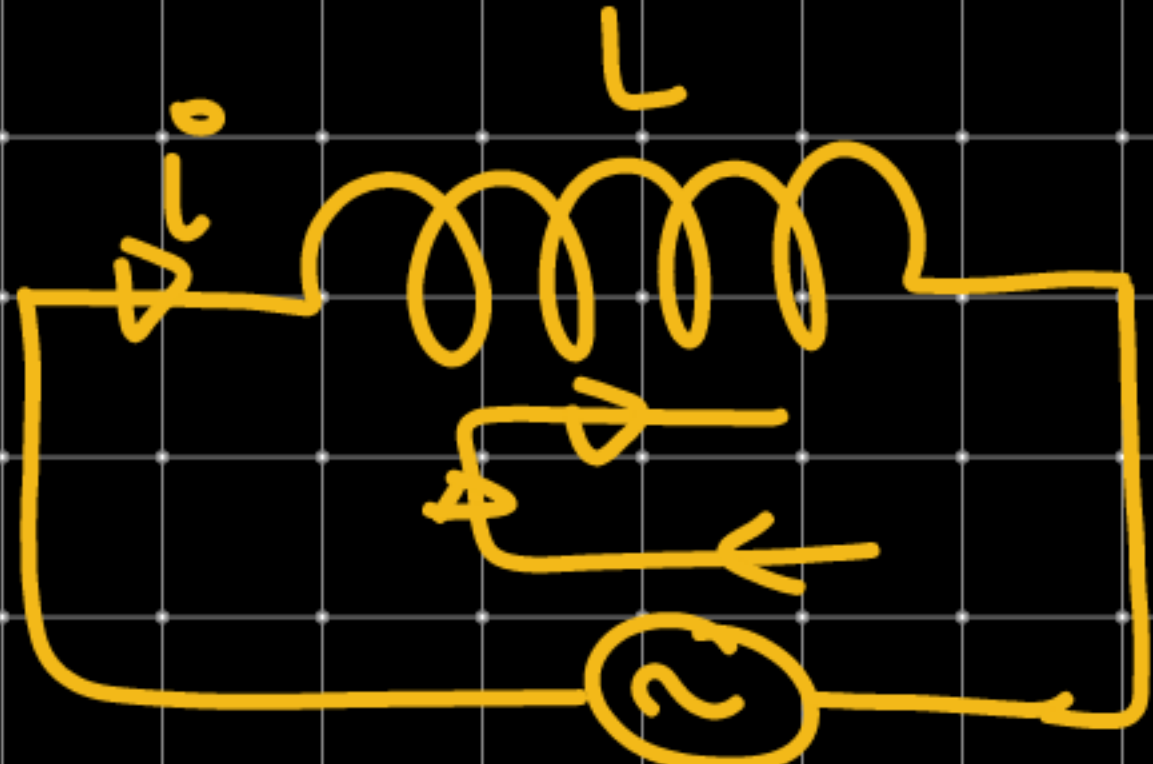When AC Source connect with pure Inductor:-



(KVL) $\varepsilon_0 \sin \omega t - L \frac{di}{dt} = 0$

$\varepsilon_0 \sin \omega t = L \frac{di}{dt}$

$\frac{di}{dt} = \frac{\varepsilon_0}{L} \sin \omega t$


$\sin 90^\circ - 0 = \cos 0$
 $-\sin 0 = \sin(-0)$

$\varepsilon = \varepsilon_0 \sin \omega t$ $\int di = \frac{\varepsilon_0}{L} \int \sin \omega t dt$

$i = \frac{\varepsilon_0}{\omega L} [-\cos \omega t] = \frac{\varepsilon_0}{\omega L} [-\cos \omega t] = \frac{\varepsilon_0}{\omega L} \left[-\sin\left(\frac{\pi}{2} - \omega t\right) \right]$

$i = \frac{\varepsilon_0}{\omega L} \left[\sin\left(\omega t - \frac{\pi}{2}\right) \right]$

$i = I_0 \sin(\omega t + \phi)$

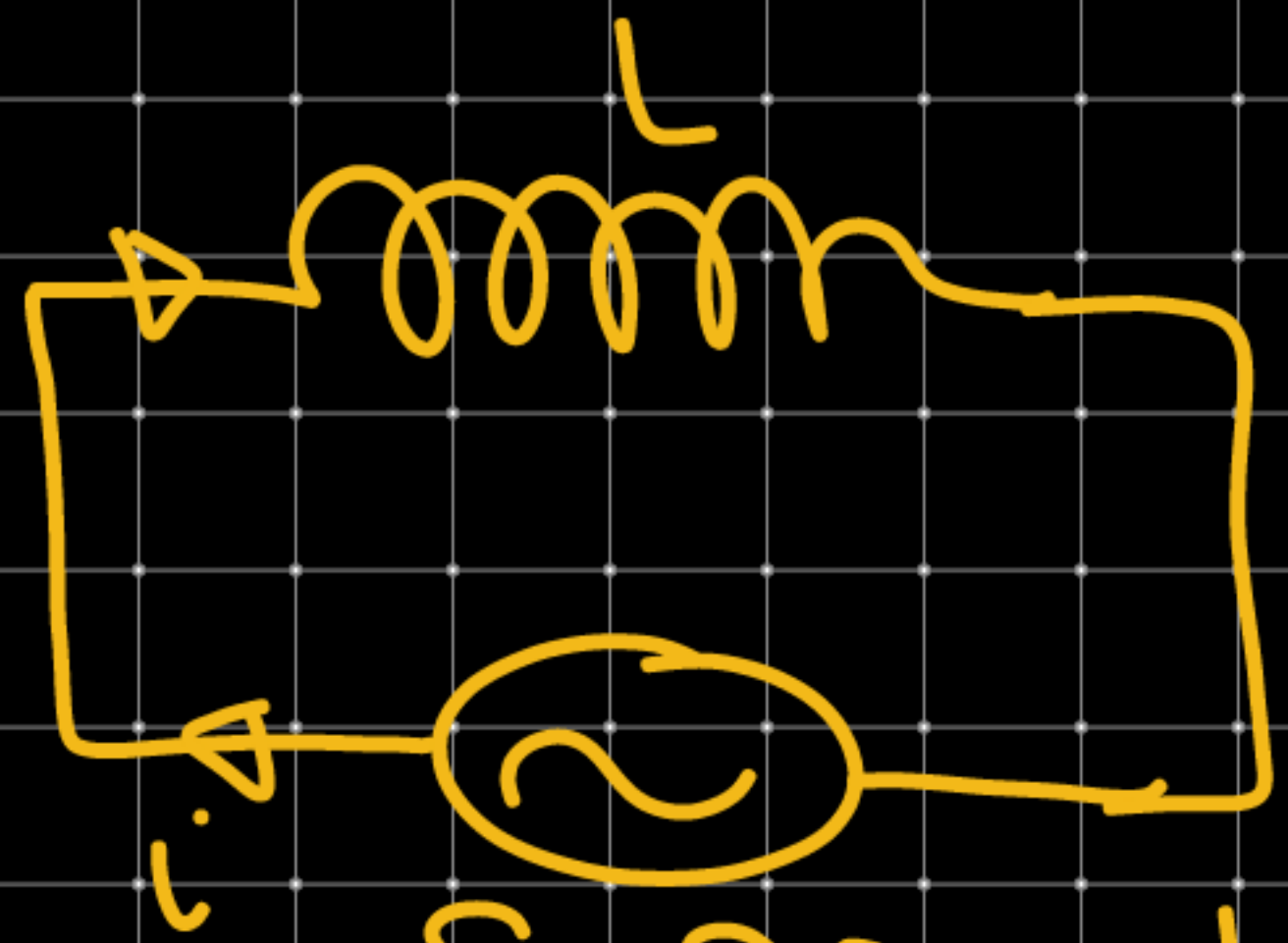

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$i = \frac{\varepsilon_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$i = i_0 \sin(\omega t + \phi)$$

$$\omega L = X_L$$

L Inductive reactance


SI unit = Ω .

$$\omega = 2\pi f$$

$$X_L = 2\pi f L$$


Phase diff b/w ε & i is $\left(\frac{\pi}{2}\right)$
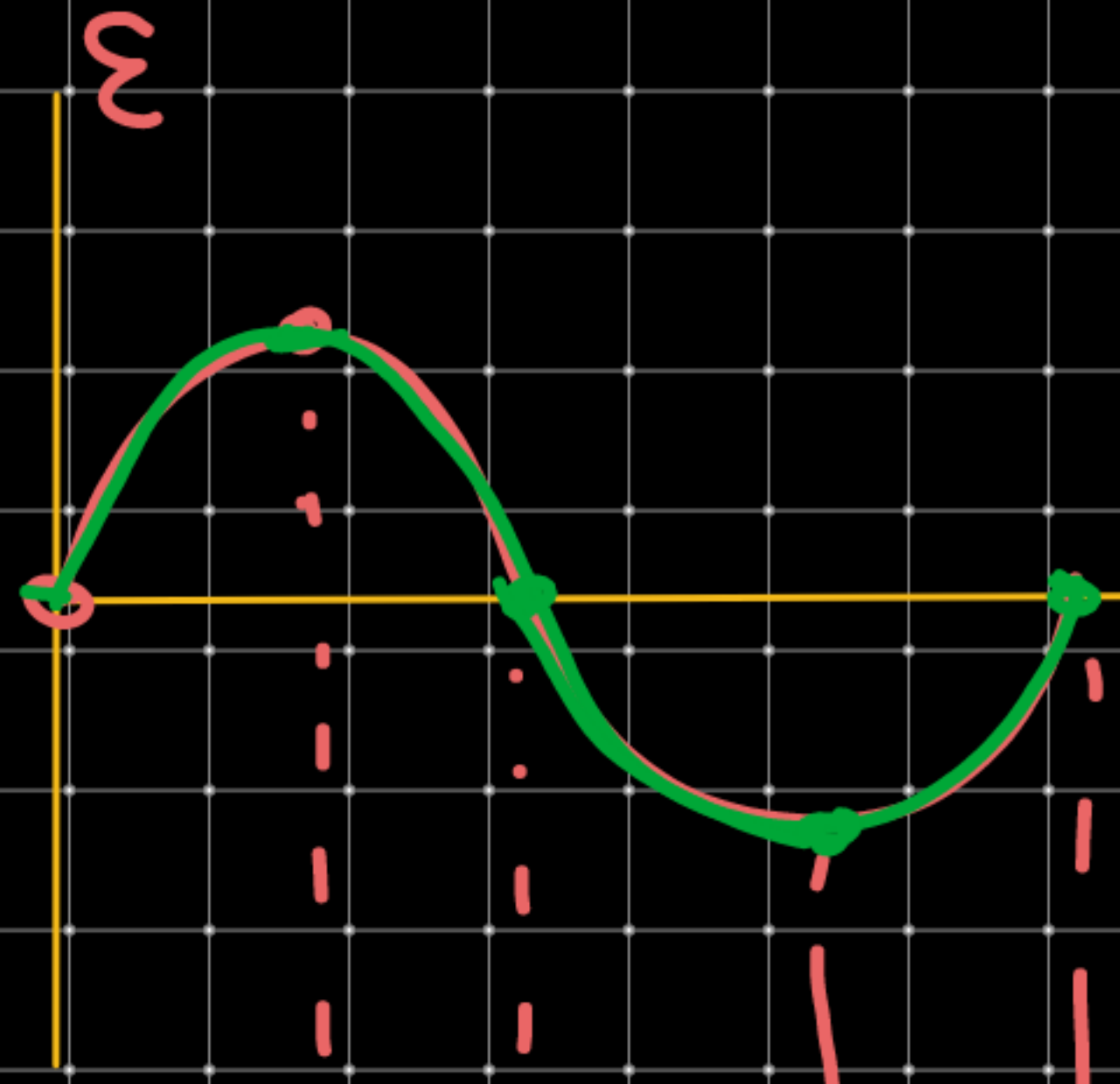
$$\left[(\omega t) - \left(\omega t - \frac{\pi}{2}\right) \right] = \frac{\pi}{2}$$



$$\underline{\epsilon = \epsilon_0 \sin \omega t}$$

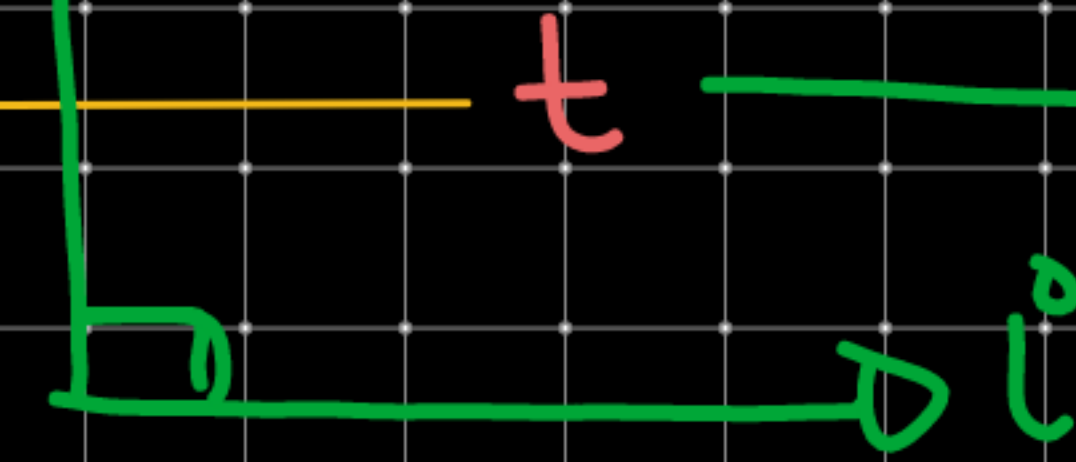
ϕv_L \hookrightarrow L lag $\frac{\pi}{2}$ with ϵ .



$$\underline{i = I_0 \sin(\omega t - \frac{\pi}{2})}$$


$$\underline{t = 0}$$
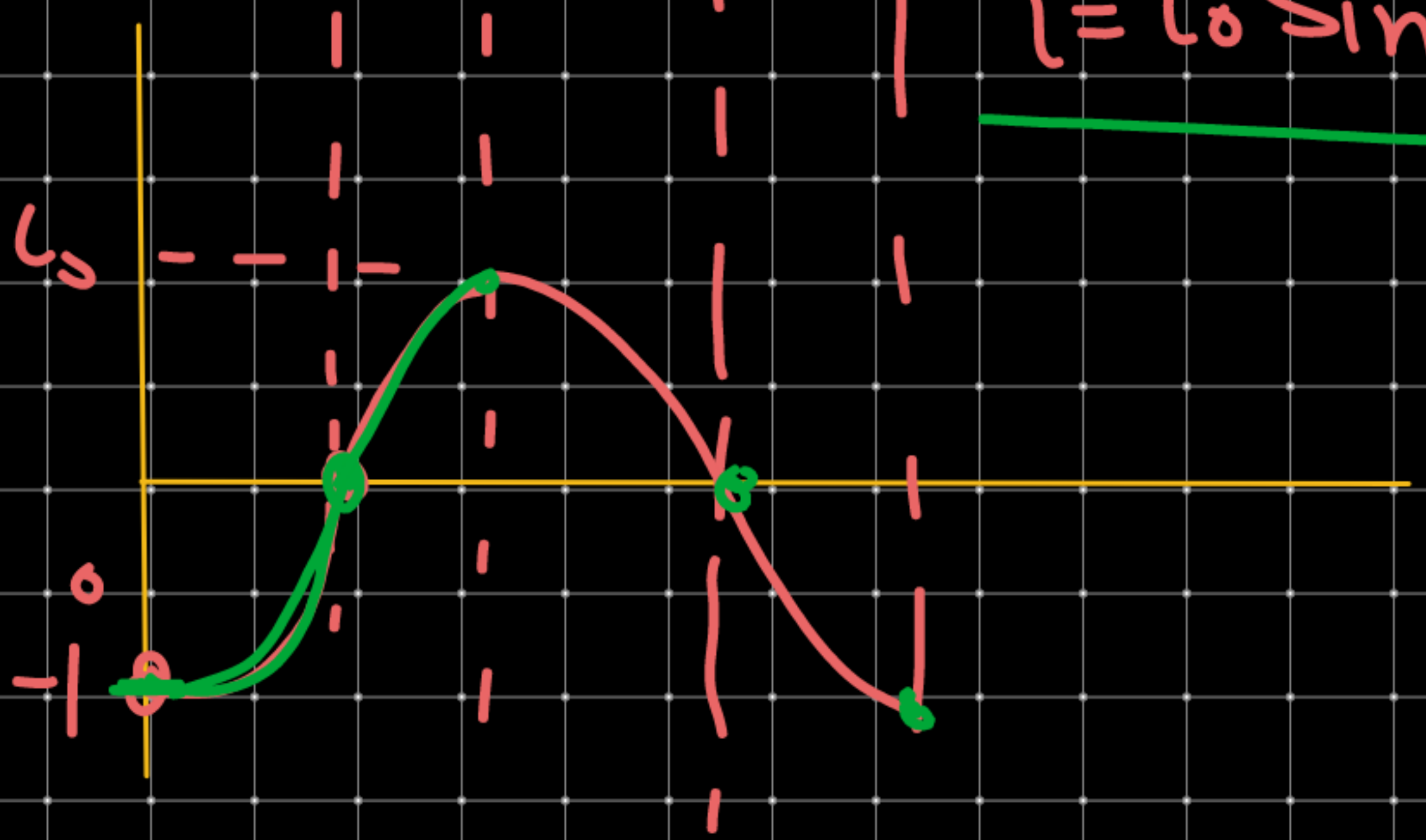
$$\begin{aligned} i &= I_0 \sin\left(\frac{\pi}{2}\right) \\ &= -I_0 \sin\frac{\pi}{2} \\ &= -I_0 \end{aligned}$$





→ AC Source connect with pure Capacitor

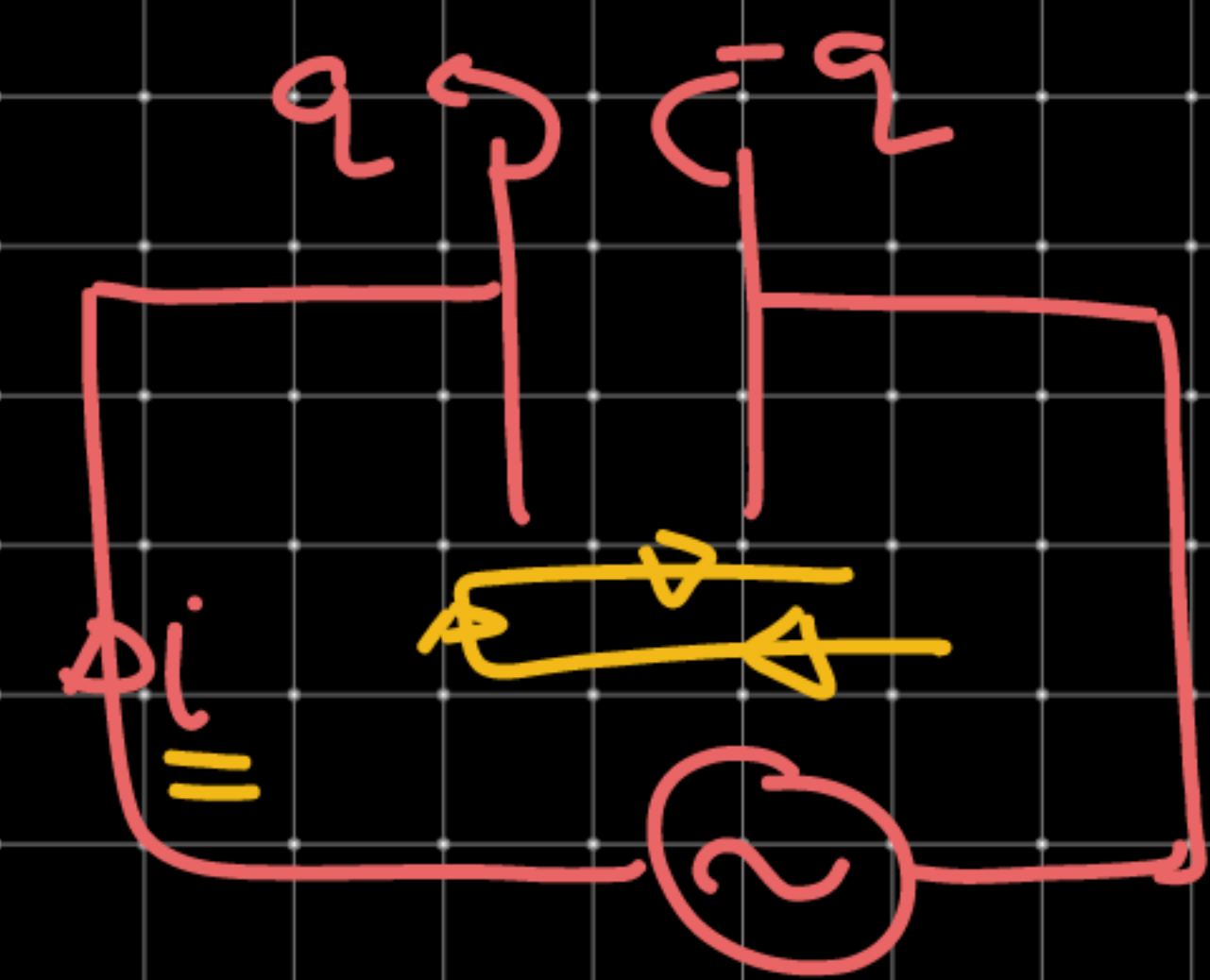

$$\epsilon_0 \sin \omega t - \frac{q}{C} = 0$$

$$\frac{q}{C} = \epsilon_0 \sin \omega t$$

$$q = C \epsilon_0 \sin \omega t$$

$$\frac{dq}{dt} = i = \frac{d}{dt} (C \epsilon_0 \sin \omega t)$$

$$i = C \epsilon_0 \cos \omega t \times \omega$$

$$i = C \omega \epsilon_0 \cos \omega t$$


$$i = \frac{\epsilon_0}{\omega C} \sin\left(\frac{\pi}{2} + \omega t\right)$$

$$abc = \frac{c}{\frac{2}{ab}}$$

$$\cos 0 = \sin\left(\frac{\pi}{2} + 0\right)$$

$$\epsilon = \epsilon_0 \sin \omega t$$

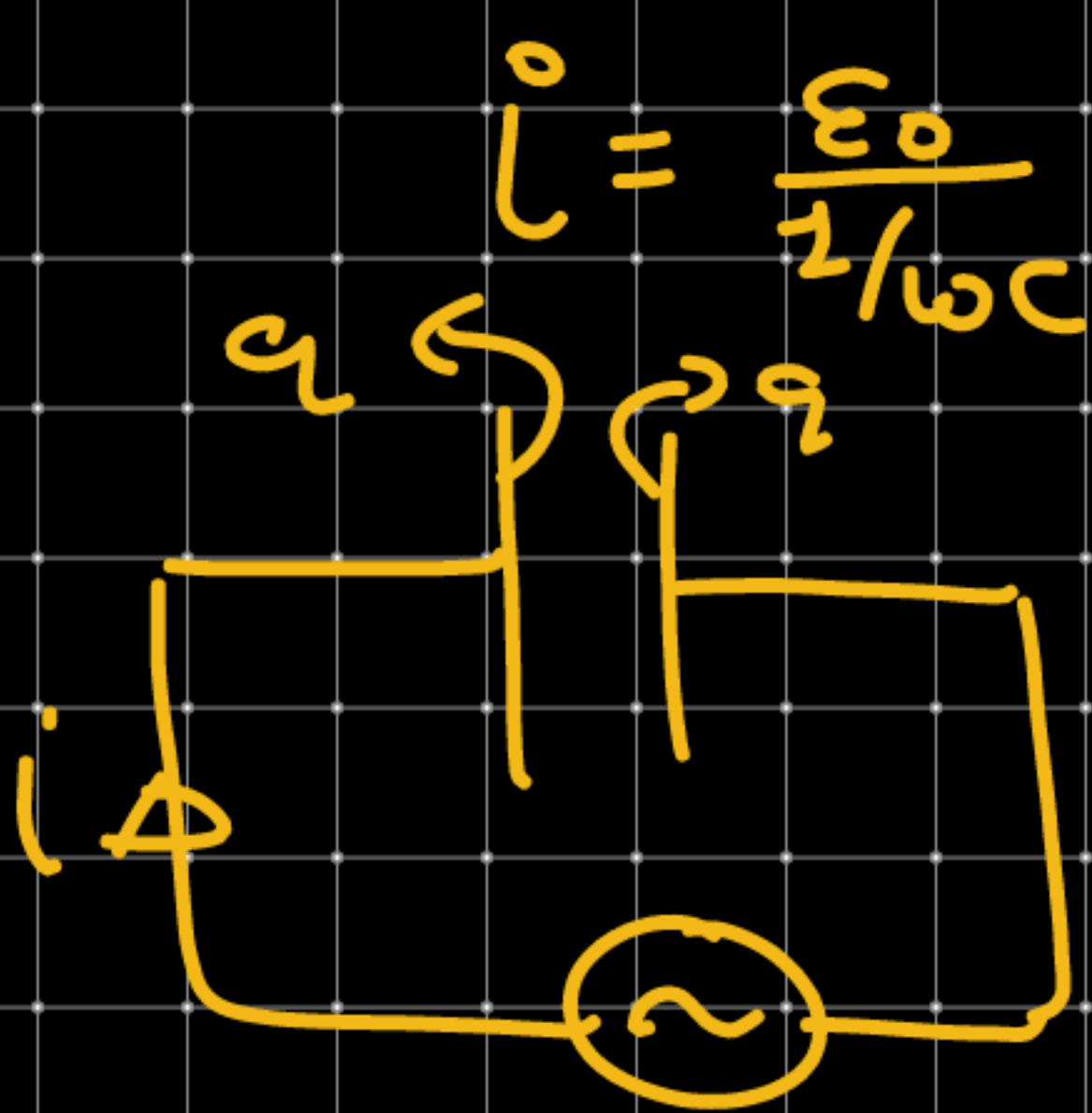$\frac{1}{\omega C} = X_C$
 Capacitive reactance
 Unit Ω



$$i = \frac{\varepsilon_0}{2/\omega C}$$

$$\sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = \frac{\varepsilon_0}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$E = E_0 \sin \omega t$$

$E = E_0 \sin \omega t$ Phase diff b/w i & $E = \frac{\pi}{2}$

i lead $\frac{\pi}{2}$ with E .


$$\mathcal{E} = E_0 \sin \omega t$$



$$i = \frac{E_0}{Z/\omega C} \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

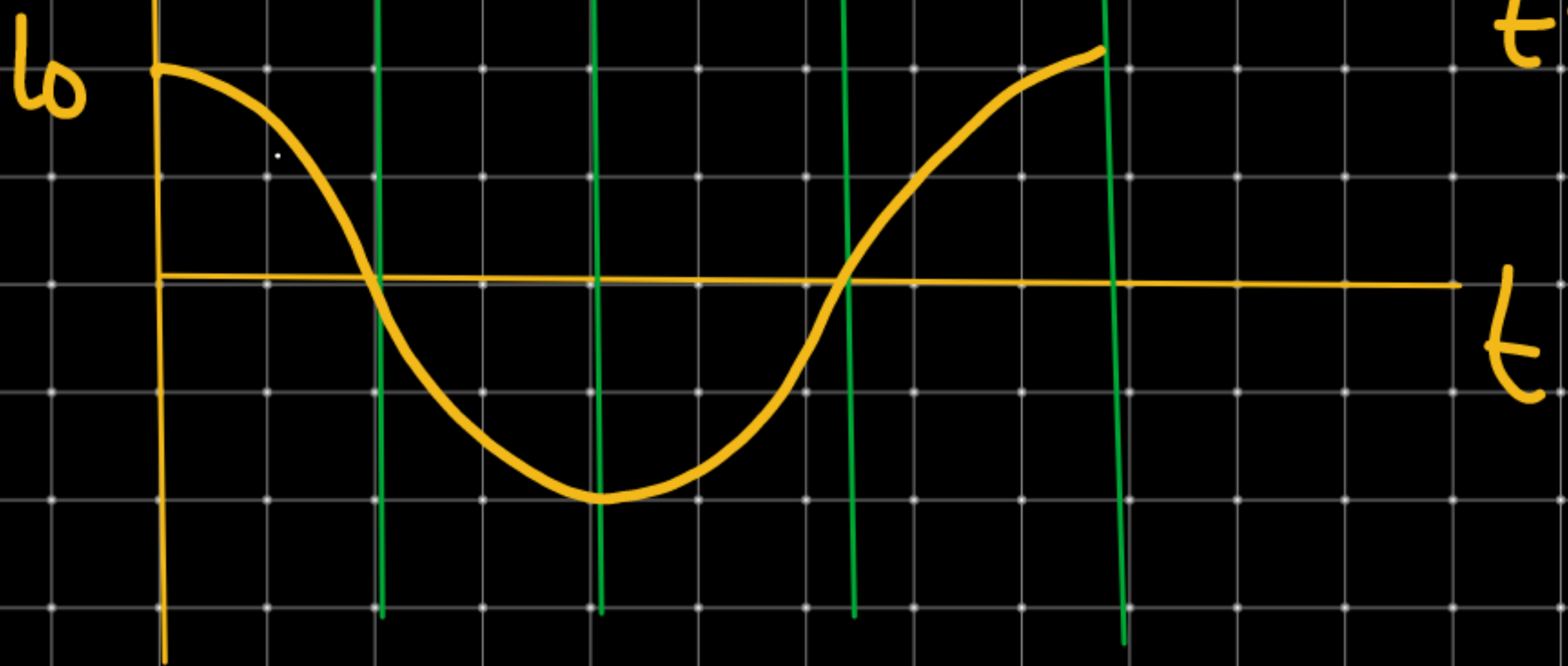
$$I_0 = \frac{E_0}{X_C} = \frac{E_0}{Z/\omega C}$$



$$t = 0$$

$$i = I_0 \sin \frac{\pi}{2}$$

$$I = I_0$$

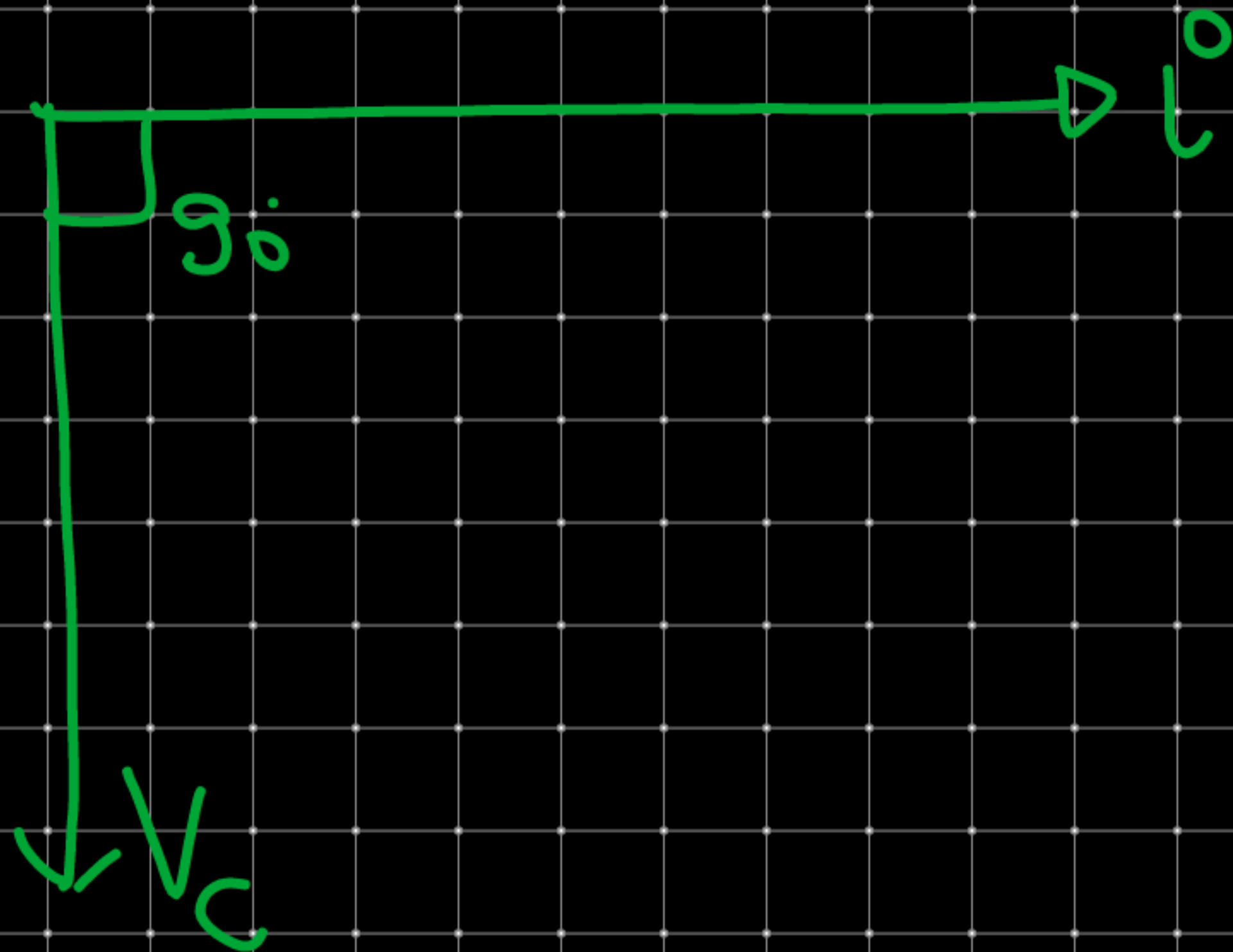


i_0 — lead $\frac{\pi}{2}$ with
 v_c



graph

$X_L = \omega L$

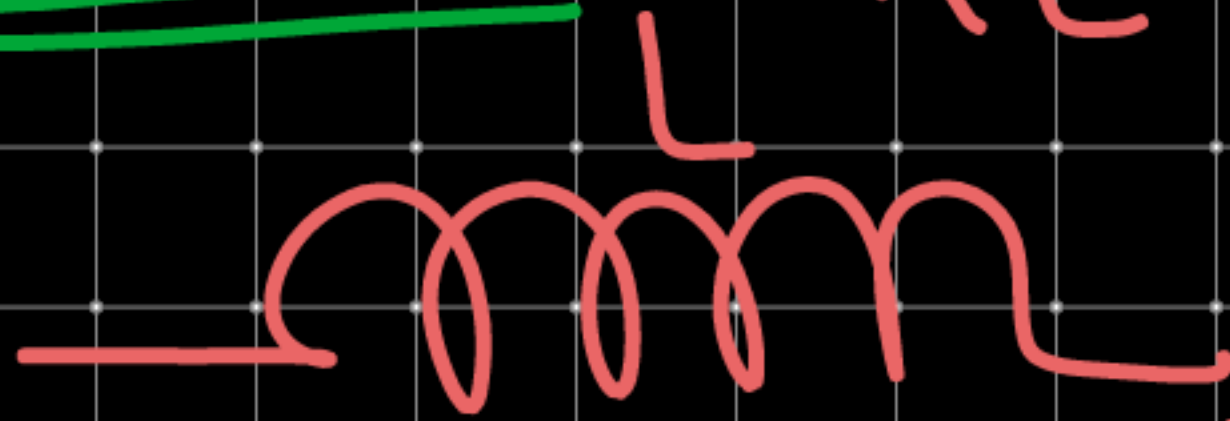

$X_L \rightarrow$ Inductive reactance.

X_L (V/s) frequency (f)

$X_L = \omega L$


$X_L = 2\pi f L$

$(\omega = 2\pi f)$

$X_L = (2\pi L) f$

$Y = mX$

ΔX_L

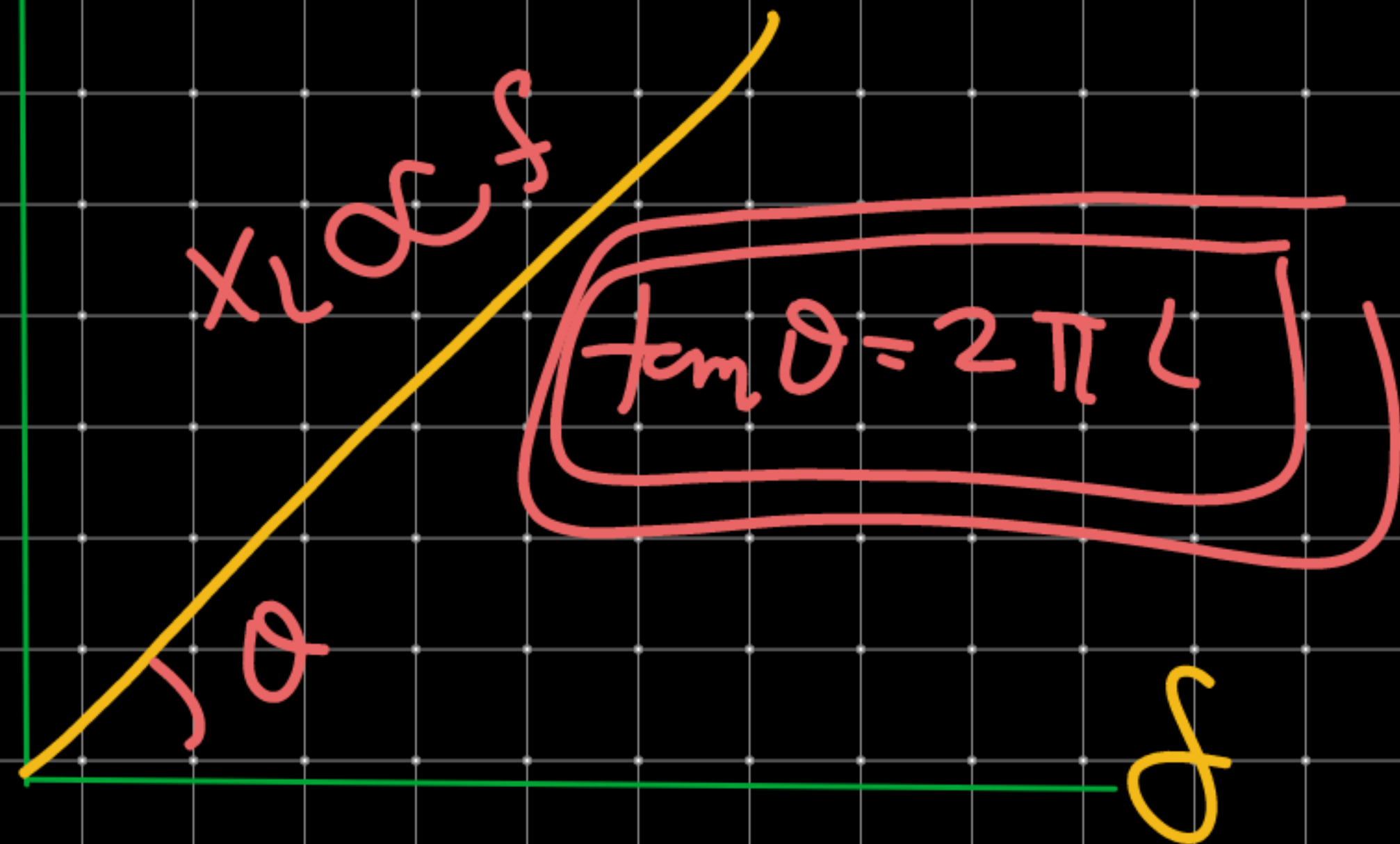

⇒ $X_C = \text{Capacitive reactance}$





$$X_C = \frac{1}{\omega C} \Rightarrow$$

$$X_C = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{(2\pi C) f}$$

$X_C \propto \frac{1}{f}$

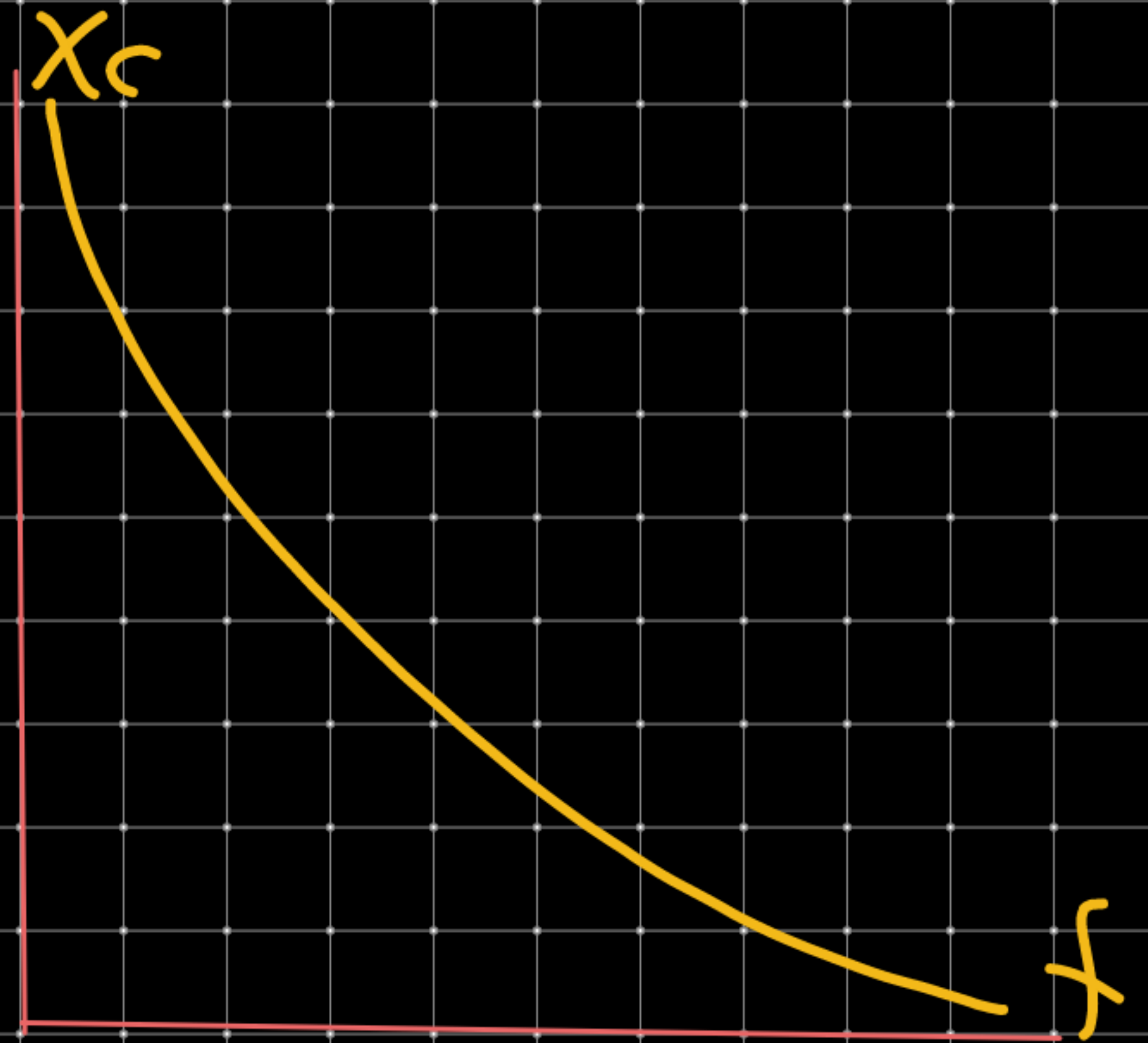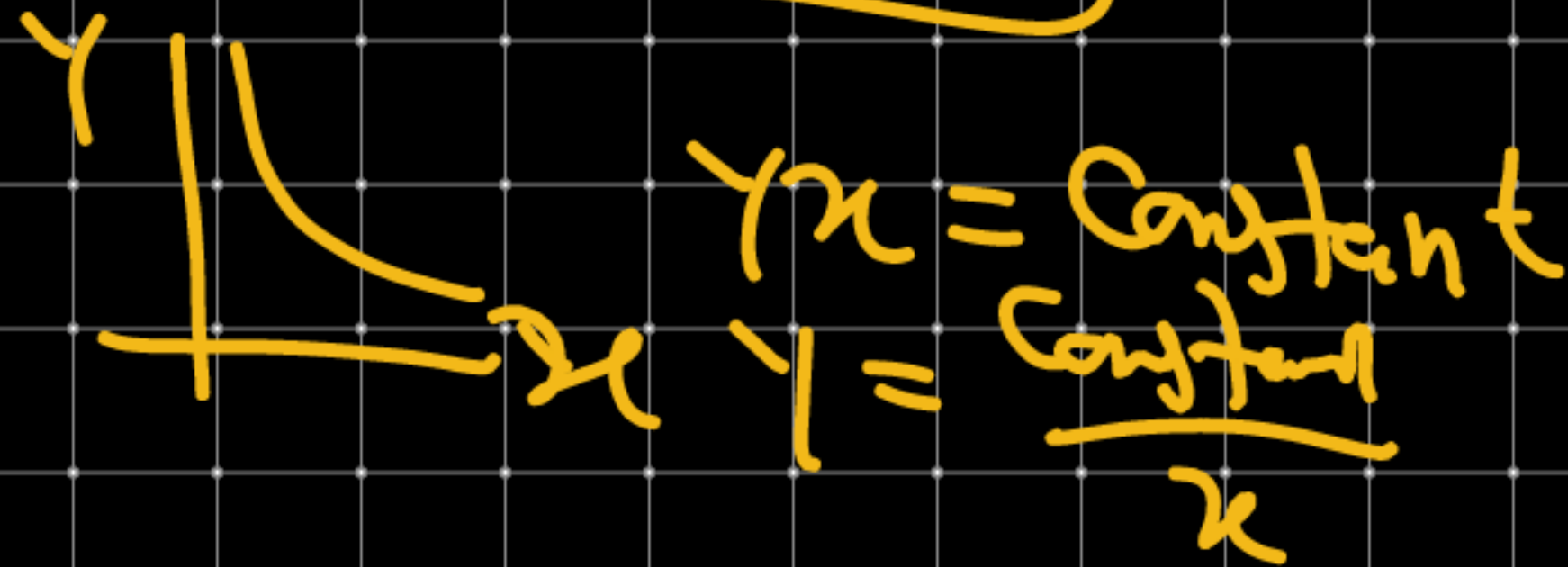$X_C \propto \frac{1}{f} \Rightarrow f \propto \frac{1}{X_C}$




$\Rightarrow \Rightarrow R \rightarrow$ does not depend on frequency of source.

$$R = \frac{\Delta V}{\Delta I}$$

$$X_L = 2\pi f L$$
$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$


$$X_C = \frac{1}{2\pi f C}$$

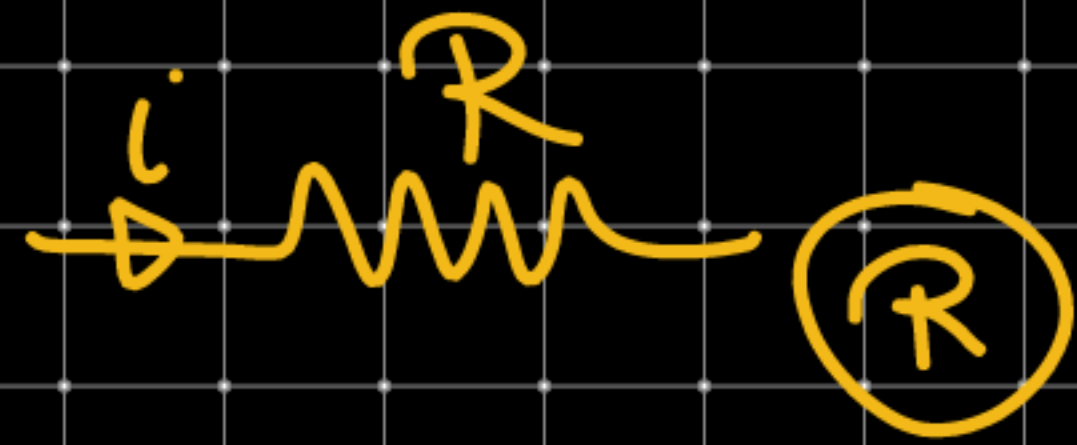

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i = i_0 \sin \omega t$$


$$\Delta \phi = 0$$

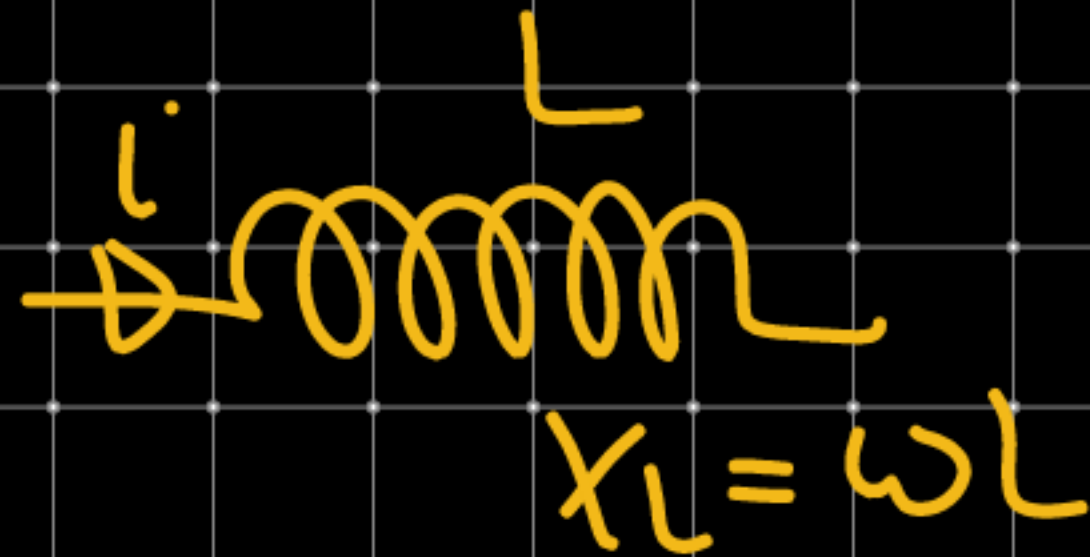

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right) \quad \Delta \phi = \frac{\pi}{2}$$

i lag $\frac{\pi}{2}$ with \mathcal{E}

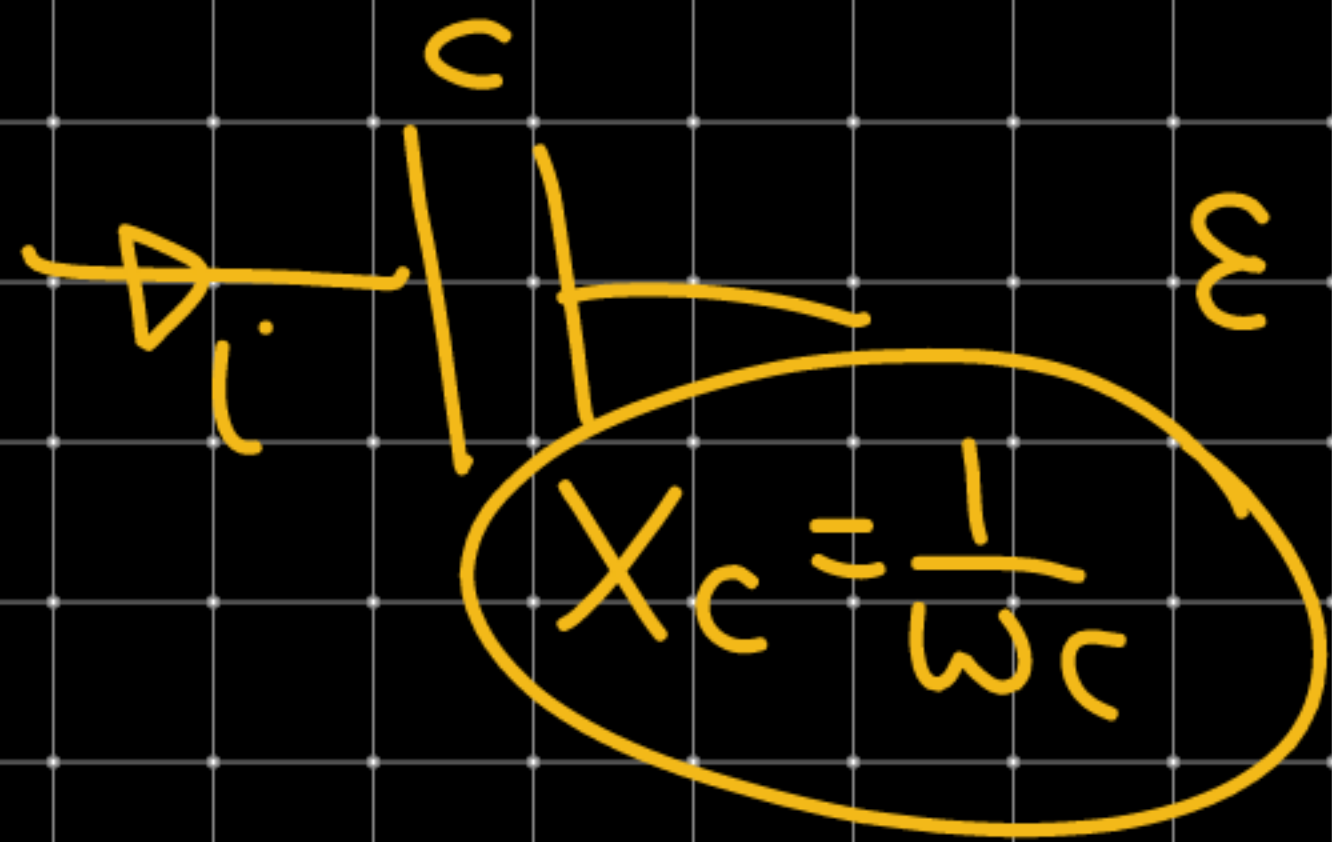


$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$


$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right) \quad \Delta \phi = \frac{\pi}{2}$$

i lead with \mathcal{E} by $\frac{\pi}{2}$

L-C-R with AC Source.

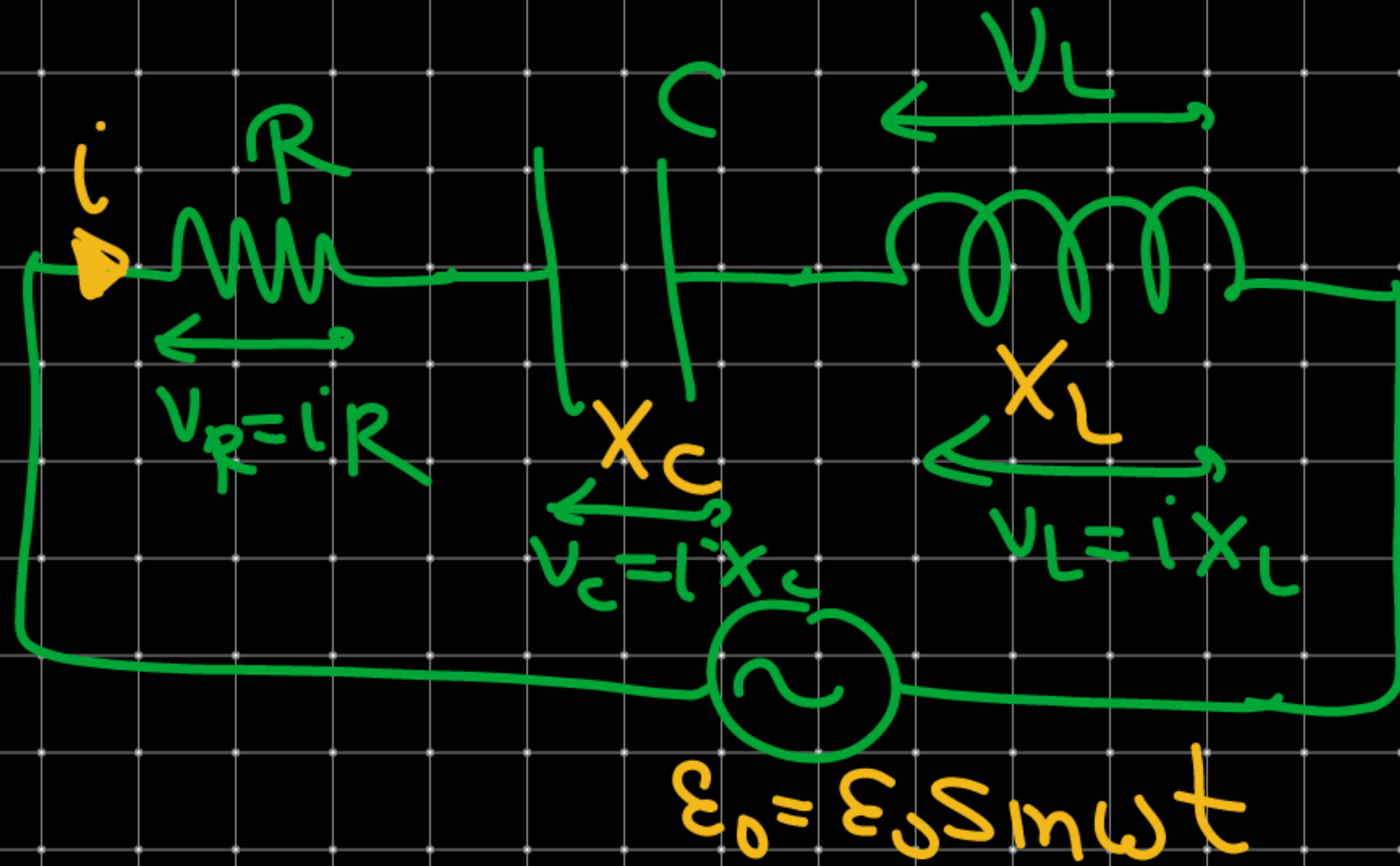
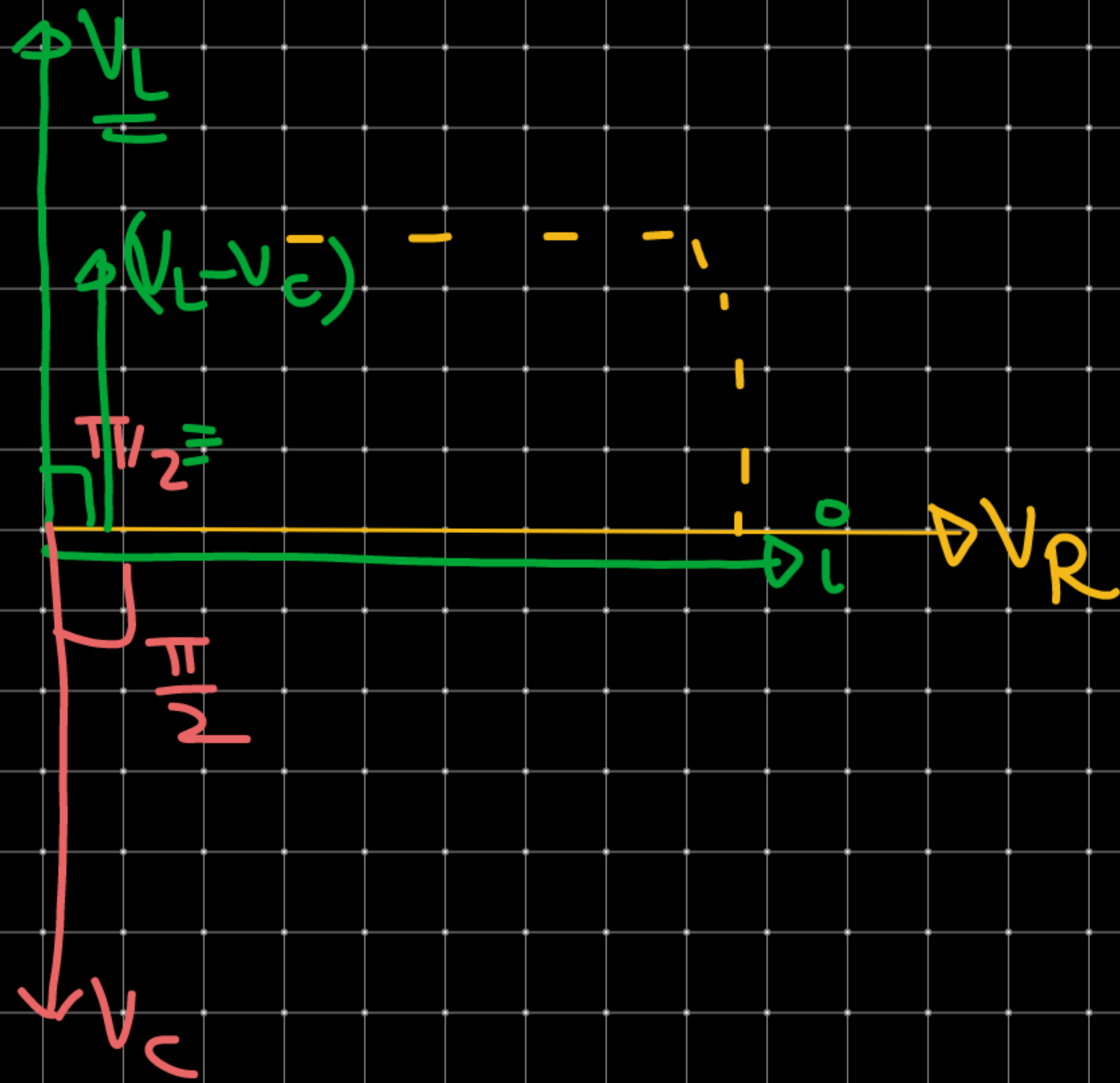
$$X_C = \frac{1}{\omega C}$$
$$X_L = \omega L$$



R

$$\begin{cases} \varepsilon = \varepsilon_0 \sin \omega t \\ i = i_0 \sin \omega t \\ \Delta \phi = 0 \end{cases}$$


L

$$\begin{cases} \varepsilon = \varepsilon_0 \sin \omega t \\ i = i_0 \sin(\omega t - \frac{\pi}{2}) \\ i \text{ lags by } \frac{\pi}{2} \end{cases}$$

C

$$\begin{cases} \varepsilon = \varepsilon_0 \sin \omega t \\ i = i_0 \sin(\omega t + \frac{\pi}{2}) \\ i \text{ leads by } \frac{\pi}{2} \end{cases}$$

If $V_L > V_C$

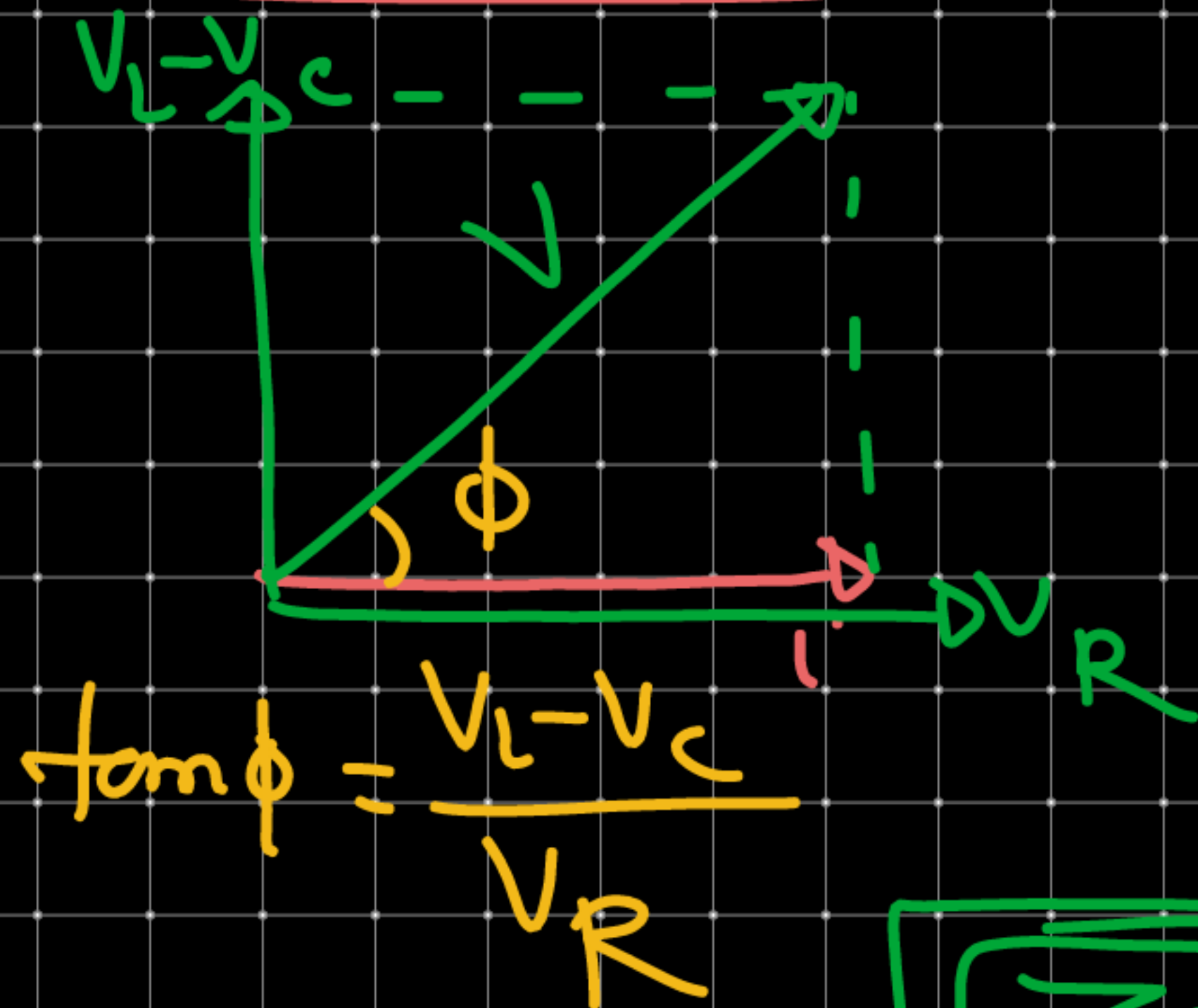

$$\tan \phi = \frac{V_L - V_C}{V_R}$$


$$V_{net} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$i = \frac{V}{Z} = \frac{V_R}{Z} = \frac{V_L - V_C}{Z}$$

$$iZ = \sqrt{R^2 + (X_L - X_C)^2}$$

$$iZ = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

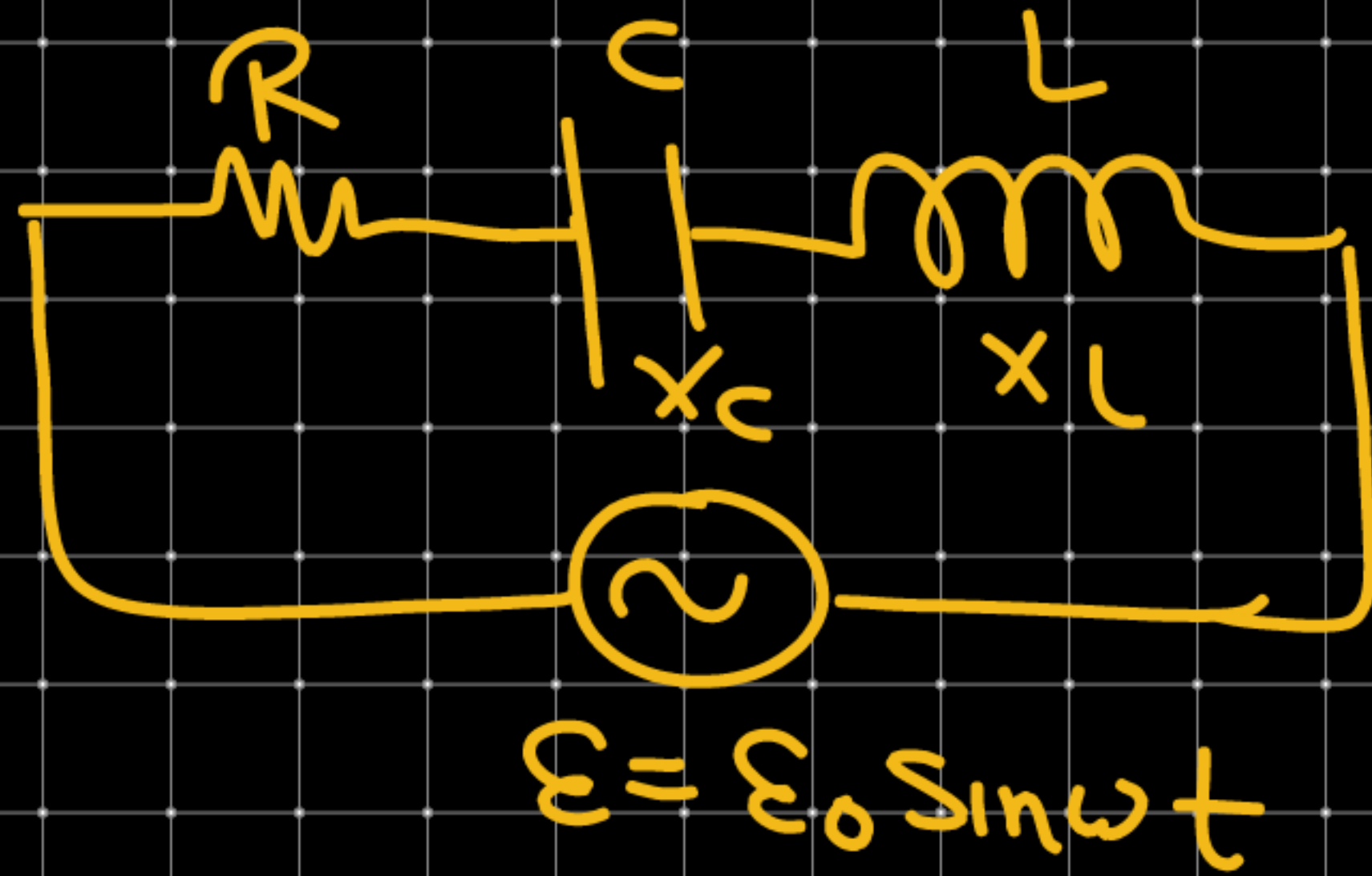

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance

\Downarrow

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{iX_L - iX_C}{iR}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

Find impedance of given L-C-R circuit



$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{4^2 + (9 - 16)^2} \\ &= \sqrt{16 + 49} = \sqrt{65} \Omega \end{aligned}$$

|||

In L-C-R ckt with an ac source

$$R = 300\Omega \quad C = 20\mu F, \quad L = 1H, \quad f = \frac{50}{\pi} \text{ Hz}$$

find Z & I_{rms} if $(E_{rms} = 50V)$

Soln) L-C-R

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$R = 300\Omega$$

$$\underline{X_L = 100\Omega}$$

$$Z = \sqrt{(300)^2 + (100 - 500)^2}$$

$$X_L = \omega L = 2\pi fL$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

$$\boxed{Z = 500\Omega}$$

$$= 2\pi \times \frac{50}{\pi} \times 1$$

$$= \underline{100\Omega}$$

$$X_C = \frac{1}{2\pi \times \frac{50}{\pi} \times 2 \times 10^{-5}}$$

$$= \frac{1}{100 \times 2 \times 10^{-5}} = \frac{1000}{2}$$

$$\underline{X_C = 500\Omega}$$

Time taken by current to its rms value to


$$\omega = 2\pi f$$

$$= 2\pi \times 50$$

$$= 100\pi$$


$$R = 40\Omega$$

$$220V, 50Hz$$

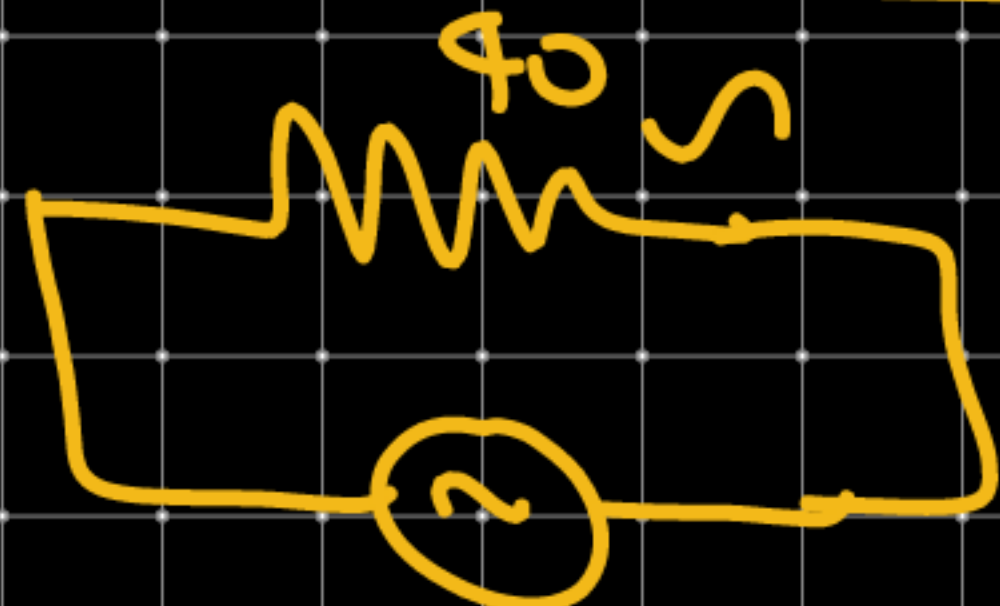

$$E = E_0 \sin \omega t$$

$$E_{rms} = \frac{E_0}{\sqrt{2}}$$

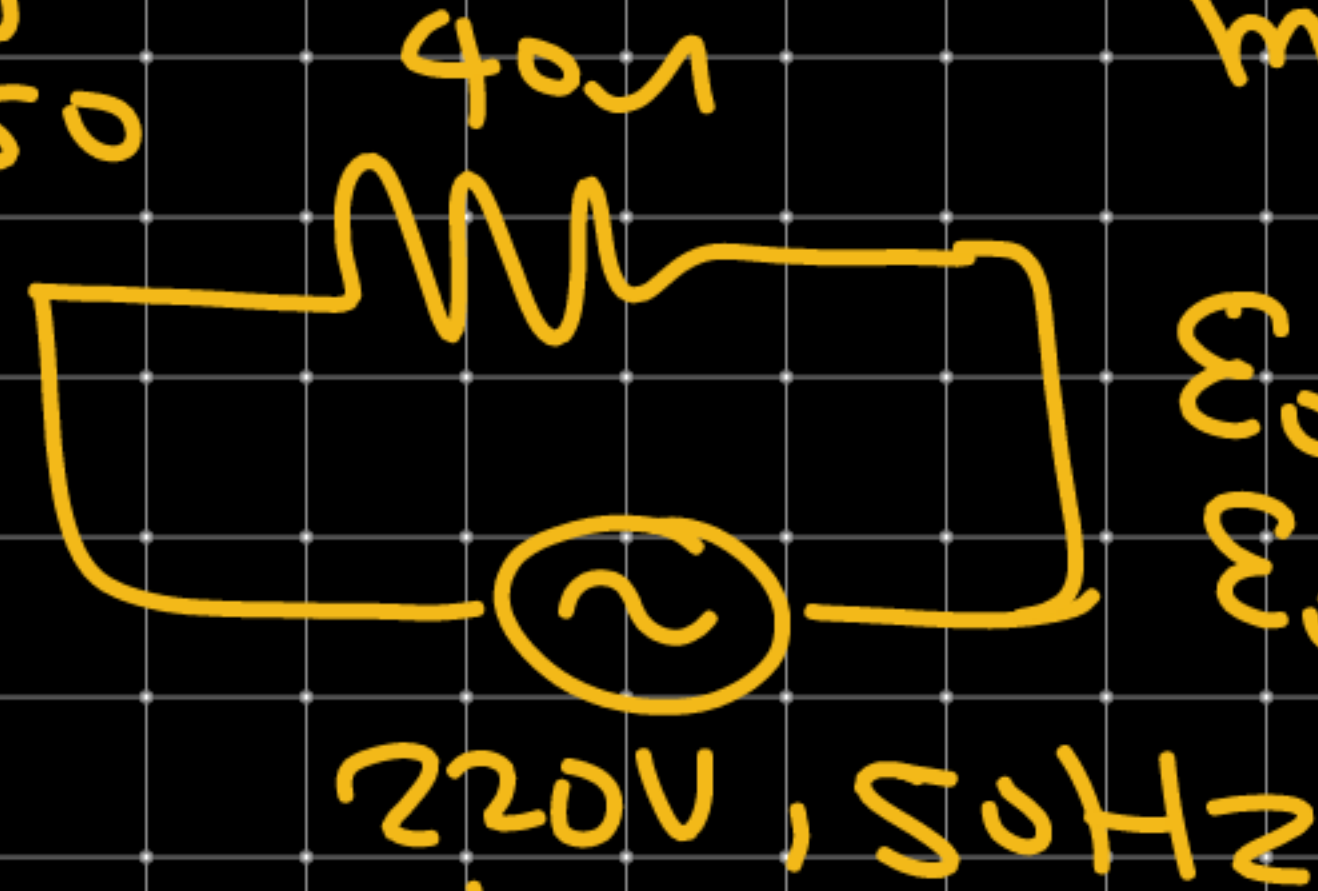

$$E = 220\sqrt{2} \sin 100\pi t$$

rms value.

max value

$$E_0 = \sqrt{2} E_{rms}$$

$$E_0 = 220\sqrt{2}$$

$$\varepsilon = \underline{220\sqrt{2}} \sin 100\pi t.$$

\Rightarrow

$$\cancel{220} = \cancel{220}\sqrt{2} \sin 100\pi t$$

$$\frac{1}{\sqrt{2}} = \sin 100\pi t$$

$$\sin \frac{\pi}{4} = \sin 100\pi t$$

$$\frac{\pi}{4} = 100\pi t \quad \text{or} \quad t = \frac{1}{500} \text{ sec}$$

$$\xi = \xi_0 \sin \omega t$$

$$\xi = 220\sqrt{2} \sin \omega t$$

\Rightarrow

$$220 = 220\sqrt{2} \sin \omega t$$

$$i_{avg} = \frac{\sum i_{avg}}{N}$$

$$i_{avg} = \frac{5\phi}{50\phi} = \frac{1}{10} = \underline{\underline{0.2 \text{ Amp}}}$$