

Q 2) The relation b/w an AC voltage source and time in SI unit $V = 120 \sin(100\pi t) \cos 100\pi t$.
 The peak value of voltage & frequency

(a) 60V & 100Hz. Sol) $E = E_0 \sin \omega t$

(b) 60V & 200Hz. $V = 120 \sin 100\pi t \cos 100\pi t$

(c) 120V & 100Hz. $= 60 \times (2 \sin 100\pi t \cdot \cos 100\pi t)$

(d) $\frac{120}{\sqrt{2}}$ & 100Hz. $V = 60 \sin 200\pi t$

Peak value $\Rightarrow V_0 = 60 \text{ Volt}$. $\omega = 200\pi$
 $V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{60}{\sqrt{2}} = 30\sqrt{2} \text{ V}$. $f = \frac{1}{T} = \frac{2\pi}{2\pi} = 100 \text{ Hz}$

$$\sin 2\theta = 2 \sin \theta \cdot \cos \theta.$$

$$\begin{aligned} \sin 2(\omega\pi t) &= 2 \sin \omega\pi t \cos \omega\pi t \\ &= \sin 2\omega\pi t. \end{aligned}$$

Q2) $I = I_0 \cos \omega t$ find I_{avg} & I_0 .

ABLES[®] KOTA

Sol $I = I_0 \sin \omega t$

$$I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$I_{\text{peak}} = I_0$$


$$I_{\text{avg}} = \frac{I_0}{\sqrt{2}}$$

$$\cos \omega t = \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$\sin(90^\circ - 0) = \cos 0$$

$$\sin\left(\frac{\pi}{2} - \omega t\right) = \cos \omega t$$

Q3)

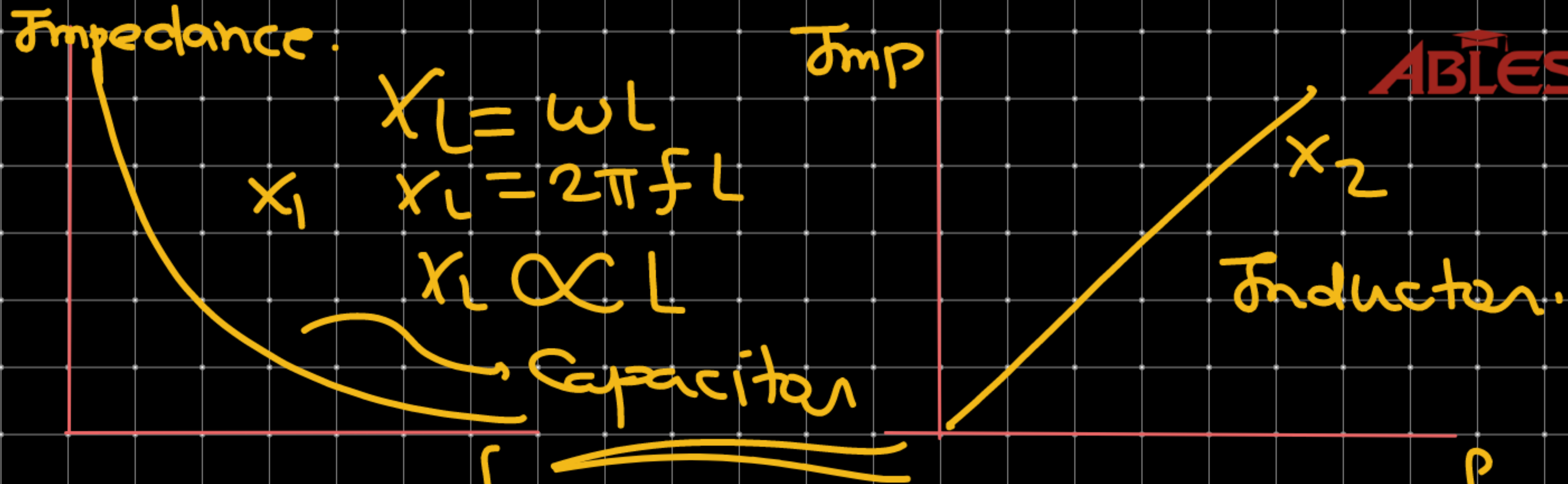

(a) X_1 is Capacitor & X_2 is Inductor.


(b) X_2 is " " X_1 " " .

(c) X_1 is Inductor & X_2 is Capacitor.

(d) N.O.T.

$$X_L = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_C \propto \frac{1}{f}$$

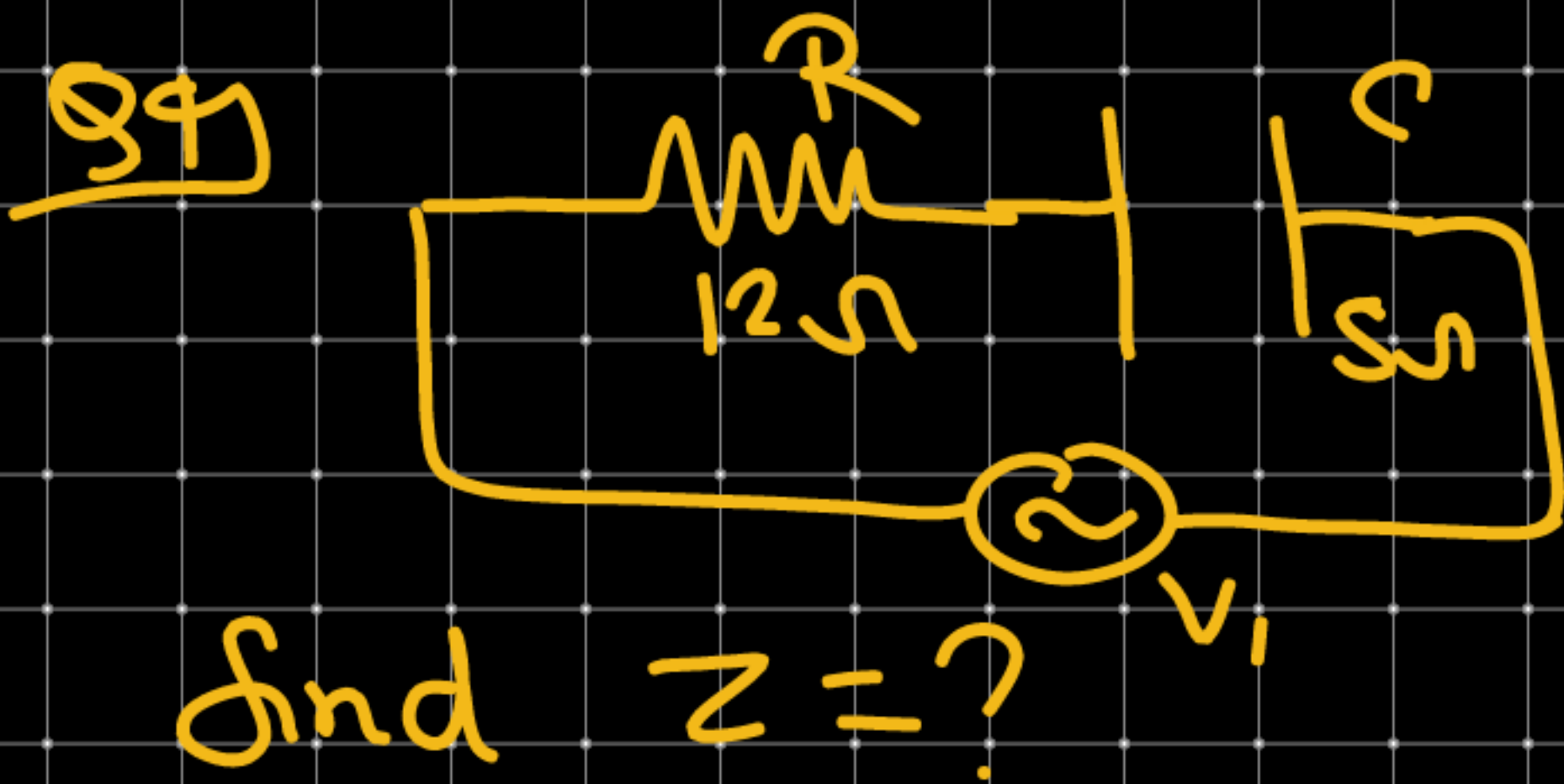

$$X_L = 0$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(12)^2 + (0 - 5)^2}$$

$$= \sqrt{144 + 25}$$

$$= \sqrt{169}$$

$$= 13\Omega$$


|||

(a) 13Ω ✓

(b) $\sqrt{119}\Omega$

(c) 6Ω


(d) 8Ω

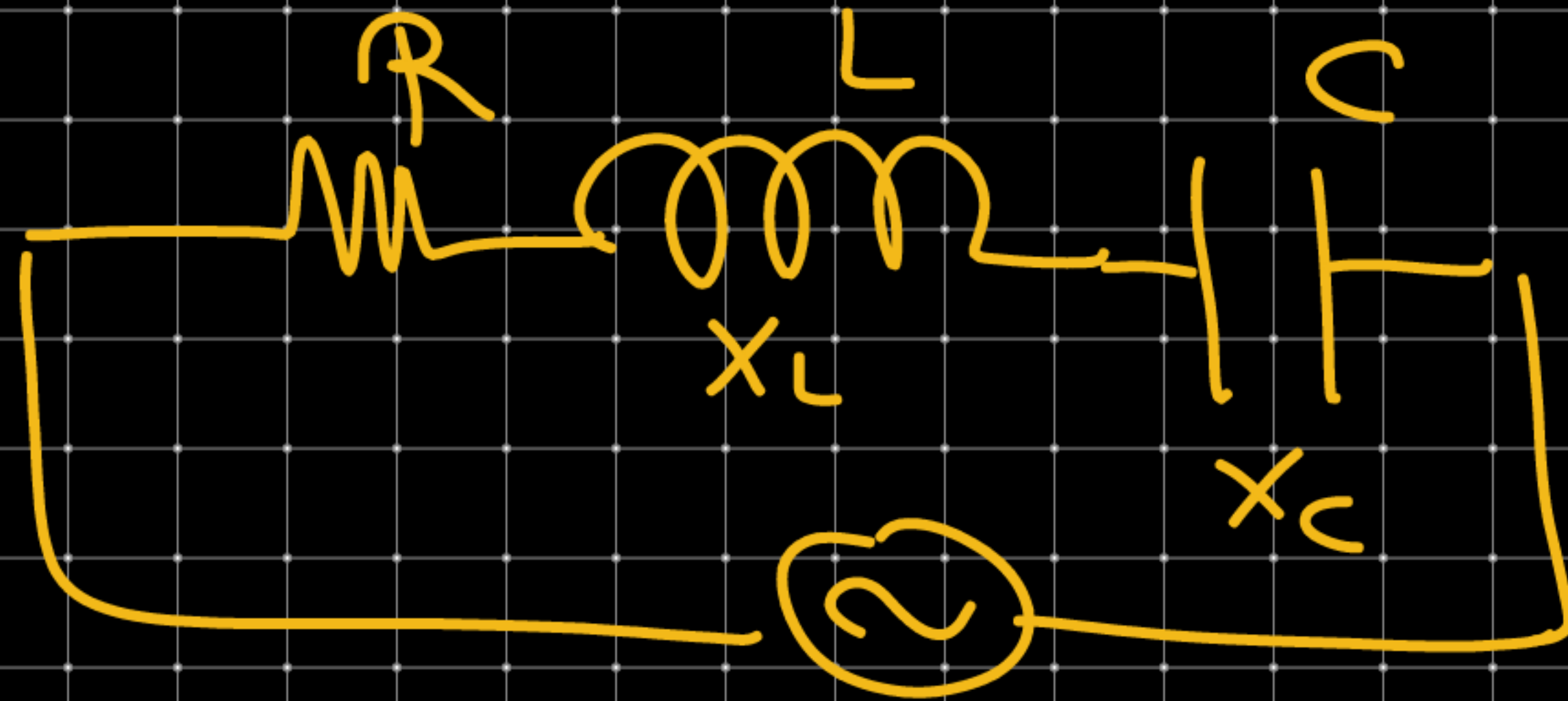

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$Z \rightarrow$ Impedance

95)

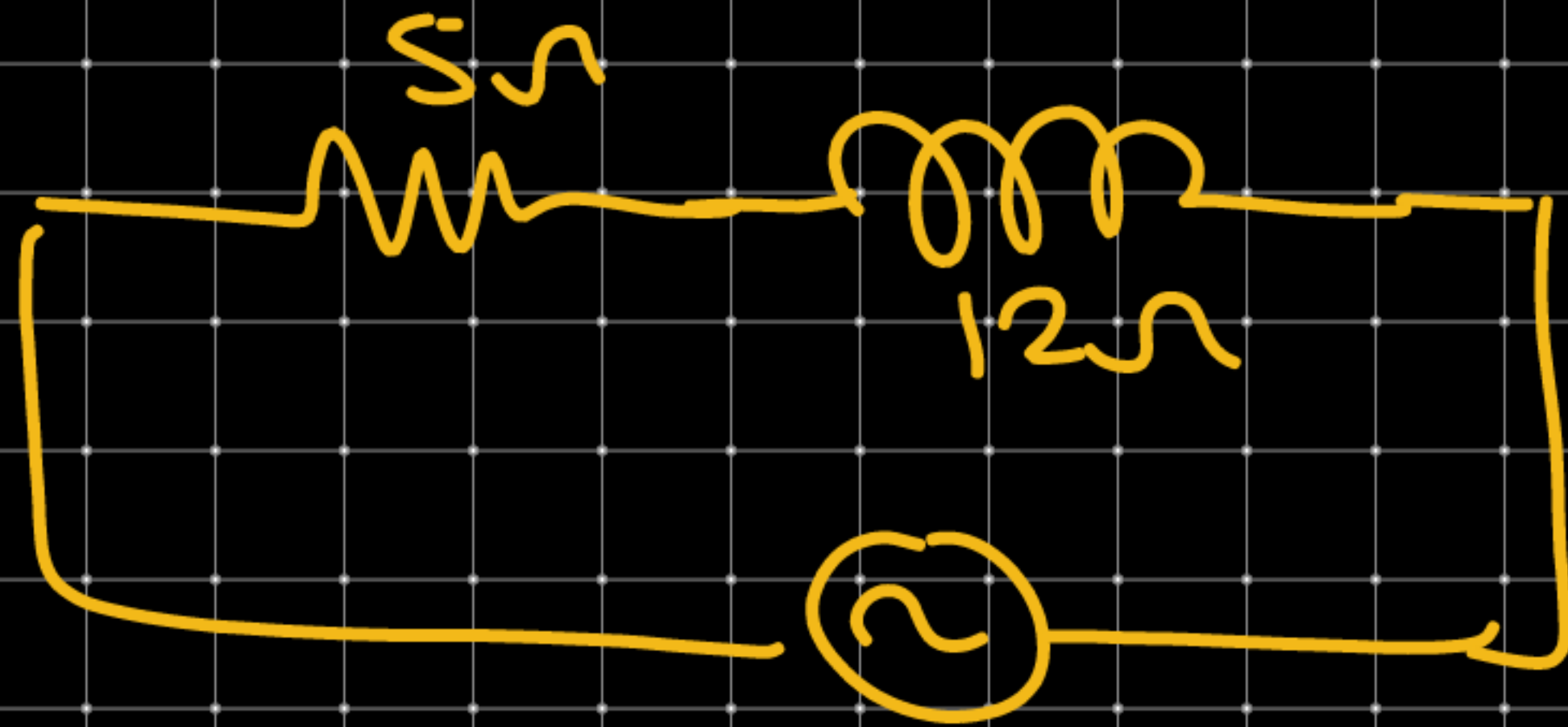

X_L — Inductive reactance
 X_C — Capacitive reactance


$Z = ?$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{5^2 + (12 - 0)^2}$$

$$= \sqrt{25 + 144} = \sqrt{169} = 13 \Omega$$

Q6:

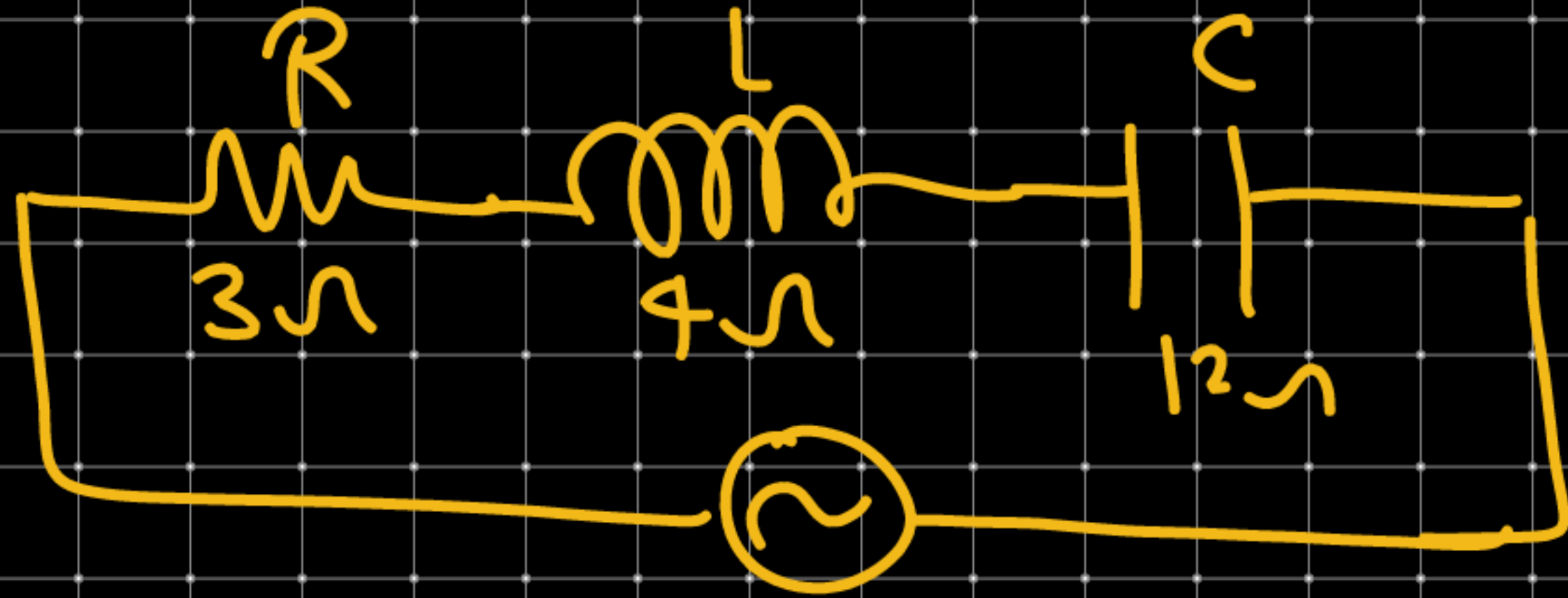

$Z = ?$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{3^2 + (4 - 12)^2}$$

$$= \sqrt{9 + 64} = \sqrt{73} \Omega$$

73 Ω

Q7)



$$X_C = \frac{1}{\omega C}$$

$$\omega = 2\pi f$$

If capacitance is 2 MF & frequency is 100 Hz. find $X_C = ?$

$$X_C = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{2\pi \times 100 \times 2 \times 10^{-6}}$$

$$= \frac{1}{4\pi \times 10^{-4}} = \frac{10^4}{4\pi} \Omega$$

Q7)



$$\Rightarrow V_{rms} = 20\sqrt{2}\text{ Volt}$$

$$I_{rms} = \frac{V_{rms}}{R}$$

$$= \frac{20\sqrt{2}}{10} = 2\sqrt{2}\text{ Amp}$$

Q2)




$$\epsilon_0 = 20\sqrt{2}\text{ Volt}$$

$$\epsilon_{rms} = \frac{\epsilon_0}{\sqrt{2}} = \frac{20\sqrt{2}}{\sqrt{2}} = 20\text{ Volt}$$

$$I_{rms} = \frac{\epsilon_{rms}}{R} = \frac{20}{10} = 2\text{ Amp}$$



L-C-R Circuit.

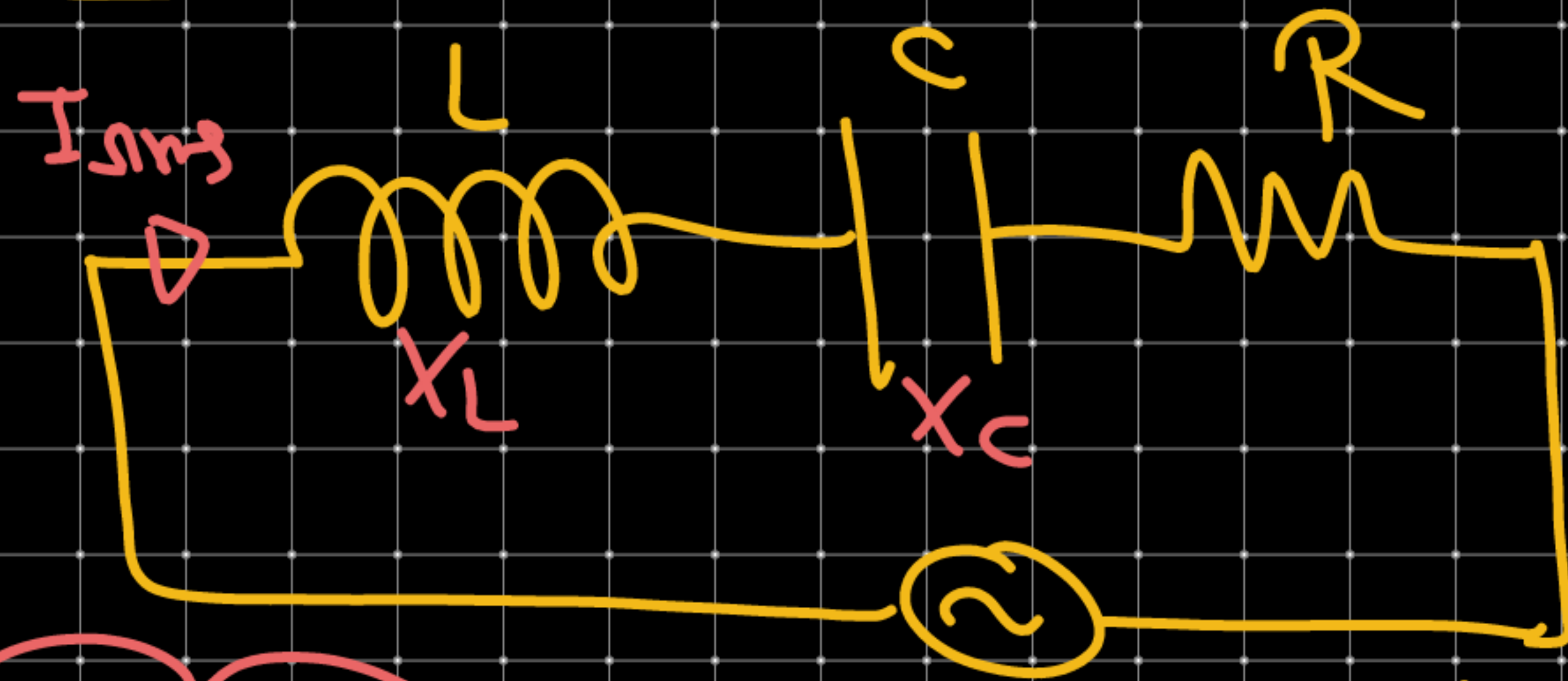

→ Find Potential Across each C, L, R

Step I)
$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t.$$
 Step II:
$$I_{rms} = \frac{E_0}{\sqrt{2}}$$

Step III)
$$I_{rms} = \frac{E_{rms}}{Z}$$


$$V_L = I_{rms} X_L$$

$$V_C = I_{rms} X_C$$

$$V_R = I_{rms} X_R$$

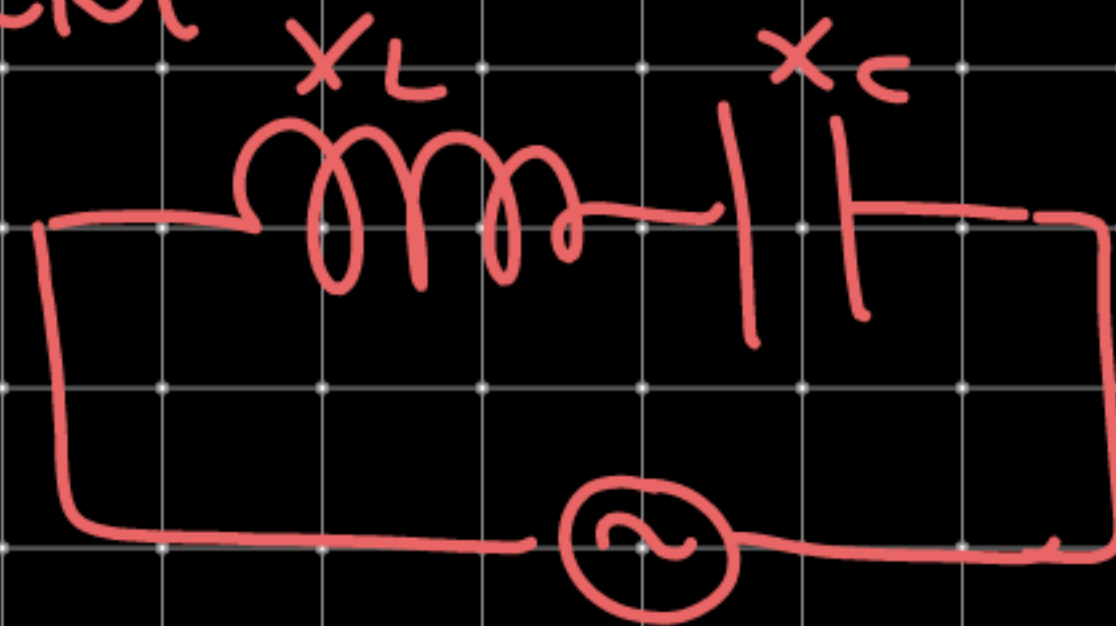Q8] If $X_L = 50\Omega$ & $X_C = 40\Omega$. Calculate effective value of current in given ckt

Solve] [Note \rightarrow effective value
 \downarrow
 [rms value]




$$\begin{aligned} \textcircled{i} \quad Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{0 + (50 - 40)^2} \\ &= \sqrt{10^2} = \underline{\underline{10\Omega}} \\ Z &= \underline{\underline{10\Omega}} \end{aligned}$$

$$\textcircled{ii} \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{40}{\sqrt{2}} = 20\sqrt{2} \text{ V}$$

$$\begin{aligned} \textcircled{iii} \quad I_{\text{rms}} &= \frac{V_{\text{rms}}}{Z} = \frac{20\sqrt{2}}{10} = \\ &= \underline{\underline{2\sqrt{2} \text{ Amp}}} \end{aligned}$$

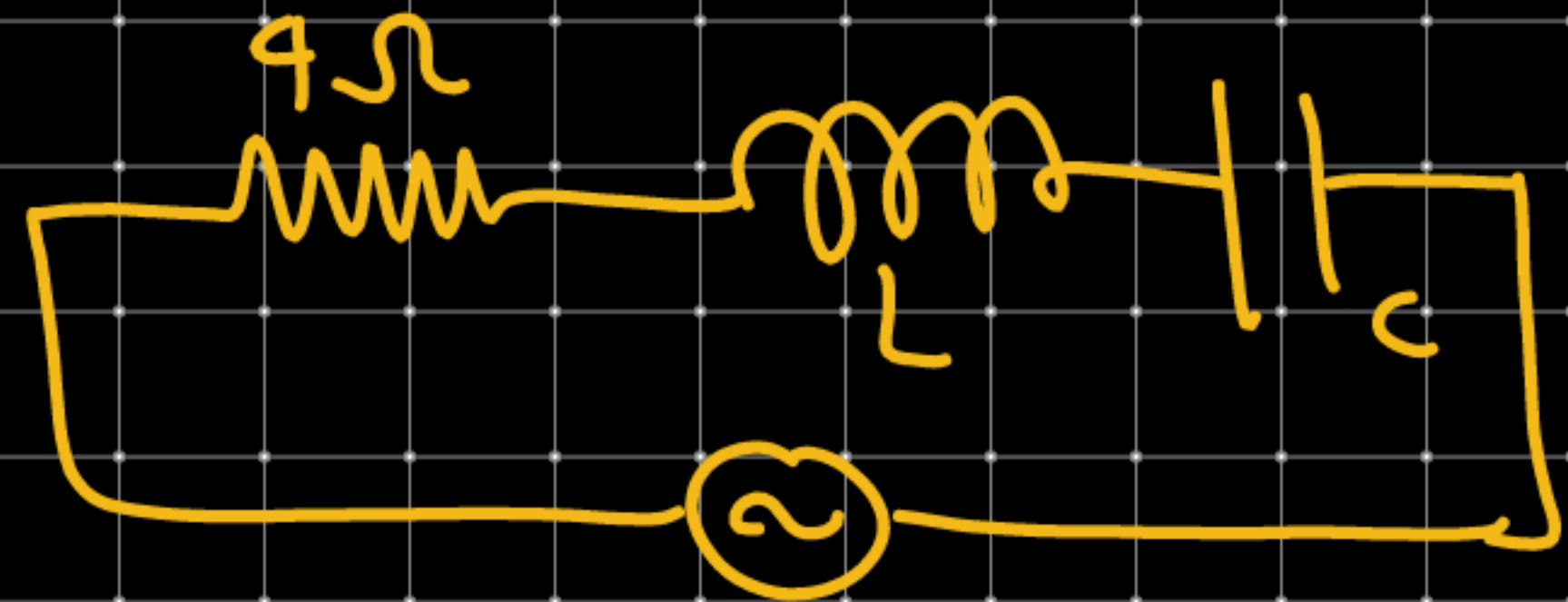Q9) Find I_{rms} , $X_L = 24 \Omega$ $X_C = 21 \Omega$



$$\textcircled{i} Z = \sqrt{4^2 + (24 - 21)^2}$$
$$Z = \sqrt{16 + 9} = 5 \Omega.$$

$$\textcircled{ii} V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{200\sqrt{2}}{\sqrt{2}}$$
$$V_{rms} = 200 \text{ Volt.}$$

Step I) Z

Step II) V_{rms}


$$\text{Step III) } I_{rms} = \frac{V_{rms}}{Z}$$

$$V = 200\sqrt{2} \sin 100\pi t$$

$$\textcircled{iii} I_{rms} = \frac{V_{rms}}{Z} = \frac{200}{5}$$

$$= \underline{\underline{40 \text{ Am}}}$$

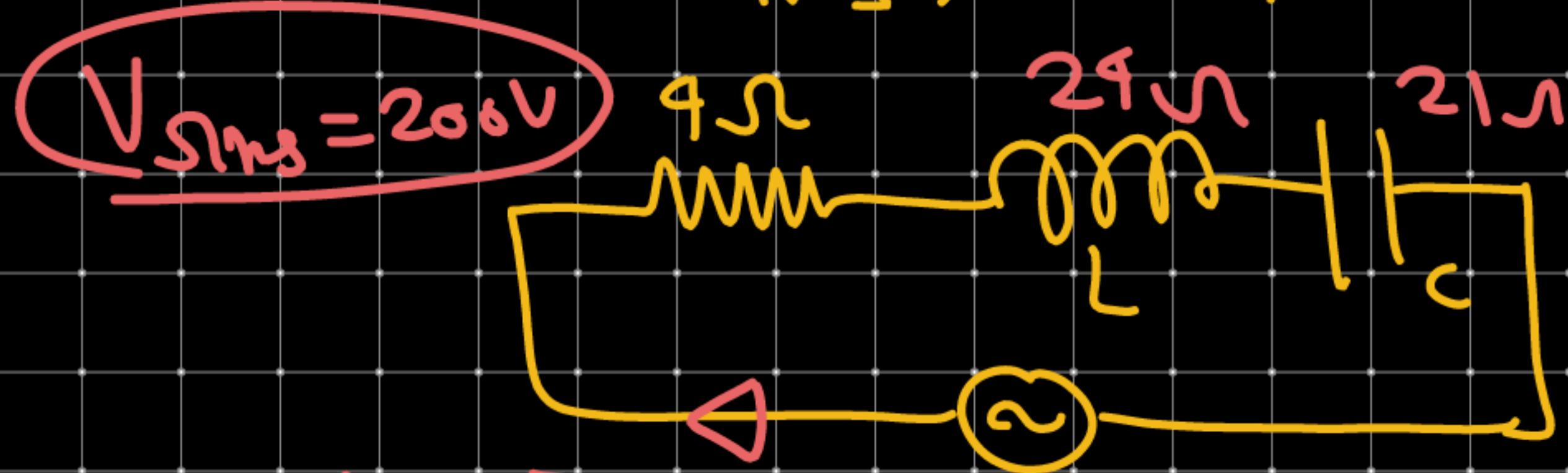99) Find I_{rms} , $X_L = 24 \Omega$ $X_C = 21 \Omega$



$$40A = I_{rms} \quad V = 200\sqrt{2} \sin 100\pi t$$

$$\begin{aligned} V_L &= I_{rms} X_C \\ &= 40 \times 21 \\ &= 210 \times 4 = \underline{840 \text{ Volt}} \end{aligned}$$


$$\begin{aligned} V_R &= I_{rms} X_R \\ &= 40 \times 4 \\ &= 160 \text{ Volt} \end{aligned}$$

$$\begin{aligned} V_L &= I_{rms} X_L \\ &= 40 \times 24 \\ &= 240 \times 4 = 960V \end{aligned}$$

ΔV_L


$-V_C$

$\Delta i^0, V_R \equiv$

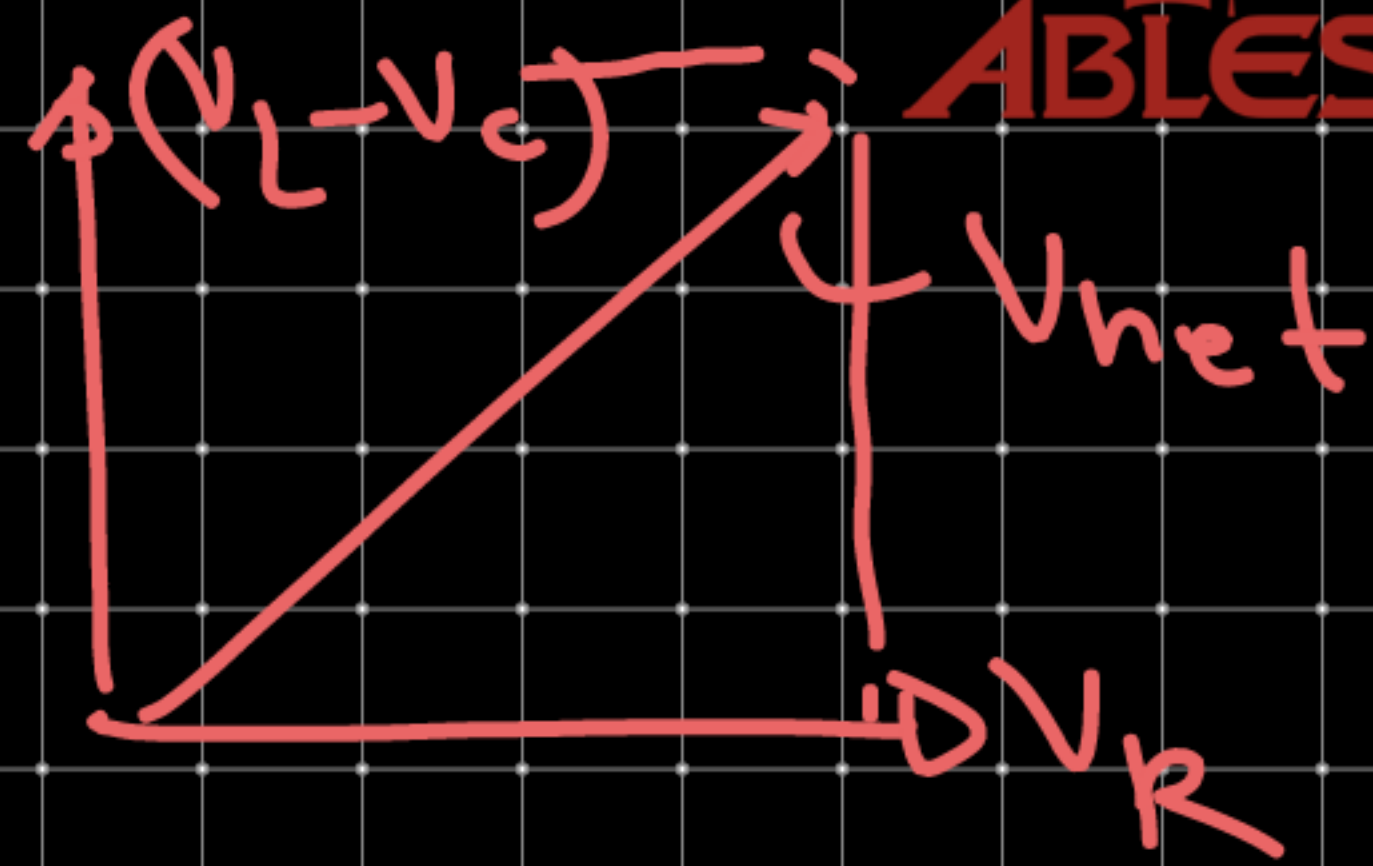

$$\begin{aligned} V_{net} &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{(160)^2 + (960 - 840)^2} \\ &= \sqrt{(160)^2 + (120)^2} \\ &= \underline{\underline{1200 \text{ Volt}}} \end{aligned}$$

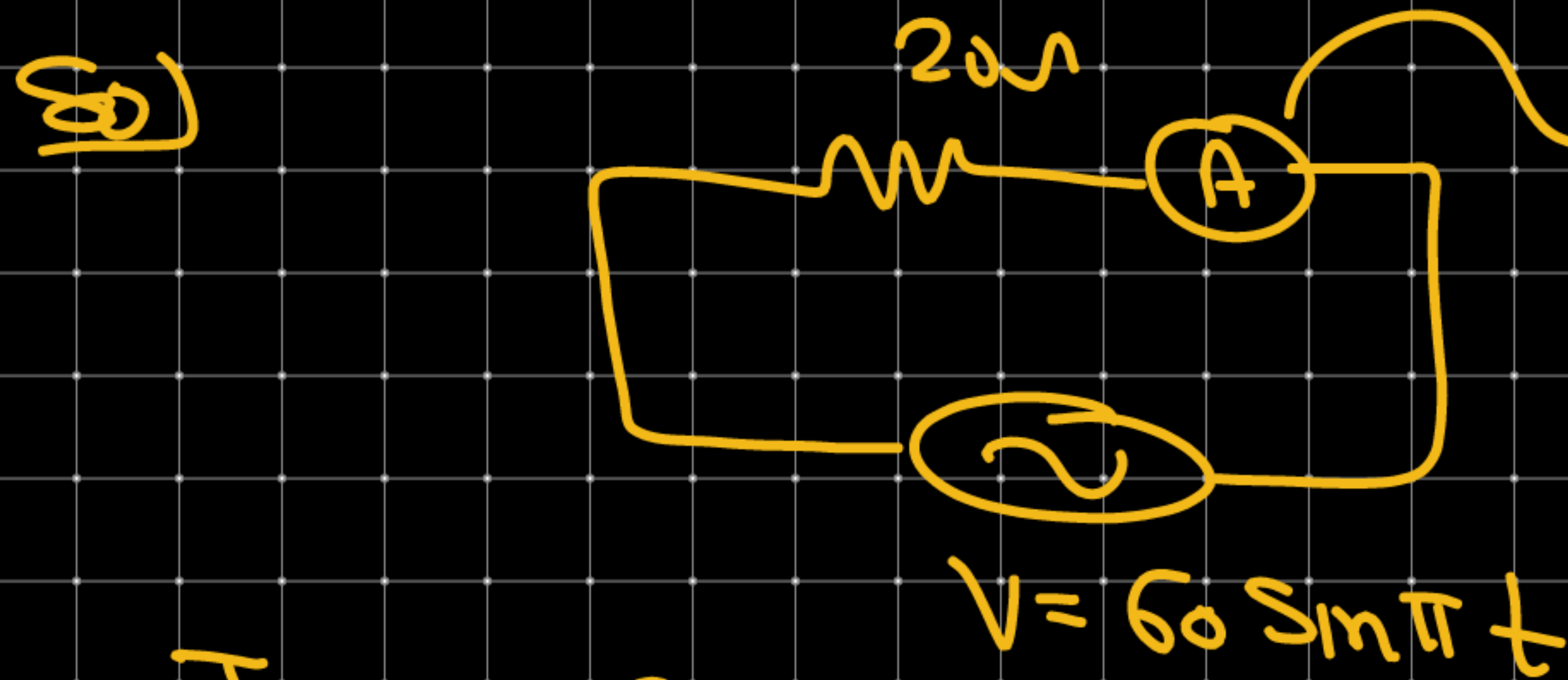Q10) A voltage $V = 60 \sin \pi t$ Volt is applied across a 20Ω resistor. What will be ac ammeter in series with the resistor is read



$$E_{rms} = \frac{60}{\sqrt{2}} = 30\sqrt{2}$$


$$I_{rms} = \frac{E_{rms}}{R}$$

$$= \frac{30\sqrt{2}}{20} = \frac{3}{\sqrt{2}} \text{ Amp}$$

$$\underline{\underline{I_{rms} = ?}}$$

Q11) An AC Source $E = 100 \sin(1000t)$ Volt is connected through an inductor of 20 mH . then Write the eqn of current.

Sol

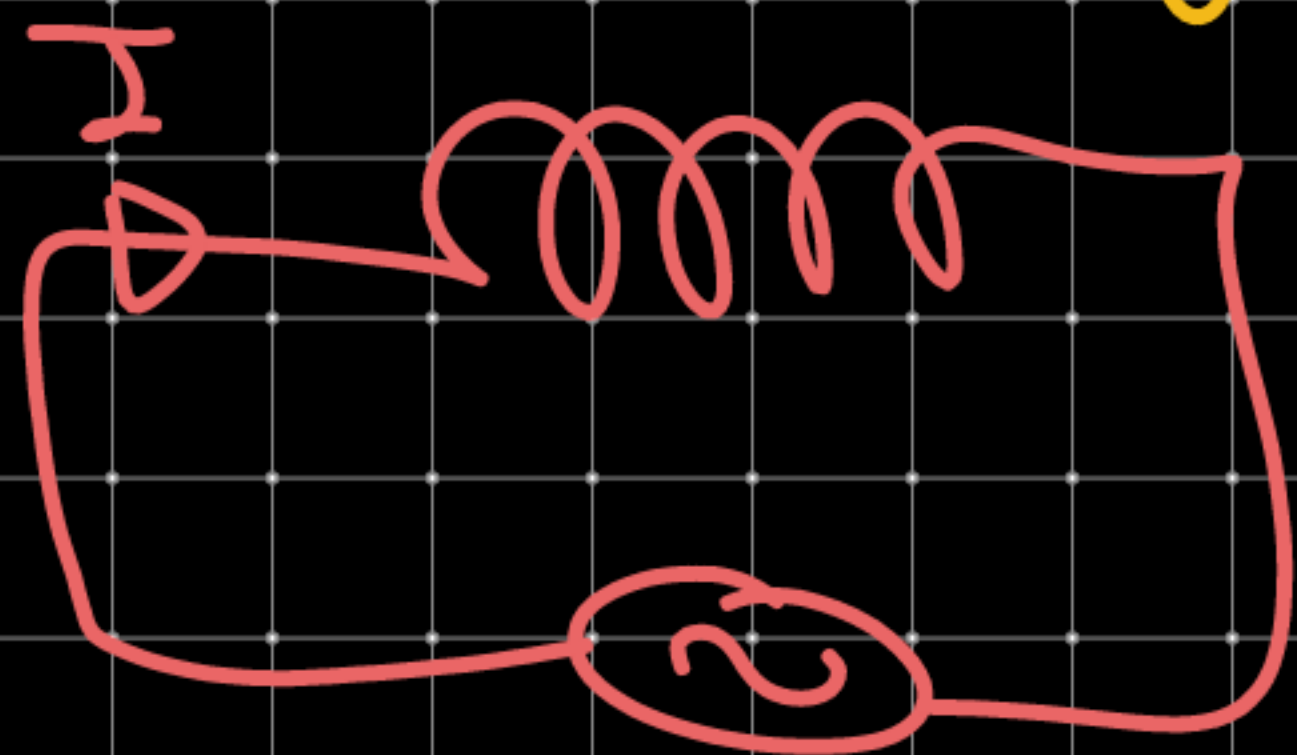

$$E = 100 \sin(1000t)$$

$$E = 100 \sin(1000t)$$
$$i = \frac{100 \sin(1000t - \frac{\pi}{2})}{X_L}$$

Q12) A Capacitor of Capacity C is connected in AC circuit. The applied emf is $V = V_0 \sin \omega t$ then current is

(a) $I = \frac{V_0}{\omega L} \sin \omega t$

(b) $I = \frac{V_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$

(c) $I = V_0 \omega C \sin \omega t$

~~(d) $I = V_0 \omega C \sin(\omega t + \frac{\pi}{2})$~~


2018

$$V = V_0 \sin \omega t$$

$$i = \frac{V_0}{X_C} \sin(\omega t + \frac{\pi}{2})$$

$$= \frac{V_0}{\frac{1}{\omega C}} \sin(\omega t + \frac{\pi}{2})$$

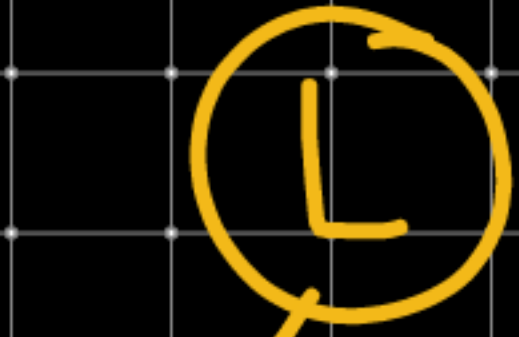
$$= V_0 \omega C \sin(\omega t + \frac{\pi}{2})$$



$$e = e_0 \sin \omega t$$


$$i = \frac{e_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

i lags by $\pi/2$ with e

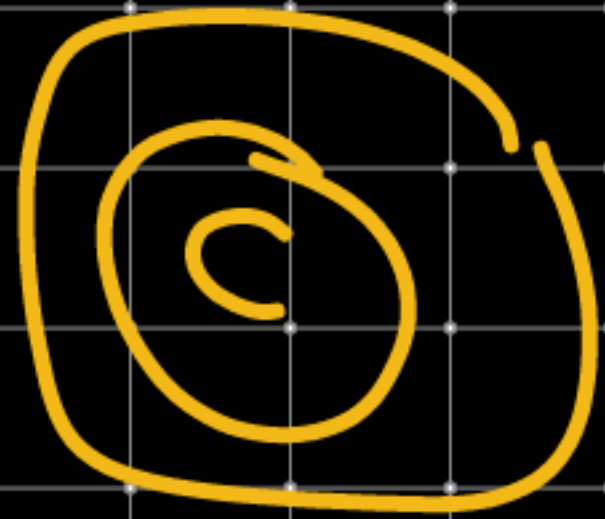

$$e = e_0 \sin \omega t$$
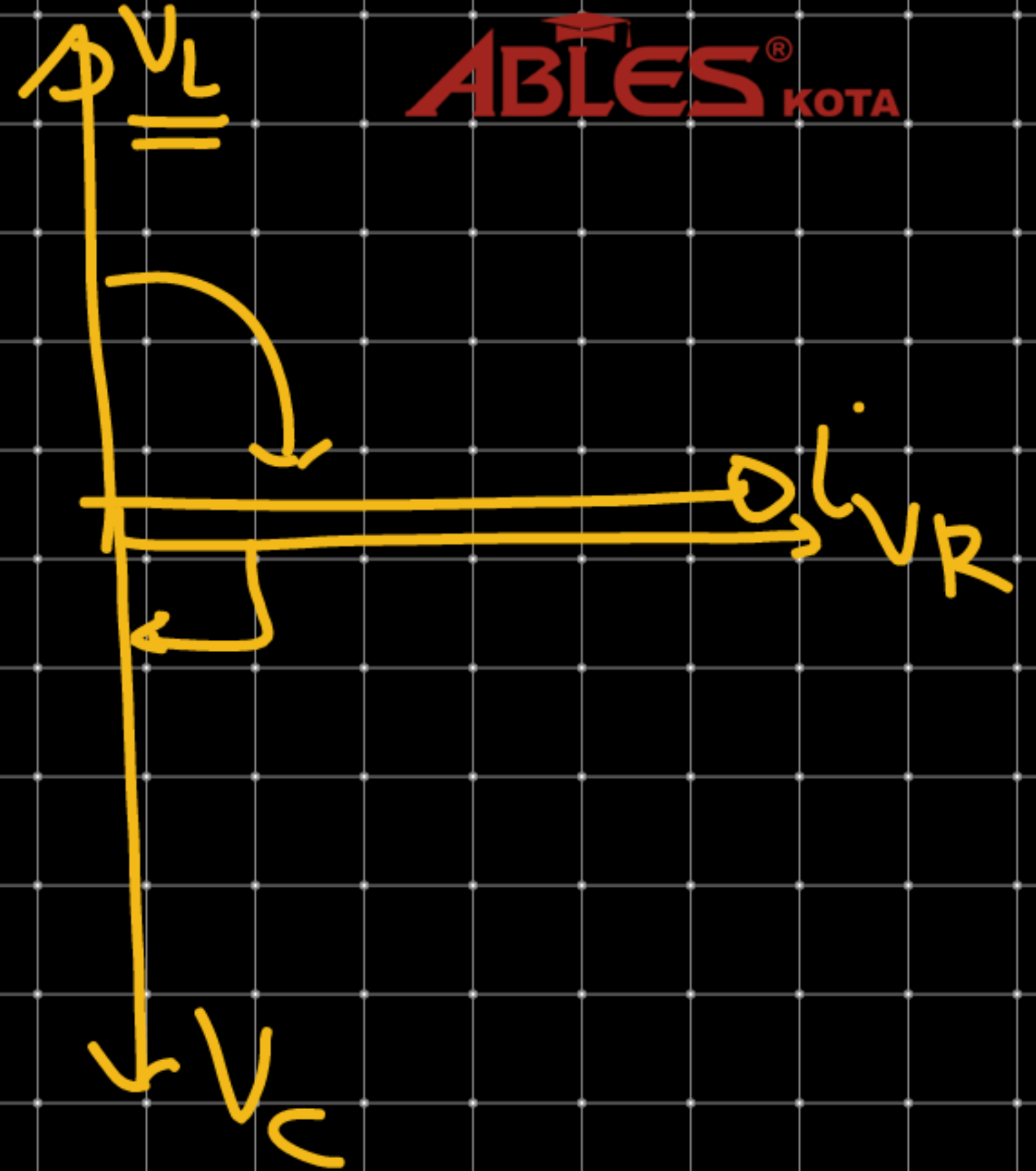
$$i = \frac{e_0}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right)$$



In Inductor

$$E = E_0 \sin \omega t$$

$$I = \frac{E_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

In Capacitor

$$E = E_0 \sin \omega t$$

$$i = \frac{E_0}{\omega C} \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = \frac{E_0}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right)$$

In Inductor

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$I = \frac{\varepsilon_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$