

AC

→ Queues based on AC with R

→ AC with C

→ AC with L


AC with LCP

L, R

R, C

C, L

↳ L-C-R Resonance:-

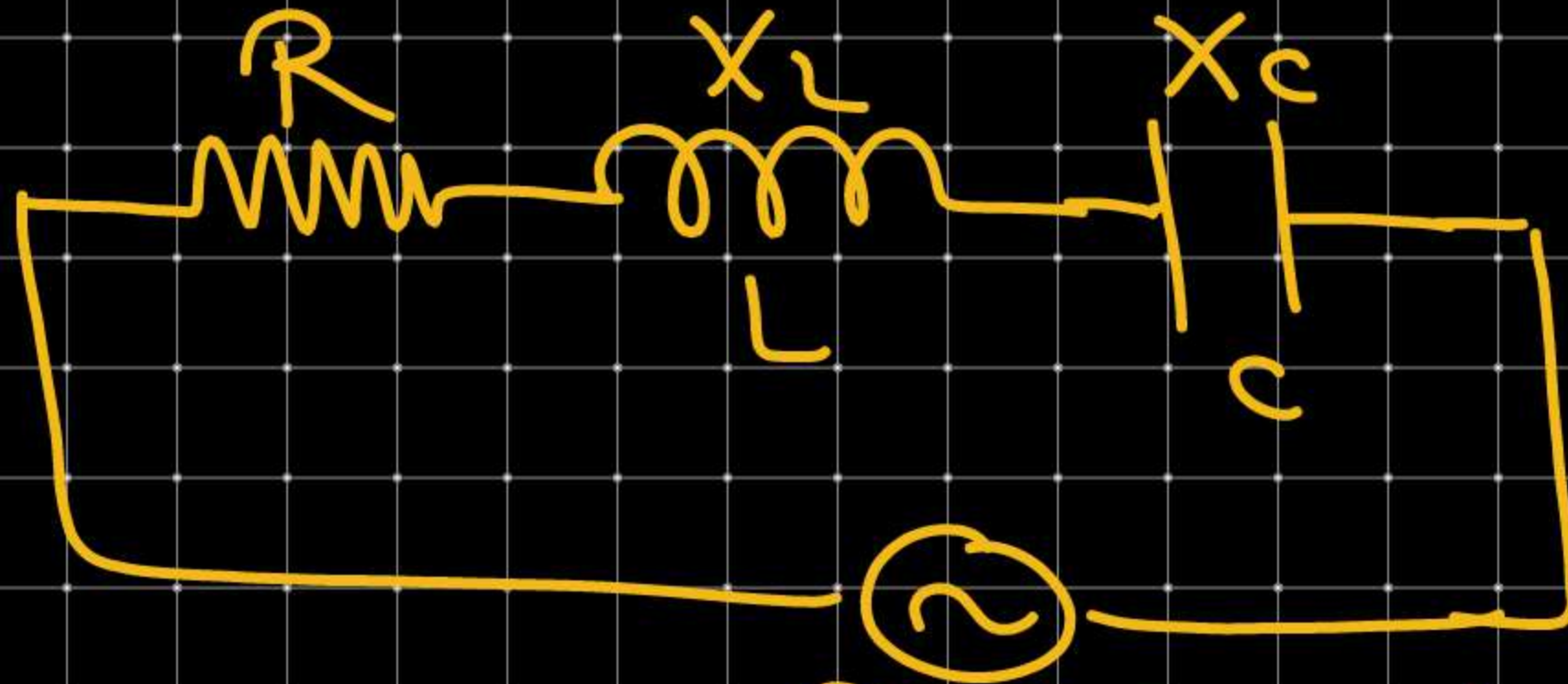


$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Angular frequency = ω

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi}$$

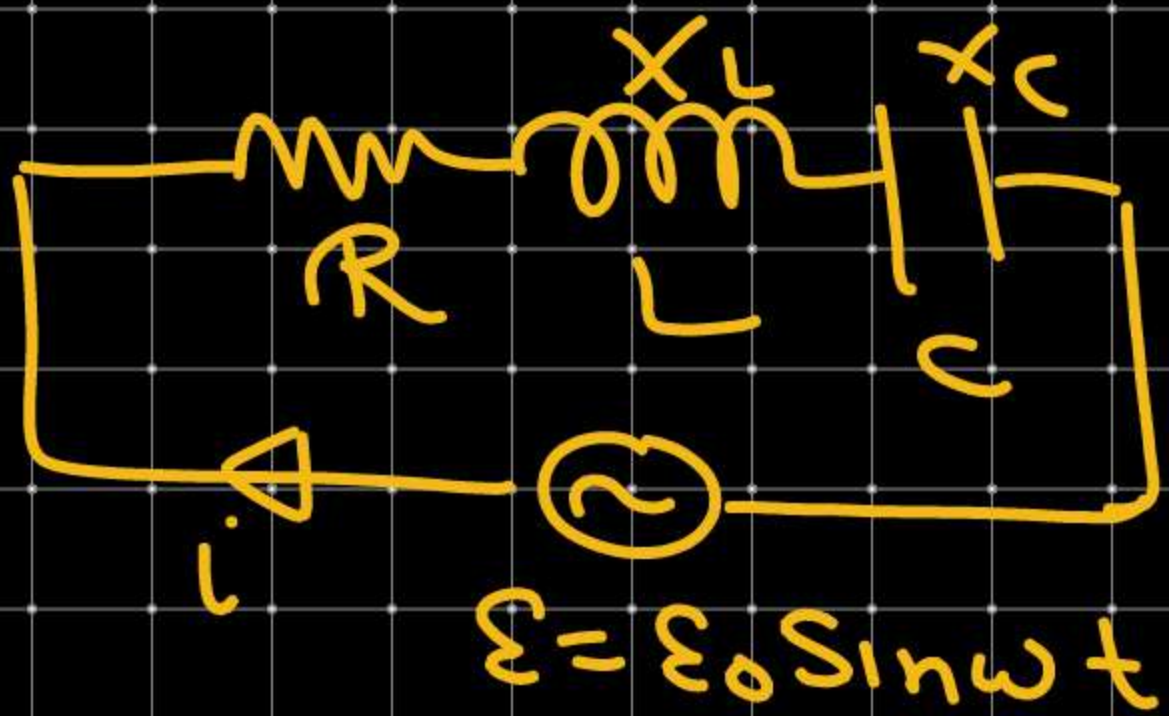

$$R = \frac{\rho l}{A}$$

$R \rightarrow$ w Pn depend
Kanta Rai.

$$\underline{X_L = \omega L} \rightarrow \text{depends on } \omega.$$

$$\rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2} \quad X_C = \frac{1}{\omega C} \rightarrow \omega \rightarrow \text{depend.}$$

\hookrightarrow At Resonance. $X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C}$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega^2 = \frac{1}{LC}$$

At Resonance $X_L = X_C$

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

↳ Natural frequency

↳ Resonance frequency.

↳ i_{max}

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


At Resonance

$$X_L = X_C$$

$$X_L - X_C = 0$$

$$Z = \sqrt{R^2} = R$$

$$Z_{min} = R$$

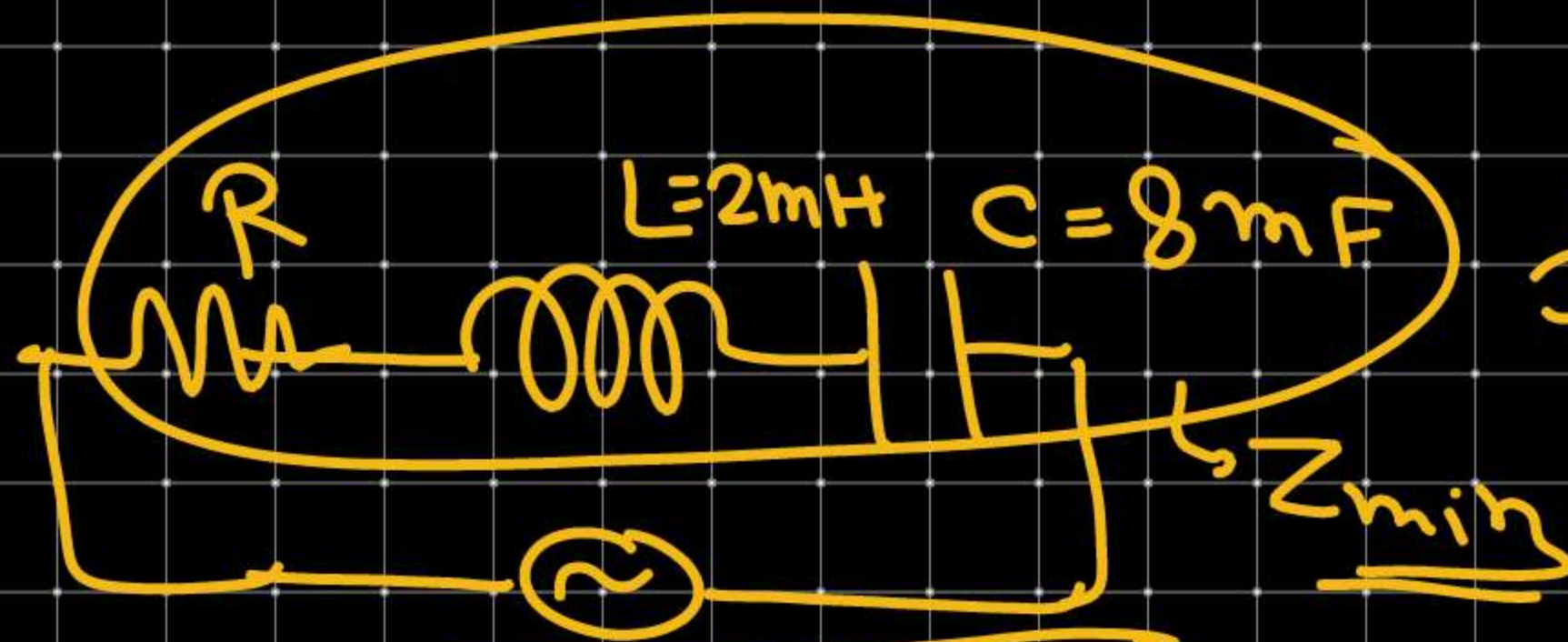

Find Resonance frequency

$$\omega = \frac{1}{\sqrt{LC}}$$


$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$\omega = \frac{1}{\sqrt{2 \times 10^{-3} \text{ H} \times 8 \times 10^{-3} \text{ F}}}$$

$$= \frac{1}{\sqrt{16 \times 10^{-6}}} = \frac{1}{4 \times 10^{-3}} = \frac{1000}{4} = \underline{\underline{250}}$$

Resonance frequency.

$$X_L = X_C$$

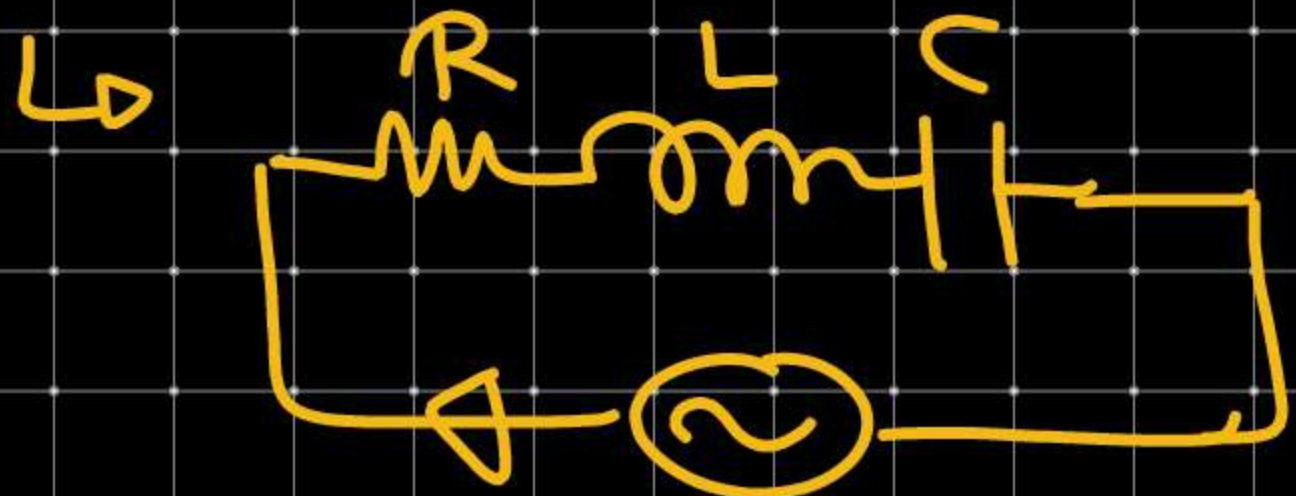

$$\varepsilon = \varepsilon_0 \sin \omega t$$

→ At resonance $X_L = X_C$

Angular frequency. $\omega = \frac{1}{\sqrt{LC}}$

$$Z = R \rightarrow \underline{\underline{Z_{min}}}$$

$$\underline{\underline{I_{max}}}$$


$$f = \frac{\omega}{2\pi}$$

$$f = \frac{1}{\sqrt{LC} \times 2\pi}$$

$$\underline{\underline{f = \frac{1}{2\pi\sqrt{LC}}}}$$

L →

$$X_L = X_C$$

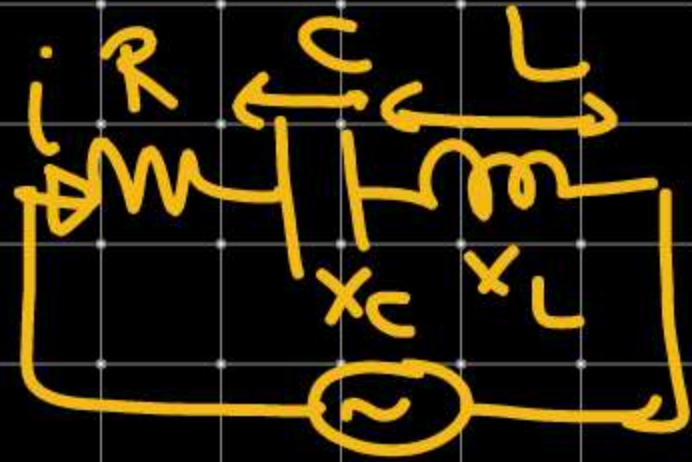

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

At Resonance


ABLES[®] KOTA

⇒

$$X_L = X_C$$

$$iX_L = iX_C$$

$$V_L = V_C$$

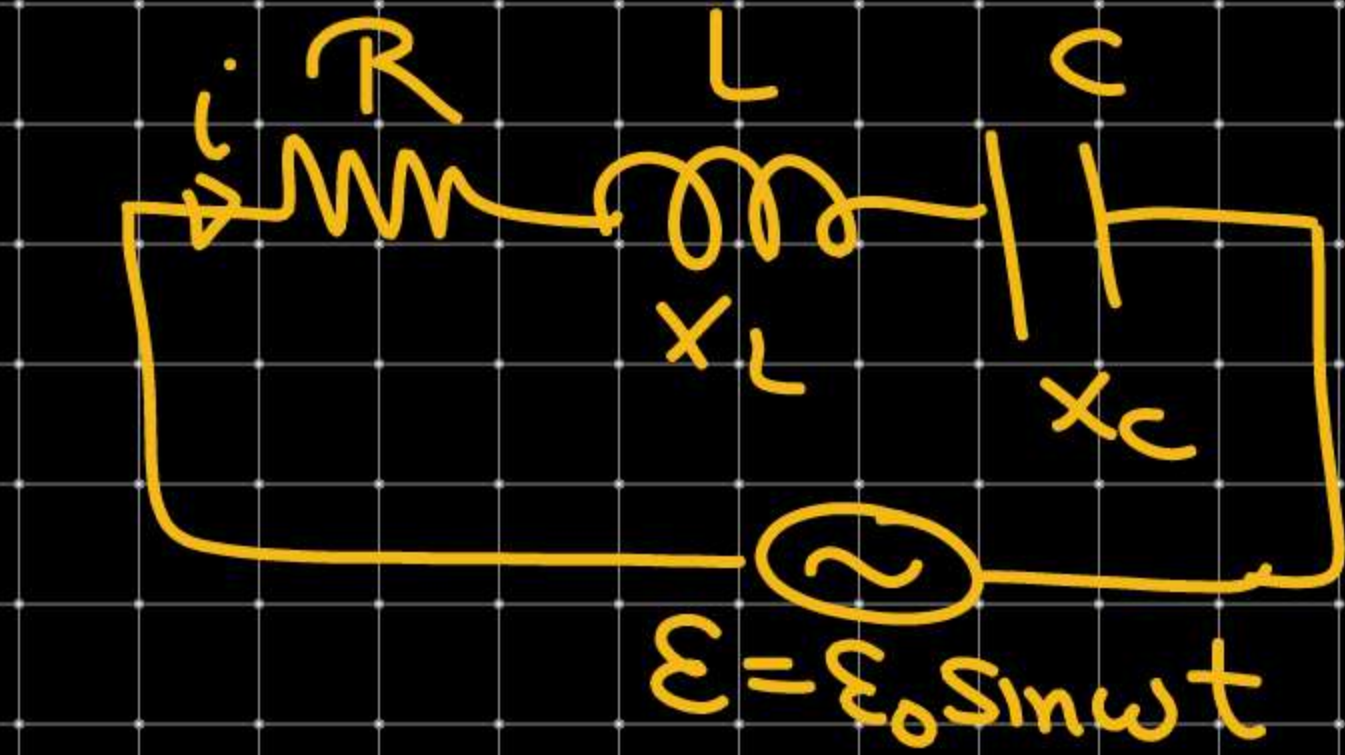




$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i = \frac{\mathcal{E}_0}{R} \sin \omega t$$

$$i = i_0 \sin \omega t$$

$$\Delta \phi = 0$$

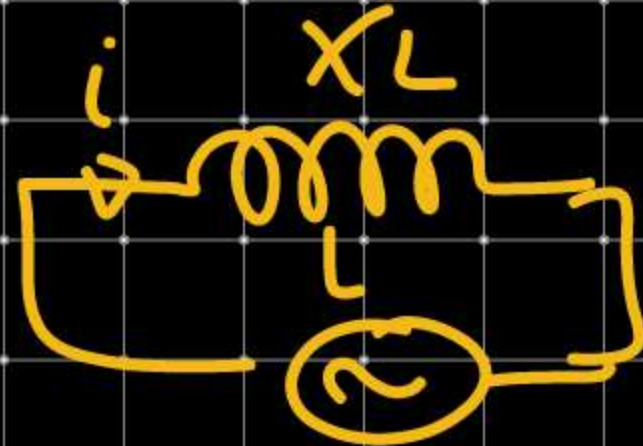


$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i_0 = \frac{\mathcal{E}_0}{X_L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$\cos \phi = 1$$

V_L lead $\frac{\pi}{2}$ with i

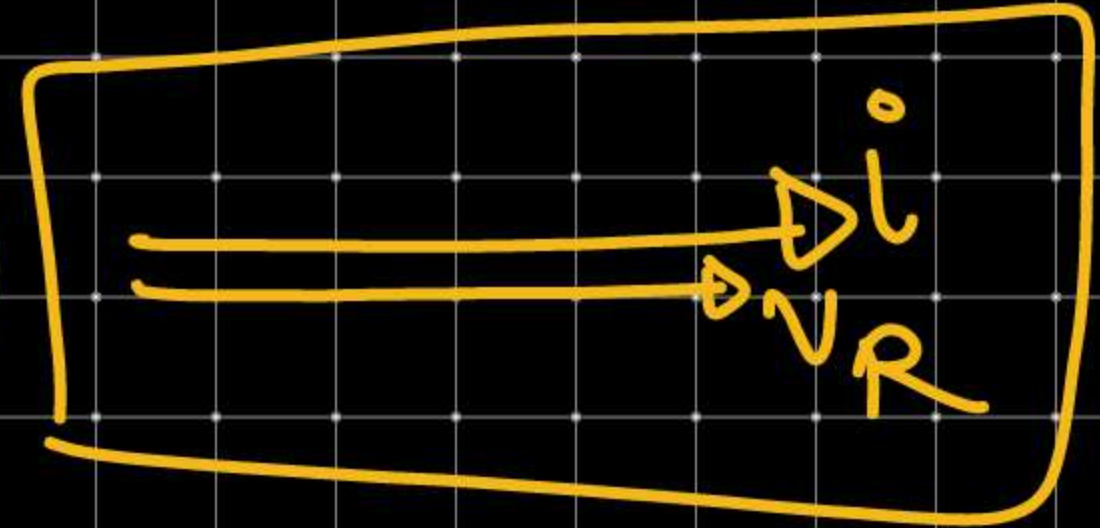





i lead $\frac{\pi}{2}$ with ε

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$\Rightarrow I = \frac{\varepsilon_0}{X_c} \sin\left(\omega t + \frac{\pi}{2}\right)$$

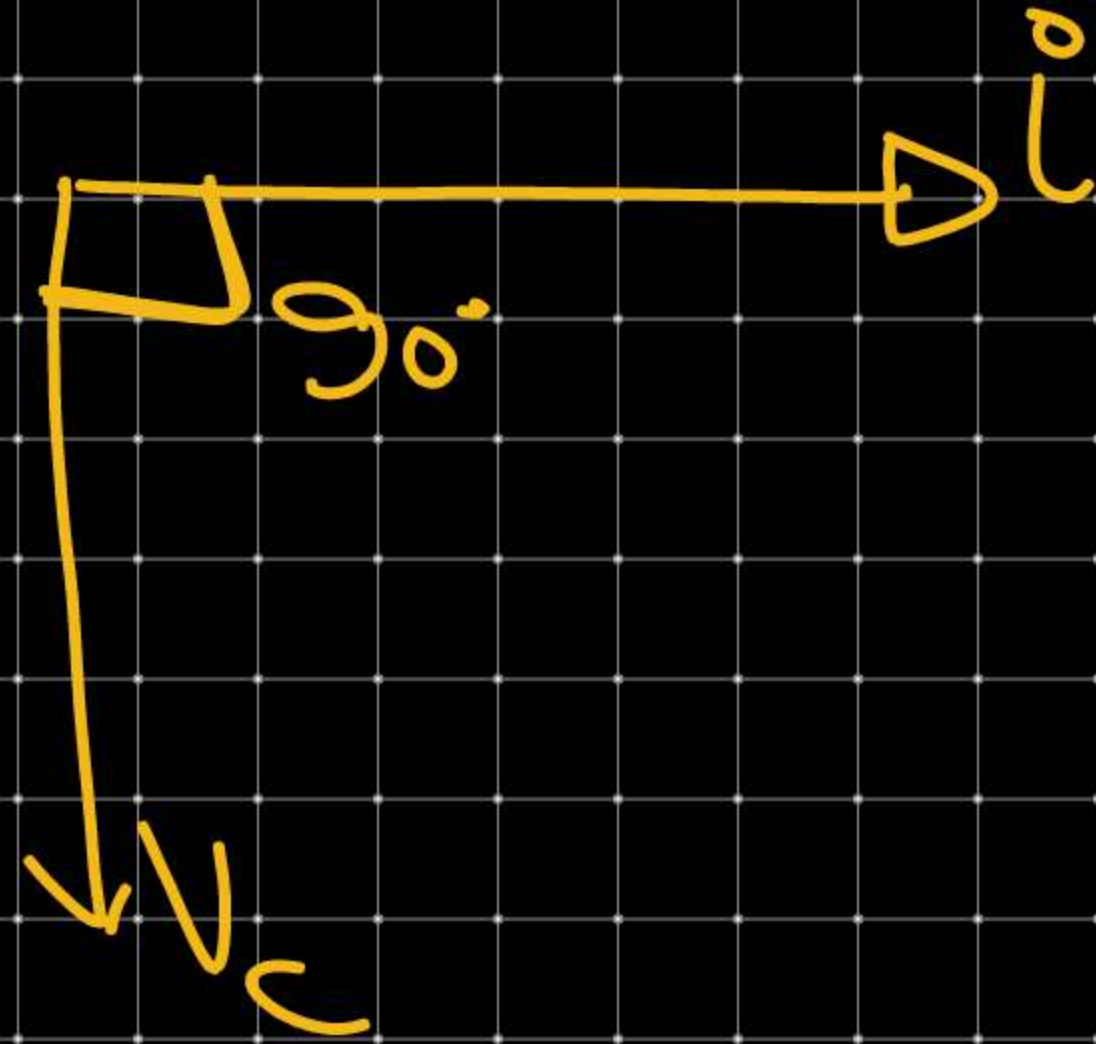
$$I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$



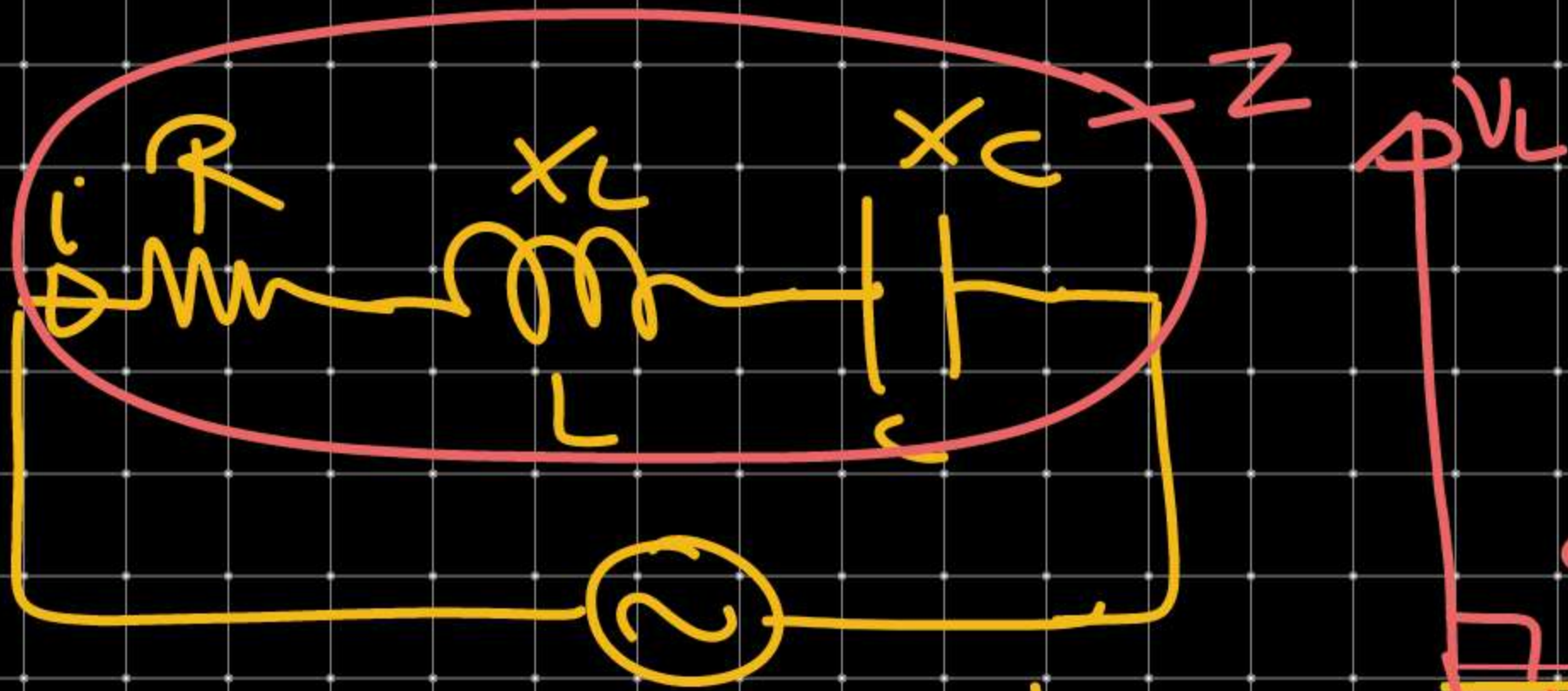


$\epsilon = \epsilon_0 \sin \omega t$
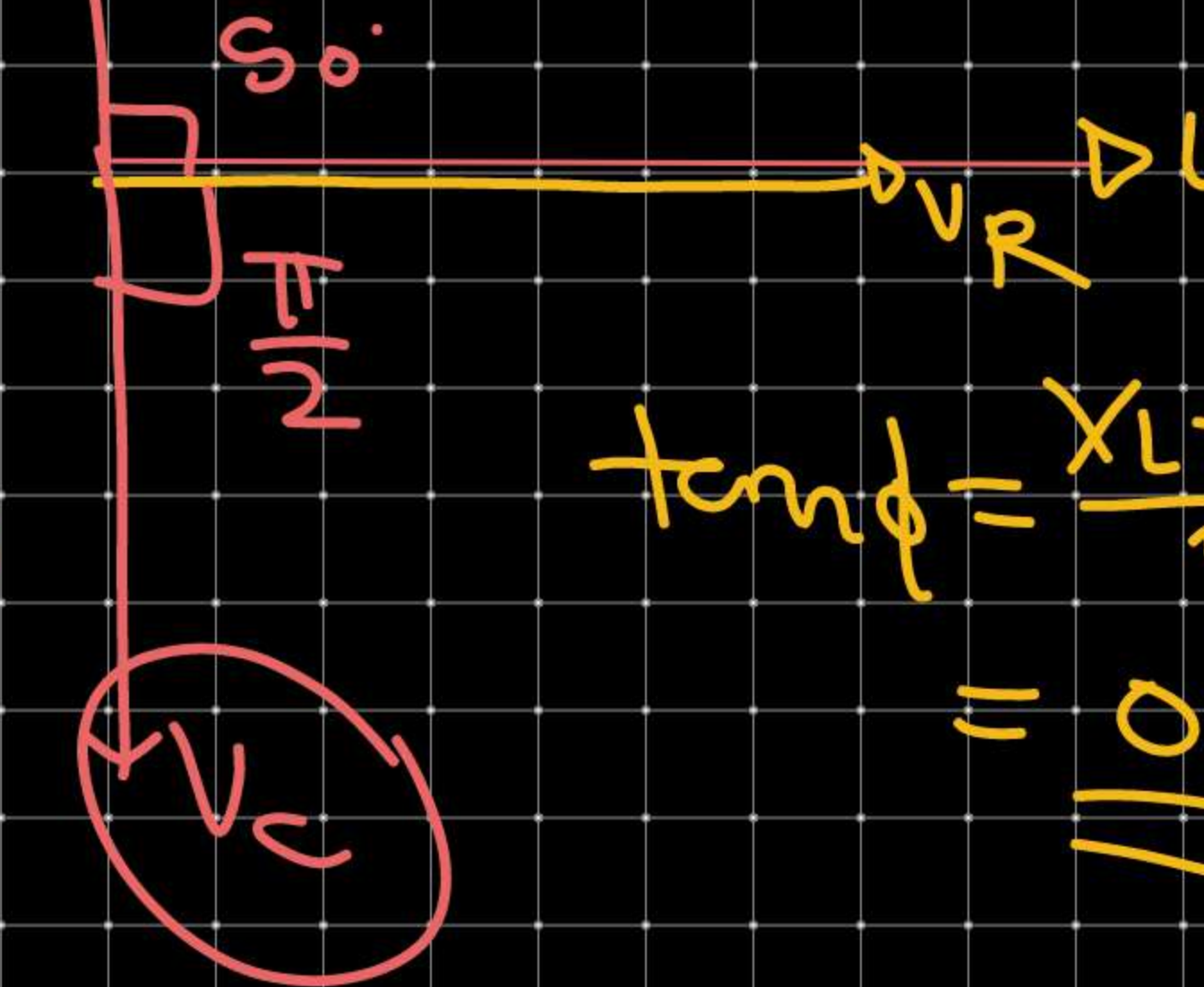
#. If $X_L = X_C$
 $V_L = V_C$ $V_L - V_C = 0$



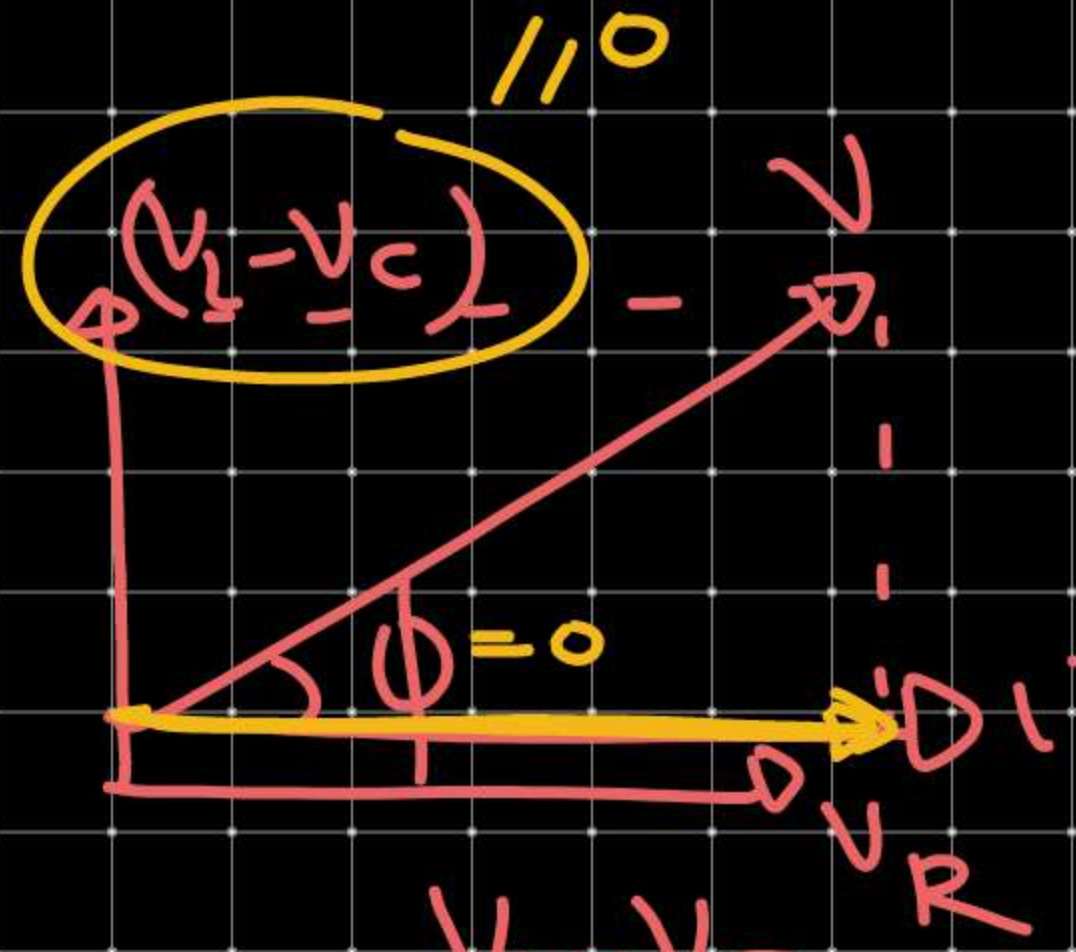$\tan \phi = \frac{X_L - X_C}{R}$
 $\parallel 0 \parallel$



$$V_{net} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$iZ = \sqrt{(IR)^2 + (iX_L - iX_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$\uparrow V_L$

$Z = \sqrt{R^2 + (X_L - X_C)^2}$

$Z_{min} = R$

$V = \sqrt{V_R^2 + (V_L - V_C)^2}$


$\downarrow V_C$

⇒ At Resonance condition


$\phi = 0$

$\epsilon f i = 0$

Phase diff = 0

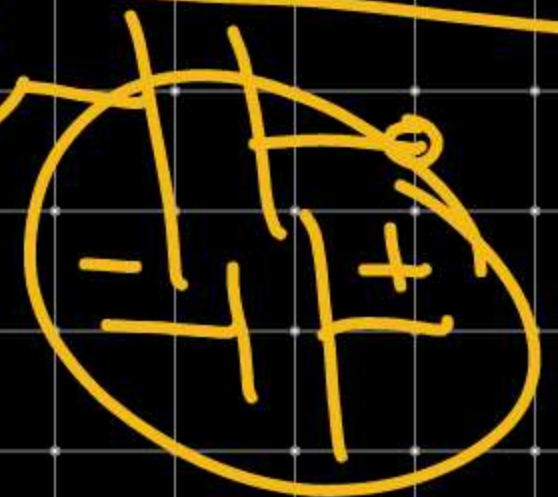

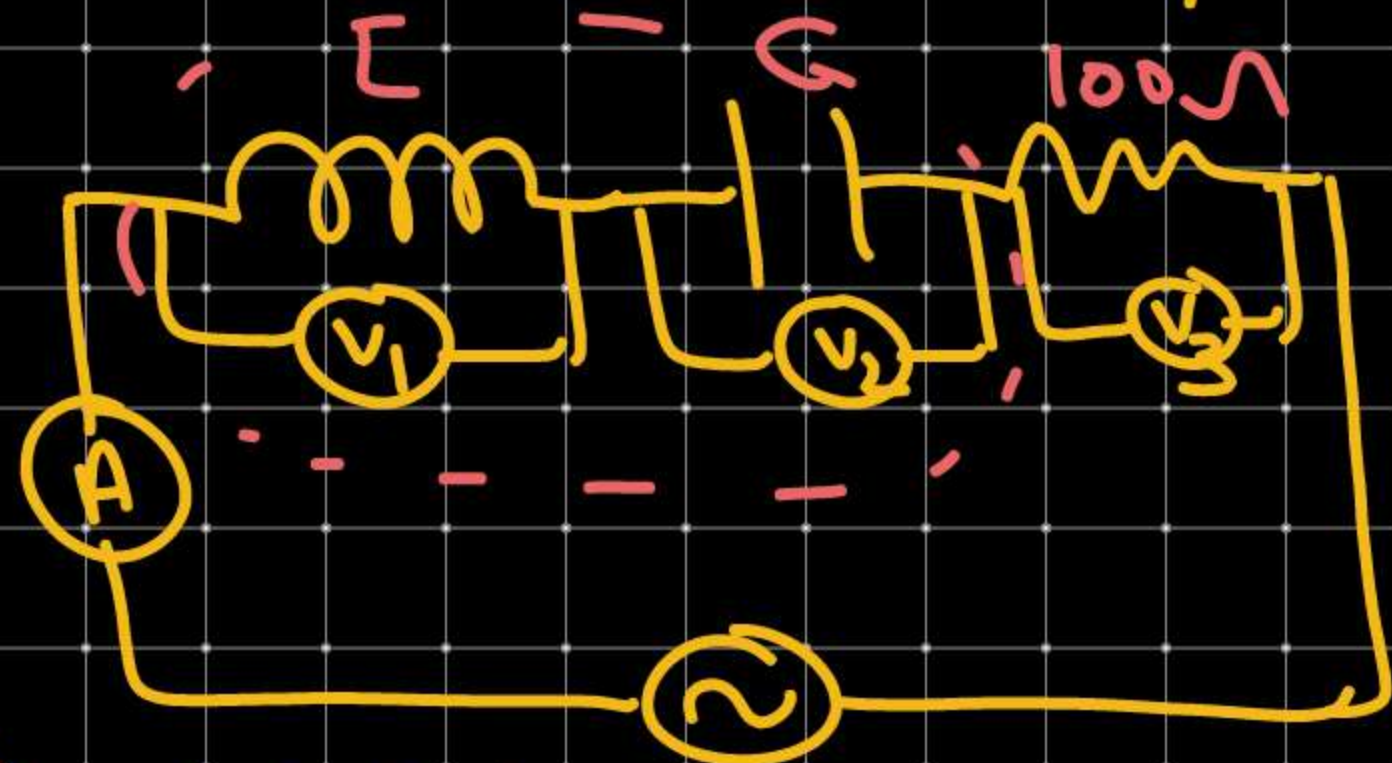
In the given ckt the reading of Voltmeter **ABLES** KOTA V_1 & V_2 are 300V each. the reading of V_3 & Ammeter A are respectively.



Sol

$$V_C = V_L$$

$$V_2 = V_1$$

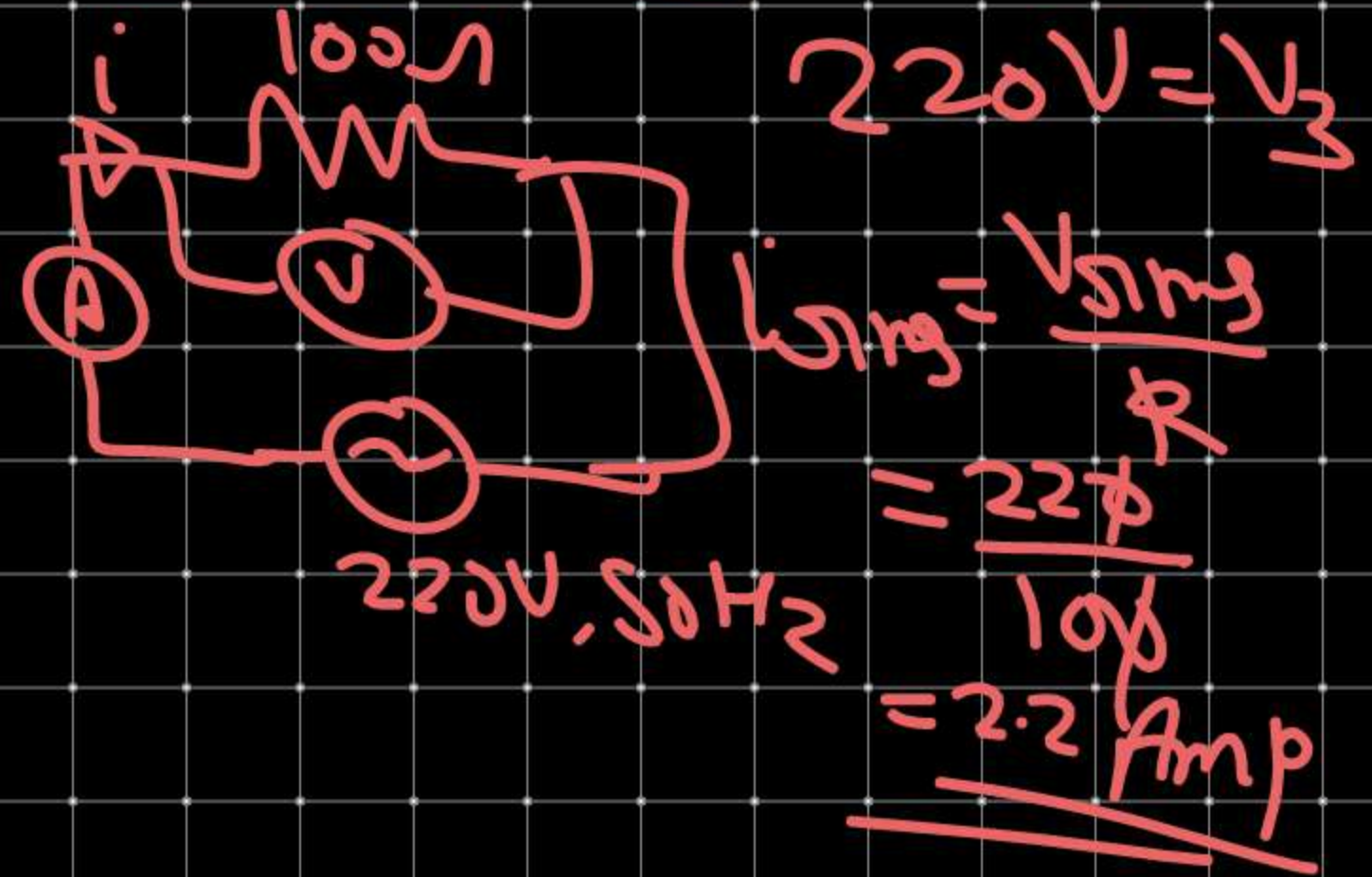


(a) 220V, 2.0A 220V, 50Hz

~~(b) 220V, 2.2A~~

(c) 100V, 2.0A

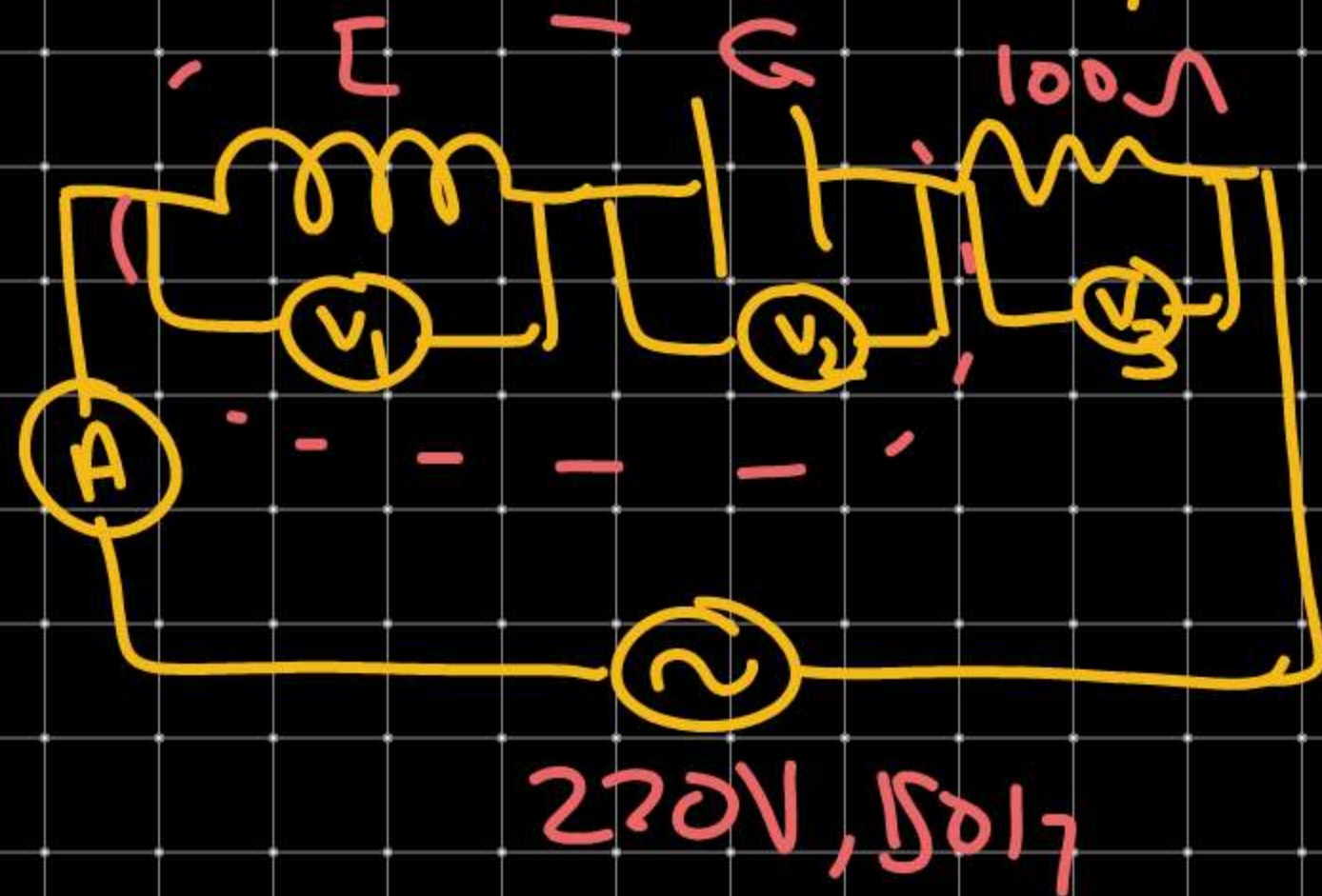(d) 150V, 2.2A

In the given ckt the reading of Voltmeter **ABLES**[®] KOTA V_1 & V_2 are 300V each. The reading of V_3 & Ammeter A are respectively.




$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$


$$220V = \sqrt{V_R^2 + 0}$$

$$\rightarrow 220V = V_R$$

$$220 = I \times 100$$


$$I = 2.2 \text{ Ams}$$

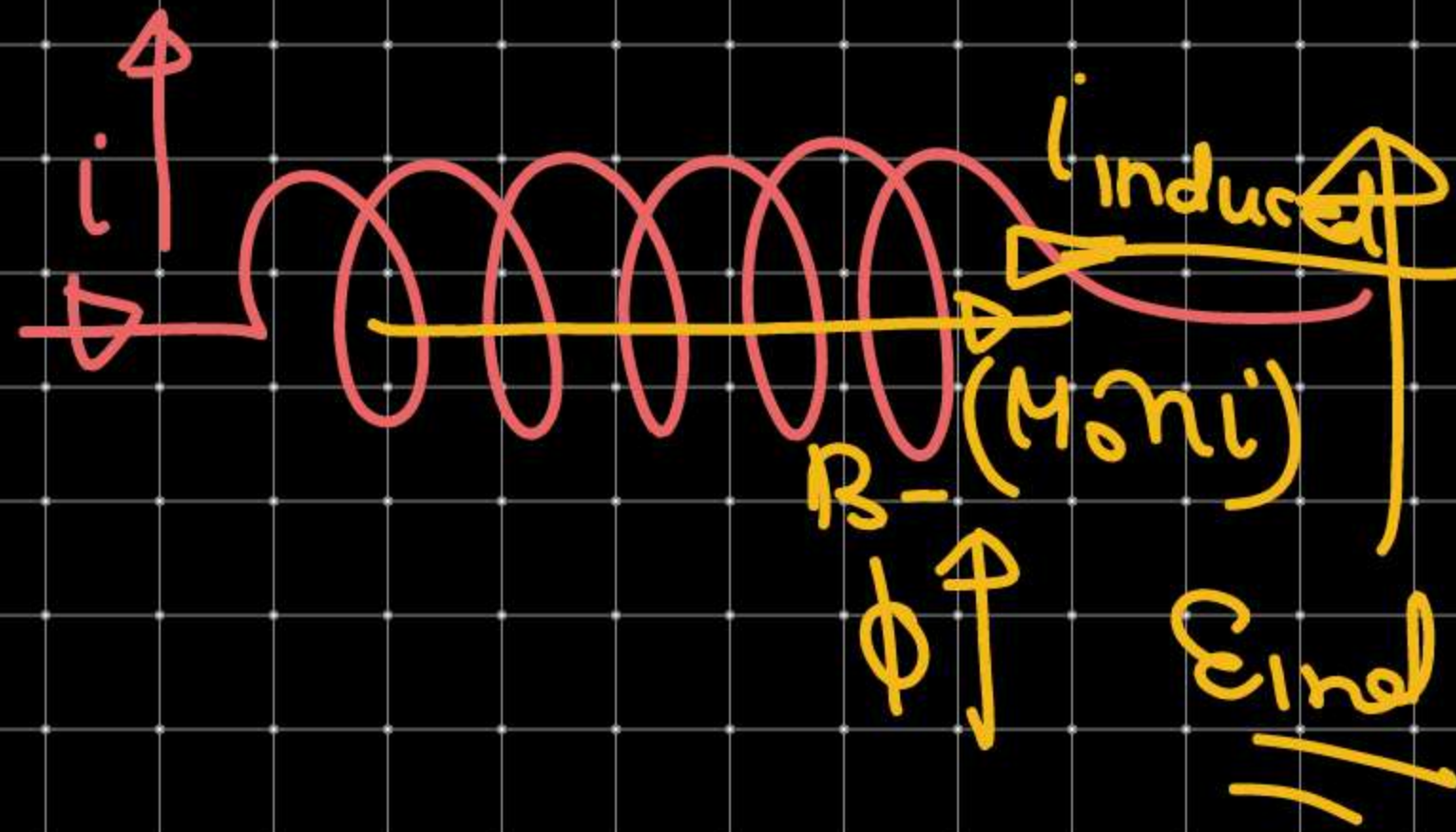

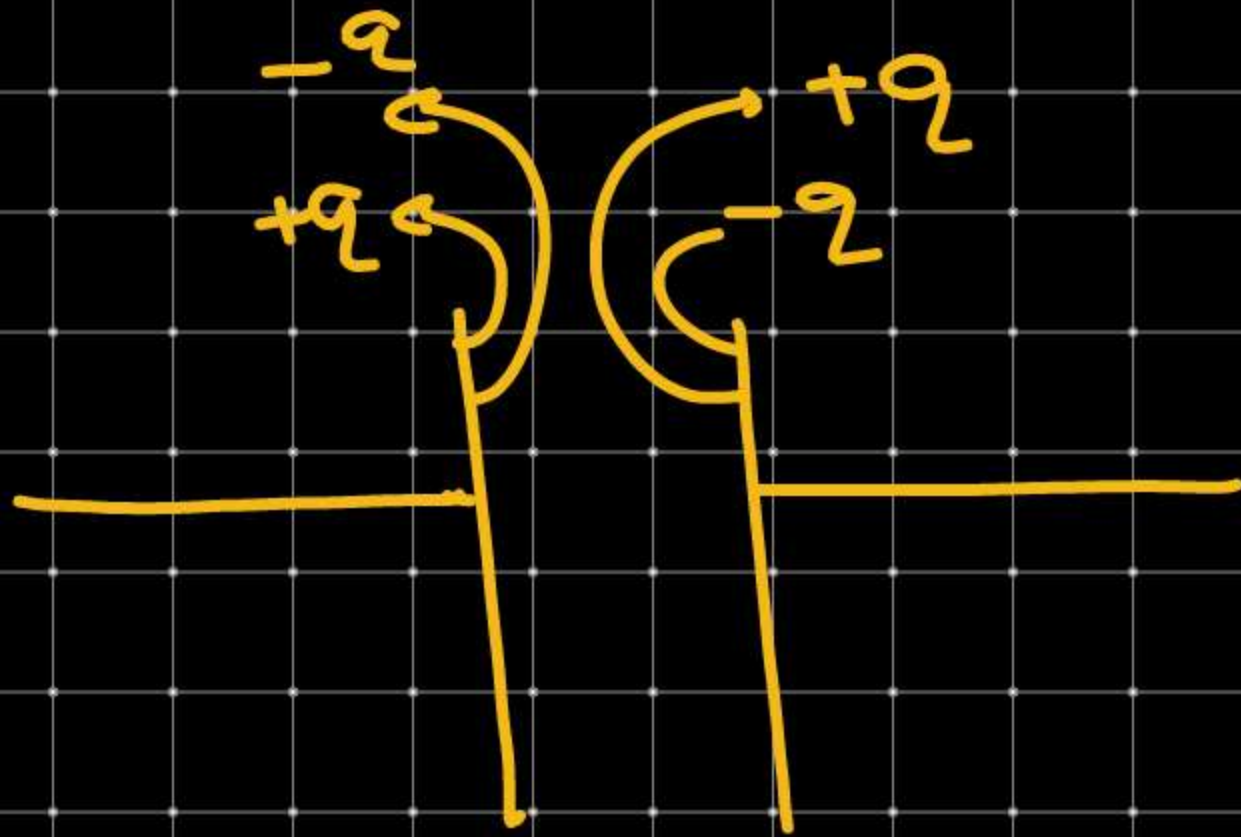

$$E = E_0 \sin \omega t$$

Power in LCR

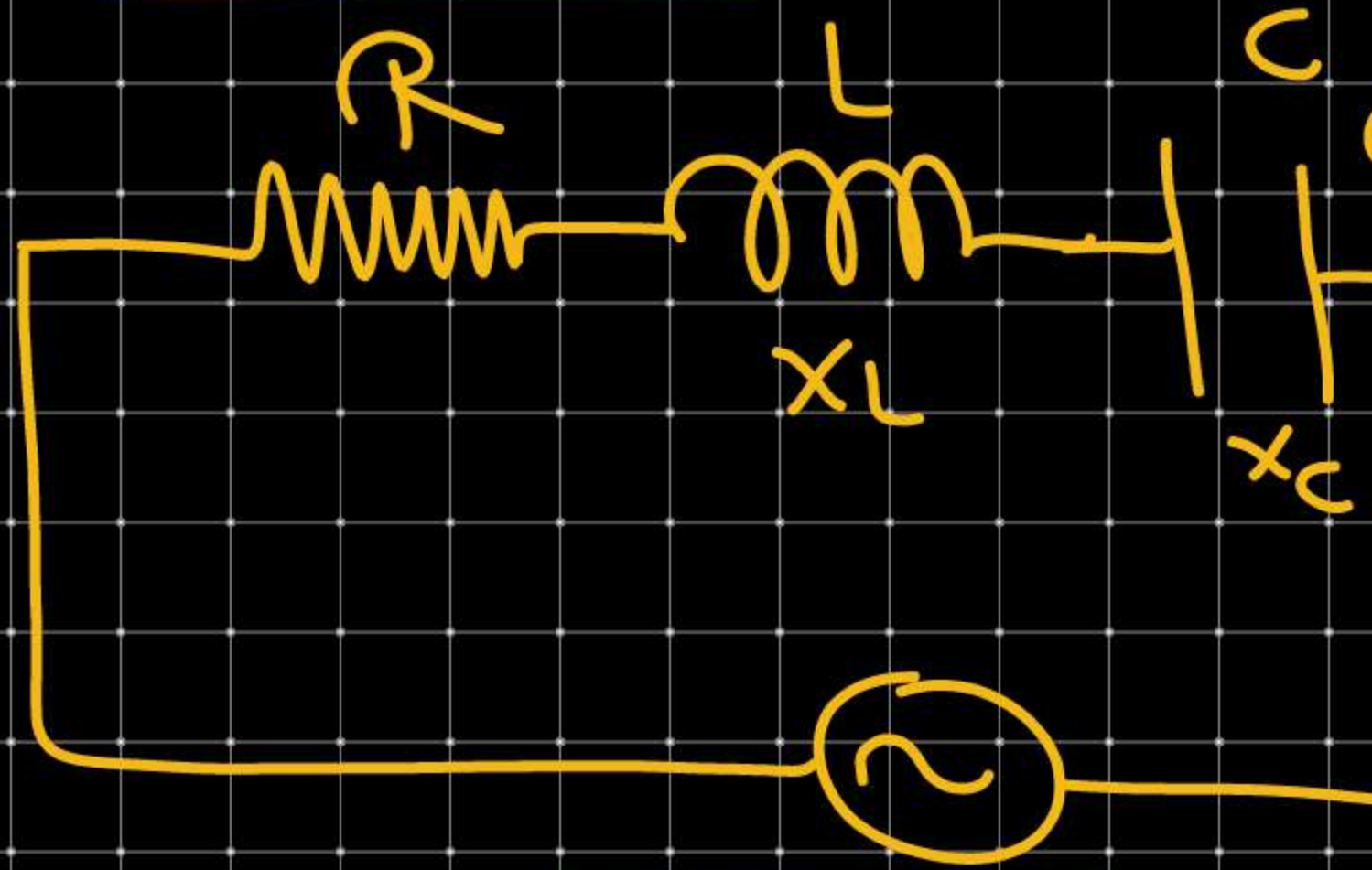


$$\cos \phi = \frac{V_R}{V}$$


$$= \frac{X_R}{X_Z}$$

$$\cos \phi = \frac{P}{VI}$$


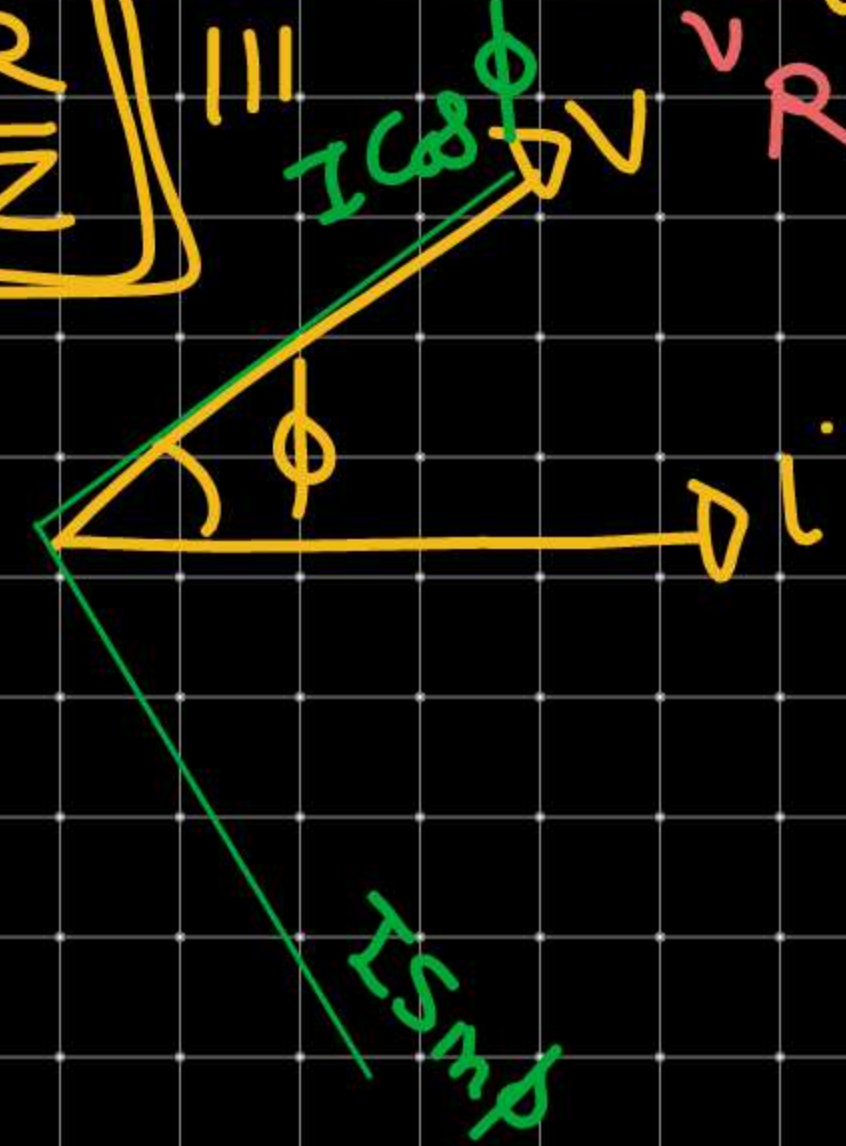
$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$



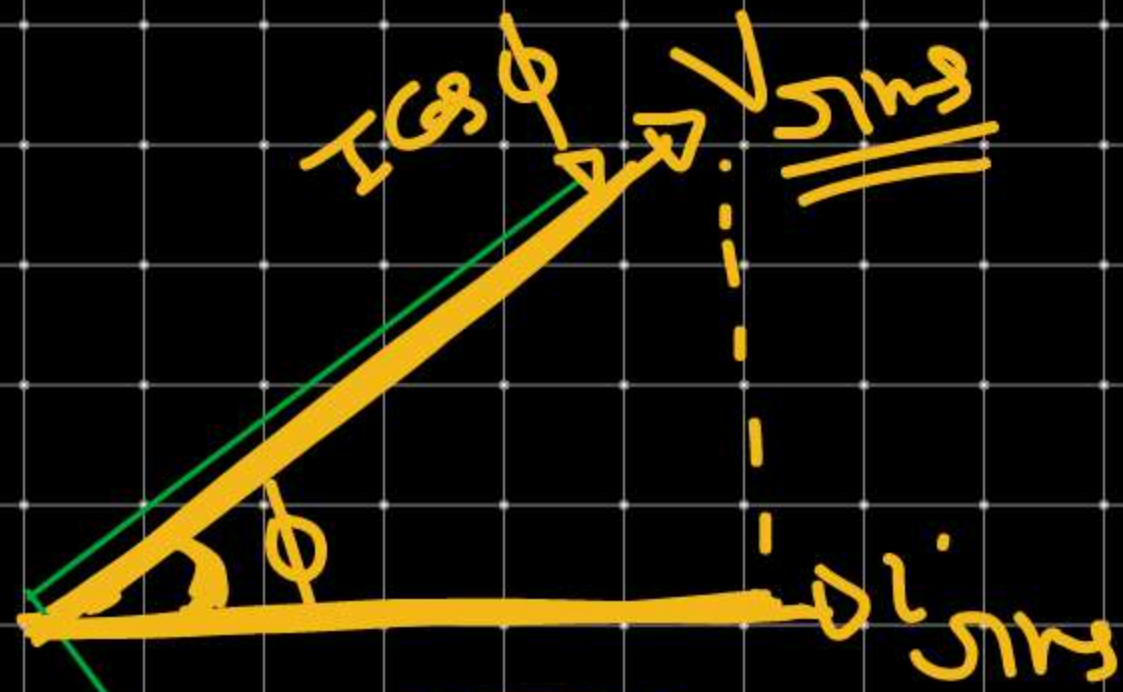

Power is AC with LCR

$$P = VI \cos \phi$$

$\sin \omega t \sin \omega t$

**

$\cos \phi \rightarrow$ Power factor

Wattless current

$I \sin \phi$

$$\cos \phi = \frac{P}{VI}$$

$$\cos \phi = \frac{P}{VI} = \frac{VR}{V^2}$$

We full $\rightarrow I \cos \phi$ current

Power In AC Circuit

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

V_{rms} → rms value of voltage

I_{rms} → rms value of current

V_0 → Peak value of voltage

I_0 → Peak value of current


$$P = \frac{V_0}{\sqrt{2}} \times \frac{I_0}{\sqrt{2}} \cos \phi$$

$$P = \frac{V_0 I_0 \cos \phi}{2}$$

$$P = \frac{V_0 I_0 \cos \phi}{2}$$

A Coil of inductive reactance $31\ \Omega$ has a resistance $8\ \Omega$. it is placed in series with a Capacitive of Capacitive reactance $25\ \Omega$. The Comb is connected by an AC Source 110 Volt. The Power factor of Circuit is:

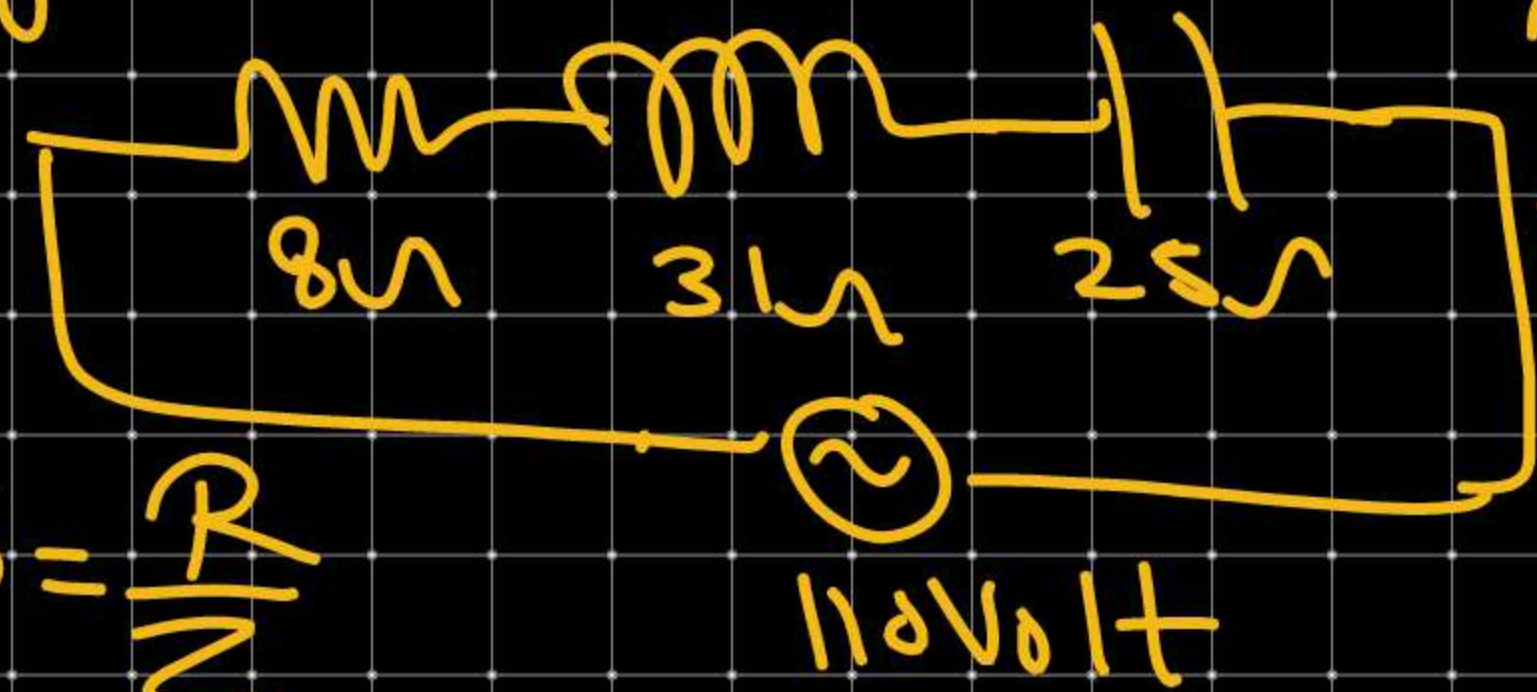- Ⓐ 0.33 lag ϕ
- ~~Ⓑ 0.80~~
- Ⓒ 0.64
- Ⓓ 0.80



$$R = 8\ \Omega$$

$$Z = \sqrt{8^2 + (31 - 25)^2}$$

$$= \sqrt{64 + 36}$$

$$= 10\ \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$\cos \phi = \frac{8}{10} = \underline{\underline{0.8}}$$

Q2)

$$E = E_0 \sin \omega t$$

$$I = I_0 \sin(\omega t - \phi)$$

(Power) = ?

(a)

(b)

(c)

(d)

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$i = i_0 \sin(\omega t - \phi)$$

Phase diff = ϕ .

(P_{av}) = ?

$$P = \frac{V_0 I_0}{2} \cos \phi$$

(a) $\frac{E_0 I_0}{2} \cos \phi$

(b) $E_0 I_0$

(c) $\frac{E_0 I_0}{2}$

(d) $\frac{E_0 I_0}{2} \sin \phi$

$$P = V \sin \omega t \cdot I \sin \omega t \cos \phi$$

$\phi =$ phase diff
b/w ε & I

$$P_{av} = \frac{E_0 I_0}{2} \cos \phi$$

$$i = \frac{1}{\sqrt{2}} \sin 100\pi t$$

$$e = \frac{1}{\sqrt{2}} \sin \left(100\pi t + \frac{\pi}{3} \right)$$

$(P_{av}) = ?$

$$P_{av} = V_{rms} I_{rms} \cos \phi$$

$$= \frac{1}{\sqrt{2} \times \sqrt{2}} \times \frac{1}{\sqrt{2} \times \sqrt{2}} \cos \frac{\pi}{3}$$

$$= \frac{1}{2} \times \frac{1}{2} \times \frac{1}{2} = \frac{1}{8} \text{ Watt}$$