

Q1: AJPMT 2011

In an AC circuit an alternating voltage $e = 200\sqrt{2} \sin 100t$ Volt is connected to a capacitor of capacity $1\mu\text{F}$. The rms value of the current in the circuit.

- (a) 20mA
- (b) 200mA
- (c) 100mA
- (d) 10mA



$$C = 1 \times 10^{-6} \text{ F.}$$

$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{100 \times 10^{-6}}$$

$$E = 200\sqrt{2} \sin 100t \quad X_C = \frac{10^6}{10^2} = 10^4 \underline{\underline{\Omega}}$$

$$E = E_0 \sin \omega t$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{200}{10^4}$$

$$V_{\text{rms}} = \frac{200\sqrt{2}}{\sqrt{2}} = 200 \text{ Volt}$$

$$= \frac{2 \times 10^2 \times 10^{-4}}{1} = 2 \times 10^{-2} = 20 \times 10^{-3} \text{ A}$$

$$= \underline{\underline{20 \text{ mA}}}$$


≅ NEET 2020 ∴ A $40 \mu\text{F}$ Capacitor is connected to a 200V 50Hz ac supply. The rms value of current in the circuit is nearly.

(a) 2.5A [✓]

(b) 25.1A

(c) 1.7A

(d) 2.0A

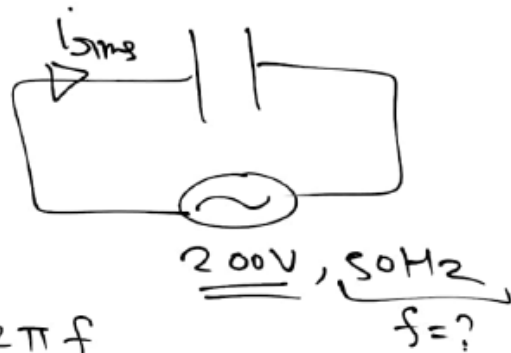

$$\omega = 2\pi f$$

$$= 2\pi \times 50$$

$$\omega = 100\pi$$

$$i_{\text{rms}} = \frac{200 \phi \times \pi}{25\pi}$$

$$= \frac{4}{5} \times \pi = 0.8 \times 3.1416$$

$$= \underline{\underline{\approx 2.5 \text{ Amp}}}$$

$$V_{\text{rms}} = 200\text{V}$$



$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{100\pi \times 40 \times 10^{-6}}$$

$$= \frac{1}{4\pi \times 10^3}$$

$$= \frac{1000}{4\pi} = \frac{500}{2\pi} = \left(\frac{250}{\pi} \right) \Omega$$

Resonance in LCR :-

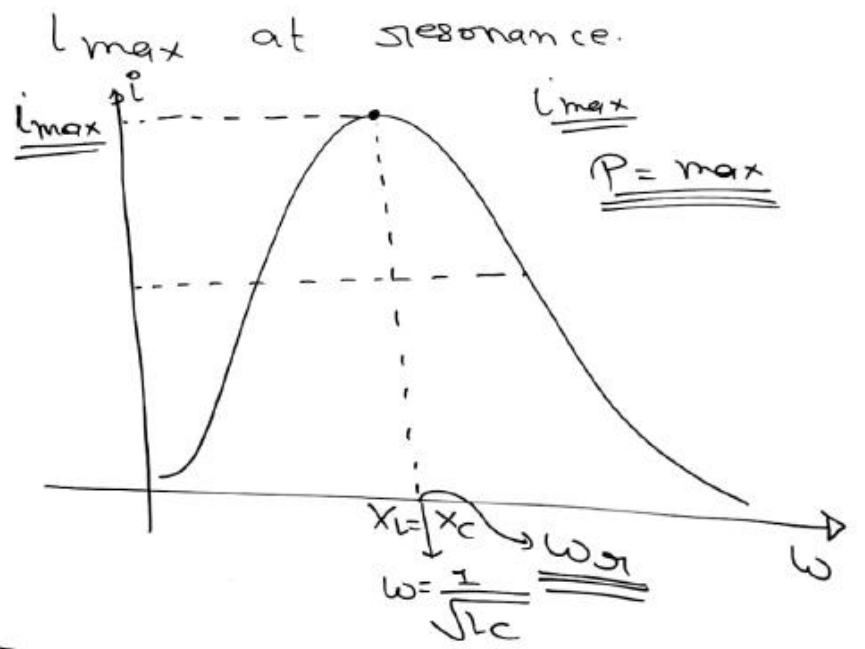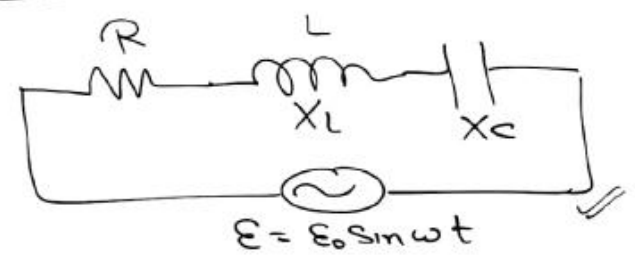

At resonance

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$


$$\omega = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}} //$$

$$\Rightarrow \underline{X_L - X_C = 0} \quad Z = \sqrt{R^2 + (X_L - X_C)^2} //$$

$$\boxed{Z = R} \text{ minimum}$$

Resonance in LCR :-

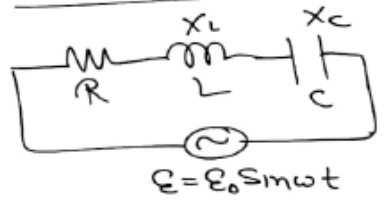

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Z_{min} at resonance

$X_L = X_C \rightarrow Z = R \rightarrow \text{min}$

$\omega = \frac{1}{\sqrt{LC}} \quad f = \frac{1}{2\pi\sqrt{LC}} \rightarrow \begin{matrix} \text{I}_{max} \\ \text{max} \end{matrix}$

$$i = \frac{V_{rms}}{Z}$$



⊕

$X_L = \omega L$
 $X_C = \frac{1}{\omega C}$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$\omega > \omega_{01}$

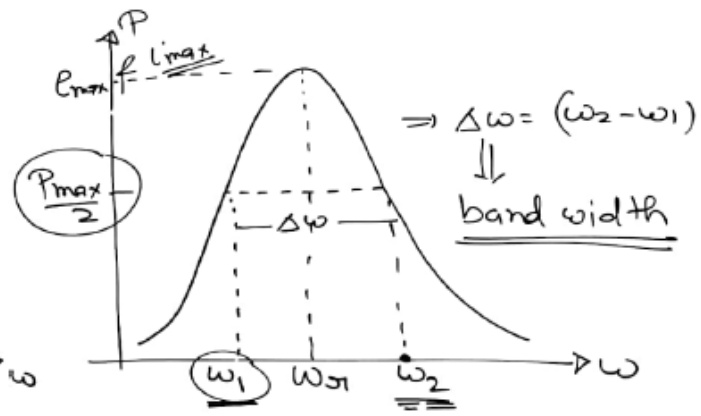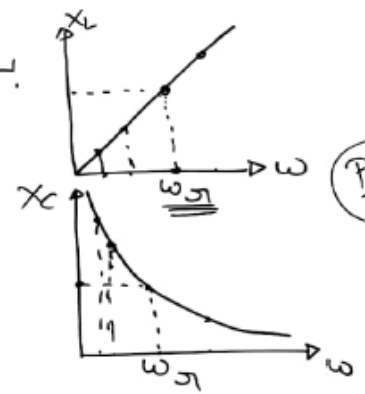

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (X_L - X_C)^2 = I_{rms}^2$$


$\omega > \omega_{01} \Rightarrow Z \uparrow \quad X_L \uparrow \quad X_C \downarrow \Rightarrow (X_L - X_C) \uparrow$

$\omega < \omega_{01} \Rightarrow \omega \downarrow \quad X_C \uparrow \quad X_L \downarrow \Rightarrow (X_L - X_C)^2 \uparrow$

$\Delta\omega \rightarrow$ band width

$$\Delta\omega = \frac{R_v}{L}$$

Imp Question


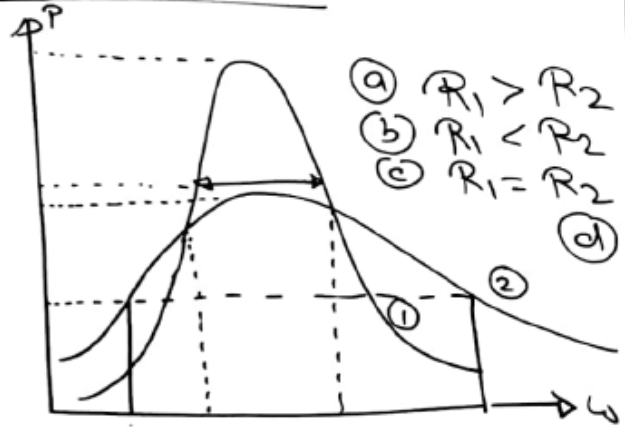


- ① $R_1 > R_2$
- ② $R_1 < R_2$
- ③ $R_1 = R_2$

No O.T.

② $(\Delta\omega)_2 > (\Delta\omega)_1$

$$R_2 > R_1$$

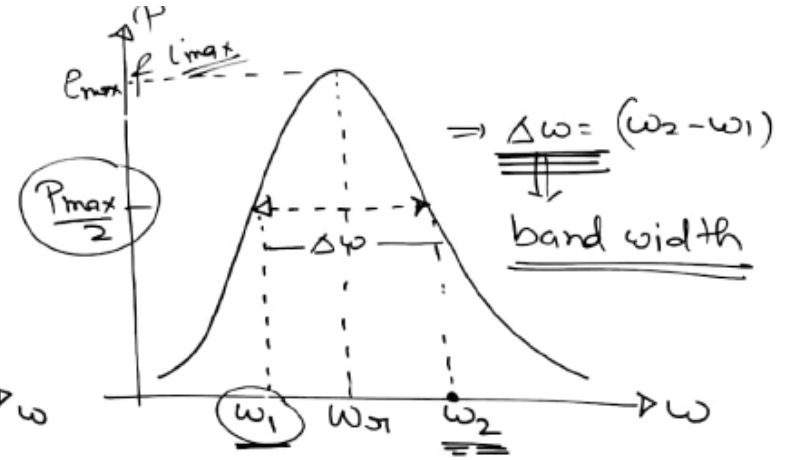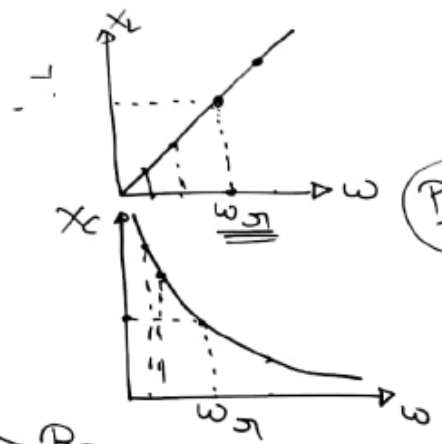

$\Delta\omega \rightarrow$ band width

$$\Delta\omega = \frac{R}{L}$$

\Rightarrow Quality factor (Q)

$$Q = \frac{\omega_{01}}{\Delta\omega}$$

$$= \frac{1}{\sqrt{LC} \times R}$$

$$= \frac{1}{\sqrt{LC} \times R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

R \rightarrow Resistance

L \rightarrow Inductance

C \rightarrow Capacitance

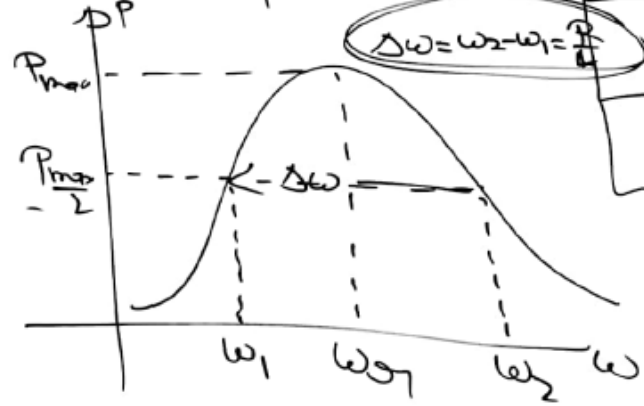

For Q High

- \rightarrow R \rightarrow Low
- \rightarrow L \rightarrow High
- \rightarrow C \rightarrow Low

\Rightarrow Q \rightarrow Low

R High

L \rightarrow Low

C \rightarrow High.

Q) Which of the following combination should be selected for better tuning of an L-C-R CKT used for communication.

(a) $R = 25 \Omega$ $L = 2.5 \text{ mH}$ $C = 45 \text{ mF}$

(b) $R = 20 \Omega$ $L = 1.5 \text{ mH}$ $C = 35 \text{ mF}$

(c) $R = 25 \Omega$ $L = 1.5 \text{ mH}$ $C = 45 \text{ mF}$

(d) $R = 15 \Omega$ $L = 3.5 \text{ mH}$ $C = 30 \text{ mF}$

Q_1

Q_2

Q_3

Q_4

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$


Q - High

$R \rightarrow$ Low

$L \rightarrow$ High

$C \rightarrow$ low

L-C-R in parallel :-

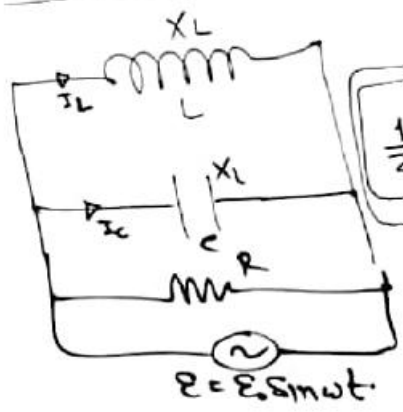





$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}$$

$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$


$$\frac{V}{Z} = \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_C} - \frac{V}{X_L}\right)^2}$$

$$\frac{V}{Z} = \sqrt{\frac{V^2}{R^2} + V^2 \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}$$
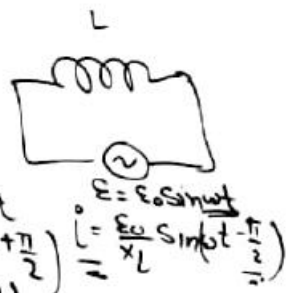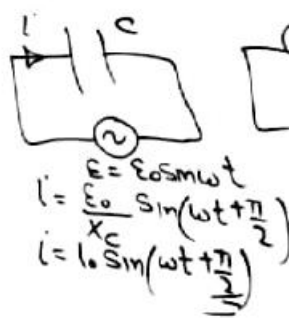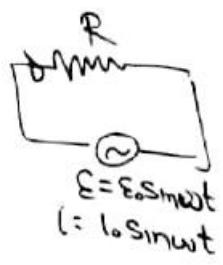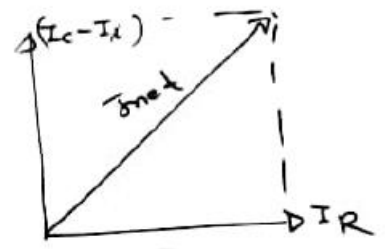
$$\frac{V}{Z} = V \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}$$



Q1)

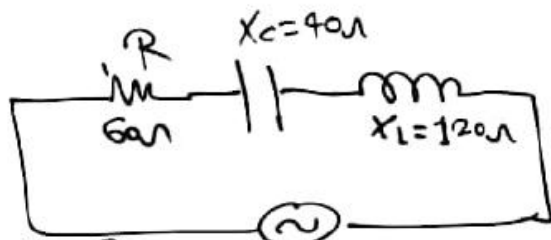

$$\cos \phi = \frac{R}{Z}$$

$$\therefore \frac{60}{100} = \frac{3}{5}$$

$$V_{rms} = \frac{E_0}{\sqrt{2}} = 220V$$

$$E = 220\sqrt{2} \sin 100\pi t$$

i) $Z = ?$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

ii) I_{rms}

$$Z = \sqrt{(60)^2 + (120 - 40)^2}$$

$$= \sqrt{(60)^2 + (80)^2}$$

iii) V_{rms}

iv) P_{avg}

$$Z = 100\Omega \quad P_{avg} = \frac{V_0 I_0}{2} \cos \phi$$


$$I_{rms} = \frac{V_{rms}}{Z} = \frac{220}{100} = 2.2 \text{ Amp} = V_{rms} I_{rms} \cos \phi$$

$$= 220 \times 2.2 \times \frac{3}{5}$$

iii) $V_{rms} = \frac{E_0}{\sqrt{2}} = \frac{220\sqrt{2}}{\sqrt{2}} = 220V = \frac{22 \times 22 \times 3}{5}$

$$= 290.8 \text{ watt}$$

Q2)

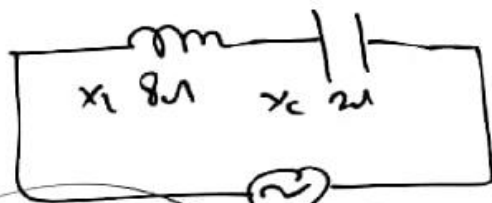

220V, 50Hz

a) I_{rms} b) $Z = ?$

$$Z = \sqrt{(X_L - X_C)^2}$$

$$= \sqrt{(8 - 2)^2}$$

$$= \sqrt{(6)^2} = 6\Omega$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{220}{6}$$

$$I_{rms} = \frac{110}{3} \text{ Amp}$$