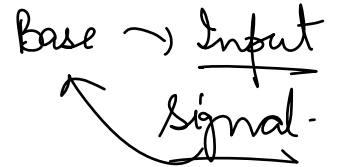


Transistor as a switch:

Cut off Region & Saturation Region:


Transistor as an amplifier

[Common Emitter]



Transistor as an amplifier works in the active region.

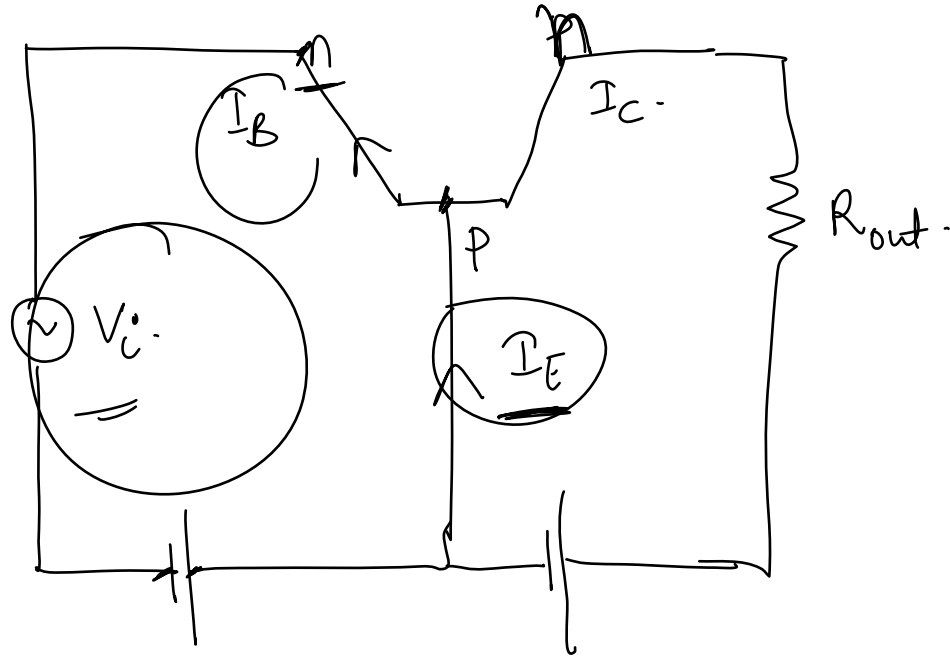
A transistor can take a very small weak signal through base junction and release the amplified signal



Base emitter junction is forward biased

Output circuit is reverse biased

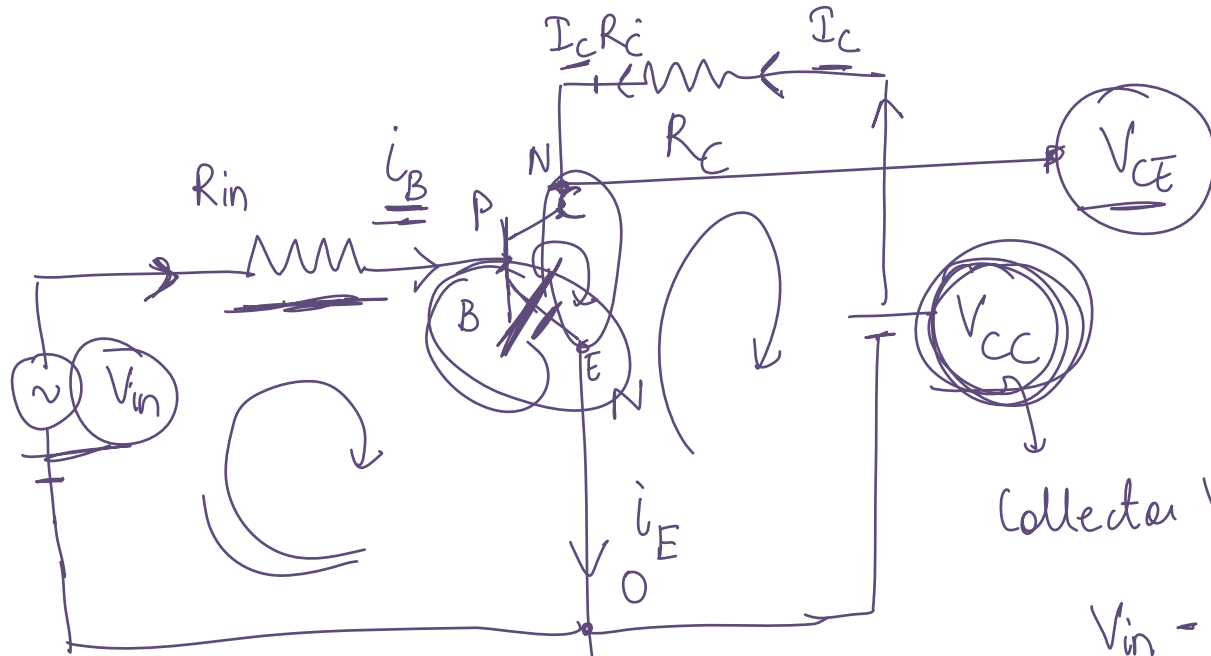A small change in signal voltage results in the change in the emitter current due to low resistance in the circuit.



Collector voltage -

$$V_{in} - i_B R_B - V_{BE} = 0$$

$$V_o = V_{CE} \Rightarrow V_{CC} - i_C R_C \quad \text{--- (1)}$$

$$V_{in} = i_B R_B + V_{BE}$$

$$V_o = V_{cc} - i_c R_c$$

$$V_i = i_B R_B + V_{BE}$$

$$\Delta V_i = \Delta i_B R_B + \Delta V_{BE} \quad \Delta V_{BE} \ll \Delta i_B R_B$$

$$\Delta V_i = \Delta i_B R_B \quad \text{--- (1)}$$

$$\Delta V_o = \cancel{\Delta V_{cc}} - \Delta i_c R_c$$

0.

$$\Delta V_o = - \Delta i_c R_c \quad \text{--- (2)}$$

$$\beta = \frac{\Delta i_c}{\Delta i_b} \quad \Delta i_c \gg \Delta i_b$$

$$\beta > 1$$

Current Amplification
factor
Current gain

Voltage gain: The gain in terms of voltage when there is change in input and output current is called voltage gain.


$$\frac{\Delta V_o}{\Delta V_i} = \frac{\Delta i_c R_c}{\Delta i_b R_b}$$

$$\frac{\Delta V_o}{\Delta V_i} = \frac{\beta \cdot R_c}{R_b} = \beta \frac{R_{out}}{R_{in}}$$

$$\begin{aligned} \text{Power gain} &= V_{\text{gain}} \cdot I_{\text{gain}} \\ &= \beta \frac{R_{out}}{R_{in}} \cdot \beta \end{aligned}$$

$$\text{Power gain} \Rightarrow \beta^2 \frac{R_{out}}{R_{in}}$$

Ques.

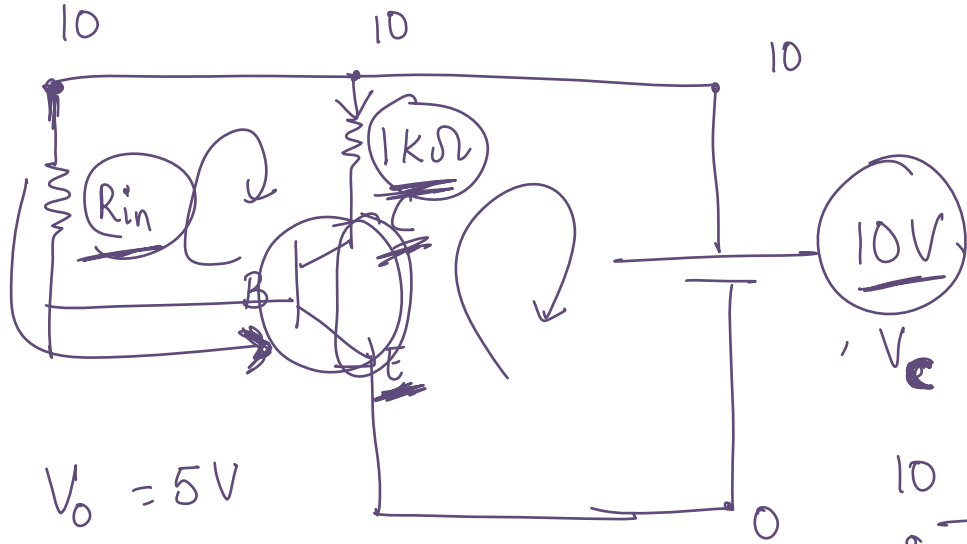

$\beta = 100$

$R_{in} = ?$

$V_o = 5V$

$V_{BE} = 0V$

$V_c = i_c R_C + V_{CE}$

$10 = i_c \times 1k\Omega + 5$

$i_c = \frac{5}{1000} A = \frac{5}{1000} A$

$10 = i_b R_{in} + V_{BE}$
 $10 = i_b R_B$
 $i_b = \frac{10}{R_B}$



$$\beta = \frac{i_c}{i_b}$$

$$100 = \frac{5/1000}{\frac{10^2}{R_B}}$$

$$100 \times 1000 = \frac{R_B}{2}$$


$$R_B = \frac{200 \times 1000 \Omega}{1} = \underline{\underline{200 \text{ K}\Omega}}$$

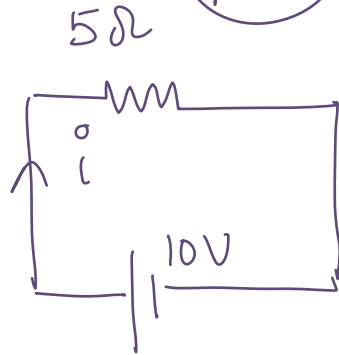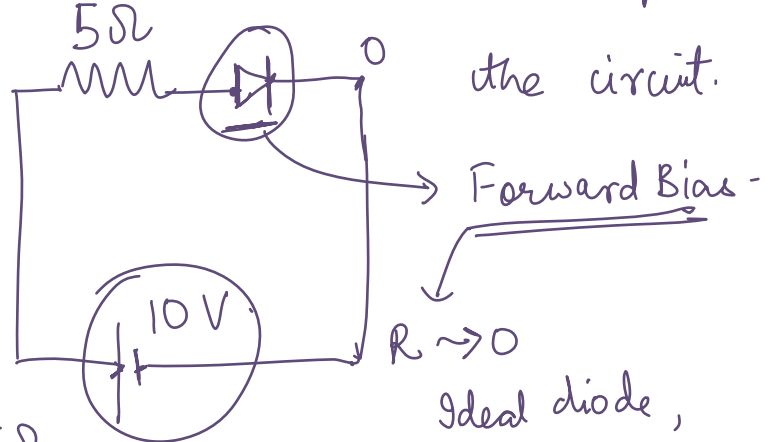Ques Calculate the current flowing in the circuit.




$$i = \frac{10}{5} = \underline{\underline{2 \text{ A}}}$$

Ques

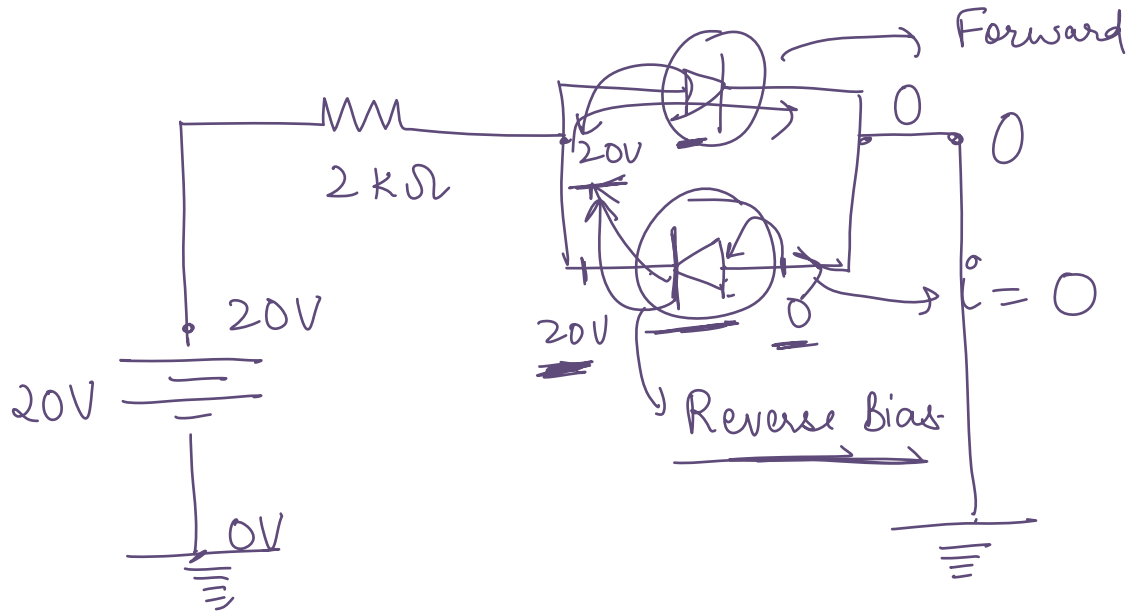

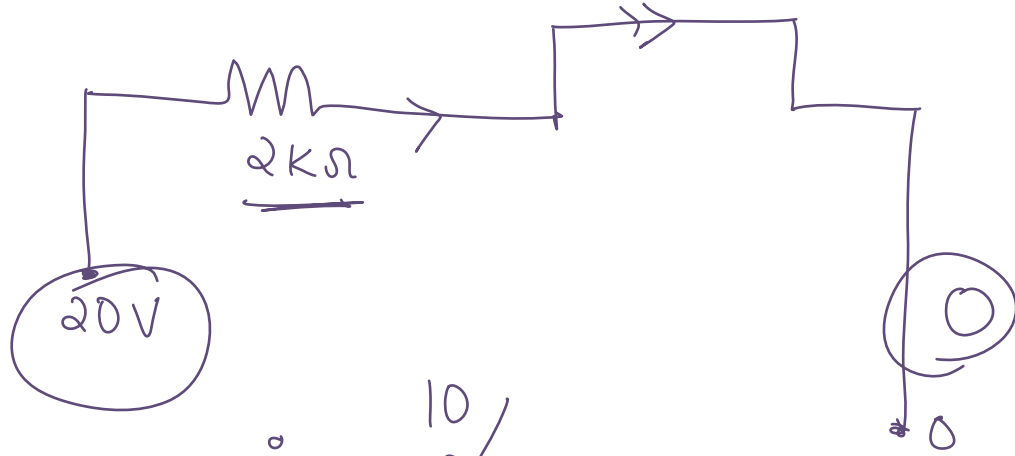Calculate current flowing in the circuit, assume resistance in forward bias = 0.



D_2 is reverse biased.
 So, 0 current


$$i = \frac{10}{20 - 0} \times 10^3$$

$$= 10 \times 10^{-3} \text{ A} = \underline{\underline{10^{-2} \text{ A}}}$$

In half wave rectifier peak value of sinusoidal signal is 10V

Determine the output voltage -- (Average value).

$$V_{in} = 10 \sin \omega t$$

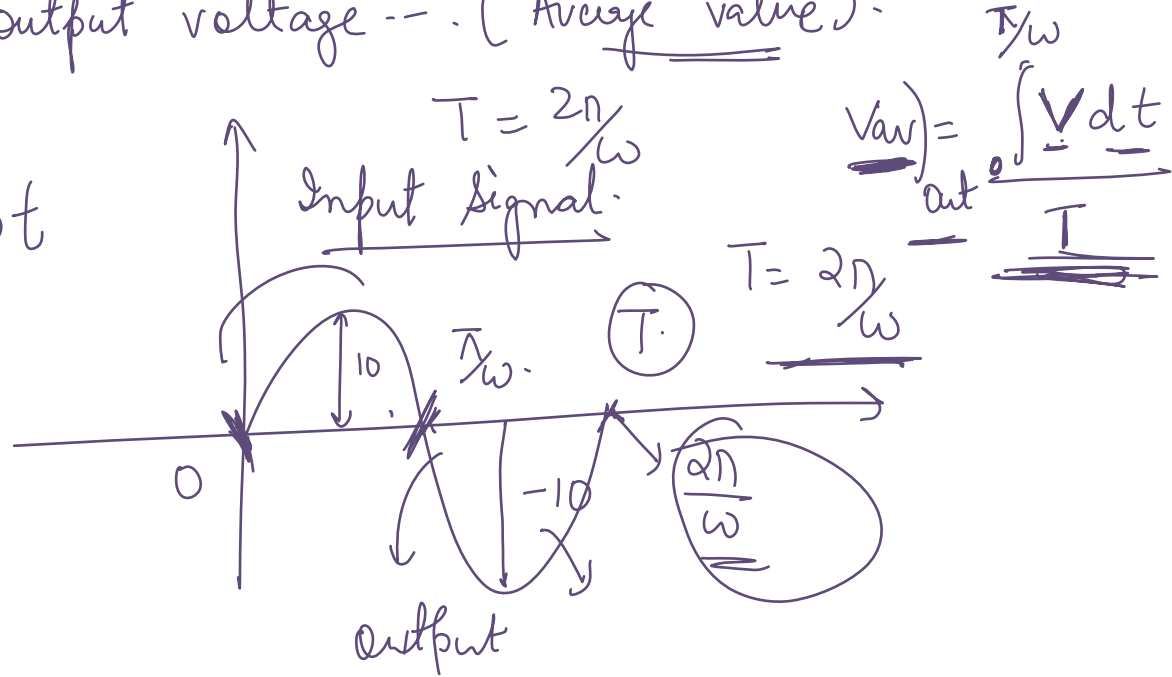

$$\Rightarrow \frac{\int_0^{\pi/\omega} 10 \sin \omega t \, dt}{\omega}$$

$$\Rightarrow \frac{5 \int_0^{\pi/\omega} \sin \omega t \, dt}{\omega}$$

$$\Rightarrow \frac{5\omega}{\pi} \left[-\frac{\cos \omega t}{\omega} \right]_0^{\pi/\omega}$$

$$\Rightarrow \frac{5\omega}{\pi} \left[-\cos \omega \times \frac{\pi}{\omega} - (-\cos 0) \right]$$

$$\Rightarrow \frac{5}{\pi} \left[-\cos \pi + 1 \right]$$

$$\Rightarrow \frac{5}{\pi} \left[-1(-1) + 1 \right]$$

$$\Rightarrow \frac{5}{\pi} (1+1) = \frac{10}{\pi} \text{ A.}$$